

The University of Alabama in Huntsville
Electrical & Computer Engineering
CPE/EE 422/522 01
Homework #1 Solution
Spring 2005

1. (10 points) Prove that the following identities are valid using algebraic manipulation.

a. $ab' + bc' + ca' = a'b + b'c + c'a$
 $ab' + bc' + ca' = ab'(c+c') + bc'(a+a') + ca'(b+b')$
 $= ab'c + ab'c' + abc' + a'bc' + a'bc + a'b'c$
 $= a'b(c'+c) + b'c(a+a') + ac'(b'+b)$
 $= a'b + b'c + c'a$

b. $ab + a'c + bcd = ab + a'c$
 $ab + a'c + bcd = ab(c+c')(d+d') + a'c(b'+b)(d+d') + bcd(a'+a)$
 $= abc'd' + abc'd + abcd' + abcd + a'b'cd' + a'b'cd + a'bcd' + a'bcd + a'bcd + abcd$
 $= abc(d'+d) + abc(d'+d) + a'b'c(d'+d) + a'bc(d'+d)$
 $= ab(c'+c) + a'c(b'+b)$
 $= ab + a'c$

2. (10 points) Find the complements of the following functions.

a. $f = a + bc$
 $f' = (a + bc)' = a'(bc)' = a'(b' + c') = a'b' + a'c'$

b. $f = ab + b'c + ca'd$
 $f' = (ab + b'c + ca'd)' = (ab)'(b'c)'(ca'd)' = (a' + b')(b + c')(c' + a + d') = (a'b + a'c' + b'b + b'c')(c' + a + d') = (a'b + a'c' + b'c')(c' + a + d') = a'bc' + a'ba + a'bd' + a'c'c' + a'c'a + a'c'd' + b'c'c' + ab'c' + b'c'd' = a'bc' + a'bd' + a'c' + a'c'd' + b'c' + ab'c' + b'c'd' = a'c'(b + 1 + d') + b'c'(1 + a + d) + a'bd' = a'c' + b'c' + a'bd'$

3. (15 points) Obtain the truth table of the following functions and express each function in sum of minterms and product of maxterms,

a. $xyz + xy'z'$
 $= \Sigma m(4, 7) = \Pi M(0, 1, 2, 3, 5, 6)$

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

b. $abc + ab'c' + a'b'c'$
 $= \Sigma m(0, 4, 7) = \Pi M(1, 2, 3, 5, 6)$


a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

c. $\bar{Y}Z + WX\bar{Y} + WX\bar{Z} + \bar{W}\bar{X}Z = \Sigma m(1, 3, 5, 9, 12, 13, 14) = \Pi M(0, 2, 4, 6, 7, 8, 10, 11, 15)$


W	X	Y	Z	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

4. (20 points) Simplify the following expressions by means of a four-variable map.

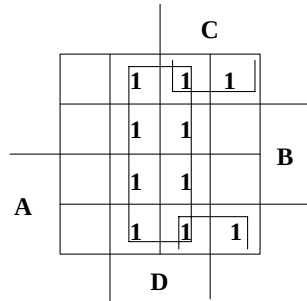
a. $\overline{A}D + BD + \overline{B}C + A\overline{B}D = D + \overline{B}C$



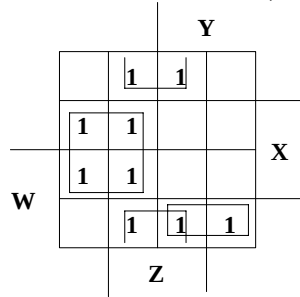
b. $\overline{X}Z + \overline{W}XY + W(\overline{X}Y + X\overline{Y}) = \overline{X}Z + W\overline{X}Y + X\overline{Y}$



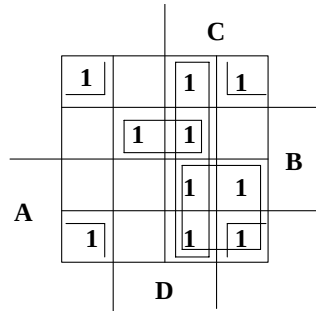
c. $\overline{A}BC + \overline{B}C\overline{D} + BCD + AC\overline{D} + \overline{A}BC + \overline{A}B\overline{C}D = \overline{B}D + CD + AC + \overline{A}BD$



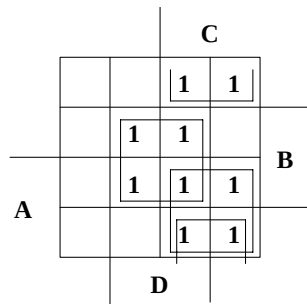d. $ABC + CD + \overline{B}C\overline{D} + \overline{B}C = AC + BD + \overline{B}C$







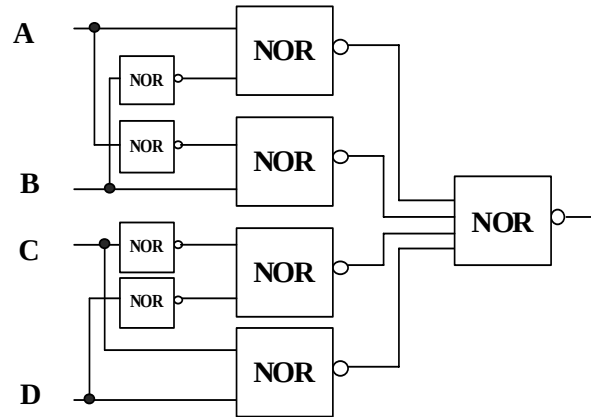5. (10 points) Implement the following expression with two-input NOR gates.
 $(AB + \overline{AB})(\overline{CD} + \overline{CD})$



6. (15 points) Design a combinational circuit whose input is a four-bit number and whose output is the 2's complement of the input number.

$A_3 A_2 A_1 A_0$	$F_3 F_2 F_1 F_0$
0 0 0 0	0 0 0 0
0 0 0 1	1 1 1 1
0 0 1 0	1 1 1 0
0 0 1 1	1 1 0 1
0 1 0 0	1 1 0 0
0 1 0 1	1 0 1 1
0 1 1 0	1 0 1 0
0 1 1 1	1 0 0 1
1 0 0 0	1 0 0 0
1 0 0 1	0 1 1 1
1 0 1 0	0 1 1 0
1 0 1 1	0 1 0 1
1 1 0 0	0 1 0 0
1 1 0 1	0 0 1 1
1 1 1 0	0 0 1 0
1 1 1 1	0 0 0 1

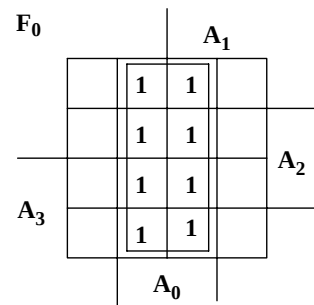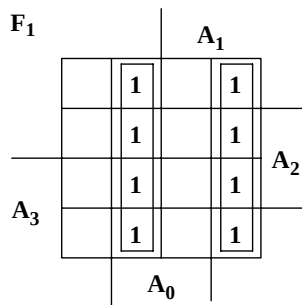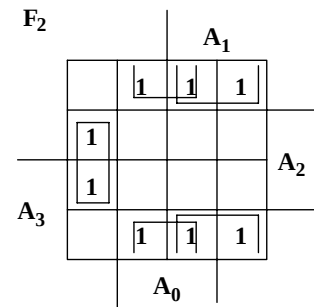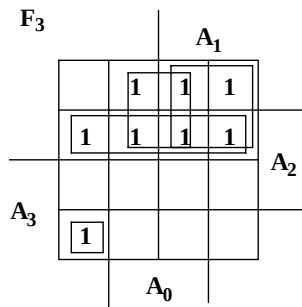


$$F_3 = \overline{A_3}A_2 + \overline{A_3}A_1 + \overline{A_3}A_0 + A_3\overline{A_2}\overline{A_1}\overline{A_0}$$

$$F_2 = \overline{A_2}A_0 + \overline{A_2}A_1 + A_2\overline{A_1}\overline{A_0}$$

$$F_1 = A_1\overline{A_0} + \overline{A_1}A_0$$

$$F_0 = A_0$$

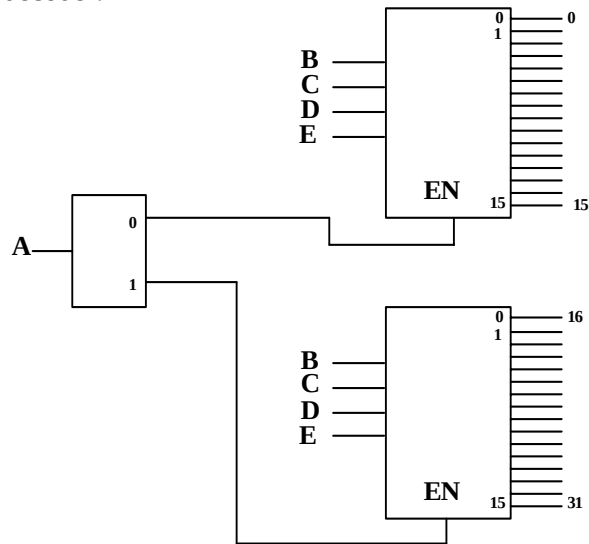7. (10 points) Construct a 5-to-32-line decoder with two 4-to-16 decodes with enable input and one 1-to-2-line decoder.



8. (10 points) Construct a 5-to1 line multiplexer with as many 2-to-1 line multiplexers as are needed.

