 


The University of Alabama in Huntsville
Electrical and Computer Engineering
CPE/EE 422/522
Spring 2005
Homework #5 Solution


3.2 (a)(10), (e)(20), 3.3(30), 3.6(20), 4.6(a)(20)

3.2 An older-model Thunderbird car has three left and three right tail lights, which flash in unique patterns to indicate left and right turns.

Left-turn pattern:




Right-turn pattern:

 

Design a Moore sequential network to control these lights. The network has three inputs, LEFT, RIGHT, and HAZ. LEFT and RIGHT come from driver's turn-signal switch and cannot be 1 at the same time. As indicated above, when LEFT = 1, the lights flash in a pattern LA on, LA and LB on, LA, LB, and LC on and all off; then the sequence repeats. When RIGHT = 1, the light sequence is similar. IF a switch from LEFT to RIGHT (or vice versa) occurs in the middle of a flashing sequence, the network should immediately go to the IDLE state (lights off) and then start the new sequence. HAZ comes from the hazard switch, and when HAZ = 1, all six lights flash on and off in unison. HAZ takes precedence if LEFT or RIGHT is also on. Assume that a clock signal is available with a frequency equal to the desired flashing rate.

(a) Draw the state graph (8 states).

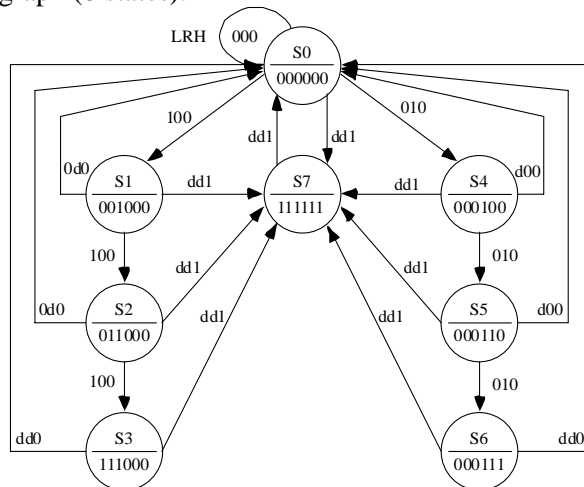

(e) Write a VHDL model

```
library ieee;
use ieee.std_logic_1164.all;

entity THUNDERBIRD is
    port (L, R, H, CLK : in std_logic;
          LC, LB, LA, RA, RB, RC : out std_logic);
end THUNDERBIRD;
```

```

architecture BEHAVE of THUNDERBIRD is
    type STATE_TYPE is (S0, S1, S2, S3, S4, S5, S6, S7);
    signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
begin
    process(CURRENT_STATE, L, R, H)
        variable INPUTS : std_logic_vector(2 downto 0);
    begin
        INPUTS := L&R&H;
        case CURRENT_STATE is
            when S0 => if (INPUTS = "000") then
                NEXT_STATE <= S0;
            elsif (INPUTS = "100") then
                NEXT_STATE <= S1;
            elsif (INPUTS = "010") then
                NEXT_STATE <= S4;
            else
                NEXT_STATE <= S7;
            end if;
            when S1 => if (INPUTS(0) = '1') then
                NEXT_STATE <= S7;
            elsif (INPUTS = "100") then
                NEXT_STATE <= S2;
            else
                NEXT_STATE <= S0;
            end if;
            when S2 => if (INPUTS(0) = '1') then
                NEXT_STATE <= S7;
            elsif (INPUTS = "100") then
                NEXT_STATE <= S3;
            else
                NEXT_STATE <= S0;
            end if;
            when S3|S6 => if (INPUTS(0) = '1') then
                NEXT_STATE <= S7;
            else
                NEXT_STATE <= S0;
            end if;
            when S4 => if (INPUTS(0) = '1') then
                NEXT_STATE <= S7;
            elsif (INPUTS = "010") then
                NEXT_STATE <= S5;
            else
                NEXT_STATE <= S0;
            end if;
            when S5 => if (INPUTS(0) = '1') then
                NEXT_STATE <= S7;
            elsif (INPUTS = "010") then
                NEXT_STATE <= S6;
            else
                NEXT_STATE <= S0;
            end if;
            when S7 => NEXT_STATE <= S0;
        end case;
    end process;
end architecture;

```


3.6 (modified) Write a VHDL model on a 6-bit binary up-down counter with reset. Simulate the model and verify that the counter works.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity UP_DOWN_COUNTER is
  port (UP, DOWN, CLK, RESET : std_logic;
        QOUT : out UNSIGNED(5 downto 0));
end UP_DOWN_COUNTER;

architecture BEHAVE of UP_DOWN_COUNTER is
begin
  process(UP, DOWN, RESET, CLK)
    variable QTEMP : UNSIGNED(5 downto 0);
  begin
    if (RESET = '1') then
      QTEMP := "000000";
    elsif (CLK'event and CLK = '1') then
      if (UP = '1') then
        if (QTEMP = UNSIGNED'("111111")) then
          QTEMP := "000000";
        else
          QTEMP := QTEMP + '1';
        end if;
      elsif (DOWN = '1') then
        if (QTEMP = UNSIGNED'("000000")) then
          QTEMP := "111111";
        else
          QTEMP := QTEMP - '1';
        end if;
      end if;
    end if;
    QOUT <= QTEMP;
  end process;
end BEHAVE;
```

4.6 In Section 4.4 we developed an algorithm for multiplying signed binary fractions, with negative fractions represented in 2's complement. (a) Illustrate this algorithm by multiplying 1.0111 by 1.101.

0	.	0	0	0	0					
1	.	0	1	1	1					
1	.	0	1	1	1					add
1	.	1	0	1	1	1				shift w/sign extend
1	.	1	1	0	1	1	1			shift w/sign extend
1	.	0	1	1	1					
1	.	0	1	0	0	1	1			add
1	.	1	0	1	0	0	1	1		shift w/sign extend
0	.	1	0	0	1					
0	.	0	0	1	1	0	1	1		add 2's complement