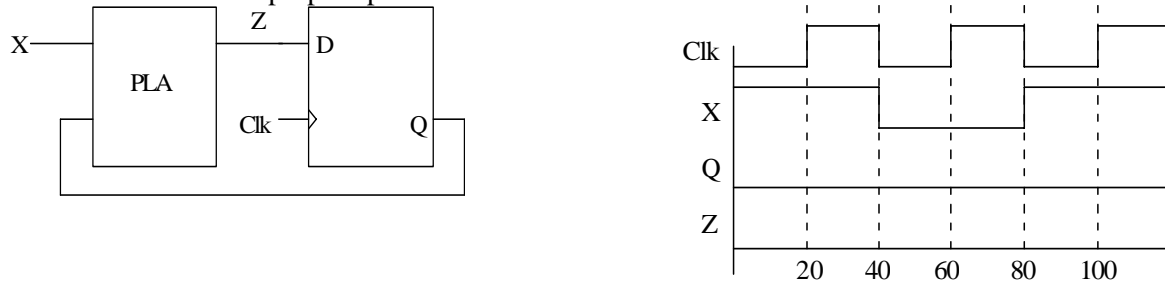


The University of Alabama in Huntsville
ECE Department
CPE/EE 422/522 01
Midterm Exam Solution

1. (10 points) A sequential network consists of a PLA and a D flip-flop, as shown. The propagation delay for the PLA is in the range 5 to 10 ns, and the propagation delay from clock to output of the D flip-flop is 5 to 10 ns. Assuming that X always changes at the same time as the falling edge of the clock, what is the maximum setup and hold time specifications that the flip-flop can have and still maintain proper operation of the network?



For both the setup time and hold time, there are two paths to consider, one from X to the D input of the flip-flop and the other from Q to the D input of the flip-flop. From the timing diagram, $t_{ck} = 40$ ns, $t_x = 20$ ns and $t_y = 20$ ns, where t_{ck} is the clock period, t_x is the time from a change on X to the active edge of the clock and t_y is the time from the active edge of the clock to a change on X. The following equations apply: For Q: (1) $t_{ck} \geq t_{pdmax} + t_{cmax} + t_{su}$, (2) $t_h \geq t_{pdmin} + t_{cmin}$

For X: (3) $t_x \geq t_{su} + t_{cmax}$, (4) $t_h \geq t_y + t_{cmin}$

where t_{pd} is the propagation delay through the flip-flop and t_c is the propagation delay through the combinational circuit (PLA)

So, for setup,

- (1) $40 \text{ ns} \geq 10 \text{ ns} + 10 \text{ ns} + t_{su}$, $t_{su} \leq 20 \text{ ns}$
(3) $20 \text{ ns} \geq t_{su} + 10 \text{ ns}$, $t_{su} \leq 10 \text{ ns}$

So, for hold,

- (2) $t_h \geq 5 \text{ ns} + 5 \text{ ns}$, $t_h \geq 10 \text{ ns}$
(4) $t_h \geq 20 \text{ ns} + 5 \text{ ns}$, $t_h \geq 25 \text{ ns}$

For both the setup and the hold times to be always satisfied, we must take the smaller numbers so
 $t_{su} = t_h = 10 \text{ ns}$

2. (10 points) Write a short VHDL description of a 4-to-1 multiplexer using a VHDL process.

```
entity MUX4_1 is
  port (I3, I2, I1, I0, S1, S0 : in bit;
        F : out bit);
end MUX4_1;
architecture MUX4_1of MUX4_1 is
begin
  process (I3, I2, I1, I0, S1, S0)
  begin
    if (S1 = '0' and S0 = '0') then
      F <= I0;
    elsif (S1 = '0' and S0 = '1') then
      F <= I1;
    elsif (S1 = '1' and S0 = '0') then
      F <= I2;
    else
      F <= I3;
    end if;
  end process;
end MUX4_1;
```

3. (15 points) For the following VHDL, assume that A changes to '1' at 5 ns. Give the values of A, B, C, D, E, and F each time a change occurs. Carry this out until no further change occurs. I

```

entity prob is
  port (D : inout bit);
end prob;

architecture PROB of PROB is
  signal A, B, C, E, F : bit;
begin
  P1: process (A, C)
  begin
    B <= A after 3 ns;
    E <= C after 5 ns;
  end process P1;
  C1: C <= A after 10 ns;
  P2: process (C, E)
  begin
    F <= C and E after 4 ns;
  end process P2;
  C2: D <= A or B or C or F after 1 ns;
end PROB;

```

Time	A	B	C	D	E	F
0 ns	0	0	0	0	0	0
5 ns	1	0	0	0	0	0
6 ns	1	0	0	0	0	0
8 ns	1	1	0	1	0	0
15 ns	1	1	1	1	0	0
20 ns	1	1	1	1	1	0
24 ns	1	1	1	1	1	1

Time	Event	Process Triggered	Scheduled Transaction	Event?
5 ns	A → '1'	P1	B '1' 8 ns	Yes
		P1	E '0' 10 ns	No
		C1	C '1' 15 ns	Yes
		C2	D '1' 6 ns	Yes
6 ns	D → '1'	none		
8 ns	B → '1'	C2	D '1' 9 ns	No
15 ns	C → '1'	P1	B '1' 18 ns	No
		P1	E '1' 20 ns	Yes
		P2	F '0' 19 ns	No
		C2	D '1' 16 ns	No
20 ns	E → '1'	P2	F '1' 24 ns	Yes
24 ns	F → '1'	C2	D '1' 25 ns	No

4. (5 points) Obtain a minimum product of sums expression for the following function:
 $f(A, B, C, D) = \Pi M(0, 1, 2, 4, 5, 8, 9, 10)$

		C	
A	B	0	1
		0	1
	1	1	
	0	0	
		D	


$$\begin{aligned}
 f' &= (B'C' + A'C' + B'D')' \\
 &= (B'C')'(A'C')'(B'D') \\
 &= (B + C)(A + C)(B + D)
 \end{aligned}$$

5. (15 points) A Mealy sequence detector detects a sequence of four consecutive 1 inputs. The detector has a single binary input, X, and a single binary output, Z. Signal Z should be logic 1 if and only if the last four inputs were all logic 1. Here is an example input-output sequence:

X 010111111101101011110
Z 000000111100000000010


Derive a Mealy state graph and table with a minimum number of states for this sequence detector

Present State	Next State		Output	
	X = 0	X = 1	X = 0	X = 1
S0	S0	S1	0	0
S1	S0	S2	0	0
S2	S0	S3	0	0
S3	S0	S3	0	1

 

6. (10 points) For the following Ft, find all static-1 hazards. For each hazard, specify the values of the input variables and which variable is changing when the hazard occurs.

$$F_t = ab' + ac' + bb' + bc' + a'd'$$

 

For hazard 1, a is changing and bcd = 000
For hazard 2, a is changing and bcd = 010

7. (10 points) Reduce the following state table to a minimum number of states. Show all your work in determining the state equivalents

Present State	Next State		Output
	X = 0	X = 1	
A	I	C	1
B	B	I	1
C	C	G	1
D	I	C	0
E	D	E	0
F	I	C	0
G	E	F	0
H	H	A	1
I	A	C	1

Present State	Next State		Output
	X = 0	X = 1	
A	A	C	1
B	B	A	1
C	C	G	1
D	A	C	0
E	D	E	0
G	E	D	0

B	I=B C=I							
C	I=C C=G	I=G						
D								
E				I=D C=E				
F					D=E I=C			
G						I=E C=F		
H	I=H C=A	I=A	A=G				E=H F=A	
I	I=A	A=B C=I	A=C C=G				E=A F=C	H=A A=C
	A	B	C	D	E	F	G	H

B	I=B C=I							
C	I=C C=G	I=G						
D								
E				I=D C=E				
F					D=E I=C			
G						I=E C=F		
H	I=H C=A	I=A	A=G				E=H F=A	
I	I=A	A=B C=I	A=C C=G				E=A F=C	H=A A=C
	A	B	C	D	E	F	G	H


B	I=B C=I							
C	I=C C=G	I=G						
D								
E				I=D C=E				
F					D=E I=C			
G						I=E C=F		
H	I=H C=A	I=A	A=G				E=H F=A	
I	I=A	A=B C=I	A=C C=G				E=A F=C	H=A A=C
	A	B	C	D	E	F	G	H

8. (5 points) Write out the truth table for the following equation.

$$F = (A \bullet B') + C$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

 9. (5 points) Draw a timing diagram that illustrates the difference between a D flip-flop and a D latch.



10. (1 point) __Synchronous__ design is a technique that uses a clock to coordinate the operation of all flip-flops, registers and counters in the system.
11. (1 point) The value of a __variable__ changes instantaneously in VHDL
12. (1 point) A process with a sensitivity list is activated whenever _an event occurs on any signal_ __in the sensitivity list__.
13. (1 point) VHDL is case-sensitive (True/False) __False__
14. (1 point) __Sequential__ networks commonly use flip-flops as storage devices.
15. (10 points) Draw the state diagram for the following state machine. Is it a Moore machine or a Mealy machine?

```

ENTITY state_machine IS
  PORT (sig_in ; IN BIT; clk : IN BIT;
        sig_out : OUT BIT);
END state_machine;


ARCHITECTURE state_machine OF state_machine IS
  TYPE state_type IS (a, b, c, d, e);
  SIGNAL current_state, next_state : state_type;
BEGIN
  PROCESS (sig_in, current_state)
  BEGIN
    sig_out <= '0'; next_state <= b;
    CASE current_state
    WHEN a =>
      IF sig_in = '0' THEN next_state <= e; sig_out <= '1';
      ELSE next_state <= d;
      END IF;
    WHEN b =>
      IF sig_in = '0' THEN next_state <= b;
      ELSE next_state <= d; sig_out <= '1';
      END IF;
    WHEN c =>
      IF sig_in = '1' THEN next_state <= a;
  
```

```


    ELSE next_state <= d;
  END IF;
  WHEN d =>
    IF sig_in = '0' THEN next_state <= e;
    END IF;
  WHEN e =>
    IF sig_in = '1' THEN next_state <= a;
    END IF;
  END CASE;
END PROCESS;
PROCESS (clk)
BEGIN
  IF (clk'EVENT AND clk = '1') THEN
    current_state <= next_state;
  END IF;
END PROCESS;
END state_machine;

```

Mealy

 

 Extra Credit (5 points): Rework problem 6 using a Moore machine.



Present State	Next State		Output
	X = 0	X = 1	
S0	S0	S1	0
S1	S0	S2	0
S2	S0	S3	0
S3	S0	S4	0
S4	S0	S4	1