

The University of Alabama in Huntsville
Electrical & Computer Engineering Department
CPE 426 01
Final Exam Solution

1. (12 points) Modify the following VHDL model to use process(es) instead of blocks.

```
use WORK.TSL.all,WORK.SYS.all;
entity I8212 is
  generic (GDEL,FFDEL,BUFDEL: TIME);
  port (DI: in WORD;
        DO: out WORD;
        NDS1,DS2,MD,STB,NCLR: in BIT;
        NINT: out BIT := '1');
end I8212;

architecture BEHAVIOR of I8212 is
begin
  I8212_BLK: block
    signal S0,S1,S2,S3,S4: BIT;
    signal SRQ: BIT;
    signal Q: WORD;
  begin
    INT_BLK:
    block (S1='1' and S4='1')
    begin
      Q <= guarded DI after FFDEL;
      Q <="00000000" after FFDEL when (S1='0' and S4='0') else
        Q;
      DO <= Q after BUFDEL when (S3 = '1') else
        "ZZZZZZZZ" after BUFDEL;
    end block INT_BLK;

    S0 <= not NDS1 and DS2 after GDEL;
    S1 <= (S0 and MD) or (STB and not MD) after (2*GDEL);
    S2 <= (S0 nor (not S4)) after GDEL;
    S3 <= (S0 or MD) after GDEL;
    S4 <= (S1 OR NCLR) after GDEL;
    SRQ <= '1' after FFDEL when (S2= '0') else
      '0' after FFDEL when (S2= '1') and (not STB'STABLE) and (STB='0') else
      SRQ;
    NINT <= not SRQ nor S0 after GDEL;
  end block I8212_BLK;
end BEHAVIOR;
```

Solution:

```
use WORK.TSL.all,WORK.SYS.all;
entity I8212 is
  generic (GDEL,FFDEL,BUFDEL: TIME);
  port (DI: in WORD;
        DO: out WORD;
        NDS1,DS2,MD,STB,NCLR: in BIT;
        NINT: out BIT := '1');
end I8212;
```

```

architecture BEHAVIOR of I8212 is
    signal S0,S1,S2,S3,S4: BIT;
    signal SRQ: BIT;
    signal Q: WORD;
begin
    process (S1, S4, DI, S3, Q)
    begin
        if (S1 = '1' and S4 = '1') then
            Q <= DI after FFDEL;
        elsif (S1 = '0' and S4 = '0') then
            Q <="00000000" after FFDEL;
        end if;
        if (S3 = '1') then
            DO <= Q after BUFDEL;
        else
            DO <= "ZZZZZZZZ" after BUFDEL;
        end if;
    end process;
    S0 <= not NDS1 and DS2 after GDEL;
    S1 <= (S0 and MD) or (STB and not MD) after (2*GDEL);
    S2 <= (S0 nor (not S4)) after GDEL;
    S3 <= (S0 or MD) after GDEL;
    S4 <= (S1 OR NCLR) after GDEL;
    SRQ <= '1' after FFDEL when (S2= '0') else
        '0' after FFDEL when (S2= '1') and (not STB'STABLE) and (STB='0') else
        SRQ;
    NINT <= not SRQ nor S0 after GDEL;
end BEHAVIOR;

```

2. (5 points) What kind of hardware element will be inferred by a synthesis tool from the following model?

Solution: A latch, since the behavior is level sensitive.


```

library ieee;
use ieee.std_logic_1164.all;
entity WIDGET is
    Port (A, B : in SIGNED (0 to 2);
          CLK, RESET : in std_logic;
          Z : out SIGNED(0 to 2));
end WIDGET;
architecture EXAMPLE of WIDGET is
begin
    process (CLK, RESET)
    begin
        if (RESET = '1' then)
            Z <= '0';
        elsif (CLK = '1') then
            Z <= A nor B;
        end if;
    end process;
end EXAMPLE;

```

3. (5 points) Draw the transistor-level diagram of a CMOS inverter.

Solution:

 


Consider the following VHDL code:

```
-----  
-- Entity declaration  
-----  
  
entity SCHED2 is  
    port (A, B, C, D, E, F: in INTEGER;  
          CLK : in BIT;  
          W, X, Y: out INTEGER);  
end SCHED2;  
  
-----  
-- Architecture declaration  
-----  
  
architecture HIGH_LEVEL of SCHED2 is  
    signal Z: INTEGER;  
begin  
    X <= (A - B) * Z;  
    Y <= (A * B) + Z;  
    Z <= (C * D) + D * (E + F);  
end HIGH_LEVEL;
```

4. (18 points) The following tasks refer to the VHDL code above. Assume that there are no hardware constraints.


a. (6 points) Draw a data flow graph.

Solution:

 

b. (6 points) Derive an ASAP schedule.

Solution:

 


Ready
 {1, 2, 3, 4}
 {5}
 {6}
 {7, 8}

Schedule
 {1, 2, 3, 4}
 {5}
 {6}
 {7, 8}

Solution:

c. (6 points) Derive an ALAP schedule.

Solution:

 


Ready
 {7, 8}
 {1, 4, 6}
 {2, 5}
 {3}

Schedule
 {7, 8}
 {1, 4, 6}
 {2, 5}
 {3}

5. (10 points) Derive a list schedule using the critical path priority metric for the VHDL code above, using the following hardware constraint; all operations are done in an ALU module and there are two ALU modules available.

Solution:

Op	Length
1	2
2	3
3	4
4	2
5	3
6	2
7	1
8	1

 

List {3, 2, 5, 1, 4, 6, 7, 8}	
Ready	Schedule
{1, 2, 3, 4}	{3, 2}
{1, 4, 5}	{1, 5}
{4, 6}	{4, 6}
{7, 8}	{7, 8}

6. (10 points) For the data lifetime chart shown, use the left edge algorithm to obtain an efficient register allocation.

	A	B	C	D	E	F	G	H	I	J	K	L
S1			X	X			X					
S2		X	X		X		X			X		
S3		X				X	X	X		X		
S4	X	X				X			X			X
S5	X					X			X		X	X


Solution:

	D	C	G	E	J	B	H	F	A	I	L	K
S1	X	X	X									
S2		X	X	X	X	X						
S3			X		X	X	X	X				
S4						X		X	X	X	X	
S5								X	X	X	X	X

	R1	R2	R3	R4	R5
S1	D	C	G	--	--
S2	E	C	G	J	B
S3	H	F	G	J	B
S4	A	F	I	L	B
S5	A	F	I	L	K

7. (1 point) ____Synthesis_____ is the process of transforming a behavioral description into a structural gate-level circuit.

 8. (18. points) Design a Moore state machine in VHDL which converts NRZ (non-return-to-zero) coding to Manchester coding. In NRZ coding, each bit is transmitted for one bit time without any change. For the Manchester code, a 0 is transmitted as 0 for the first half of the bit time and 1 for the second half, but a 1 is transmitted as 1 for the first half and 0 for the second half. In order to do this conversion, use a clock(CLOCK2) that is twice the frequency of the basic clock. Note that if the NRZ bit is 0, it will be 0 for two CLOCK2 periods. Similarly, if the NRZ bit is 1, it will be 1 for two CLOCK2 periods. Your design should have an active low synchronous reset and work with CLOCK2.



Solution:

```
entity NRZ2MAN is
    port (NRZ, CLOCK2, RESET : in BIT;
          MAN : out BIT);
end NRZ2MAN;

architecture BEHAVE of NRZ2MAN is
    type STATE_TYPE is (S0, S1, S2, S3);
    signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
begin
    process (CURRENT_STATE)
    begin
        case CURRENT_STATE is
            when S0 => if (NRZ = '0') then
                NEXT_STATE <= S1;
            else
                NEXT_STATE <= S3;
            end if;
            when S1 => NEXT_STATE <= S2;
            when S2 => if NRZ = '0' then
                NEXT_STATE <= S1;
            else
                NEXT_STATE <= S3;
            end if;
            when S3 => NEXT_STATE <= S0;
            when OTHERS => NEXT_STATE <= S0;
        end case;
    end process;
    process (RESET, CLOCK2)
    begin
        if (CLOCK2'EVENT and CLOCK2 = '1') then
            if (RESET = '0') then
                CURRENT_STATE <= S0;
            else
                CURRENT_STATE <= NEXT_STATE;
            end if;
        end if;
    end process;
end architecture;
```

```

        end if;
    end process;
    process (CURRENT_STATE)
    begin
        case CURRENT_STATE is
            when S0 | S1 => MAN <= '0';
            when S2 | S3 => MAN <= '1';
            when OTHERS => MAN <= '0';
        end case;
    end process;
end BEHAVE;

```

9. (12 points) Write a VHDL entity and architecture of a two-input AND gate with the generics, TPLH and

Solution:

```

entity AND2 is
    generic (TPLH, TPHL : time);
    port (I1, I2 : in BIT;
          O : out BIT);
end AND2;
architecture BEHAVE of AND2 is
begin
    process (I1, I2)
        variable O_INT, LAST : BIT;
    begin
        O_INT := I1 and I2;
        if (LAST = '0' and O_INT = '1') then
            O <= '1' after TPLH;
        elsif (LAST = '1' and O_INT = '0') then
            O <= '0' after TPHL;
        end if;
        LAST := O_INT;
    end process;
end BEHAVE;

```

10. (5 points) If the NRE costs for FPGA and CBIC circuits are \$21,000 and \$187,000, respectively, and the cost of individual parts for FPGA and CBIC circuits are \$18 and \$5, respectively, what is the break-even manufacturing volume for these two types of circuits?

Solution:

x — the number of units

$$18x + 21,000 = 5x + 187,000$$

$$13x = 166,000$$

$$x = 12769$$

11. (1 point) A(n) ASIC is an integrated circuit produced for a specific application and produced in relatively small volumes.

12. (1 point) ____VHDL_____ is an annoyingly strongly typed language.

13. (1 point) ____Flattening_____ removes the hierarchy in a circuit, so the circuit has a single level.

14. (1 point) ____Communication_____ is the hardest problem.