The University of Alabama in Huntsville ECE Department CPE 426 01 Final Exam April 29, 2004

Name: _____

Posting Code: _____

1. (7 points) Draw the transistor-level diagram of a CMOS two-input NOR gate.

2. (10 points) Write a VHDL entity (3 points) and architecture (7 points) of a two-input OR gate with the generics, TPLH and TPHL, which reflect the time for the output to make a low to high or high to low transition, respectively.

3. (1 point) ______ is the process of making the connections between standard cells.

4. (5 points) If the NRE costs for FPGA and CBIC circuits are \$21,000 and \$187,000, respectively, and the cost of individual parts for FPGA and CBIC circuits are \$15 and \$7, respectively, what is the breakeven manufacturing volume for these two types of circuits?

5. (5 points) What kind of hardware element will be inferred by a synthesis tool from the following model?

```
library ieee;
use ieee.std_logic_1164.all;
entity WIDGET is
 Port (A, B : in SIGNED (0 to 2);
       CLK, RESET : in std_logic;
        Z : out SIGNED(0 to 2));
end WIDGET;
architecture EXAMPLE of WIDGET is
begin
 process (CLK, RESET)
 begin
    if (CLK'event and CLK = '1') then
      if (RESET = 1') then
        Z <= `0';
      else
       Z <= A nor B;
      end if;
   end if;
  end process;
end EXAMPLE;
```

6. (10 points) For the data lifetime chart shown, use the left edge algorithm to obtain an efficient register allocation.

	Α	В	С	D	Е	F	G	Η	Ι	J	Κ	L
S 1			Х	Х			Х					
S2		Х	Х				Х			Х		
S 3		Х				Х	Х		Х	Х	Х	
S 4	Х	Х				Х			Х		Х	Х
S 5	Х				Х	Х		Х	Х		Х	Х
S 6	Х				Х			Х	Х			Х
S 7					Х				Х			Х

7. (1 point) Typically, a ______ is developed to validate a VHDL behavioral model.

8. (1 point) A(n) ______ provides the gate-level circuit with accurate timing backannotated from the layout.

9. (1 point) ______ are inserted into VHDL models to give instructions to synthesis or other tools.

10. (18 points) Create a VHDL entity named en_dec_{328} that represents a 3-to-8 decoder with an active-low enable input which has an architecture which uses a case statement to represent the functionality of the decoder. Create a second entity and its accompanying architecture that represents a 4-to-16 decoder by using two instances of the en_dec_{328} entity.

11. (15 points) Modify the following VHDL model to use block(s) instead of processes.

```
library ieee;
use ieee.std logic 1164.all;
entity BUFF_REG is
generic (STRB DEL, EN DEL, ODEL: TIME);
port (DI: in std_logic_vector (1 to 8);
        DS1, NDS2, STRB : in std_logic;
       DO: out std logic vector (1 to 8));
end BUFF REG;
architecture THREE PROC of BUFF REG is
  signal REG : std_logic_vector (1 to 8);
  signal ENBLD : std logic;
begin
  PREG: process (STRB)
  begin
    if (STRB = '1') then
     REG <= DI after STRB DEL;
    end if;
  end process PREG;
  ENABLE : process (DS1, NDS2)
  begin
    ENBLD <= DS1 and not NDS2 after EN DEL;
  end process ENABLE;
  OUTPUT : process (REG, ENBLD)
 begin
    if (ENBLD = '1') then
      DO <= REG after ODEL;
    else
      DO <= "ZZZZZZZZ" after ODEL;
    end if;
  end process OUTPUT;
end THREE PROC;
```

Consider the following VHDL code:

_____ -- Entity declaration _____ entity SCHED2 is port (A, B, C, D, E, F: in INTEGER; CLK : in BIT; W, X, Y: out INTEGER); end SCHED2; _____ -- Architecture declaration _____ architecture HIGH_LEVEL of SCHED2 is signal Z: INTEGER; begin X <= (A - B) * Z;Y <= (A * B) + Z; Z <= (C * D) + D * (E + F);W <= A/F + C*C + D* (A - B);end HIGH_LEVEL;

12. (14 points) The following tasks refer to the VHDL code above. Assume that there are no hardware constraints..

- a. (7 points) Derive an ASAP schedule.
- b. (7 points) Derive an ALAP schedule.

13. (10 points) Derive a list schedule using the critical path priority metric for the VHDL code above, using the following hardware constraint; all operations are done in an ALU module and there are two ALU modules available.

14. (1 point) ______ is one algorithmic-level synthesis task.

15. (1 point) ______ is the hardest problem.