

CPE 426 Spring 2004 Midterm Solutions:

1.

```
package LOGIC_PKG is
  component AND2_OP
    port (A, B : in BIT; Z : out BIT);
  end component;
  component NAND2_OP
    port (A, B : in BIT; Z : out BIT);
  end component;
  component OR4_OP
    port (A, B, C, D : in BIT; Z : out BIT);
  end component;
end LOGIC_PKG;

use work.LOGIC_PKG.ALL;

entity EXPRESSION is
  port (A, B, C, D : in BIT;
        F : out BIT);
end EXPRESSION;

architecture STRUCTURAL of EXPRESSION is
  signal temp : bit_vector (0 to 7);
begin
  U1 : NAND2_OP port map (A, A, TEMP(0));
  U2 : NAND2_OP port map (B, B, TEMP(1));
  U3 : NAND2_OP port map (C, C, TEMP(2));
  U4 : AND2_OP port map (TEMP(0), TEMP(1), TEMP(2));
  U5 : AND2_OP port map (TEMP(2), C, TEMP(3));
  U6 : AND2_OP port map (TEMP(3), D, TEMP(4));
  U7 : AND2_OP port map (A, B, TEMP(5));
  U8 : AND2_OP port map (TEMP(5), C, TEMP(6));
  U9 : AND2_OP port map (TEMP(1), TEMP(2), TEMP(7));
  U10 : OR4_OP port map (TEMP(4), TEMP(6), TEMP(7), '0', F);
end STRUCTURAL;
```

2. A hardware description language is a high-level programming language with specialized constructs for modeling hardware.

3.

```
package MINE is
  function REVERSE(X : in bit_vector) return bit_vector;
end MINE;

package body MINE is
  function REVERSE(X : in bit_vector) return bit_vector is
    variable Y : bit_vector(X'range);
    variable low : integer;
    variable high : integer;
  begin
    if (X'left = X'low) then
      for i in 0 to X'length - 1 loop
        Y(X'low + X'length - i - 1) := X(i + X'low);
      end loop;
    else

```

```

        for i in 0 to X'length - 1 loop
            Y(X'low + i) := X(X'low + X'length - 1 - i);
        end loop;
    end if;
    return Y;
end REVERSE;
end MINE;

use work.MINE.all;
entity TEST_REVERSE is
end TEST_REVERSE;

architecture TWISTED of TEST_REVERSE is
    signal A : bit_vector(5 downto 0) := "111000";
    signal B : bit_vector(24 to 35) := "000110001101";
    signal C : bit_vector(40 downto 34) := "1111110";
    signal D : bit_vector(40 downto 35);
    signal E : bit_vector(0 to 11);
    signal F : bit_vector(0 to 6);
begin
    process
    begin
        wait for 10 ns;
        D <= REVERSE(A);
        E <= REVERSE(B);
        F <= REVERSE(C);
        wait;
    end process;
end TWISTED;

```

4. Inertial delay is the delay which represents gate delay in VHDL.

5. All statements inside of a block are concurrent.

6. For the following function call, which function will be called? A

VARIABLE a, b : INTEGER;

b := decrement (a);

(a) FUNCTION decrement (x : INTEGER) RETURN INTEGER;

(b) FUNCTION decrement (x : REAL) RETURN REAL;

7. An array is an aggregate type in VHDL.

8.

entity GRAY2BCD is

port (GRAY : in bit_vector(3 downto 0);

BCD : out bit_vector(3 downto 0));

end GRAY2BCD;

architecture CONCURRENT of GRAY2BCD is

begin

BCD <= "0000" when GRAY = "0000" else

"0001" when GRAY = "0001" else

"0010" when GRAY = "0011" else

"0011" when GRAY = "0010" else

"0100" when GRAY = "0110" else

"0101" when GRAY = "1110" else

```

        "0110" when GRAY = "1010" else
        "0111" when GRAY = "1011" else
        "1000" when GRAY = "1001" else
        "1001" when GRAY = "1000"; --else
    --      "1111";
end CONCURRENT;

```

9.

```

entity SMODEL is
    port
        (P1 : in BIT;
         P2 : out BIT;
         P3 : inout BIT);
end SMODEL;

```

```

architecture STRUCTURE of SMODEL is
    component UNIT
        port (C1, C2 : in BIT;
              C3 : out BIT);
    end component;
begin
    U1 : UNIT port map (C1 => P1, C2 => P3, C3=> P2);
end STRUCTURE;

```

```

architecture STRUCTURE_A of SMODEL is
    component UNIT
        port (C1, C2 : in BIT;
              C3 : out BIT);
    end component;
begin
    U2 : UNIT port map (C1 => P3, C2 => P1, C3=> P2);
end STRUCTURE_A;

```

10.

```

library ieee;
use ieee.std_logic_1164.all;

```

```

package TYPES is
    type MVL3 is ('Z', '0', '1');
    type SEASON_OF_YEAR is (SPRING, SUMMER, FALL, WINTER);
    type MONTH_NUMBER is range 1 to 12;
    type COST is range 0.0 to 1405.0;
    type HIGH_WORD is range 63 downto 32;
    type REG_32_HIGH is array HIGH_WORD of MVL3;
    type TABLE_3D is array (std_logic, std_logic, std_logic) of
std_logic;
end TYPES;

```

10. An entity X, when used in another entity, becomes a component in entity Y.

11. Boolean is an example of a built-in enumerated type.

12.

Present State	Next State		Output
	sig_in='0'	sig_in='1'	
a	a	d	1
b	b	c	0
c	d	a	1
d	e	b	0
e	b	c	0

This is a Moore machine, because the output depends only on the state.

13. Communication is the hardest problem.