 


**The University of Alabama in Huntsville**  
**ECE Department**  
**CPE 526 01**  
**Midterm Exam Solution**  
**March 2, 2006**

1. (15 points) A barrel shifter is a shift register in which the data can be shifted either by one bit position, as in a normal shift register, or by multiple positions. Design a four-bit barrel shifter that can shift to the right or left by 0, 1, 2, or 3 bits and has clear and parallel load capabilities. If DIR = '0', shift left, else shift right. The binary value of S1 and S0 dictate the amount of shift, for example S1S0 = 10 means shift by 2 bit positions.



(a) (4 points) Write an entity for the barrel shifter. (c) (11 points) Write an architecture for the barrel shifter

```
entity BARREL is
    port (D : in std_logic_vector(3 downto 0);
          CLK, LOAD, CLR, DIR : in std_logic;
          S : in std_logic_vector(1 downto 0);
          Q : out std_logic_vector(3 downto 0));
end BARREL;

architecture BARREL of BARREL is
    signal TEMP : std_logic_vector (3 downto 0);
begin
    process (CLK)
    begin
        if (CLK'event and CLK = '1') then
            if (CLR = '0') then TEMP <= "0000";
            elsif (LOAD = '1') then TEMP <= D;
            elsif (DIR = '0') then
                case S is
                    when "00" => TEMP <= TEMP;
                    when "01" => TEMP <= TEMP(2 downto 0) & '0';
                    when "10" => TEMP <= TEMP(1 downto 0) & "00";
                    when "11" => TEMP <= TEMP(0) & "000";
                    when others => TEMP <= TEMP;
                end case;
            else
                case S is
                    when "00" => TEMP <= TEMP;
                    when "01" => TEMP <= '0' & TEMP(3 downto 1);
                    when "10" => TEMP <= "00" & TEMP(3 downto 2);
                    when "11" => TEMP <= "000" & TEMP(3);
                    when others => TEMP <= TEMP;
                end case;
            end if;
        end if;
        Q <= TEMP;
    end process;
end BARREL;
```

2. (1 point) A function is a primary design unit. (True/False) \_\_False\_\_

3. (20 points). (a) (12 points) Write a VHDL function to compare two IEEE std\_logic\_vectors to see whether they are equal. Report an error if any bit in either vector is not '0', '1', or '-' (don't care), or if the lengths of the vectors are not the same. The function call should pass only the vectors. The function should return TRUE if the vectors are equal, else FALSE. When comparing the vectors, consider that '0' = '-' and '1' = '-'. Make no assumptions about the index range of the two vectors. (b) (8 points) Show an architecture that includes three calls to the function with the following properties. 1 - returns TRUE, 2 - returns FALSE and 3 - triggers an error message

```
package NEED_IT is
    function "=" (l, r : in std_logic_vector) return BOOLEAN;
end NEED_IT;

library ieee;
use ieee.std_logic_1164.all;

package body NEED_IT is
    function "=" (l, r : in std_logic_vector) return BOOLEAN is
        alias L_NEW : std_logic_vector(L'length - 1 downto 0) is L;
        alias R_NEW : std_logic_vector(R'length - 1 downto 0) is R;
        variable MATCH : BOOLEAN;
    begin
        assert (L'length = R'length)
        report "Vectors are not the same length"
        severity ERROR;
        MATCH := TRUE;
        for I in L_NEW'range loop
            if ((L_NEW(I) /= '0' and L_NEW(I) /= '1' and L_NEW(I) /= '-') or
                (R_NEW(I) /= '0' and R_NEW(I) /= '1' and R_NEW(I) /= '-')) then
                report "Vectors have illegal values"
                severity ERROR;
            end if;
            if (L_NEW(I) = '0') then
                if (R_NEW(I) /= '0' and R_NEW(I) /= '-') then
                    MATCH := FALSE;
                end if;
            elsif (L_NEW(I) = '1') then
                if (R_NEW(I) /= '1' and R_NEW(I) /= '-') then
                    MATCH := FALSE;
                end if;
            end if;
        end loop;
        return MATCH;
    end;
end NEED_IT;

use work.NEED_IT.all;
architecture TEST_EQUAL of TEST_EQUAL is
    signal EQUAL : BOOLEAN;
begin
    process
        variable A : std_logic_vector(8 downto 3) := "0-1011";
        variable B : std_logic_vector(93 downto 86) := "00000000";
        variable C : std_logic_vector(47 to 52) := "011--1";
        variable D : std_logic_vector(0 to 5) := "011-10";
    begin
        EQUAL <= A = B after 10 ns;
        EQUAL <= transport A = C after 20 ns;
        EQUAL <= transport A = D after 30 ns;
        wait;
    end process;
end TEST_EQUAL;
```

4. (1 point) A process may have both a sensitivity list and wait statements (True/False) \_\_\_False\_\_\_
5. (1 point) In order to specify edge behavior the \_\_\_'STABLE\_\_\_ attribute is used in concurrent statements.
6. (1 point) A \_\_\_configuration\_\_\_ binds an instantiated component to a library model
7. (8 points) Design a two-out-of-five code detector. The device receives as input a 5-bit parallel word. The detector output is a logic 1 for any code word that has exactly two 1's in it and is a logic 0, otherwise. (a) (2 points) Write a VHDL entity for the detector. (b) (6 points) Write a VHDL architecture for the detector.

```
entity TWO_OF_FIVE is
  port (I : in std_logic_vector(4 downto 0);
        O : out std_logic);
end TWO_OF_FIVE;

architecture BEHAV of TWO_OF_FIVE is
begin
  process(I)
    variable ONES_COUNT : integer range 0 to 5;
  begin
    ONES_COUNT := 0;
    for J in I'range loop
      if (I(J) = '1') then
        ONES_COUNT := ONES_COUNT + 1;
      end if;
    end loop;
    if (ONES_COUNT = 2) then
      O <= '1';
    else
      O <= '0';
    end if;
  end process;
end BEHAV;
```

8. (7 points) A clocked T flip-flop with synchronous CLEAR and PRESET operates in the following manner: At the falling edge of CLK,  $Q = '0'$  and  $QB = '1'$  if  $CLEAR = '1'$ ,  $Q = '0'$  and  $QB = '1'$  if  $PRESET = '1'$  and  $Q = \text{not } Q$  and  $QB = \text{not } QB$  if  $T = '1'$  and  $Q$  and  $QB$  remain unchanged if  $T = '0'$ . The delay associated with CLEAR and PRESET is TPCPQ, the delay associated with T is TPTQ. (a) (2 points) Write an entity for this flip-flop. (b) (5 points) Write an architecture for this flip-flop.

```
entity TFF is
    generic (TPCPQ, TPTQ : time);
    port (CLEAR, PRESET, CLK, T : in std_logic;
          Q, QB : out std_logic);
end TFF;

architecture BEHAV of TFF is
    signal TEMP : std_logic;
begin
    process(CLK)
    begin
        if (CLK = '0' and CLK'event) then
            if (CLEAR = '1') then
                TEMP <= '0' after TPCPQ;
            elsif (PRESET = '1') then
                TEMP <= '1' after TPCPQ;
            elsif (T = '1') then
                TEMP <= not TEMP after TPTQ;
            else
                TEMP <= TEMP;
            end if;
        end if;
    end process;
    Q <= TEMP;
    QB <= not TEMP;
end BEHAV;
```

9. (5 points) Consider the following structural VHDL model.

```
entity SMODEL is
    port
        (P1 : in BIT;
         P2 : out BIT;
         P3 : inout BIT);
end SMODEL;

architecture STRUCTURE of SMODEL is
    component UNIT
        port (C1, C2, : in BIT; C3 : out BIT);
    end component;

begin
    U1 : UNIT port map (C1 => P3, C2 => P1, C3 => P2);
end STRUCTURE;
```

- (a) (3 points) Complete the structural description by giving a legal set of port-to-port connections for entity ports P1, P2, and P3 and component ports C1, C2, and C3.
- (b) (2 points) Is there more than one possible set of legal port-to-port connections? Yes  
P1, P3, P2 or P3, P1, P2

10. (10 points) For the following VHDL, assume that A changes to '1' at 5 ns and back to '0' at 12 ns. Give the values of A, B, C, D, E, and F each time a change occurs. Carry this out until no further change occurs.

```
entity prob is
    port (D : inout bit);
end prob;

architecture PROB of PROB is
    signal A, B, C, E, F : bit;
begin
    P1: process (A, C)
    begin
        B <= A after 2 ns;
        E <= C after 7 ns;
    end process P1;
    C <= A and B after 6 ns;
    P2: process (C, E)
    begin
        F <= C and E after 4 ns;
    end process P2;
    D <= A or B or C or F;
end PROB;
```

Time	A	B	C	D	E	F
0 ns	0	0	0	0	0	0
5 ns	1	0	0	0	0	0
5+Δ ns	1	0	0	1	0	0
7 ns	1	1	0	1	0	0
12 ns	0	1	0	1	0	0
14 ns	0	0	0	1	0	0
14+Δ ns	0	0	0	0	0	0

Time	Activity	Triggered	Scheduled	Event?
5ns	A 0→1	P1	B '1' 7ns	Yes
			E '0' 12 ns	No
		C	C '0' 12 ns	No
		D	D '1' 5+Δ ns	Yes
5+Δ	D 0→1	None		
7	B 0→1	C	C '1' 13 ns	Yes
		D	D '1' 7+Δ ns	No
12	A 1→0	P1	B '0' 14 ns	Yes
			E '0' 19 ns	No
		C	C '0' 18 ns	Overwrites C '1' 13 ns, No
		D	D '1' 12+Δ ns	No
14	B 1→0	C	C '0' 20 ns	No
		D	D '0' 14+Δ ns	Yes
14+Δ	D 1→0	None		

11. (4 points) (a) (2 points) Specify a DAY\_OF\_WEEK enumeration data type. (b) (2 points) Write a variable declaration CURRENT\_DAY that has a value equal to the current day of the week.

```
package TRY is
    type DAY_OF_WEEK is (SU, MO, TU, WE, TH, FR, SA);
    variable CURRENT_DAY : DAY_OF_WEEK := TH;
end TRY;
```

12. (10 points) Design a 2 to 4 decoder with enable. All outputs are tristated when the enable input = '0'. When the enable input = '1', one of the four output D0, D1, D2, D3 is selected based on the binary value of the two select inputs S1 and S0. (a) (2 points) Write a VHDL entity. (b) (4 points) Use concurrent signal assignments to implement the architecture. (c) (4 points) Use sequential statements to implement the architecture. Include any necessary library references.

```
library ieee;
use ieee.std_logic_1164.all;

entity TWO_TO_FOUR is
```

```

    port (I : in std_logic_vector(1 downto 0);
          EN : in std_logic;
          O : out std_logic_vector(3 downto 0));
end TWO_TO_FOUR;

architecture CONCURRENT of TWO_TO_FOUR is
    signal TEMP : std_logic_vector(3 downto 0);
begin
    with I select
        TEMP <= "0001" when "00",
                "0010" when "01",
                "0100" when "10",
                "1000" when "11",
                "0000" when others;
    O <= TEMP when EN = '1' else
        "ZZZZ";
end CONCURRENT;

architecture SEQUENTIAL of TWO_TO_FOUR is
begin
    process(I)
        variable TEMP : std_logic_vector(3 downto 0);
    begin
        case I is
            when "00" => TEMP := "0001";
            when "01" => TEMP := "0010";
            when "10" => TEMP := "0100";
            when "11" => TEMP := "1000";
            when others => TEMP := "0000";
        end case;
        if (EN = '1') then
            O <= TEMP;
        else
            O <= "ZZZZ";
        end if;
    end process;
end SEQUENTIAL;

```

13. (1 points) \_\_\_Communication\_\_\_ is the hardest problem.

14. (6 points) (a) (4 points) Write a declaration of a record data type, PERSONNEL, with fields for last name (LAST) (up to twenty characters); first name (FIRST) (up to twenty characters); middle initial (MID); and social security number (SOC\_SEC). (b) (2 points) Write a declaration for a constant MY\_PERSONNEL\_RECORD that defines your own data, consistent with type PERSONNEL.

```

package MINE is
    type PERSONNEL is record
        LAST : string(20 downto 1);
        FIRST : string(20 downto 1);
        MID : character;
        SOC_SEC : integer range 0 to 999999999;
    end record;
    constant MY_PERSONNEL_RECORD : PERSONNEL
        := ("Gaede", "Rhonda", 'K', 999274819);
end MINE;

```

15. (10 points) Draw the state diagram for the following state machine. Is it a Moore machine or a Mealy machine?

```
ENTITY state_machine IS
    PORT (sig_in ; IN BIT; clk : IN
    BIT;
        sig_out : OUT BIT);
END state_machine;
```

```
ARCHITECTURE state_machine OF
    state_machine IS
        TYPE state_type IS (a, b, c, d, e);
        SIGNAL current_state, next_state :
        state_type;
    BEGIN
        PROCESS (sig_in, current_state)
        BEGIN
            sig_out <= '0';
            next_state <= e;
            CASE current_state
            WHEN a =>
                IF sig_in = '0' THEN
                    next_state <= a;
                    sig_out <= '1';
                ELSE
                    next_state <= d;
                END IF;
            WHEN b =>
                IF sig_in = '0' THEN
                    next_state <= b;
                ELSE
                    next_state <= c;
                    sig_out <= '1';
                END IF;
            WHEN c =>
                IF sig_in = '1' THEN
                    sig_out <= '1';
                    next_state <= a;
                ELSE
                    next_state <= e;
                END IF;
            WHEN d =>
                IF sig_in = '0' THEN
                    sig_out <= '1';
                    next_state <= e;
                END IF;
            WHEN e =>
                IF sig_in = '1' THEN
                    next_state <= c;
                END IF;
            END CASE;
        END PROCESS;
        PROCESS (clk)
        BEGIN
            IF (clk'EVENT AND clk = '1') THEN
                current_state <= next_state;
            END IF;
        END PROCESS;
    END state_machine;
```

