

The University of Alabama in Huntsville
ECE Department
CPE 426 01
Midterm Exam Solution
Spring 2009

1. (15 points) (a) (4 points) Create a VHDL entity named 32_bit_adder.(b) (11 points) Create a VHDL architecture representing a structural model of the 32 bit adder using as many 8_bit_adder components as are needed. You do not need to write an entity or an architecture for 8_bit_adder. You may also assume that a component has already been declared and that no configuration statement is required.

```
library ieee;
use ieee.std_logic_1164.all;

entity ADDER_32_BIT is
    port (A, B : in std_logic_vector(31 downto 0);
          CIN : in std_logic;
          COUT : out std_logic;
          C : out std_logic_vector(31 downto 0));
end ADDER_32_BIT;

architecture EXAMPLE of ADDER_32_BIT is
    component ADDER_8_BIT is
        port (A, B : in std_logic_vector(7 downto 0);
              CIN : in std_logic;
              COUT : out std_logic;
              C : out std_logic_vector(7 downto 0));
    end component;
    signal CARRY : std_logic_vector(2 downto 0);
begin
    U0: ADDER_8_BIT
        port map (A => A(7 downto 0), B => B(7 downto 0),
                  C => C(7 downto 0), CIN => CIN,
                  COUT => CARRY(0));
    U1: ADDER_8_BIT
        port map (A => A(15 downto 8), B => B(15 downto 8),
                  C => C(15 downto 8), CIN => CARRY(0),
                  COUT => CARRY(1));
    U2: ADDER_8_BIT
        port map (A => A(23 downto 16), B => B(23 downto 16),
                  C => C(23 downto 16), CIN => CARRY(1),
                  COUT => CARRY(2));
    U3: ADDER_8_BIT
        port map (A => A(31 downto 24), B => B(31 downto 24),
                  C => C(31 downto 24), CIN => CARRY(2),
                  COUT => COUT);
end EXAMPLE;
```

2. (1 point) _False_ (True/False) There is no difference between CLK'event and not CLK'stable.
3. (1 point) _True_ (True/False) Operators may be overloaded in VHDL.
4. (1 point) _Transport_ delay is the delay which represents wire delay in VHDL.
5. (1 point) _False_ (True/False) Functions are primary design units.

6. (20 points) (a) (12 points) Write a VHDL function that takes two `std_logic_vectors`. The function searches the first argument to see whether the second argument appears as a subvector of the first. If the second argument is found, the function returns the bit position of the first match, otherwise it returns -1. You may assume that both arguments have the form `std_logic_vector(x'length-1 downto 0)` where `x` is the name of the argument. Output an error if the length of the second argument exceeds that of the first. (b)(8 points) Show an architecture that includes three calls to the function with the following properties. 1 - returns a value, 2 – triggers an error message, 3 – returns -1.

```
library ieee;
use ieee.std_logic_1164.all;

package MINE is
  function SEARCH(VECTOR, SUBVECTOR : std_logic_vector) return integer;
end MINE;
package body MINE is
  function SEARCH(VECTOR, SUBVECTOR : std_logic_vector) return integer is
    variable POSITION : integer;
    variable FOUND : boolean := FALSE;
  begin
    POSITION := -1;
    if (VECTOR'length < SUBVECTOR'length) then
      report "Incorrect usage of SEARCH function"
        severity error;
      return POSITION;
    end if;
    for I in VECTOR'length - 1 downto SUBVECTOR'length - 1 loop
      if not FOUND then
        if (VECTOR(I downto I - (SUBVECTOR'length - 1)) = SUBVECTOR) then
          POSITION := I;
          FOUND := TRUE;
        end if;
      end if;
    end loop;
    return POSITION;
  end SEARCH;
end MINE;

use work.MINE.all;
library ieee;
use ieee.std_logic_1164.all;

entity TEST_SEARCH is
end TEST_SEARCH;
architecture TEST of TEST_SEARCH is
  signal A : std_logic_vector(2 downto 0) := "000";
  signal B : std_logic_vector(7 downto 0) := "11111111";
  signal C : std_logic_vector(32 downto 0) :=
    "1100101011110001111111111100101011";
  signal D, E, F : integer;
begin
  D <= SEARCH(C, A) after 1 ns;
  E <= SEARCH(B, A) after 2 ns;
  F <= SEARCH(A, B) after 3 ns;
end TEST;
```

7. (3 points) (a) (2 points) Specify a `CLASSIFICATION` enumeration data type that spells out the various classifications for undergraduate students.(b) (1 point) Write a signal declaration `MY_CLASS` that has a value equal to the rightmost element of the type.

```
type CLASSIFICATION is (FRESHMAN, SOPHOMORE, JUNIOR, SENIOR);
signal MY_CLASS : CLASSIFICATION := CLASSIFICATION'right;
```

8. (1 point) _b_ Multiple Choice: Which of the following cannot occur outside a process?
 (a) Signal Assignment (b) Variable Declaration (c) Signal Declaration
9. (4 points) (a) (3 points) Write a declaration of an array that can be used to hold the email addresses of the students in this class. (b) (1 point) Initialize the first element of this array with your email address.

```
type EMAILS_TYPE is array(0 to 15) of string(17 downto 1);
signal EMAILS : EMAILS_TYPE := (0 => "gaede@ece.uah.edu",
                                others => " ");
```

10. (18 points) Given the following VHDL, indicate all transactions and events. Give the values of A, B, C, D, E, and F each time a change occurs. Carry this out until no further change occurs.

```
entity prob is
  port (D : out bit);
end prob;

architecture PROB of PROB is
  signal A, B, C, E, F : bit;
begin
  process
    A <= '1' after 5 ns;
    wait;
  end process;
  P1: process (D, C)
  begin
    B <= D after 2 ns;
    E <= C after 7 ns;
  end process P1;
  C <= transport A or E
    after 6 ns;
  P2: process (C, E)
  begin
    F <= (C and E) after 4 ns;
  end process P2;
  D <= A xor B xor C after 1 ns;
end PROB;
```

Time	A	B	C	D	E	F
0 ns	0	0	0	0	0	0
5 ns	1	0	0	0	0	0
6 ns	1	0	0	1	0	0
8 ns	1	1	0	1	0	0
9 ns	1	1	0	0	0	0
11 ns	1	0	0	0	0	0
18 ns	1	0	0	0	1	0
22 ns	1	0	0	0	1	1

Time	Event	Processes Triggered	Scheduled Transactions	Event?
5 ns	A→1	C1	C '1' 11 ns	Y
		C2	D '1' 6 ns	Y
6 ns	D→1	P1	B '1' 8 ns	Y
		P1	E '0' 13 ns	N
8 ns	B→1	C2	D '0' 9 ns	Y
9 ns	D→0	P1	B '0' 11 ns	Y
		P1	E '0' 16 ns	N
11 ns	B→0	C2	D '0' 12 ns	N
	C→1	P1	B '0' 13 ns	N
		P1	E '1' 18 ns	Y
		P2	F '0' 15 ns	N
18 ns	E→1	C1	C '1' 24 ns	N
		P2	F '1' 22 ns	Y
22 ns	F→1	none		

11. (15 points) Design a new type of positive-edge-triggered flip-flop called the LH flip-flop. It has a clock C, a data input D, and a load input L. If, at the positive edge of C, L equals 1, then the data on D is stored in the flip-flop. If, at the positive edge of C, L equals 0, then the current stored value in the flip-flop is held. (a) (3 points) Write a VHDL entity. (b) (6 points) Use concurrent signal assignments to implement the architecture. (c) (6 points) Use sequential statements to implement the architecture. Include any necessary library references.

```
library ieee;
use ieee.std_logic_1164.all;

entity LHFF is
    port (C, L, D : in std_logic;
          Q, QB : out std_logic);
end LHFF;

architecture CON of LHFF is
    signal TEMP : std_logic;
begin
    A: block (not C'STABLE and C = '1')
        begin
            TEMP <= GUARDED D when (L = '1');
        end block A;
    Q <= TEMP;
    QB <= not TEMP;
end CON;

architecture SEQ of LHFF is
    signal TEMP : std_logic;
begin
    process(C)
    begin
        if (C'EVENT and C = '1') then
            if (L = '1') then
                TEMP <= D;
            end if;
        end if;
    end process;
    Q <= TEMP;
    QB <= not TEMP;
end SEQ;
```

12. (10 points) Draw the state diagram for the following state machine. Is it a Moore machine or a Mealy machine? Mealy

ENTITY state_machine **IS**

PORT (sig_in ; **IN** BIT; clk, rst : **IN** BIT;
sig_out : **OUT** BIT);

END state_machine;

ARCHITECTURE state_machine **OF** state_machine **IS**

TYPE state_type **IS** (a, b, c, d, e);

SIGNAL current_state, next_state : state_type;

BEGIN

PROCESS (sig_in, current_state)

BEGIN

sig_out <= '0';

next_state <= c;

CASE current_state

WHEN a =>

IF sig_in = '0' **THEN**

next_state <= c;

sig_out <= '1';

ELSE

next_state <= d;

END IF;

WHEN b =>

IF sig_in = '0' **THEN**

next_state <= b;

ELSE

next_state <= c;

END IF;

sig_out <= '1';

WHEN c =>

IF sig_in = '1' **THEN**

sig_out <= '1';

next_state <= a;

ELSE

next_state <= b;

END IF;

sig_out <= '1';

WHEN d =>

IF sig_in = '0' **THEN**

next_state <= e;

END IF;

WHEN e =>

IF sig_in = '1' **THEN**

next_state <= c;

END IF;

END CASE;

END PROCESS;

PROCESS (clk)

BEGIN

IF (rst = '0') **then**

current_state <= a;

ELSIF (clk'EVENT **AND** clk = '1') **THEN**

current_state <= next_state;

END IF;

END PROCESS;

END state_machine;

