

The University of Alabama in Huntsville
ECE Department
CPE 426 01
Final Exam
May 11, 2010

Name: _____

1. (6 points) Draw the transistor-level diagram of a CMOS AND gate.

2. (6 points) What is wrong with the following model of a 4-to-1 MUX? (It is not a syntax error.)

```
architecture mux_behavioral of 4to1mux is
  signal sel: integer range 0 to 3;
begin
  process(A, B, I0, I1, I2, I3)
  begin
    sel <= 0;
    if A = '1' then
      sel <= sel + 1;
    end if
    if B = '1' then
      sel <= sel + 2;
    end if;
    case sel is
      when 0 => F <= I0;
      when 1 => F <= I1;
      when 2 => F <= I2;
      when 3 => F <= I3;
    end case;
  end process
end mux_behavioral;
```

3. (18 points) A synchronous sequential circuit has one input and one output plus a synchronous reset which is active low. If the input sequence 1001 or 0101 occurs, an output of two successive 1s will occur. The first of these 1s should occur coincident with the last input of the 1001 or 0101 sequence. The network should reset when the second 1 output occurs. For example,

Input sequence: 01101100010010 1101010

Output sequence: 00000000000011 0000011

- a) (4 points) Write a VHDL entity for this circuit.
b) (14 points) Write a VHDL architecture for this circuit.

4. (4 points) List the four types of paths that must be considered when doing timing analysis of sequential circuits.

5. (1 point) _____ are primitives that are all the same height and varying widths.

6. (10 points) A synchronous (4-bit) up/down decade counter with outputs COUNT and CO works as follows: All state changes occur on the rising edge of the CLK input, except the asynchronous clear (CLR). When CLR = 0, the counter is reset regardless of the values of the other inputs. The inputs are DATA, CLR, LOAD, EN, UP.

If the LOAD input is 0, the data input D is loaded into the counter.

If LOAD = EN = UP = 1, the counter is incremented.

If LOAD = EN = 1, and UP = 0, the counter is decremented.

If LOAD = EN = UP = 1, the carry output (CO) = 1 when the counter is in state 9.

If LOAD = EN = 1 and UP = 0, the carry output (CO) = 1 when the counter is in state 0.

Create a SystemVerilog interface for this circuit that has a clocking block that defines directions relative to the test bench.

7. (20 points) a) (15 points) Write a VHDL model of a D flip-flop which has asynchronous Preset and Clear and which is negative edge triggered. Your model should have 6 generics, with default values of 5 ns, as listed in the table below. (Clear has priority over Reset)
- b) (5 points) Create an instantiation of the flip-flop which has the following timing specifications.

Parameter	From Input	To Output	Specification
TPLH	Preset	Q	16 ns
TPHL	Preset	Q	25 ns
TPLH	Clear	Q	13 ns
TPHL	Clear	Q	22 ns
TPLH	Clock	Q or Q'	11 ns
TPHL	Clock	Q or Q'	20 ns

8. (5 points) If the NRE costs for FPGA and ASIC circuits are \$35,000 and \$1,500,000, respectively, and the cost of individual parts for FPGA and ASIC circuits are \$45 and \$7, respectively, what is the break-even manufacturing volume for these two types of circuits?
9. (12 points) Write a procedure that accepts a `std_logic_vector` of arbitrary length and returns integers which represent the total number of '1's, the total number of '0's and the total number of 'Z's contained in the `std_logic_vector`.

10. (2 points) A _____ is similar to a class and contains cover points, options, formal arguments, and an optional trigger.
11. (2 points) _____ True or False? Having both designer and verifier create independent interpretations of the specification provides redundancy.
12. (4 points) _____ and _____ are two types of code coverage.

13. (6 points) What kind of hardware element will be inferred by a synthesis tool from the following model?

```
library ieee;
use ieee.std_logic_1164.all;

entity WIDGET is
  Port (A, B : in SIGNED (0 to 2);
        CLK, RESET : in std_logic;
        Z : out SIGNED(0 to 2));
end WIDGET;

architecture EXAMPLE of WIDGET is
begin
  process (CLK, RESET)
  begin
    if (CLK = '1' and CLK'EVENT) then
      if (RESET = '1') then
        Z <= '0';
      else
        Z <= A nor B;
      end if;
    end if;
  end process;
end EXAMPLE;
```

14. (2 points) _____(True or False) The SystemVerilog standard specifies the meaning of constraint expressions, the legal values that are created, and the precise order in which the solver should operate.
15. (2 points) Which of the following are true? _____ Multiple choice
- a. Verification starts with interpretation of the specification.
 - b. All testbenches share some common structure of stimulus generation and response checking.
 - c. The testbench simulates the design under test.
 - d. a and b
 - e. a, b and c