

The University of Alabama in Huntsville
ECE Department
CPE 426 01
Midterm Exam
February 25, 2016

Name: _____

1. (20 points) Write a VHDL function that accepts a `std_logic_vector` of arbitrary length and an integer that specifies the number of bits the `std_logic_vector` is to be rotated to the left and returns the rotated `std_logic_vector`. Issue an error message if the integer is greater than the length of the input. Make no assumptions about the range of the indices. For example:


Input: 0101111, 2
Output: 0111101

2. (10 points) . (6 points) Translate the following VHDL to two with-select-when statements:

```
case state is
  when idle => a <= "11"; b <= "00";
  when terminate | increase => a <= "01"; b <= "--";
  when maintain | decrease => a <= "10"; b <= "11";
  when others => a <= "11"; b <= "01";
end case;
```

3. (1 point) All statements inside of a process are _____.
4. (1 point) _____ is an example of an unconstrained array.
5. (1 point) _____ (True or False) Multiple assignments to a signal within a process can cause that signal to have multiple drivers.
6. (1 point) _____ (True or False) A process may have both a sensitivity list and wait statements
7. (1 point) _____ (True or False) Functions are primary design units.

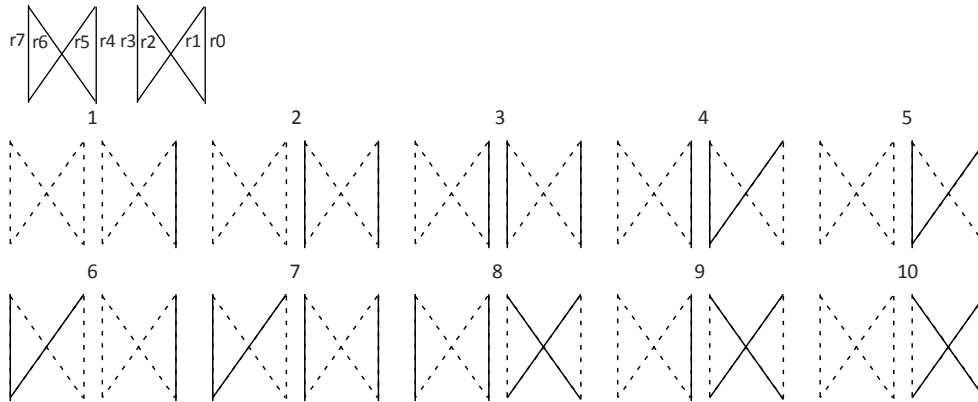
8. (15 points) Design a system which has as its inputs a number from 1 to 10 and provides as its outputs (eight of them) the signals to drive the following display. The inputs are labeled w, x, y, and z and are normal binary. The input combinations 0000, 1011, 1100, 1101, 1110, and 1111 will never occur; they are to be treated as don't cares. The display allows for the representation of Roman numerals (except that IIX is used to represent 8, whereas it is normally written as VIII). There are a total of eight segments in the display, labeled A through H, as shown. To light a segment, a 1 is placed on the appropriate display input (r7, r6, r5, r4, r3, r2, r1, r0). The following illustration shows all digits as they should be coded for each of these, with a lit segment represented by a bold line and an unlit segment represented by a dashed line.



Use the following entity

```
entity roman is
  port (d : in std_logic_vector (3 downto 0);
        r : out std_logic_vector (7 downto 0));
end entity roman;
```

 9. (20 points) A description of a 74194 4-bit bi-directional shift register follows: The CLRb input is asynchronous and active low and overrides all the other control inputs. All other state changes occur following the rising edge of the clock. If the control inputs $S1 = S0 = 1$, the register is loaded in parallel. If $S1 = 1$ and $S0 = 0$, the register is shifted right and SDR (serial data right) is shifted into Q3. If $S1 = 0$ and $S0 = 1$, the register is shifted left and SDL is shifted into Q0. If $S1 = S0 = 0$, no action occurs. Use 74194s to build an 8-bit bi-directional shift register that has 3 select lines. The operation of the register is specified by the table below.



```
entity shifter is
  port (x : in std_logic_vector (7 downto 0);
        y : out std_logic_vector (7 downto 0);
        r, l, clrb : in std_logic;
        clock : in std_logic;
        sel : in std_logic_vector (2 downto 0));
end entity shifter;
```

sel	Operation
000	No Change
001	Shift Left serial input
010	Shift Right, serial input
011	Load
100	No Change
101	Rotate Left
110	Rotate Right
111	Load Zeros

11. (10 points) Draw the state diagram for the following state machine. Is it a Moore machine or a Mealy machine?

```

library ieee;
use ieee.std_logic_1164.all;

entity ALARM is
  port (CLK, FS, MS, R, C : in std_logic;
        FM, MM : out std_logic);
end ALARM;

architecture SYNTH of ALARM is
  type STATE_TYPE is (S_init, S_wait, S_front,
                      S_motion, S_MM1, S_MM2);
  signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
begin
  process (CLK, R)
  begin
    if (R = '1') then
      CURRENT_STATE <= S_init;
    elsif (CLK'event and CLK = '1') then
      CURRENT_STATE <= NEXT_STATE;
    end if;
  end process;
  process (FS, MS, C, CURRENT_STATE)
  begin
    case CURRENT_STATE is
      when S_init => NEXT_STATE <= S_wait;
      when S_wait => if (FS = '1') then
        NEXT_STATE <= S_front;
      elsif (MS = '1') then
        NEXT_STATE <= S_motion;
      end if;
      when S_front => if (C = '1') then
        NEXT_STATE <= S_wait;
      else
        NEXT_STATE <= S_front;
      end if;
      when S_motion => NEXT_STATE <= S_MM1;
      when S_MM1 => NEXT_STATE <= S_MM2;
      when S_MM2 => NEXT_STATE <= S_wait;
    end case;
  end process;
  process (CURRENT_STATE)
  begin
    case CURRENT_STATE is
      when S_init | S_wait => FM <= '0'; MM <= '0';
      when S_front => FM <= '1'; MM <= '0';
      when S_motion => FM <= '0'; MM <= '1';
      when S_MM1 | S_MM2 => FM <= '0'; MM <= '1';
    end case;
  end process;
end SYNTH;

```