

The University of Alabama in Huntsville
ECE Department
CPE 526 01
Midterm Exam Solution
Spring 2020

1. (20 points)
- a. (12 points) Write a VHDL function that has inputs `vect` of type `std_logic_vector`, `sub` of type `std_logic_vector`, and `ins_pos` of type `natural`. You may assume that `vect` has the form `std_logic_vector(vect'length-1 downto 0)` and `sub` has the form `std_logic_vector(sub'length-1 downto 0)`. The function creates a new vector that is the size of `vect` plus `sub`. If `ins_pos = 0`, `sub` is appended to `vect` and if `ins_pos = 1`, `sub` is prepended to `vect`. Output an error if `ins_pos` doesn't equal 0 or 1.
- b. (8 points) Show an architecture that includes three calls to the function with the following properties. 1 – appends (inserts after), 2 – prepends (inserts before), 3 – triggers error message.

```

library ieee;
use ieee.std_logic_1164.all;
package needit is
    function pre_app(vect : in std_logic_vector; sub : in std_logic_vector;
                    ins_pos : in natural) return std_logic_vector;
end needit;
package body needit is
    function pre_app(vect : in std_logic_vector; sub : in std_logic_vector;
                    ins_pos : in natural)
        return std_logic_vector is
        variable result : std_logic_vector(vect'length + sub'length - 1 downto 0);
    begin
        if (ins_pos = 0) then
            result := vect & sub;
        elsif (ins_pos = 1) then
            result := sub & vect;
        else
            report "invalid value of ins_pos";
        end if;
        return result;
    end pre_app;
end package body needit;

use work.needit.all;
library ieee;
use ieee.std_logic_1164.all;
entity test_pre_app is
end test_pre_app;

architecture mine of test_pre_app is
begin
    process
        variable a : std_logic_vector(10 downto 0) := "00000011100";
        variable b : std_logic_vector(3 downto 0) := "0010";
        variable c : std_logic_vector(14 downto 0);
    begin
        c := pre_app(a, b, 0);
        wait for 10 ns;
        c := pre_app(a, b, 1);
        wait for 10 ns;
        c := pre_app(a, b, 2);
        wait;
    end process;
end mine;

```

2. (11 points) Modify the following VHDL model by adding an enable input. When enable = '0', the outputs are set to "ZZZZ" and as specified when enable = '1'. Further, translate the process into concurrent signal assignment statements that include the new functionality.

```
library ieee;
use ieee.std_logic_1164.all;

entity TWO_TO_4_DEC is
  generic (DEL: TIME);
  port (I: in  std_logic_vector(1 downto 0);
        EN : in std_logic;
        O: out std_logic_vector(3 downto 0));
end TWO_TO_4_DEC;
```

```
architecture ALG of TWO_TO_4_DEC is
begin
  process (I)
  begin
    if (EN = '0') then
      O <= "ZZZZ";
    elsif (EN = '1') then
      case I is
        when "00" => O <= "0001" after DEL;
        when "01" => O <= "0010" after DEL;
        when "10" => O <= "0100" after DEL;
        when "11" => O <= "1000" after DEL;
      end case;
    end if;
  end process;
end ALG;
```

```
library ieee;
use ieee.std_logic_1164.all;

entity TWO_TO_4_DEC is
  generic (DEL: TIME);
  port (I: in  std_logic_vector(1 downto 0);
        EN : in std_logic;
        O: out std_logic_vector(3 downto 0));
end TWO_TO_4_DEC;

architecture ALG of TWO_TO_4_DEC is
  signal O_INT : std_logic_vector(3 downto 0);
begin
  O_INT <= "0001" after DEL when I = "00" else
    "0010" after DEL when I = "01" else
    "0100" after DEL when I = "10" else
    "1000" after DEL when I = "11" else
    O_INT;
  O <= "ZZZZ" when EN = '0' else
    O_INT when EN = '1';
end ALG;
```

3. (15 points) Write a VHDL description for a D-type latch with an asynchronous active low reset, `r`, and an active high clock, `clk`. Create three generics – TPDQ, TPCQ and TPRQ which represent the propagation delay from `d`, `clk`, and `r`, respectively.

- a. (5 points) Write an entity using `std_logic` inputs and outputs.
b. (10 points) Write a behavioral architecture

```
library ieee;
use ieee.std_logic_1164.all;

entity DLATCH is
    generic (TPDQ, TPCQ, TPRQ : time);
    port (d, clk, r : in std_logic;
          q, qb : out std_logic);
end entity DLATCH;

architecture DLATCH of DLATCH is
    signal q_temp : std_logic;
begin
    process(d, clk, r)
    begin
        if (r = '0' and r'event) then
            q_temp <= '0' after TPRQ;
        elsif (clk = '1' and d'event) then
            q_temp <= d after TPDQ;
        elsif (clk = '1' and clk'event) then
            q_temp <= d after TPCQ;
        end if;
    end process;
    q <= q_temp;
    qb <= not q_temp;
end DLATCH;
```

4. (12 points) Construct an 8 bit ALU using two 4- bit ALUs (entity shown below).

- a. (4 points) Entity
b. (8 points) Architecture

```
library ieee;
use ieee.std_logic_1164.all;
entity ALU is
    generic (DEL: TIME);
    port (A,B: in std_logic_vector(3 downto 0); CI: in std_logic;
          FSEL: in std_logic_vector(1 downto 0);
          F: out std_logic_vector(3 downto 0); COUT: out std_logic);
end ALU;

library ieee;
use ieee.std_logic_1164.all;
entity ALU8 is
    generic (DEL : TIME);
    port (A, B : in std_logic_vector(7 downto 0); CI : in std_logic;
          FSEL : in std_logic_vector(1 downto 0);
          F : out std_logic_vector(7 downto 0); COUT : out std_logic);
end ALU8;

architecture ALU8 of ALU8 is
    signal TEMP : std_logic;
begin
    U0 : entity work.ALU generic map (DEL)
        port map (A => A(3 downto 0), B => B(3 downto 0), CI => CI, FSEL => FSEL,
                  F => F(3 downto 0), COUT => TEMP);
    U1 : entity work.ALU generic map (DEL)
        port map (A => A(7 downto 4), B => B(7 downto 4), CI => TEMP, FSEL => FSEL,
                  F => F(7 downto 4), COUT => COUT);
end ALU8;
```

5. (15 points) Given the following VHDL, indicate all transactions and events. Give the values of A, B, C, D, E, and F each time a change occurs. Carry this out until no further change occurs.

```

entity prob is
  port (D : out bit);
end prob;
architecture PROB of PROB is
  signal A, B, C, E, F : bit;
begin
  process
    A <= '1' after 5 ns;
    wait;
  end process;
  P1: process (F, C)
  begin
    B <= F after 4 ns;
    E <= C after 6 ns;
  end process P1;
  C <= transport A or B
    after 3 ns;
  P2: process (C, E)
  begin
    F <= (C xor E) after 4 ns;
  end process P2;
  D <= F xor (B and C) after 2 ns;
end PROB;

```

Time	A	B	C	D	E	F
0 ns	0	0	0	0	0	0
5 ns	1	0	0	0	0	0
5 ns	1	0	0	0	0	0
8 ns	1	0	1	0	0	0
12 ns	1	0	1	0	0	1
14 ns	1	0	1	1	1	1
16 ns	1	1	1	1	1	1
18 ns	1	1	1	0	1	0
20 ns	1	1	1	1	1	0
22 ns	1	0	1	1	1	0
24 ns	1	0	1	0	1	0

Time	Event	Processes Triggered	Scheduled Transactions	Event?
5 ns	A → 1	C1	C (1, 8)	Y
8 ns	C → 1	P1	B (0, 12)	N
		P1	E (1, 14)	Y
		P2	F (1, 12)	Y
		C2	D (0, 10)	N
12 ns	F → 1	P1	B (1, 16)	Y
		P1	E (1, 18)	N
		C2	D (1, 14)	Y
14 ns	D → 1	none		
	E → 1	P2	F (0, 18)	Y
16 ns	B → 1	C1	C (1, 19)	N
		C2	D (0, 18)	Y
18 ns	D → 0	none		
	F → 0	P1	B (0, 22)	Y
		P1	E (1, 24)	N
		C2	D (1, 20)	Y
20 ns	D → 1	none		
22 ns	B → 0	C1	C (1, 25)	N
		C2	D (0, 24)	Y
24 ns	D → 0	none		

Scheduling Rules	Transport	Inertial
New before existing	Overwrite existing	Overwrite existing
New after existing	Append new	If $v_{\text{new}} = v_{\text{existing}}$, append new Elsif $t_{\text{new}} - t_{\text{existing}} >$ reject append new Else overwrite existing

6. (12 points) Draw the state diagram for the following state machine. You may omit reset from all the arcs.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity TAPE_PLAYER is
    port (PL, RE, FF, ST, M : in std_logic;
          P, F, R : out std_logic;
          COUNT : out unsigned (15 downto 0);
          RESET, CLK : in std_logic);
end TAPE_PLAYER;

architecture BEHAV of TAPE_PLAYER is
    type STATE_TYPE is (INIT, PUSHPLAY, PP_RE1, PP_REW, PP_FF1, PP_FF0R, PLAY);
    signal STATE : STATE_TYPE;
    signal INT_COUNT : unsigned (15 downto 0);
begin
    process (RESET, CLK)
    begin
        if (RESET = '1') then
            STATE <= INIT;
        elsif (CLK'event and CLK = '1') then
            if (STATE = INIT) then
                if (PL = '1') then
                    STATE <= PUSHPLAY;
                end if;
                INT_COUNT <= "0000000000000000";
            elsif (STATE = PUSHPLAY) then
                if (PL = '0' or ST = '1') then
                    STATE <= INIT;
                else
                    if (RE = '1') then
                        STATE <= PP_RE1;
                    elsif (FF = '1') then
                        STATE <= PP_FF1;
                    else
                        STATE <= PLAY;
                    end if;
                end if;
                INT_COUNT <= "0000000000000000";
            elsif (STATE = PP_RE1) then
                if (PL = '0' or ST = '1') then
                    STATE <= INIT;
                else
                    if (RE = '0') then
                        STATE <= PP_REW;
                    else
                        STATE <= PP_RE1;
                    end if;
                end if;
                INT_COUNT <= "0000000000000000";
            elsif (STATE = PP_REW) then
                if (ST = '1') then
                    STATE <= INIT;
                else

```

```

    if (M = '1') then
        STATE <= PP_REW;
    else
        STATE <= INIT;
    end if;
end if;
INT_COUNT <= INT_COUNT + 1;
elsif (STATE = PP_FF1) then
    if (PL = '0' or ST = '1') then
        STATE <= INIT;
    else
        if (FF = '0') then
            STATE <= PP_FFOR;
        else
            STATE <= PP_FF1;
        end if;
    end if;
    INT_COUNT <= "0000000000000000";
elsif (STATE = PP_FFOR) then
    if (ST = '1') then
        STATE <= INIT;
    else
        if (M = '1') then
            STATE <= PP_FFOR;
        else
            STATE <= INIT;
        end if;
    end if;
    INT_COUNT <= INT_COUNT + 1;
elsif (STATE = PLAY) then
    if (ST = '1') then
        STATE <= INIT;
    else
        STATE <= PLAY;
    end if;
    INT_COUNT <= INT_COUNT + 1;
end if;
end if;
COUNT <= INT_COUNT;
end process;


P <= '1' when STATE = PLAY else '0';
F <= '1' when STATE = PP_FFOR else '0';
R <= '1' when STATE = PP_REW else '0';

```

```

end BEHAV;

```

 

7. (1 point) Transport delay represents wire delay.
8. (1 point) c Multiple Choice: Which of the following cannot occur inside a process?
 - a. Signal Assignment
 - b. Variable Declaration
 - c. Signal Declaration
9. (1 point) A procedure is used when you have multiple return values.
10. (1 point) A process is triggered whenever a signal in its sensitivity list has an event on it.
11. (1 point). False (True or False) All sequential statements are synthesized into sequential circuits.

12. (10 points) In order to add floating point numbers, the numbers must first have the same exponent, so combinational shifting is required so that floating point add can be accomplished in a reasonable time. Design a 4 bit barrel shifter that has 4 data inputs and 4 data outputs, and 2 control inputs that determine the shift amount (0-3). Use the truth table below as the functionality and use the entity declaration given.

s1	s0	c3	c2	c1	c0
0	0	a3	a2	a1	a0
0	1	a0	a3	a2	a1
1	0	a1	a0	a3	a2
1	1	a2	a1	a0	a3

```
entity barrel is
  port (a : in std_logic_vector (3 downto 0); s1, s0 : in std_logic;
        c : out std_logic_vector (3 downto 0));
end entity barrel;
```

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity barrel is
  port (a : in std_logic_vector(3 downto 0);
        s1, s0 : in std_logic;
        c : out std_logic_vector(3 downto 0));
end entity barrel;
```

```
architecture synth of barrel is
  --signal control : std_logic_vector(1 downto 0);
begin
  --control <= s1 & s0;
  with std_logic_vector'(s1, s1) select
    c <= a when "00",
        a(0) & a(3 downto 1) when "01",
        a(1 downto 0) & a(3 downto 2) when "10",
        a(2 downto 0) & a(3) when "11",
        a when others;
end synth;
```