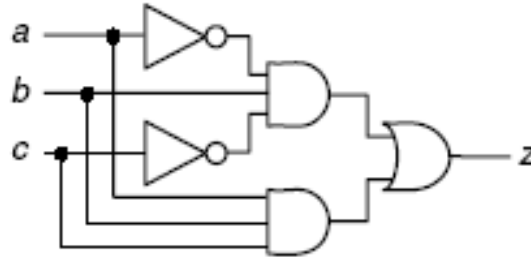


The University of Alabama in Huntsville
ECE Department
CPE 628 01
Fall 2008
Homework #1 Solution

1.1(15 points), 1.3(10 points), 1.5(10 points), 2.1(25 points), 2.2(25 points), 2.4(15 points)

- 1.1 Consider the combinational logic circuit below. How many possible single stuck-at faults does this circuit have? How many possible multiple stuck-at faults does this circuit have? How many collapsed single stuck-at faults does this circuit have?



There are 14 nodes in the circuit. Thus, there are $14 \times 2 = 28$ single stuck-at faults.

For multiple stuck-at fault, it has $(2 + 1)^{14} - 1 = 4782968$ multiple stuck-at faults.

For collapsed single stuck-at fault:

Number of collapsed faults = $2 \times (\text{number of POs} + \text{number of fanout stems})$
 $+ \text{total number of gate (including inverter) inputs}$
 $- \text{total number of inverters}$

Here number of POs = 1, number of fanout stems = 3, total number of gate inputs = 10, number of inverter = 2. Therefore, the number of collapsed faults = $2 \times (1 + 3) + 10 - 2 = 16$.

- 1.3 Generate a minimum set of test vectors to completely test an n-input NAND gate under the single stuck-at fault model. How many test vectors are needed?

To detect all single stuck-at faults of the n-input NAND, we need n+1 test vectors. In fact, in order to detect the s-a-1 fault at the inputs, the following patterns are needed:

$$\overbrace{(0111 \dots 1), (1011 \dots 1), (1101 \dots 1), (1110 \dots 1), \dots, (1111 \dots 0)}^n$$

n


In addition, $(1111 \dots 1)$ is required to detect its s-a-0 faults and the output s-a-1 fault.

- 1.5 The number of failures in 10^9 hours is a unit (abbreviated FITS) that is often used in reliability calculations. Calculate the MTBF for a system with 500 components where each component has a failure rate of 1000 FITS.


$$\lambda = \sum_{i=1}^k \lambda_i, \quad \lambda_i = \frac{1000}{10^9}. \quad \text{Thus, } \lambda = 10^{-6} \times 500 = 5 \times 10^{-4}$$

$$\text{MTBF} = \frac{1}{\lambda} = 2 \times 10^3 = 2000 \text{ hours.}$$

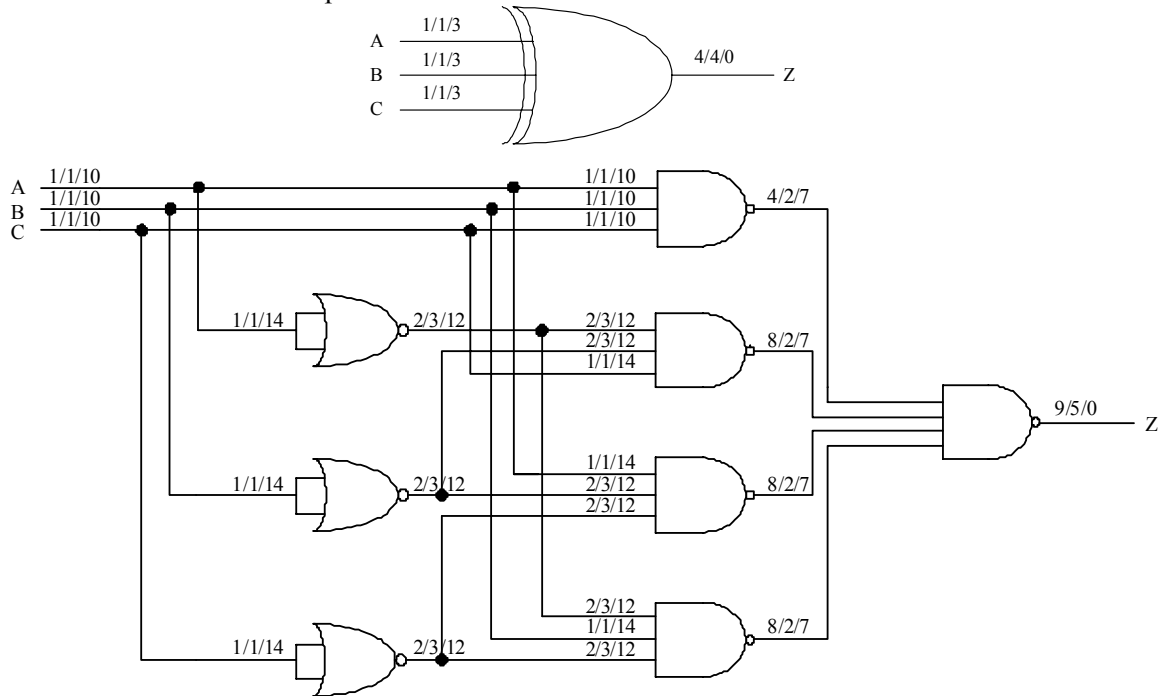
- 2.1 Calculate the SCOAP controllability and observability measures for a three-input XOR gate and for its NAND-NOR implementation.



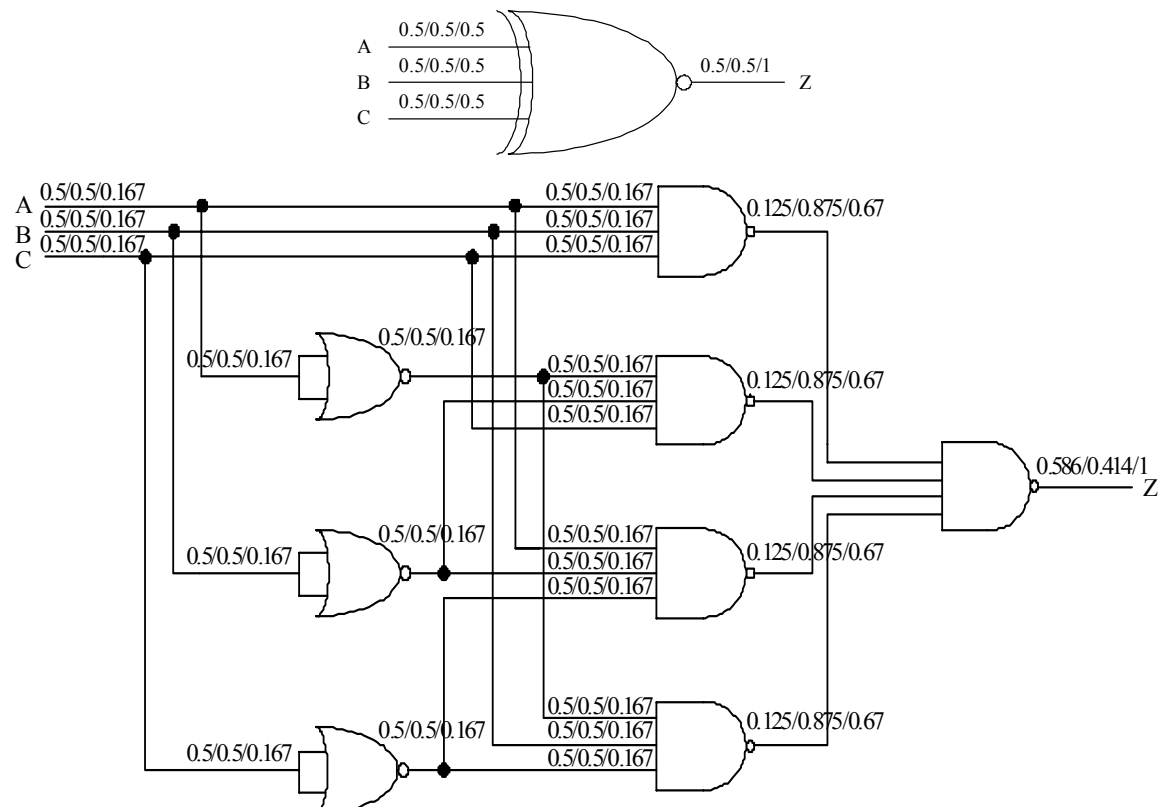- 2.2 Use the rules given in Tables 2.3 and 2.4 to calculate the probability-based testability measures for a three-input XNOR gate and for its NAND-NOR implementation. Assume that the probability-based controllability values at all primary inputs and the probability-based observability values at all the primary outputs are 0.5 and 1, respectively.



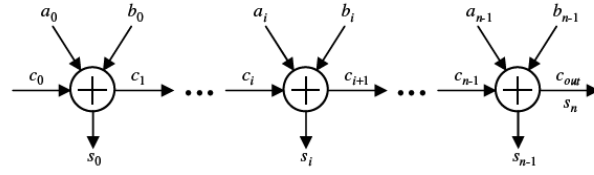- 2.4 Calculate the combinational observability of input a_i at output s_k , denoted by $O(a_i, s_k)$, where $k > i$, for the n -bit ripple-carry adder shown.



$$s_i = c_i + a_i + b_i, \quad c_{i+1} = c_i(a_i + b_i) + a_i b_i$$

$$O(a_i, s_i) = O(b_i, s_i) = O(c_i, s_i) = O(s_i),$$

$$i = 0, \dots, n-1.$$

$$O(a_i, s_k) = \left[C_1(c_i \oplus b_i) \times \prod_{j=i+1}^{k-1} C_1(a_j \oplus b_j) \right] O(s_k),$$

$$i = 0, \dots, n-1.$$