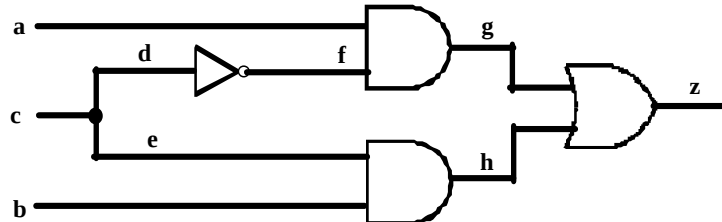


The University of Alabama in Huntsville
ECE Department
CPE 628 01
Fall 2008
Homework #3 Solution

4.2(15), 4.3(15), 4.4(15), 4.7(15), 4.8(20), 4.11(20)

4.2 Using the circuit shown, compute the detection probabilities for each of the following faults:



- a. e/0
- b. e/1
- c. c/0

Recall that the detection probability is $d_f = \frac{|T_f|}{2^n}$, where T_f is the set of vectors that can detect fault f, and n is the number of inputs in the circuit. In this circuit, we have 3 inputs, so there are a total of 8 possible vectors.

- (a) For e/0, two vectors, abc = {011, 111} can detect it. Thus $d_f = 0.25$
- (b) For e/1, one vector, abc = 010 can detect it. Thus $d_f = 0.125$
- (c) For c/0, two vectors, abc = {011, 101} can detect it, Thus $d_f = 0.25$

4.3 Using the circuit shown, compute the set of all vectors that can detect each of the following faults using the Boolean difference.

- a. e/0
- b. e/1
- c. c/0

(a) The set of vectors that can detect e/0 is

$$\begin{aligned}
 (e=1) \cdot \frac{d_z}{d_e} &= e \cdot (z \cdot (e=0) \oplus z(e=1)) \\
 &= e \cdot (g \oplus (g+b)) \\
 &= e \cdot (g \cdot g \bar{+} b + \bar{g} \cdot (g+b)) \\
 &= e \cdot \bar{g} \cdot b \\
 &= e \cdot \bar{a} \bar{c} \cdot b \\
 &= e \cdot (\bar{a} + c) \cdot b \\
 &= bc + \bar{a}bc \\
 &= bc
 \end{aligned}$$

Thus, the set of vectors is {011, 111}.

(b) The set of vectors that can detect e/1 is

$$\begin{aligned}
(e=0) \cdot \frac{d_z}{d_e} &= e \cdot (z \cdot (e=0) \oplus z(e=1)) \\
&= \bar{e} \cdot (g \oplus (g+b)) \\
&= \bar{e} \cdot (g \cdot g \bar{+} b + \bar{g} \cdot (g+b)) \\
&= \bar{e} \cdot \bar{g} \cdot b \\
&= \bar{e} \cdot \bar{a} \bar{c} \cdot b \\
&= \bar{e} \cdot (\bar{a} + c) \cdot b \\
&= b \bar{c} \bar{e} + \bar{a} b \bar{e} \\
&= \bar{a} b \bar{e} \\
&= \bar{a} b \bar{c}
\end{aligned}$$

Thus, the set of vectors is {010}.


(c) The set of vectors that can detect c/0 is

$$\begin{aligned}
(c=1) \cdot \frac{d_z}{dc} &= e \cdot (z \cdot (c=0) \oplus z(c=1)) \\
&= c \cdot (a \oplus b) \\
&= c \cdot (a \cdot \bar{b} + \bar{a} \cdot b) \\
&= \bar{a} b c + \bar{a} b c
\end{aligned}$$

Thus, the set of vectors is {011, 101}.

4.4 Using the circuit shown, compute the set of all vectors that can detect each of the following faults using the Boolean difference:

- a/1
- d/1
- g/1

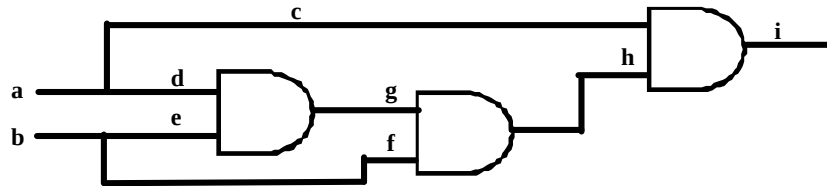

(a) The set of vectors that can detect a/1 is

$$\begin{aligned}
(a=0) \cdot \frac{d_i}{da} &= \bar{a} \cdot (i \cdot (a=0) \oplus i(a=1)) \\
&= \bar{a} \cdot (0 \oplus b) \\
&= \bar{a} b
\end{aligned}$$

Thus, the set of vectors is {01}.

(b) The set of vectors that can detect d/1 is

$$\begin{aligned}
(d=0) \cdot \frac{d_i}{dd} &= \bar{d} \cdot (i \cdot (d=0) \oplus i(d=1)) \\
&= \bar{d} \cdot (0 \oplus ab) \\
&= \bar{d} \cdot ab
\end{aligned}$$

But it is impossible to set $a=1$ and $d=0$ simultaneously. Thus, the set of vectors is $\emptyset$.

(c) The set of vectors that can detect $g/1$ is


$$\begin{aligned}
(g=0) \cdot \frac{d_i}{dg} &= \bar{g} \cdot (i \cdot (g=0) \oplus i(g=1)) \\
&= \bar{g} \cdot (0 \oplus ab) \\
&= \bar{g} \cdot ab \\
&= \bar{ab} \cdot ab \\
&= 0
\end{aligned}$$

Thus, the set of vectors is $\emptyset$.

4.7 Construct the table for the XNOR operation for the 5-valued logic similar to Tables 4.1, 4.2, and 4.3.

XNOR	0	1	D	$\bar{D}$	X
0	1	0	$\bar{D}$	D	X
1	0	1	D	$\bar{D}$	X
D	$\bar{D}$	D	1	0	X
$\bar{D}$	D	$\bar{D}$	0	1	X
x	X	X	X	X	X

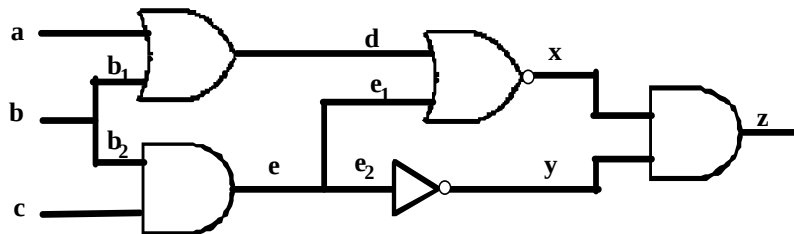4.8 Using the circuit shown, use the D-algorithm to compute a vector for the fault $b/1$. Repeat for the fault $e/0$.




Initially, we place a $\bar{D}$ on b . The D-frontier at this time includes $\{d, e\}$. Next, we pick a D-frontier to propagate the fault effect across. Suppose we pick d . Then, the decision $a=0$ is made. At this time, the D-frontier becomes $\{x, e\}$. We pick the D-frontier that is closest to a PO. Thus, we pick x . The next decision is $e1=0$. This decision implies $y=1$ and $z=D$. In other words, the fault-effect has been propagated all the way to the PO. The J-frontier consists of $\{e1=0, b=\bar{D}\}$. To justify $e1=0$, $c=0$ is sufficient. Justifying

$b = \overline{D}$ is likewise straightforward, simply by setting $b=0$. Thus the vector $abc=000$ detects the target fault $b/1$.

A similar decision process is made for the target fault $e/0$. However, in this case, one would conclude that the fault is untestable.

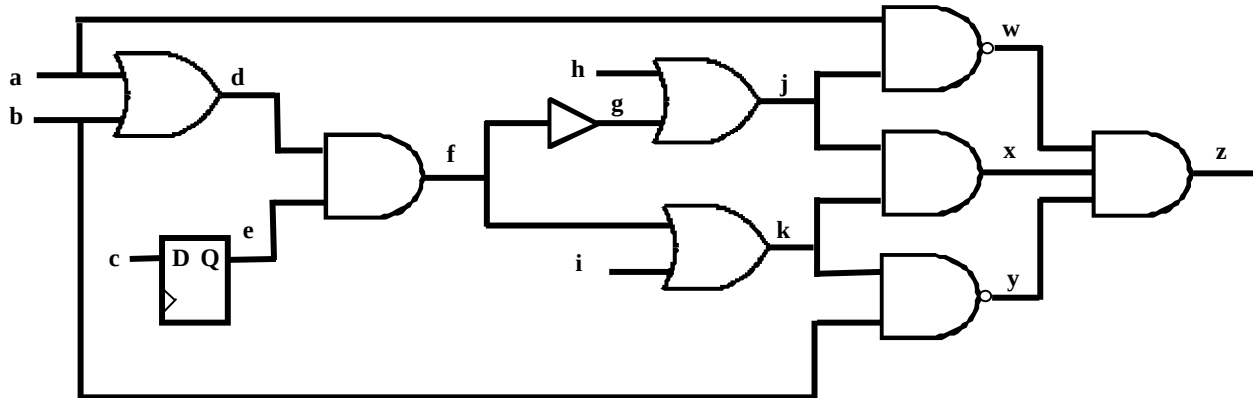4.11 Using the circuit shown and PODEM, compute the vector that can detect the fault $f/0$. Note that even though the circuit is sequential, it can be viewed as a combinational circuit because the D flip-flop does not have an explicit feedback.



Objective	Backtrace	Assignment	Implications	Decision Tree
(f, 1)	(d, 1), (e, 1), (a, 1)	a = 1	d = 1	a = 1
(f, 1)	(e, 1), (c, 1)	c = 1	e = 1, f = D, g = D	a = 1, c = 1
(h, 0)	(h, 0)	h = 0	j = D, w = D'	a = 1, c = 1, h = 0
(x, 1)	(x, 1), (k, 1), (i, 1)	i = 1	k = 1, x = D, no path	a = 1, c = 1, h = 0, i = 1
		i = 0	k = D, x = D, no path	a = 1, c = 1, h = 0, i = 0
		h = 1	j = 1, w = 0, x = 0, no path	a = 1, c = 1, h = 1
		c = 0	f = 0, no excitation	a = 1, c = 0
		a = 0	w = 1	a = 0
(f, 1)	(d, 1), (b, 1)	b = 1	d = 1	a = 0, b = 1
(f, 1)	(e, 1), (c, 1)	c = 1	f = D, g = D	a = 0, b = 1, c = 1
(h, 0)	(h, 0)	h = 0	j = D	a = 0, b = 1, c = 1, h = 0
(k, 1)	(i, 1)	i = 1	k = 1, y = 0, z = 0, no path	a = 0, b = 1, c = 1, h = 0, i = 1
		i = 0	k = D, x = D, y = D', no path	a = 0, b = 1, c = 1, h = 0, i = 0
		h = 1	j = 1	a = 0, b = 1, c = 1, h = 1
(i, 0)	(i, 0)	i = 0	k = D, y = D', x = D, no path	a = 0, b = 1, c = 1, h = 1, i = 0
		i = 1	k = 1, y = 0, z = 0, no path	a = 0, b = 1, c = 1, h = 1, i = 1
		c = 0	e = 0, f = 0, no excitation	a = 0, b = 1, c = 0
		b = 0	d = 0, f = 0, no excitation	a = 0, b = 0
No further options available, fault redundant				