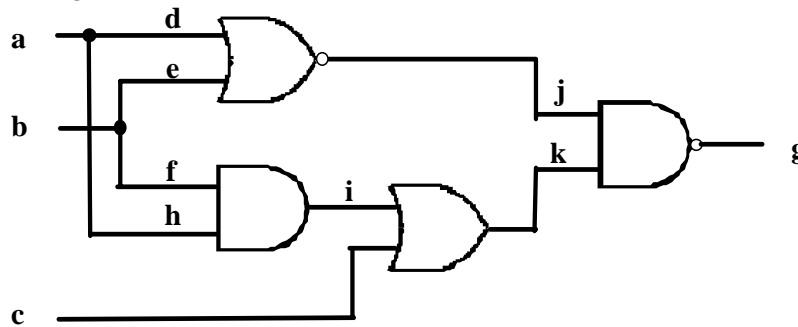


The University of Alabama in Huntsville
ECE Department
CPE 628 01
Test 1 Solution
Fall 2008

1. (10 points) For the circuit shown, calculate the probability-based observabilities given the controllabilities given.



Line 0-C/1-C/O

		f	0.5/0.5/_0.0625_
a	0.5/0.5/_0.25_	h	0.5/0.5/_0.0625_
b	0.5/0.5/_0.25_	i	0.125/0.5/_0.125_
c	0.5/0.5/_0.03125_	j	0.5/0.25/_0.5_
d	0.5/0.5/_0.25_	k	0.25/0.5/_0.25_
e	0.5/0.5/_0.25_	g	0.125/0.5/_1

$$\begin{aligned}
 O(g) &= 1 & O(j) &= O(g) * C1(k) = 1 * 0.5 = 0.5 & O(k) &= O(g) * C1(j) = 1 * 0.25 = 0.25 \\
 O(i) &= O(k) * C1(c) = 0.25 * 0.5 = 0.125 & & & O(c) &= O(k) * C1(i) = 0.25 * 0.125 = 0.03125 \\
 O(h) &= O(i) * C1(f) = 0.125 * 0.5 = 0.0625 & & & O(f) &= O(i) * C1(h) = 0.125 * 0.5 = 0.0625 \\
 O(e) &= O(j) * C1(d) = 0.5 * 0.5 = 0.25 & & & O(d) &= O(j) * C1(e) = 0.5 * 0.5 = 0.25 \\
 O(a) &= \max\{O(d), O(h)\} = \max\{0.25, 0.0625\} = 0.25 & & & & \\
 O(b) &= \max\{O(e), O(f)\} = \max\{0.25, 0.0625\} = 0.25 & & & &
 \end{aligned}$$

2. (5 points) The number of failures in 10^9 hours is a unit (abbreviated FITS) that is often used in reliability calculations. Calculate the MTBF for a system with 10 components where each component has a failure rate of 3000 FITS.

$$\lambda = \sum_{i=1}^k \lambda_i, \quad \lambda_i = \frac{3000}{10^9}. \quad \text{Thus, } \lambda = \frac{3000}{10^9} * 10 = 3 * 10^{-5}$$

$$MTBF = \frac{1}{\lambda} = 1/3 * 10^5 \text{ hours} = 33,333 \text{ hours}$$


3. (10 points) Generate a minimum set of test vectors to completely test an n-input XOR gate under the single stuck-at fault model. How many test vectors are needed? at most 3

There are two cases, n odd and n even

For n odd, two patterns are required. The test pattern $111\dots 1$ will detect all s-a-0 faults on inputs and the test pattern $000\dots 0$ will detect all s-a-1 faults on inputs. The s-a-0 fault on the output is detected by the all 1s pattern and the s-a-1 fault on the output is detected by the all 0s pattern.


For n even, a third pattern is required to detect the s-a-0 fault on the output. This pattern must have an odd number of 1s.

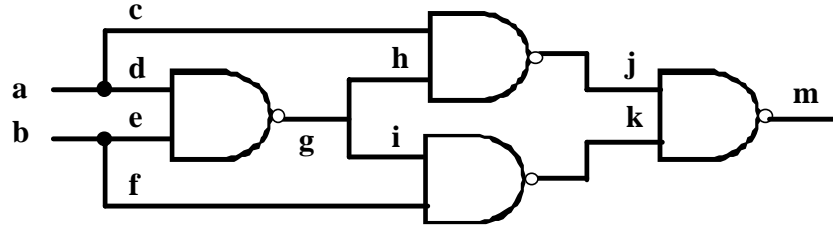4. (15 points) For the circuit given, calculate the SCOAP controllability measures.



$$\begin{aligned}
 CO(a) = CO(b) = 1 & \quad C1(a) = C1(b) = 1 & \quad C0(c) = C0(d) = C0(e) = C0(f) = 1 \\
 C1(c) = C1(d) = C1(e) = C1(f) = 1 & \quad C0(g) = C1(d) + C1(e) + 1 = 1 + 1 + 1 = 3 \\
 C1(g) = \min\{C0(d), C0(e)\} + 1 = \min\{1, 1\} + 1 = 1 + 1 = 2 & \quad C0(h) = C0(i) = C0(g) = 3 \\
 C1(h) = C1(i) = C1(g) = 2 & \quad C0(j) = C1(c) + C1(h) + 1 = 1 + 2 + 1 = 4 \\
 C1(j) = \min\{C0(c), C0(h)\} + 1 = \min\{1, 3\} + 1 = 1 + 1 = 2 \\
 C0(k) = C1(i) + C1(f) + 1 = 2 + 1 + 1 = 4 \\
 C1(k) = \min\{C0(i), C0(f)\} + 1 = \min\{3, 1\} + 1 = 1 + 1 = 2 \\
 C0(m) = C1(j) + C1(k) + 1 = 2 + 2 + 1 = 5 \\
 C1(m) = \min\{C0(j), C0(k)\} + 1 = \min\{4, 4\} + 1 = 4 + 1 = 5
 \end{aligned}$$

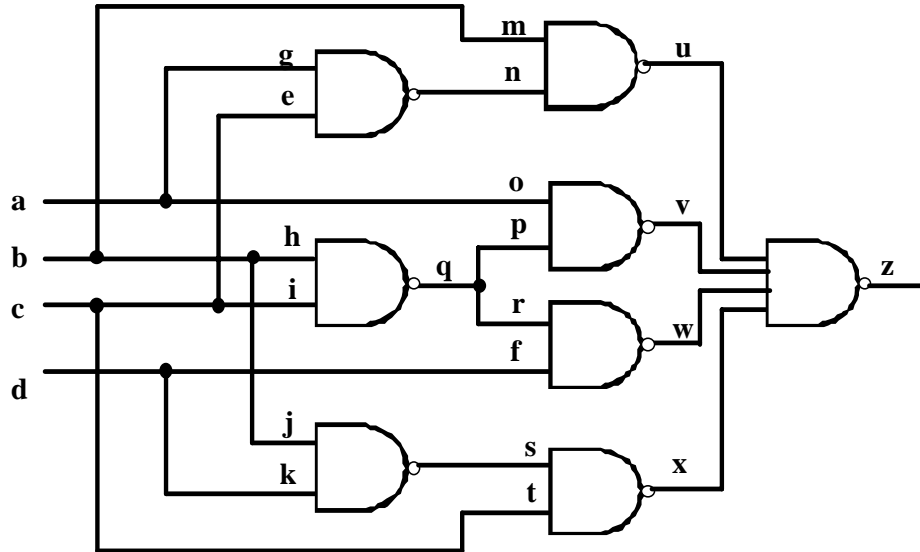
5. (1 point) The symbol _ represents the logic value unknown.
6. (10 points) For the circuit shown and the two faults $\alpha = e/0$, $\beta = f/1$, use the parallel-pattern single-fault propagation technique to identify which faults can be detected by the test patterns $(a, b, c, d) = (0, 1, 0, 1), (1, 1, 0, 1)$.



PPSFP		input					internal																	output	
fault	P	a	b	c	d	e	f	g	h	i	j	k	m	n	o	p	q	r	s	t	u	v	w	x	z
fault-free	P1	0	1	0	1	0	1	0	1	0	1	1	1	1	0	1	1	1	0	0	0	1	0	1	1
	P2	1	1	0	1	0	1	1	1	0	1	1	1	1	1	1	1	1	0	0	0	0	0	1	1
α	P1	0	1	0	1	0	1	0	1	0	1	1	1	1	0	1	1	1	0	0	0	1	0	1	1
	P2	1	1	0	1	0	1	1	1	0	1	1	1	1	1	1	1	1	0	0	0	0	0	1	1
β	P1	0	1	0	1	0	1	0	1	0	1	1	1	1	0	1	1	1	0	0	0	1	0	1	1
	P2	1	1	0	1	0	1	1	1	0	1	1	1	1	1	1	1	1	0	0	0	0	0	1	1

Neither of the faults are detected.

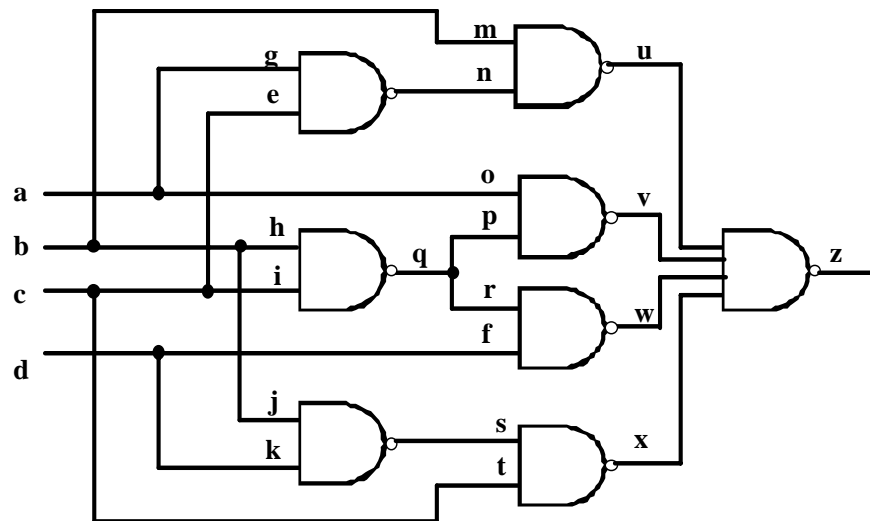
7. (1 point) A defect is a flaw or physical imperfection that may lead to a fault.
8. (1 point) The goal of test generation is to find an efficient set of test vectors that detects all faults considered for a circuit.
9. (10 points) Use the circuit, faults and patterns of problem 6 to do parallel fault simulation.



PPSFP		input		internal																		output			
fault	P	a	b	c	d	e	f	g	h	i	j	k	m	n	o	p	q	r	s	t	u	v	w	x	z
ff	P1	0	1	0	1	0	1	0	1	0	1	1	1	1	0	1	1	1	0	0	0	1	0	1	1
	α	P1	0	1	0	1	0	1	0	1	1	1	1	0	1	1	1	1	0	0	0	1	0	1	1
β	P1	0	1	0	1	0	1	0	1	0	1	1	1	1	0	1	1	1	0	0	0	1	0	1	1
ff	P2	1	1	0	1	0	1	1	1	0	1	1	1	1	1	1	1	1	0	0	0	0	0	1	1
	α	P2	1	1	0	1	0	1	1	0	1	1	1	1	1	1	1	1	0	0	0	0	0	1	1
β	P2	1	1	0	1	0	1	1	1	0	1	1	1	1	1	1	1	1	0	0	0	0	0	1	1


Neither of the faults are detected.

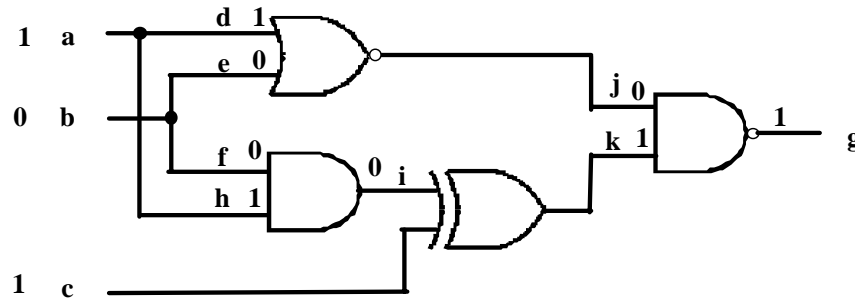10. (1 point) The most widely used structured DFT methodology is scan design.
11. (1 point) Logic simulation helps the designer verify that a design conforms to the functional specifications.
12. (15 points) For the circuit shown, use deductive fault simulation to determine the faults detected by the pattern shown.



$L_a = \{a/0\}$ $L_b = \{b/1\}$ $L_c = \{c/0\}$ $L_d = \{a/0, d/0\}$ $L_e = \{b/1, e/1\}$
 $L_f = \{b/1, f/1\}$ $L_h = \{a/0, h/0\}$ $L_i = \{b/1, f/1, i/1\}$
 $L_j = \{a/0, d/0, j/1\}$ $L_k = \{b/1, c/0, f/1, i/1, k/0\}$ $L_g = \{a/0, d/0, j/1, g/0\}$

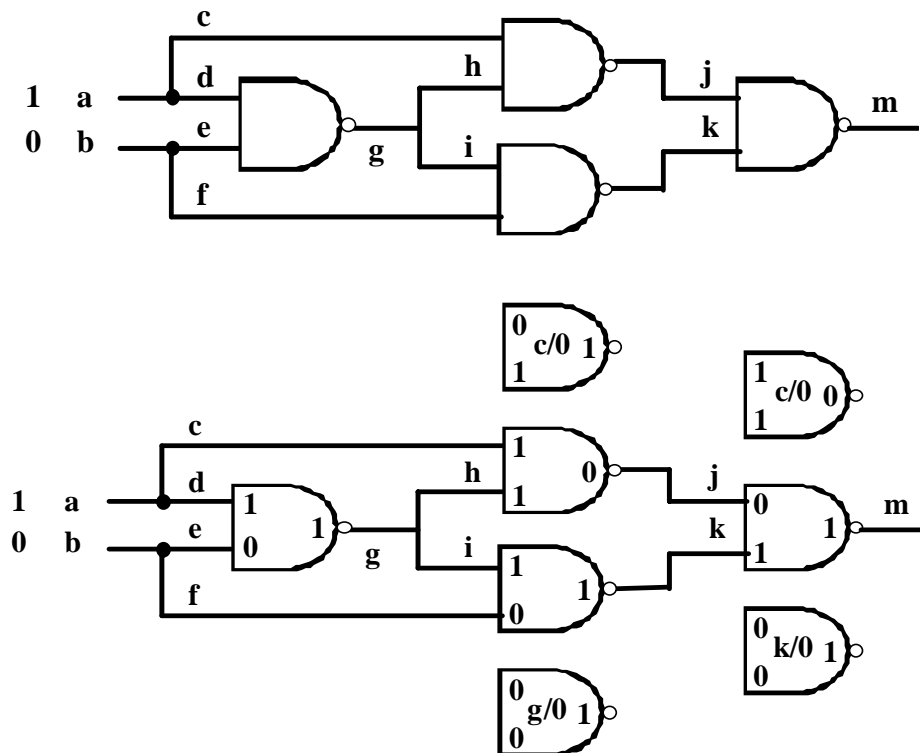13. (15 points) For the circuit shown, use concurrent fault simulation to determine whether the faults $g/0$, $c/0$, $k/0$ are detectable for the pattern given.



Only $c/0$ is detectable.