

Name: _____

-
- ```

graph TD
 00((00)) -- "00/0" --> 00
 00 -- "01/0" --> 10((10))
 00 -- "10/1" --> 01((01))
 00 -- "11/1" --> 01
 01 -- "00/1" --> 00
 01 -- "01/1" --> 11((11))
 01 -- "10/1" --> 00
 01 -- "11/1" --> 00
 10 -- "00/0" --> 00
 10 -- "01/0" --> 10
 10 -- "10/0" --> 11
 10 -- "11/0" --> 11
 11 -- "00/1" --> 01
 11 -- "01/1" --> 11
 11 -- "10/1" --> 01
 11 -- "11/1" --> 01

```

[illegible]

| J | K | $Q(t+1)$ |
|---|---|----------|
| 0 | 0 | $Q(t)$   |
| 0 | 1 | 0        |
| 1 | 0 | 1        |
| 1 | 1 | $Q'(t)$  |

| D | $Q(t+1)$ |
|---|----------|
| 0 | 0        |
| 1 | 1        |

| T | $Q(t+1)$ |
|---|----------|
| 0 | $Q(t)$   |
| 1 | $Q'(t)$  |

7. (20 points) Design a 3-bit counter which counts in the sequence 000, 010, 100, 110, 000 using clocked JK flip-flops. You do not have to draw the circuit diagram. What will happen if the counter is started in state 101?

8. (10 points) Reduce the number of states in the following state table, and tabulate the reduced state table:

| Present State | Next State |       | Output |       |
|---------------|------------|-------|--------|-------|
|               | x = 0      | x = 1 | x = 0  | x = 1 |
| S0            | S1         | S4    | 0      | 0     |
| S1            | S2         | S1    | 0      | 0     |
| S2c           | S1         | S6    | 0      | 0     |
| S3            | S1         | S3    | 0      | 0     |
| S4            | S5         | S4    | 0      | 0     |
| S5            | S2         | S1    | 0      | 0     |
| S6            | S5         | S3    | 0      | 1     |

9. (15 points) Construct a 5-to-32 line decoder with as many 2-to-4 line decoders with enable and any additional logic that you might need. Use block diagrams for the components.

10. (10 points) Construct a  $32 \times 1$  multiplexer with as many  $8 \times 1$  multiplexers and any additional logic that you might need. Use block diagrams for the components.

11. (25 points) Design a Mealy sequential circuit that has an output of 1 whenever its input string has the sequence 0101 and otherwise has an output of 0. These sequences can overlap. Use T flip-flops. You do not have to draw the circuit diagram.

Input: 001010111010001111101010101111000011001

Output: 000010100000000111100010101000000001000