

CPE/EE 427, CPE 527 VLSI Design I: Homework 1

1. (15 points) Draw a **detailed layout, cross-section and circuit diagram** of a CMOS inverter assuming:

- a. (5) Twin-tub process;
- b. (5) N-well process;
- c. (5) P-well process.


Label all relevant regions (n-well, p-well, n+, p+, metal, poly, ...) and draw connections to V_{DD} and Gnd. Show transistors as 4-terminal devices.

2. (10 points) Justify the following design rules. Be specific.

- a. (2.5) 2λ poly-poly separation;
- b. (2.5) no required poly-metal spacing;
- c. (2.5) 1λ of diffusion and metal surrounding a cut;
- d. (2.5) 2λ overhang of poly at transistor gate;


3. (20 points) An NMOS device is plugged into the test configuration shown below. The input $V_{in} = 2V$. The current source draws a constant current of $50 \mu A$. R is a variable resistor that can assume values between $10k\Omega$ and $30 k\Omega$. Transistor M1 experiences short channel effects and has following transistor parameters: $k' = 110 * 10^{-6} V/A^2$, $V_T = 0.4$, and $V_{DSAT} = 0.6V$. The transistor has a $W/L = 2.5\mu/0.25\mu$. For simplicity body effect and channel length modulation can be neglected. i.e $\lambda=0$, $\gamma=0$.

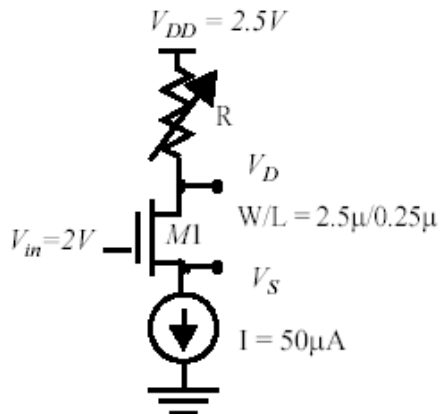- a. (10) When $R = 30k\Omega$ again determine the operation region V_D , V_S
- b. (10) For the case of $R = 10k\Omega$, would V_S increase or decrease if $\lambda \neq 0$. Explain qualitatively.



4. (10 points) The circuits below show different implementations of an inverter whose output is connected to a capacitor.

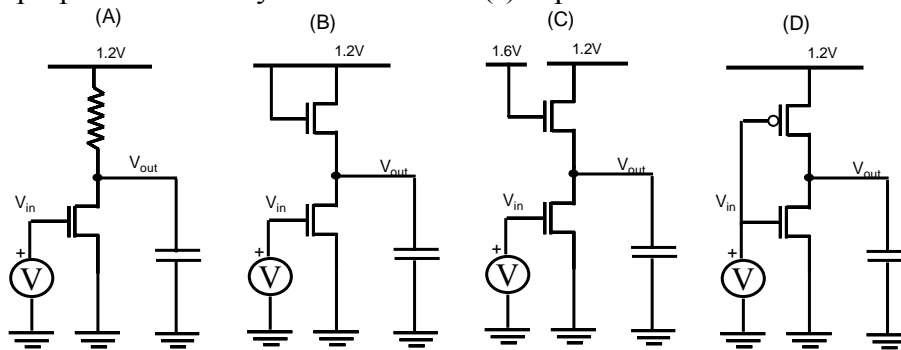- (2) Which one of the circuits consumes static power when the input is high?
- (2) Which one of the above circuits consumes static power when the input is low?
- (2) V_{OH} of which circuit(s) is 1.2V?
- (2) V_{OL} of which circuit(s) is 0V?
- (2) The proper functionality of which circuit(s) depends on the size of devices.



5. (10 points) Textbook: Exercise 2.1.

6. (15 points) Textbook: Exercise 2.2.

7. (10 points) Textbook: Exercise 2.5.

8. (10 points) Textbook: Exercise 2.6.