 


**CPE/EE 427, CPE 527
VLSI Design I
CMOS Inverter**


Department of Electrical and Computer Engineering
University of Alabama in Huntsville

Aleksandar Milenkovic


**CMOS Inverter:
A First Look**



CMOS Inverter: Steady State Response

 

$$V_{in} = 0$$

 

$$V_{in} = V_{DD}$$

$$\boxed{V_{OL} = 0 \\ V_{OH} = V_{DD} \\ V_M = f(R_n, R_p)}$$

9/11/2006

VLSI Design I; A. Milenkovic

3

CMOS Properties


- Full rail-to-rail swing \Rightarrow high noise margins
 - Logic levels not dependent upon the relative device sizes \Rightarrow transistors can be minimum size \Rightarrow ratioless
- Always a path to V_{dd} or GND in steady state \Rightarrow low output impedance (output resistance in $k\Omega$ range) \Rightarrow large fan-out (albeit with degraded performance)
- Extremely high input resistance (gate of MOS transistor is near perfect insulator) \Rightarrow nearly zero steady-state input current
- No direct path steady-state between power and ground \Rightarrow no static power dissipation
- Propagation delay function of load capacitance and resistance of transistors

9/11/2006

VLSI Design I; A. Milenkovic

4

Short Channel I-V Plot (NMOS)

 

NMOS transistor, $0.25\mu m$, $L_d = 0.25\mu m$, $W/L = 1.5$, $V_{DD} = 2.5V$, $V_T = 0.4V$


9/11/2006

VLSI Design I; A. Milenkovic

5

Short Channel I-V Plot (PMOS)

 - All polarities of all voltages and currents are reversed



PMOS transistor, $0.25\mu m$, $L_d = 0.25\mu m$, $W/L = 1.5$, $V_{DD} = 2.5V$, $V_T = -0.4V$


9/11/2006

VLSI Design I; A. Milenkovic

6

nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} <$	$V_{gsn} >$ $V_{dsn} <$	$V_{gsn} >$ $V_{dsn} >$

 


9/11/2006

VLSI Design I; A. Milenkovic

7

nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$

 

9/11/2006

VLSI Design I; A. Milenkovic


8

nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 

9/11/2006

VLSI Design I; A. Milenkovic


9

nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


9/11/2006

VLSI Design I; A. Milenkovic

10

pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} >$ $V_{dsp} >$	$V_{gsp} <$ $V_{dsp} >$	$V_{gsp} <$ $V_{dsp} <$

 


9/11/2006

VLSI Design I; A. Milenkovic

11

pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$

 

9/11/2006

VLSI Design I; A. Milenkovic

12


pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{dsp} = V_{out} - V_{DD}$$

$$V_{tp} < 0$$

 

9/11/2006

VLSI Design I; A. Milenkovic

13


pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
$V_{in} > V_{DD} + V_{tp}$	$V_{in} < V_{DD} + V_{tp}$	$V_{in} < V_{DD} + V_{tp}$
	$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$
	$V_{out} > V_{in} - V_{tp}$	$V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{dsp} = V_{out} - V_{DD}$$

$$V_{tp} < 0$$

 


9/11/2006

VLSI Design I; A. Milenkovic

14

I-V Characteristics

 - Make pMOS is wider than nMOS such that $\beta_n = \beta_p$




9/11/2006

VLSI Design I; A. Milenkovic

15

Current vs. V_{out} , V_{in}

 


9/11/2006

VLSI Design I; A. Milenkovic

16

Load Line Analysis

- $V_{in} = 0$

 


9/11/2006

VLSI Design I; A. Milenkovic

17

Load Line Analysis

- $V_{in} = 0.2V_{DD}$

 


9/11/2006

VLSI Design I; A. Milenkovic

18

Load Line Analysis

- $V_{in} = 0.4V_{DD}$

 


9/11/2006

VLSI Design I; A. Milenkovic

19

Load Line Analysis

- $V_{in} = 0.6V_{DD}$

 


9/11/2006

VLSI Design I; A. Milenkovic

20

Load Line Analysis

- $V_{in} = 0.8V_{DD}$

 


9/11/2006

VLSI Design I; A. Milenkovic

21

Load Line Analysis

- $V_{in} = V_{DD}$

 


9/11/2006

VLSI Design I; A. Milenkovic

22

Load Line Summary

 


9/11/2006

VLSI Design I; A. Milenkovic

23

DC Transfer Curve


 
- Transcribe points onto V_{in} vs. V_{out} plot



9/11/2006

VLSI Design I; A. Milenkovic


24

  

Operating Regions

- Revisit transistor operating regions

Region	nMOS	pMOS
A		
B		
C		
D		
E		

 


9/11/2006

VLSI Design I; A. Milenkovic

27

CMOS Inverter VTC

 


9/11/2006

VLSI Design I; A. Milenkovic

28

Beta Ratio

 - If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- Called *skewed gate*
- Other gates: collapse into equivalent inverter




9/11/2006

VLSI Design I; A. Milenkovic

29

Noise Margins

 - How much noise can a gate input see before it does not recognize the input?




9/11/2006

VLSI Design I; A. Milenkovic

30

Logic Levels

 - To maximize noise margins, select logic levels at




9/11/2006

VLSI Design I; A. Milenkovic

31

Logic Levels

 - To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristic




9/11/2006

VLSI Design I; A. Milenkovic

32

 CMOS Inverter: Switch Model of Dynamic Behavior




9/11/2006

VLSI Design I; A. Milenkovic

33

 CMOS Inverter: Switch Model of Dynamic Behavior



Gate response time is determined by the time to charge C_L through R_p (discharge C_L through R_n)

9/11/2006

VLSI Design I; A. Milenkovic

34

Relative Transistor Sizing

- When designing static CMOS circuits, balance the driving strengths of the transistors by making the PMOS section wider than the NMOS section to
 - maximize the noise margins and
 - obtain symmetrical characteristics

9/11/2006

VLSI Design I; A. Milenkovic

35

Switching Threshold

- V_M where $V_{in} = V_{out}$ (both PMOS and NMOS in saturation since $V_{DS} = V_{GS}$)
$$V_M \approx rV_{DD}/(1 + r)$$
 where $r = k_p V_{DSATp} / k_n V_{DSATn}$
- Switching threshold set by the ratio r , which compares the **relative driving strengths** of the PMOS and NMOS transistors
- **Want** $V_M = V_{DD}/2$ (to have comparable high and low noise margins), so want $r \approx 1$

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k_n' V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k_p' V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)}$$

9/11/2006

VLSI Design I; A. Milenkovic

36

Switch Threshold Example

- In our generic 0.25 micron CMOS process, using the process parameters from slide L03.25, a $V_{DD} = 2.5V$, and a minimum size NMOS device ((W/L)_n of 1.5)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$K'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

$$\frac{(W/L)_p}{(W/L)_n} =$$

9/11/2006

VLSI Design I; A. Milenkovic

37

Switch Threshold Example

- In our generic 0.25 micron CMOS process, using the process parameters, a $V_{DD} = 2.5V$, and a minimum size NMOS device ((W/L)_n of 1.5)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$K'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6}}{-30 \times 10^{-6}} \times \frac{0.63}{-1.0} \times \frac{(1.25 - 0.43 - 0.63/2)}{(1.25 - 0.4 - 1.0/2)} = 3.5$$


$$(W/L)_p = 3.5 \times 1.5 = 5.25 \text{ for a } V_M \text{ of } 1.25V$$

9/11/2006

VLSI Design I; A. Milenkovic

38

Simulated Inverter V_M

 

□ V_M is relatively insensitive to variations in device ratio

- setting the ratio to 3, 2.5 and 2 gives V_M 's of 1.22V, 1.18V, and 1.13V

□ Increasing the width of the PMOS moves V_M towards V_{DD}


□ Increasing the width of the NMOS moves V_M toward GND

9/11/2006

VLSI Design I; A. Milenkovic

39

 Noise Margins Determining V_{IH} and V_{IL}



By definition, V_{IH} and V_{IL} are where $dV_{out}/dV_{in} = -1$ (= gain)

$$NM_H = V_{DD} - V_{IH}$$

$$NM_L = V_{IL} - GND$$

Approximating:

$$V_{IH} = V_M - V_M/g$$

$$V_{IL} = V_M + (V_{DD} - V_M)/g$$


So high gain in the transition region is very desirable

9/11/2006

VLSI Design I; A. Milenkovic

40

CMOS Inverter VTC from Simulation

 


9/11/2006

VLSI Design I; A. Milenkovic

41

Gain Determinates

 

Gain is a strong function of the slopes of the currents in the saturation region, for $V_{in} = V_M$

$$g \approx \frac{(1+r)}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$


Determined by technology parameters, especially channel length modulation (λ). Only designer influence through **supply voltage** and V_M (**transistor sizing**).

9/11/2006

VLSI Design I; A. Milenkovic

42

Impact of Process Variation on VTC Curve

 


process variations (mostly) cause a shift in the switching threshold

9/11/2006

VLSI Design I; A. Milenkovic

43

Scaling the Supply Voltage

 

9/11/2006

VLSI Design I; A. Milenkovic

44