
CPE/EE 427, CPE 527
VLSI Design I
Delay Estimation

Department of Electrical and Computer Engineering
University of Alabama in Huntsville


Aleksandar Milenkovic (www.ece.uah.edu/~milenka)

Review: CMOS Circuit Styles

- **Static complementary CMOS** - except during switching, output connected to either VDD or GND via a low-resistance path
 - high noise margins
 - full rail to rail swing
 - VOH and VOL are at VDD and GND, respectively
 - low output impedance, high input impedance
 - no steady state path between VDD and GND (no static power consumption)
 - delay a function of load capacitance and transistor resistance
 - comparable rise and fall times (under the appropriate transistor sizing conditions)
- **Dynamic CMOS** - relies on temporary storage of signal values on the capacitance of high-impedance circuit nodes
 - simpler, faster gates
 - increased sensitivity to noise

Review: Static Complementary CMOS

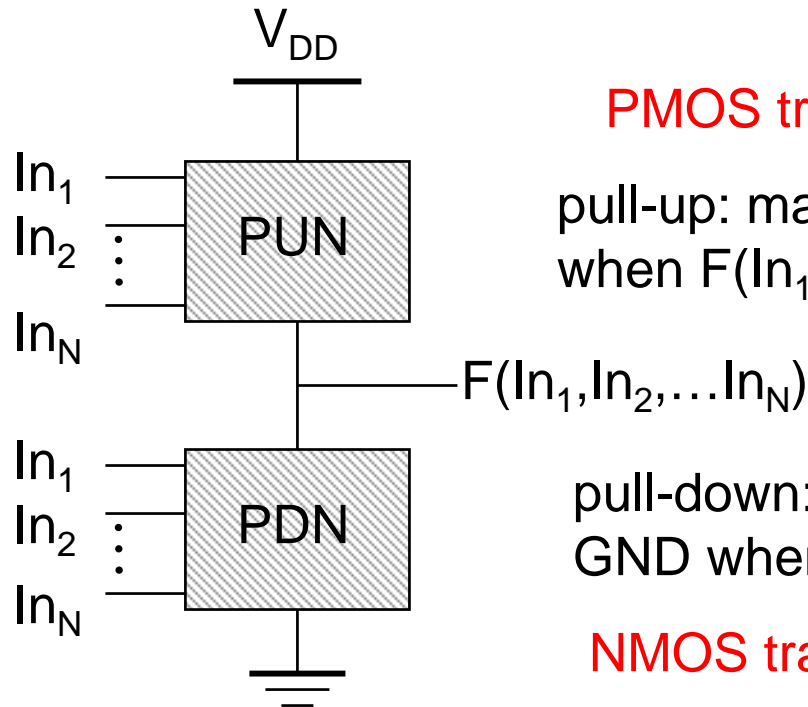Pull-up network (PUN) and pull-down network (PDN)



PMOS transistors only



pull-up: make a connection from V_{DD} to F
when $F(In_1, In_2, \dots, In_N) = 1$

pull-down: make a connection from F to
GND when $F(In_1, In_2, \dots, In_N) = 0$



NMOS transistors only

PUN and PDN are **dual** logic networks

Review: OAI22 Logic Graph

  

Review: VTC is Data-Dependent

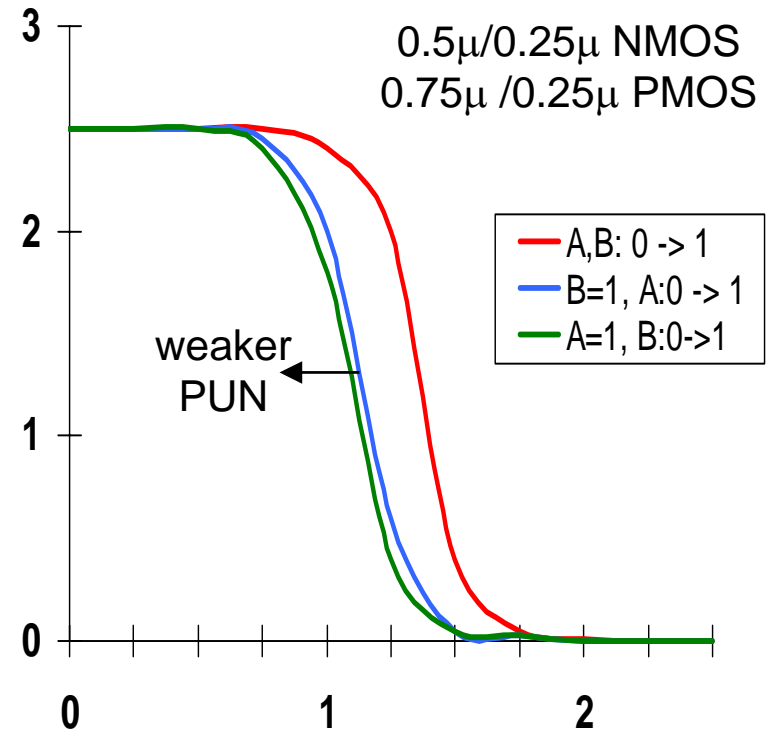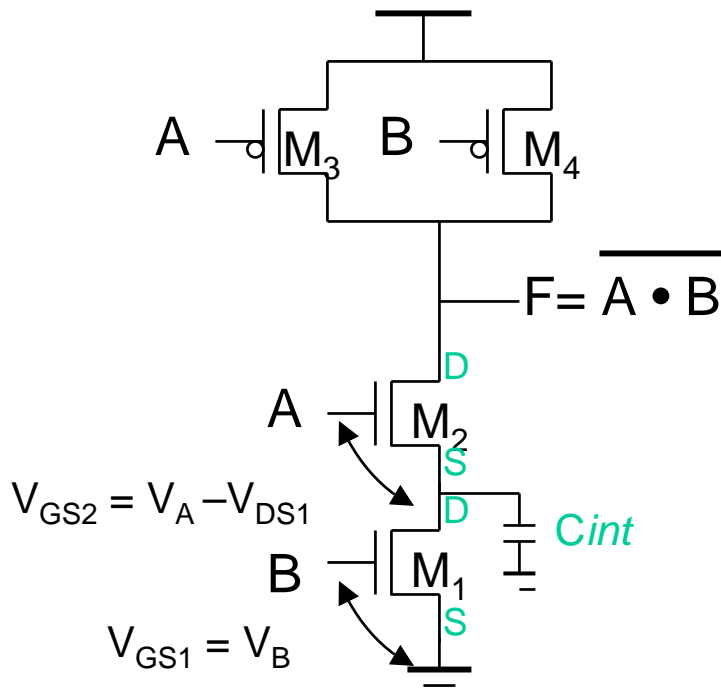


- The threshold voltage of M_2 is higher than M_1 due to the body effect (γ)

$$V_{Tn1} = V_{Tn0}$$

$$V_{Tn2} = V_{Tn0} + \gamma(\sqrt{(|2\phi_F| + V_{int})} - \sqrt{|2\phi_F|})$$


since V_{SB} of M_2 is not zero (when $V_B = 0$) due to the presence of C_{int}

Static CMOS Full Adder Circuit

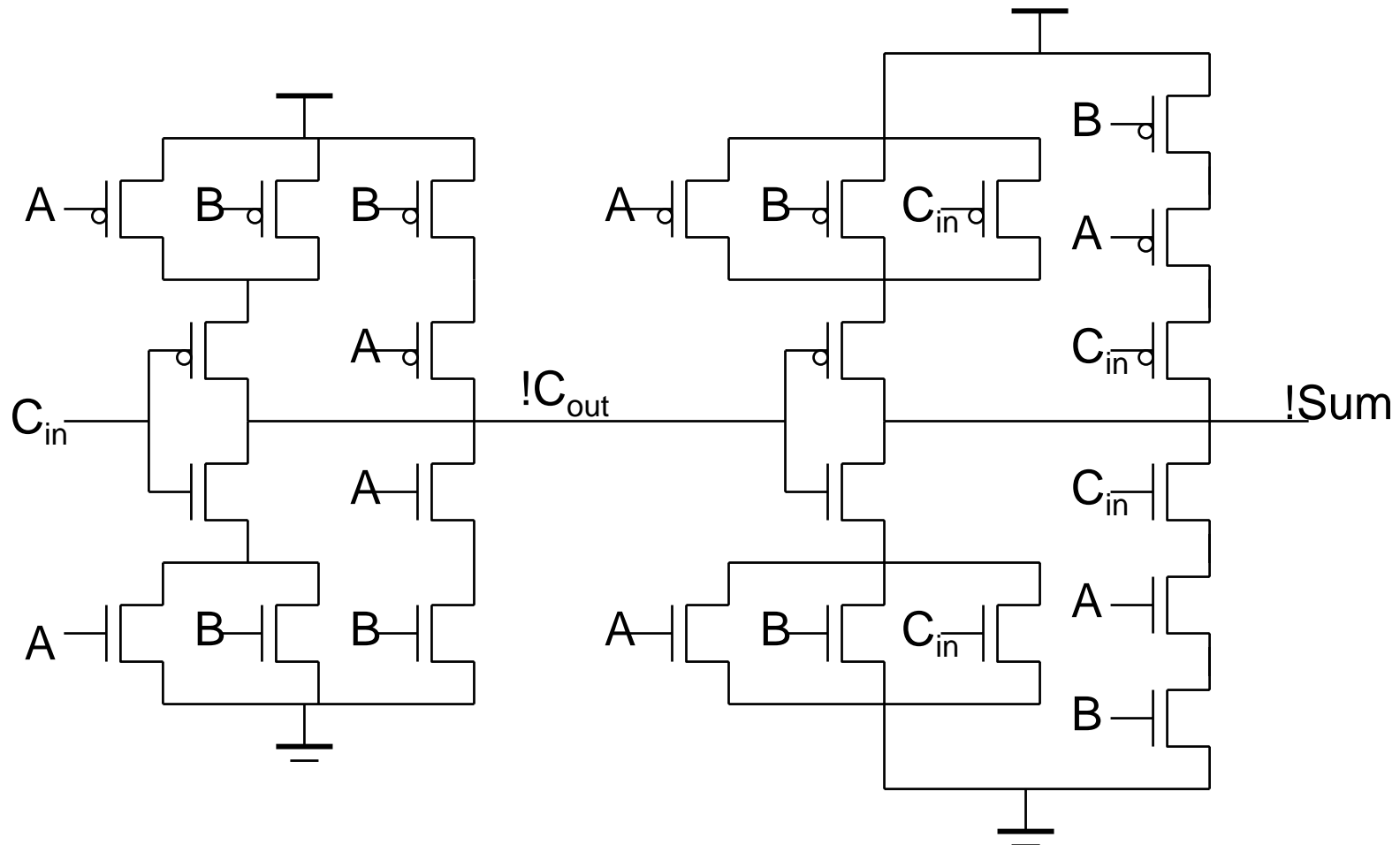

Static CMOS Full Adder Circuit
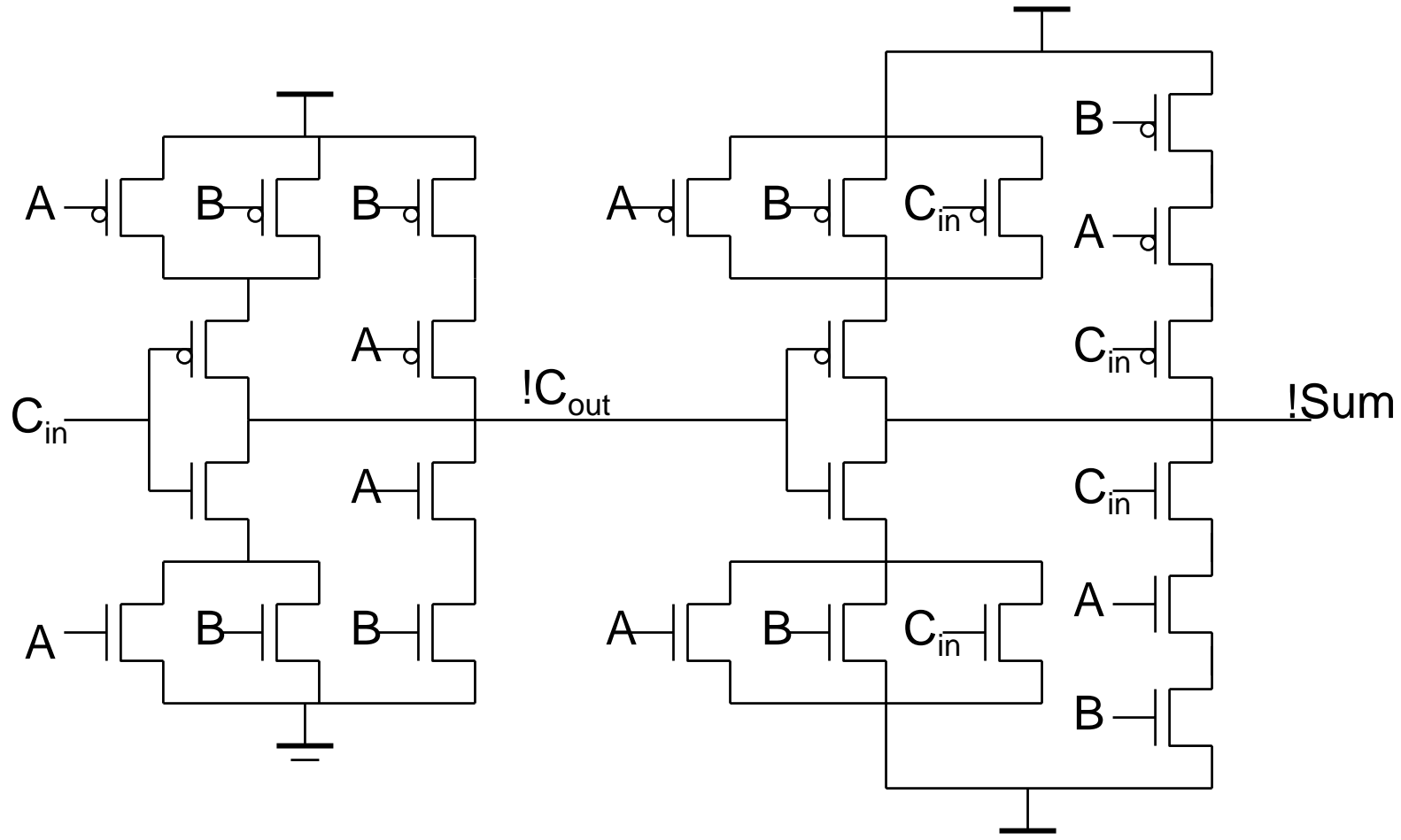
$$\neg C_{out} = \neg C_{in} \& (\neg A \mid \neg B) \mid (\neg A \& \neg B) \quad \neg Sum = C_{out} \& (\neg A \mid \neg B \mid \neg C_{in}) \mid (\neg A \& \neg B \& \neg C_{in})$$



$$C_{out} = C_{in} \& (A \mid B) \mid (A \& B)$$

$$Sum = \neg C_{out} \& (A \mid B \mid C_{in}) \mid (A \& B \& C_{in})$$

Transient Response

- *DC analysis* tells us V_{out} if V_{in} is constant
- *Transient analysis* tells us $V_{out}(t)$ if $V_{in}(t)$ changes
 - Requires solving differential equations
- Input is usually considered to be a step or ramp
 - From 0 to V_{DD} or vice versa


Inverter Step Response

- Ex: find step response of inverter driving load cap

$$V_{in}(t) =$$

$$V_{out}(t < t_0) =$$

$$\frac{dV_{out}(t)}{dt} =$$

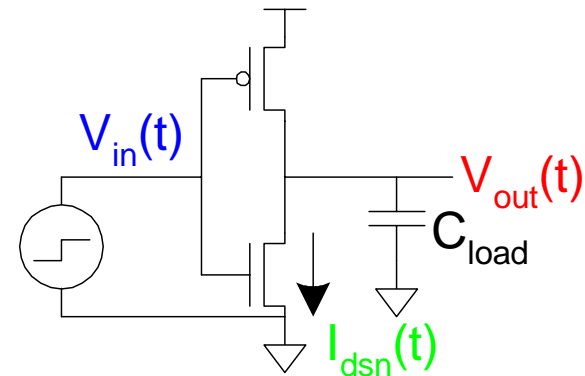


Inverter Step Response

- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) =$$

$$\frac{dV_{out}(t)}{dt} =$$

 


Inverter Step Response

- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} =$$

 

Inverter Step Response


- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
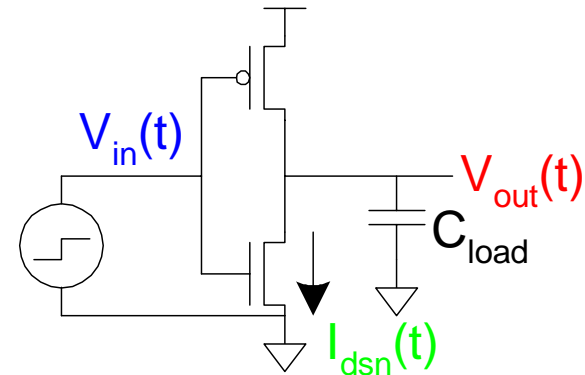
$$I_{dsn}(t) = \begin{cases} & t \leq t_0 \\ V_{out} > V_{DD} - V_t & \\ V_{out} < V_{DD} - V_t & \end{cases}$$




Inverter Step Response

- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$
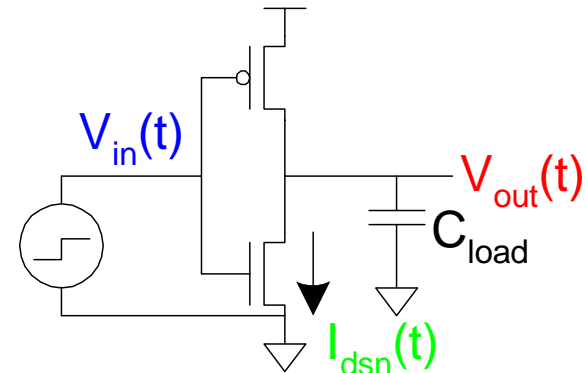
$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$



$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V)^2 & V_{out} > V_{DD} - V_t \\ \beta\left(V_{DD} - V_t - \frac{V_{out}(t)}{2}\right)V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$

Inverter Step Response



- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
 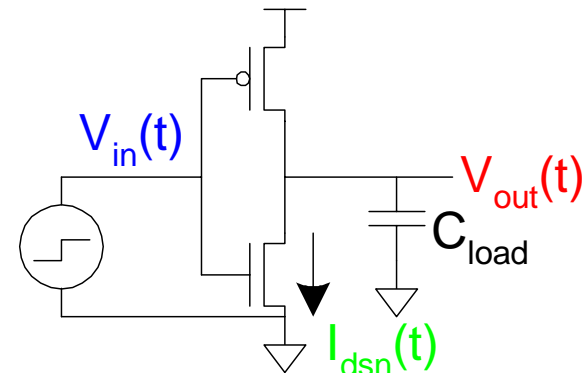
$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V)^2 & V_{out} > V_{DD} - V_t \\ \beta\left(V_{DD} - V_t - \frac{V_{out}(t)}{2}\right)V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$



Delay Definitions

- t_{pdr} :
- t_{pdf} :
- t_{pd} :
- t_r :
- t_f : *fall time*

Delay Definitions


- t_{pdr} : *rising propagation delay*
 - From input to rising output crossing $V_{DD}/2$
- t_{pdf} : *falling propagation delay*
 - From input to falling output crossing $V_{DD}/2$
- t_{pd} : *average propagation delay*
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- t_r : *rise time*
 - From output crossing $0.2 V_{DD}$ to $0.8 V_{DD}$
- t_f : *fall time*
 - From output crossing $0.8 V_{DD}$ to $0.2 V_{DD}$

Delay Definitions

- t_{cdr} : *rising contamination delay*
 - From input to rising output crossing $V_{DD}/2$
- t_{cdf} : *falling contamination delay*
 - From input to falling output crossing $V_{DD}/2$
- t_{cd} : *average contamination delay*
 - $t_{pd} = (t_{cdr} + t_{cdf})/2$

Simulated Inverter Delay

 - Solving differential equations by hand is too hard
- SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too!
- But simulations take time to write





Delay Estimation

- We would like to be able to easily estimate delay
 - Not as accurate as simulation
 - But easier to ask “What if?”
- The step response usually looks like a 1st order RC response with a decaying exponential.
- Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use *effective resistance* R
 - So that $t_{pd} = RC$
- Characterize transistors by finding their effective R
 - Depends on average current as gate switches

RC Delay Models

  - Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- Capacitance proportional to width
- Resistance inversely proportional to width




Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).

 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).



 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).




3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




3-input NAND Caps

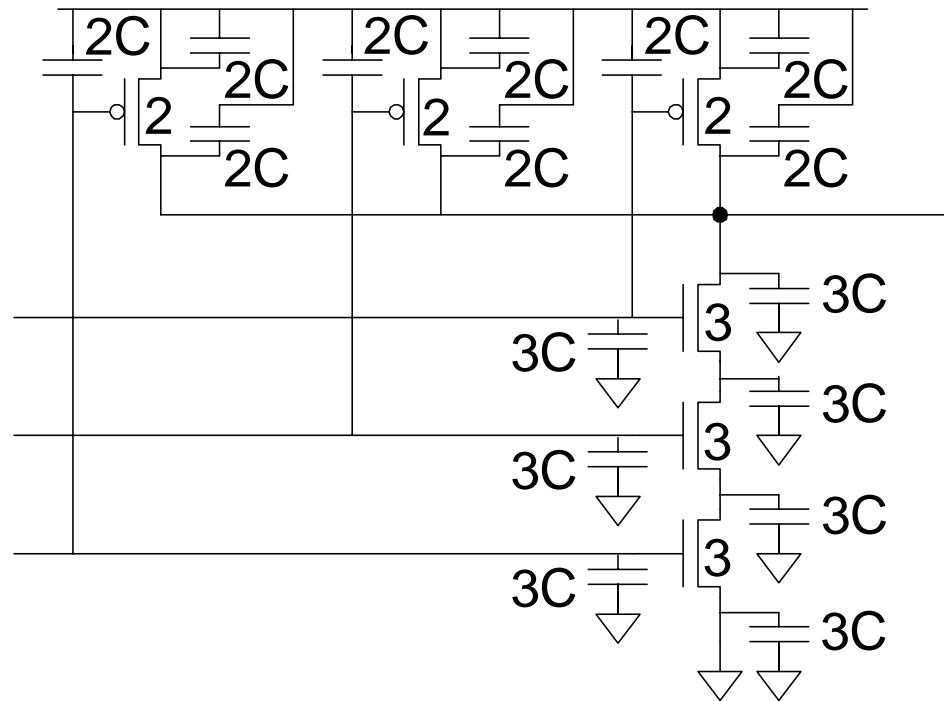- Annotate the 3-input NAND gate with gate and diffusion capacitance.



3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




Elmore Delay

- ON transistors look like resistors
- Pullup or pulldown network modeled as *RC ladder*
- Elmore delay of RC ladder


$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



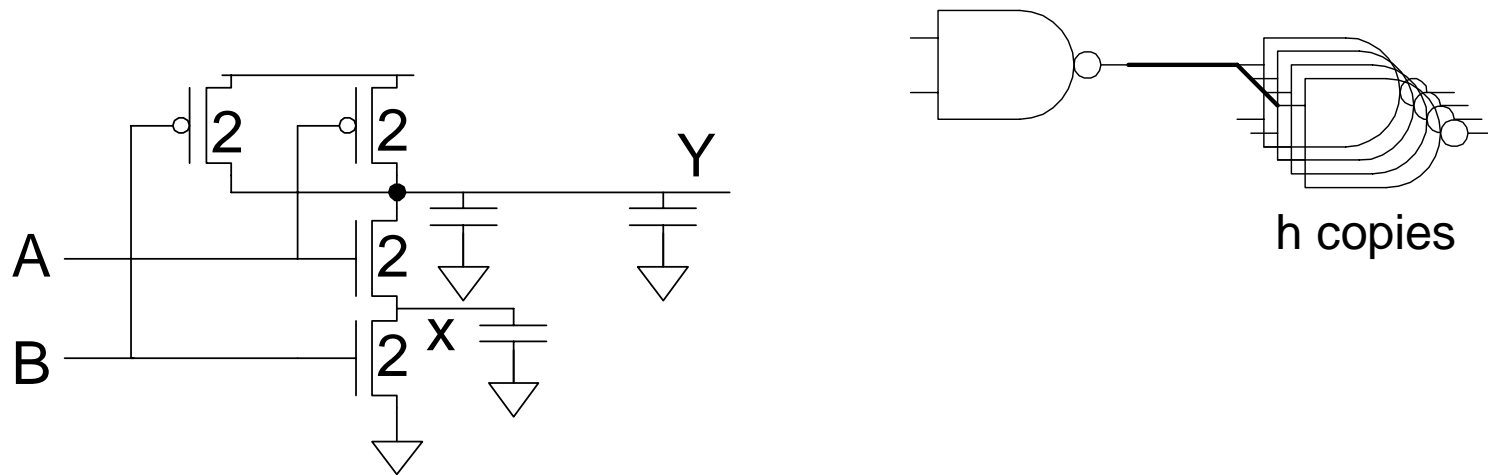
Example: 2-input NAND

- Estimate worst-case rising and falling delay of 2-input NAND driving h identical gates.



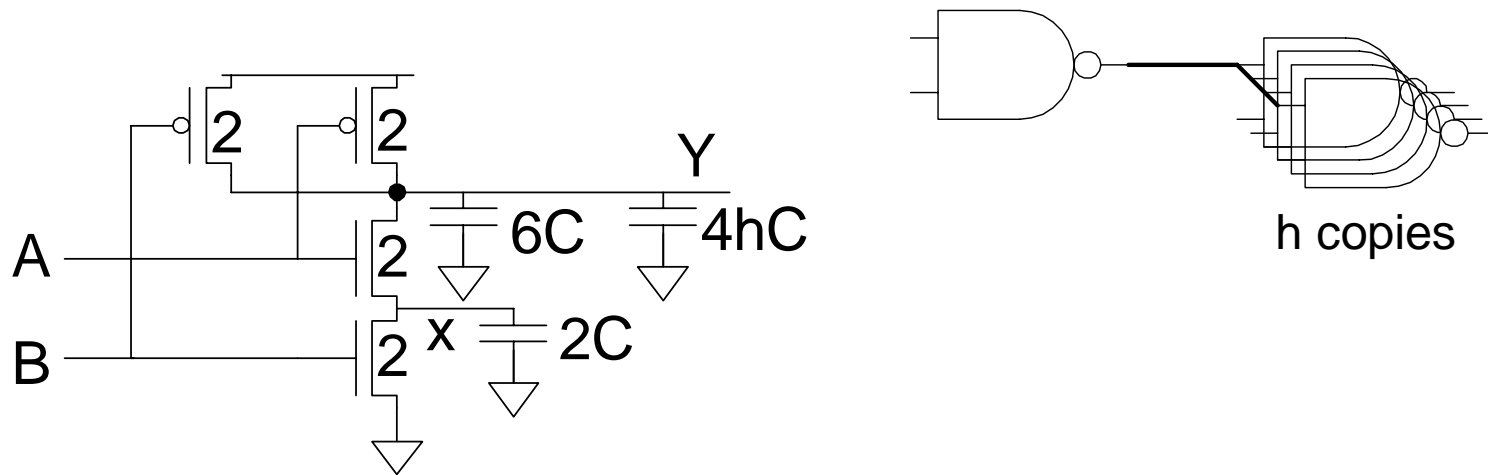
Example: 2-input NAND

- Estimate rising and falling propagation delays of a 2-input NAND driving h identical gates.



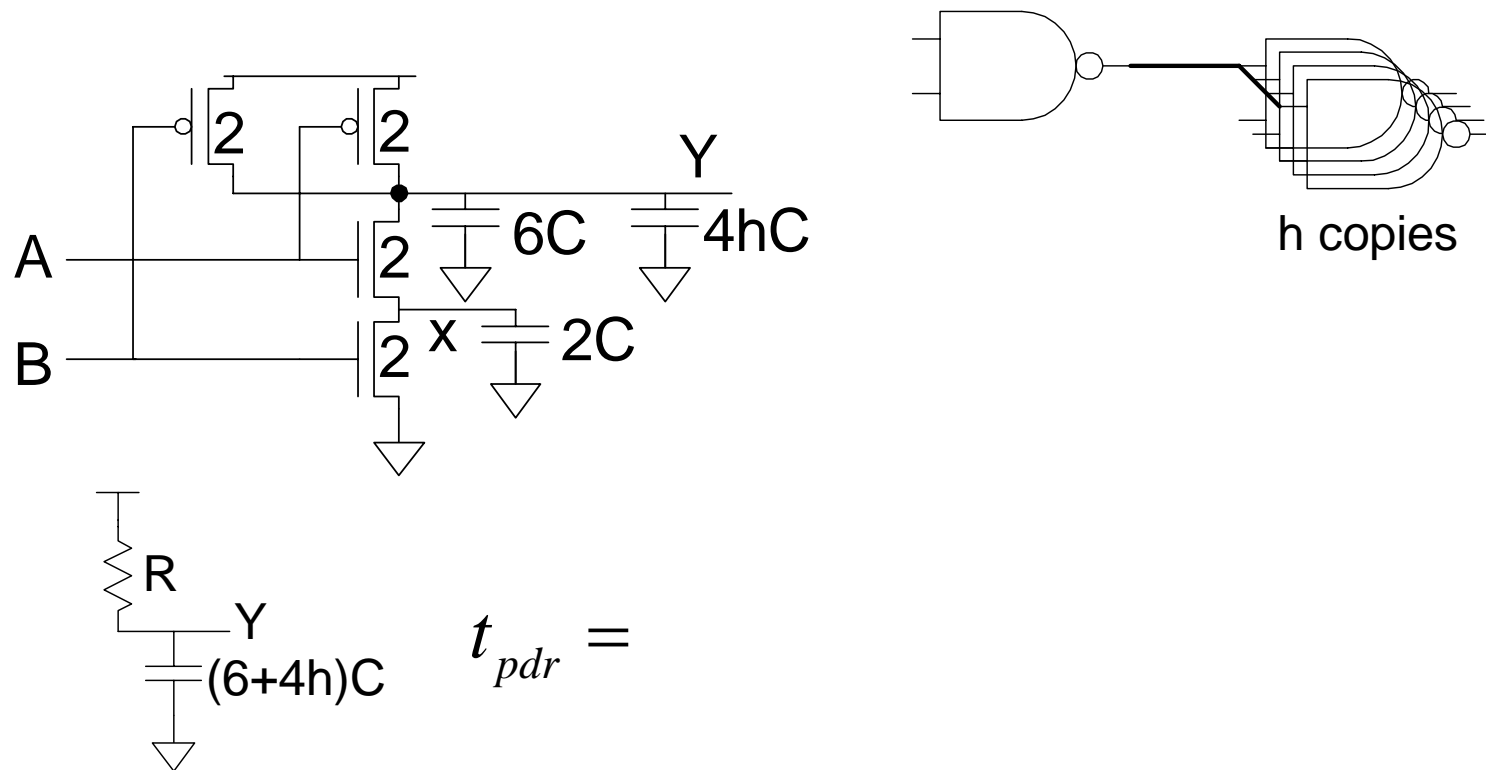
Example: 2-input NAND

- Estimate **rising** and falling propagation delays of a 2-input NAND driving h identical gates.



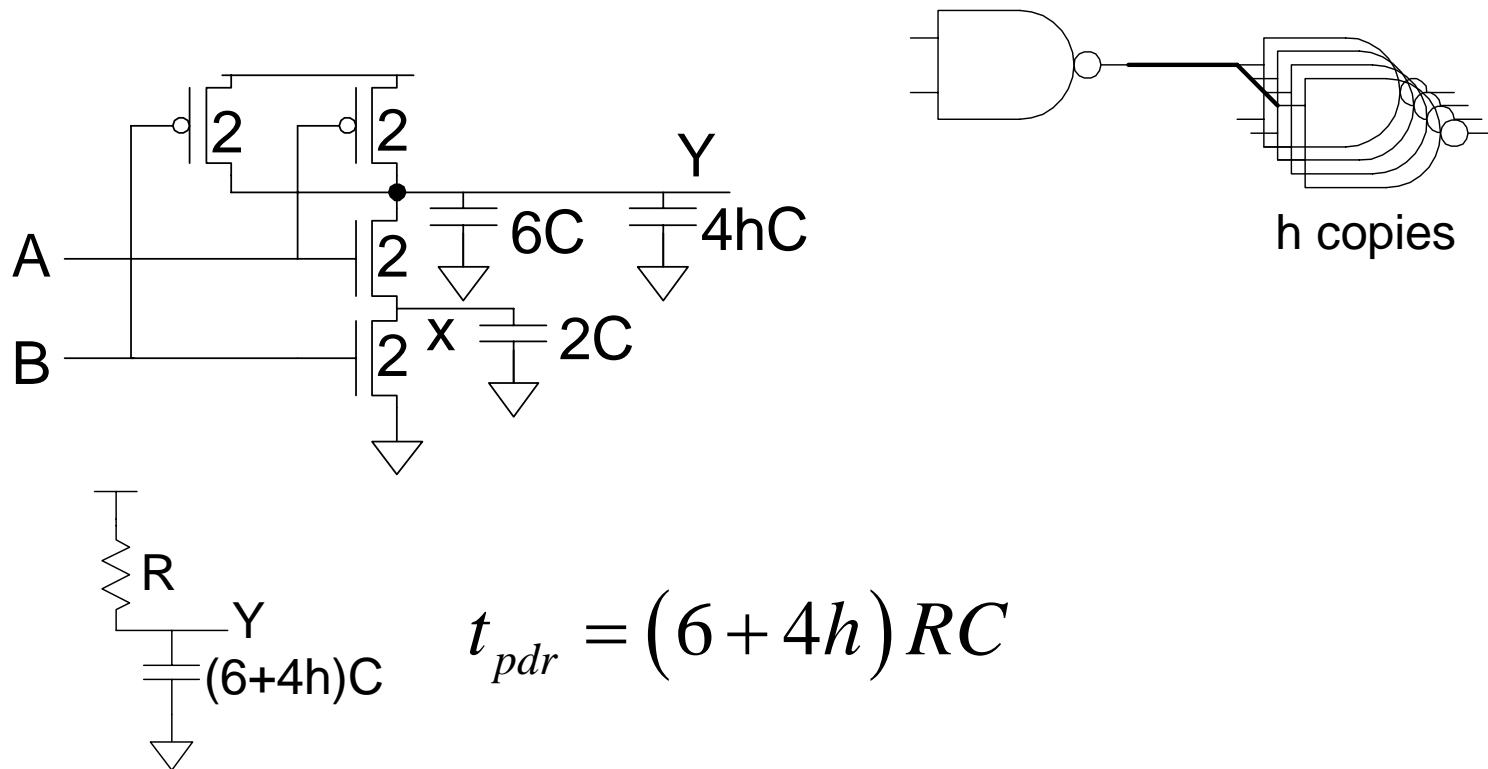
Example: 2-input NAND

- Estimate **rising** and falling propagation delays of a 2-input NAND driving h identical gates.





 
Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



  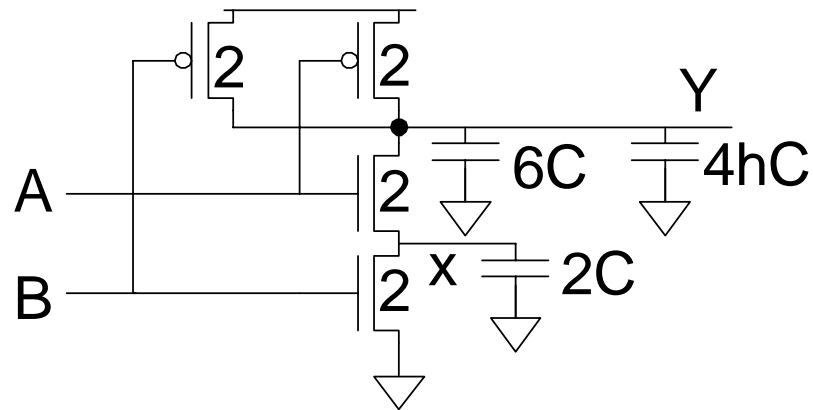
Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



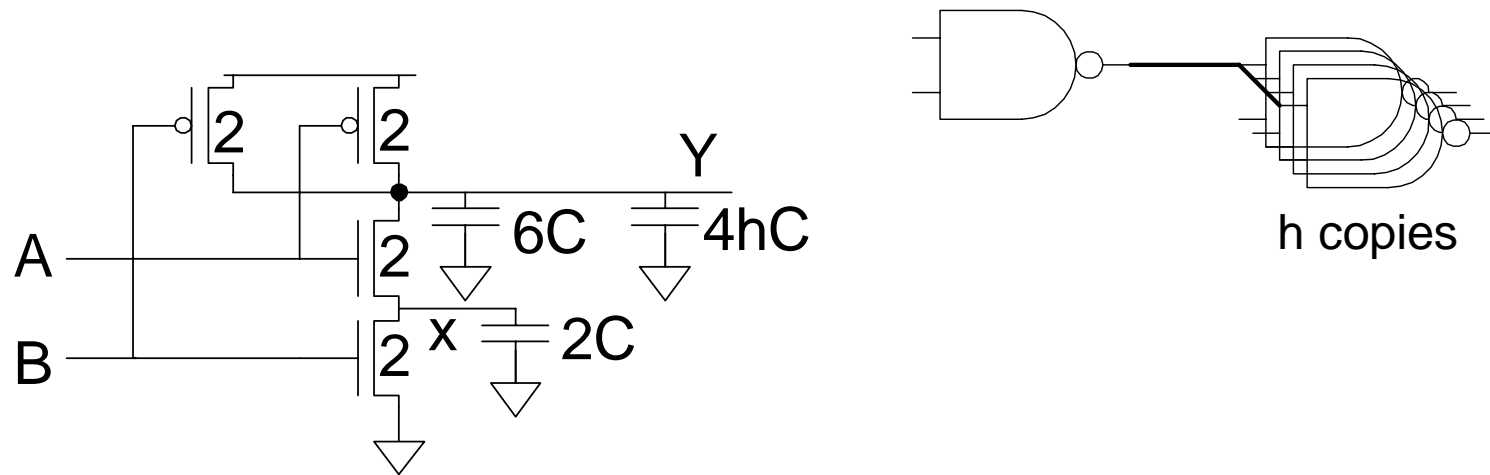Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.





$$\begin{aligned}
 t_{pdf} &= (2C)\left(\frac{R}{2}\right) + \left[(6 + 4h)C\right]\left(\frac{R}{2} + \frac{R}{2}\right) \\
 &= (7 + 4h)RC
 \end{aligned}$$

Delay Components

- Delay has two parts
 - *Parasitic delay*
 - 6 or 7 RC
 - Independent of load
 - *Effort delay*
 - 4h RC
 - Proportional to load capacitance

Contamination Delay

 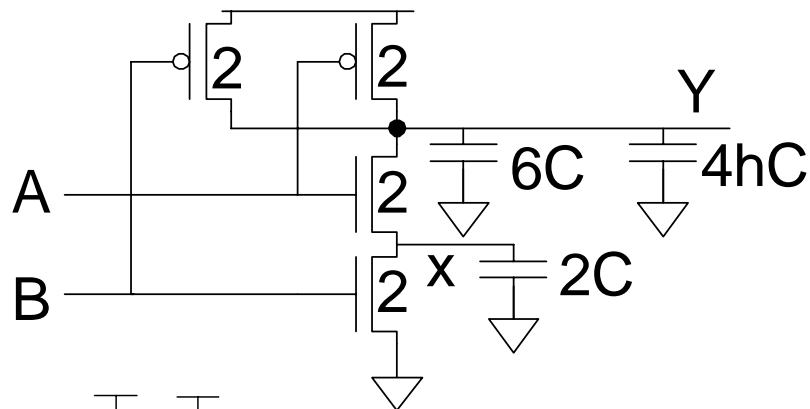
- Best-case (contamination) delay can be substantially less than propagation delay.
- Ex: If both inputs fall simultaneously



$$t_{cdr} = (3 + 2h)RC$$

Diffusion Capacitance

 - we assumed contacted diffusion on every s / d.
- Good layout minimizes diffusion area
- Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by $2C$
 - Merged uncontacted diffusion might help too



Layout Comparison

- Which layout is better?

