

---

**CPE/EE 427, CPE 527  
VLSI Design I  
Complementary CMOS Logic Gates**

Department of Electrical and Computer Engineering  
University of Alabama in Huntsville

Aleksandar Milenkovic ( [www.ece.uah.edu/~milenka](http://www.ece.uah.edu/~milenka) )

---

---

**Static CMOS Logic**

---

## CMOS Circuit Styles

- **Static complementary CMOS** - except during switching, output connected to either VDD or GND via a low-resistance path
  - high noise margins
    - full rail to rail swing
    - VOH and VOL are at VDD and GND, respectively
  - low output impedance, high input impedance
  - no steady state path between VDD and GND (no static power consumption)
  - delay a function of load capacitance and transistor resistance
  - comparable rise and fall times (under the appropriate transistor sizing conditions)
- **Dynamic CMOS** - relies on temporary storage of signal values on the capacitance of high-impedance circuit nodes
  - simpler, faster gates
  - increased sensitivity to noise


9/18/2006

VLSI Design I; A. Milenkovic

3
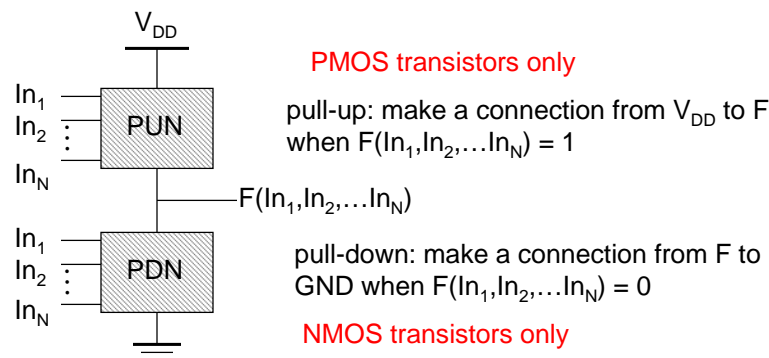
## Static Complementary CMOS

Pull-up network (PUN) and pull-down network (PDN)



PUN and PDN are **dual** logic networks



9/18/2006

VLSI Design I; A. Milenkovic



4

## Threshold Drops

PUN

  

PDN

  



9/18/2006

VLSI Design I; A. Milenkovic



5

## Threshold Drops

PUN

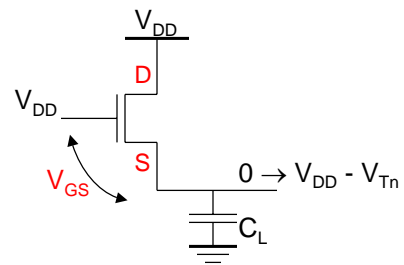 

PDN

  


9/18/2006

VLSI Design I; A. Milenkovic


6
 
## Construction of PDN

- NMOS devices in **series** implement a NAND function



 - NMOS devices in **parallel** implement a NOR function



9/18/2006

VLSI Design I; A. Milenkovic

7

## Dual PUN and PDN

- PUN and PDN are dual networks

- DeMorgan's theorems

$$\overline{A + B} = \overline{A} \cdot \overline{B} \quad [!(A + B) = !A \cdot !B \text{ or } !(A | B) = !A \& !B]$$

$$\overline{A \cdot B} = \overline{A} + \overline{B} \quad [!(A \cdot B) = !A + !B \text{ or } !(A \& B) = !A | !B]$$


- a **parallel** connection of transistors in the PUN corresponds to a **series** connection of the PDN
- Complementary gate is naturally **inverting** (NAND, NOR, AOI, OAI)
- Number of transistors for an N-input logic gate is **2N**

9/18/2006


VLSI Design I; A. Milenkovic

8

## CMOS NAND

 

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0


 


9/18/2006

VLSI Design I; A. Milenkovic

9

## CMOS NAND

 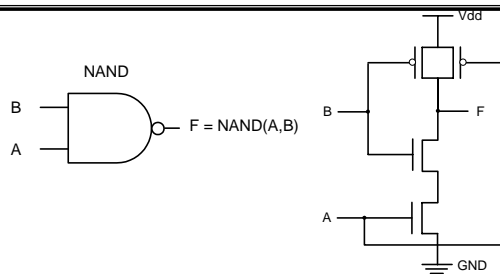


9/18/2006


VLSI Design I; A. Milenkovic

10

## CMOS NOR

 

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0






 


9/18/2006

VLSI Design I; A. Milenkovic

11

## CMOS NOR

      


9/18/2006

VLSI Design I; A. Milenkovic

12

## Complex CMOS Gate

 


9/18/2006

VLSI Design I; A. Milenkovic

13

## Complex CMOS Gate

 


9/18/2006

VLSI Design I; A. Milenkovic

14

## XNOR/XOR Implementation

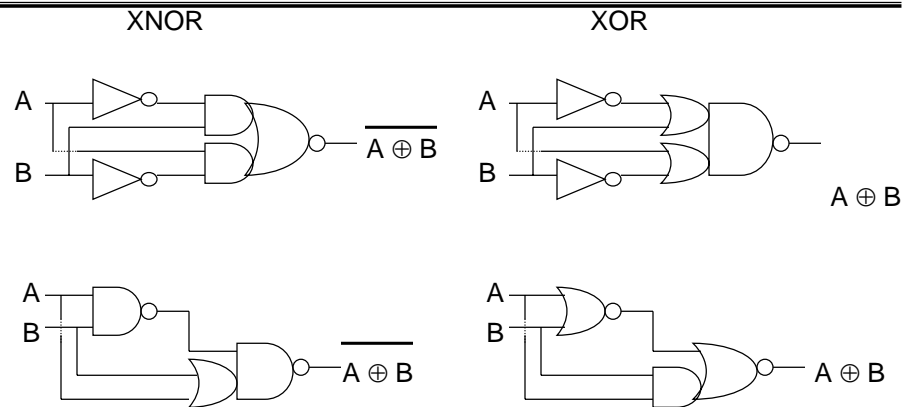

- How many transistors in each?
- Can you create the stick transistor layout for the lower left circuit?

9/18/2006

VLSI Design I; A. Milenkovic

15

## Combinational Logic Cells

- CMOS logic cells
  - AND-OR-INVERT (AOI)
  - OR-AND-INVERT(OAI)

- Example: AOI221

$$Z = (A \cdot B + C \cdot D + E)'$$

$$Z = \text{AOI221}(A, B, C, D, E)$$


Exercise: Construct this logic cell?

- Example: OAI321

$$Z = [(A+B+C) \cdot (D+E) \cdot F]'$$

$$Z = \text{OAI321}(A, B, C, D, E, F)$$

Exercise: Construct this logic cell?

 


9/18/2006

VLSI Design I; A. Milenkovic

16



## AOI221

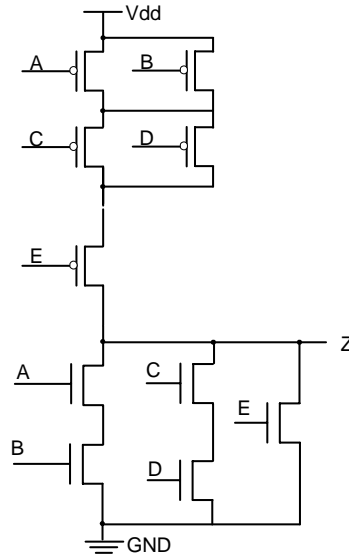


9/18/2006

VLSI Design I; A. Milenkovic

17

## Standard Cell Layout Methodology

 


What logic function is this?

9/18/2006

VLSI Design I; A. Milenkovic

18

## OAI21 Logic Graph

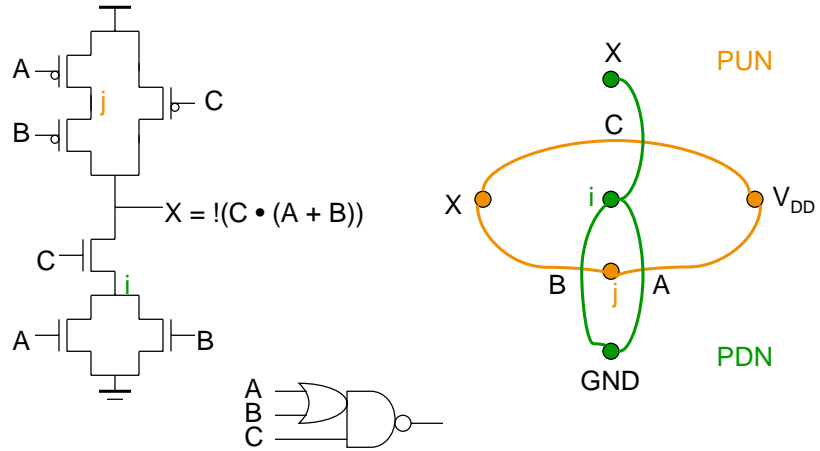


9/18/2006

VLSI Design I; A. Milenkovic

19
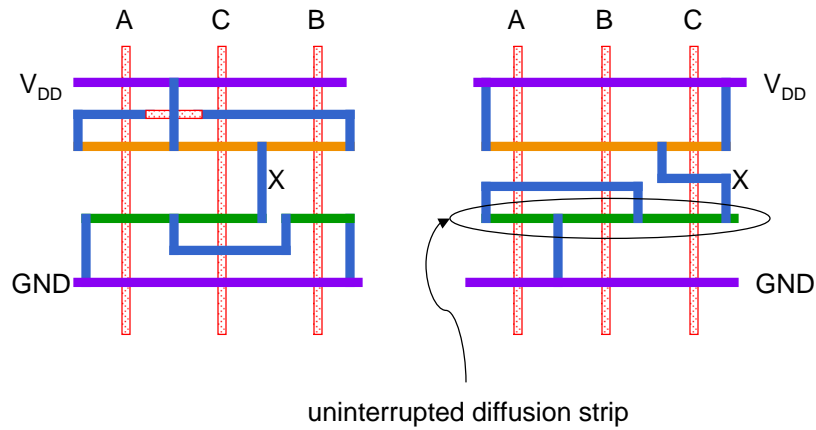
## Two Stick Layouts of $!(C \cdot (A + B))$




9/18/2006

VLSI Design I; A. Milenkovic

20
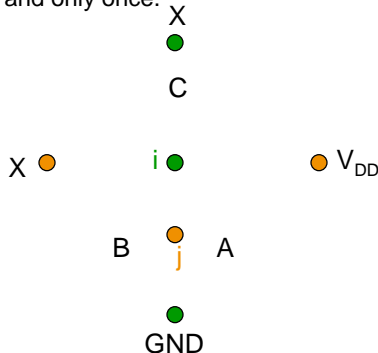
## Consistent Euler Path

- An uninterrupted diffusion strip is possible only if there exists a Euler path in the logic graph
  - Euler path: a path through all nodes in the graph such that each edge is visited once and only once.



- For a single poly strip for every input signal, the Euler paths in the PUN and PDN must be **consistent** (the same)


9/18/2006

VLSI Design I; A. Milenkovic

21
 
## Consistent Euler Path

- An uninterrupted diffusion strip is possible only if there exists a Euler path in the logic graph
  - Euler path: a path through all nodes in the graph such that each edge is visited once and only once.




- For a single poly strip for every input signal, the Euler paths in the PUN and PDN must be **consistent** (the same)

9/18/2006

VLSI Design I; A. Milenkovic

22

## OAI22 Logic Graph

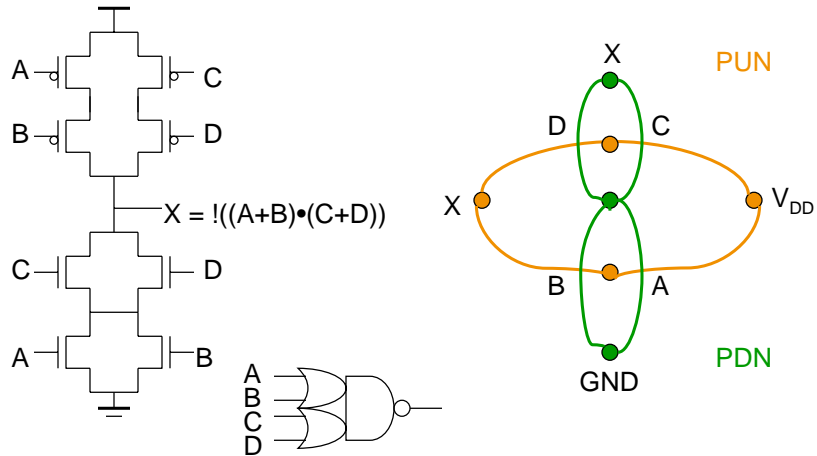


9/18/2006

VLSI Design I; A. Milenkovic

23

## OAI22 Layout

 

- Some functions have no consistent Euler path like  $x = \overline{(a + bc + de)}$  (but  $x = \overline{(bc + a + de)}$  does!)

9/18/2006

VLSI Design I; A. Milenkovic

24

## Combinational Logic Cells (cont'd)

- The AOI family of cells with 3 index numbers or less
  - $X = \{AOI, OAI, AO, OA\}; a,b,c=\{2,3\}$


Cell Type	Cells	Number of Unique Cells
Xa1	X21, X31	2
Xa11	X211, X311	2
Xab	X22, X33, X32	3
Xab1	X221, X321, X331	3
Xabc	X222, X333, X332, X322	4
<b>Total</b>		<b>14</b>

9/18/2006

VLSI Design I; A. Milenkovic

25

## VTC is Data-Dependent

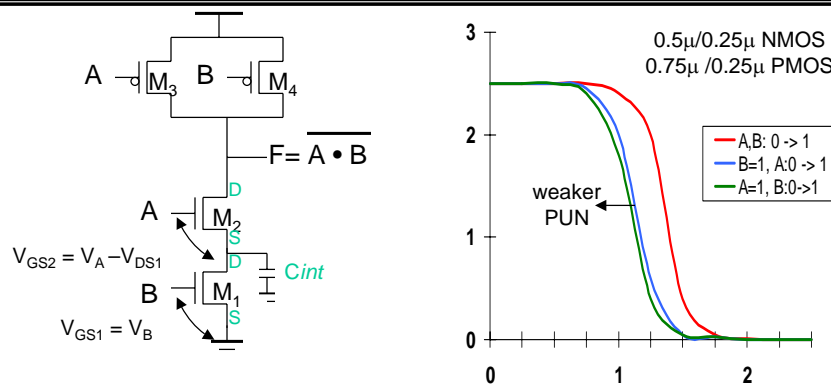

- The threshold voltage of  $M_2$  is higher than  $M_1$  due to the body effect ( $\gamma$ )

$$V_{Tn1} = V_{Tn0}$$

$$V_{Tn2} = V_{Tn0} + \gamma(\sqrt{|2\phi_F| + V_{int}} - \sqrt{|2\phi_F|})$$


since  $V_{SB}$  of  $M_2$  is not zero (when  $V_B = 0$ ) due to the presence of  $C_{int}$

9/18/2006

VLSI Design I; A. Milenkovic

26

## Static CMOS Full Adder Circuit

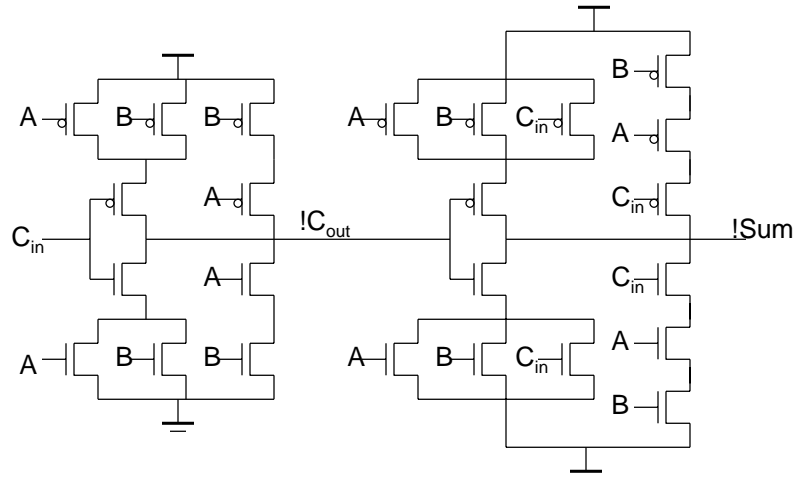


9/18/2006

VLSI Design I; A. Milenkovic

27
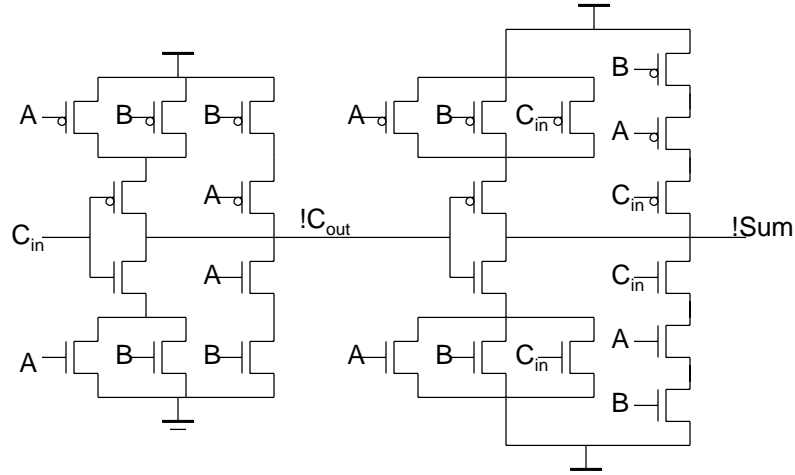
## Static CMOS Full Adder Circuit

$$\overline{C_{out}} = \overline{C_{in}} \& (\overline{A} \mid \overline{B}) \mid (A \& \overline{B}) \quad \overline{Sum} = C_{out} \& (\overline{A} \mid \overline{B} \mid \overline{C_{in}}) \mid (A \& \overline{B} \& \overline{C_{in}})$$



$$C_{out} = C_{in} \& (A \mid B) \mid (A \& B) \quad Sum = \overline{C_{out}} \& (A \mid B \mid C_{in}) \mid (A \& B \& C_{in})$$

9/18/2006

VLSI Design I; A. Milenkovic

28