

---

**CPE/EE 427, CPE 527  
VLSI Design I  
Circuit Families**

Department of Electrical and Computer Engineering  
University of Alabama in Huntsville

Aleksandar Milenkovic ( [www.ece.uah.edu/~milenka](http://www.ece.uah.edu/~milenka) )

---


---

**Outline**

- Skewed Gates
- Pseudo-nMOS Logic
- Dynamic Logic
- Pass Transistor Logic
 
## Introduction

- What makes a circuit fast?
  - $I = C \, dV/dt \rightarrow t_{pd} \propto (C/I) \, \Delta V$
  - low capacitance
  - high current
  - small swing
- Logical effort is proportional to  $C/I$
- pMOS are the enemy!
  - High capacitance for a given current
- Can we take the pMOS capacitance off the input?
- Various circuit families try to do this...





11/1/2006

VLSI Design I; A. Milenkovic

3
  
## Pseudo-nMOS

- In the old days, nMOS processes had no pMOS
  - Instead, use pull-up transistor that is always ON
- In CMOS, use a pMOS that is always ON
  - *Ratio* issue
  - Make pMOS about  $\frac{1}{4}$  effective strength of pulldown network





11/1/2006

VLSI Design I; A. Milenkovic


4

## Asymmetric Gates

  


**FIG 6.7** Resettable buffer optimized for data input

## Skewed Gates

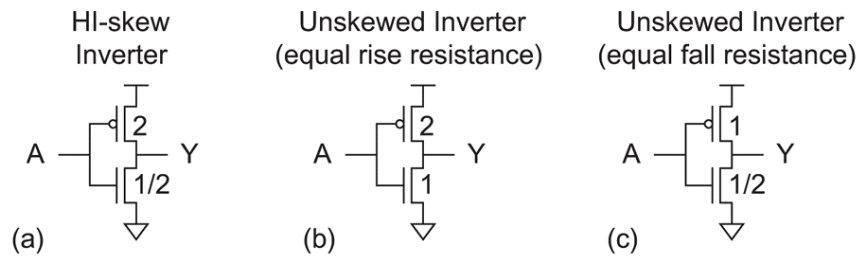

**FIG 6.9** Logical effort calculation for HI-skew inverter


## Skewed Gates

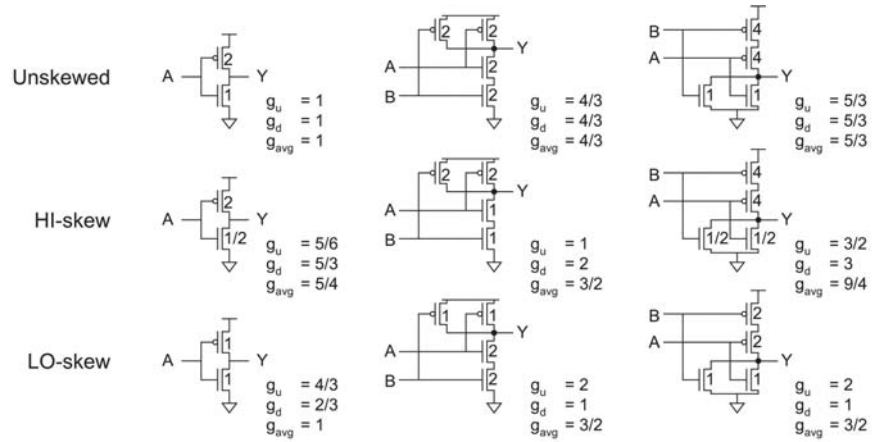


**FIG 6.10** Catalog of skewed gates
 
## Pseudo-nMOS Gates


- Design for unit current on output to compare with unit inverter.
- pMOS fights nMOS




Inverter

 

NAND2

 


NOR2

 

 
## Pseudo-nMOS Gates

- Design for unit current on output to compare with unit inverter.
- pMOS fights nMOS




Inverter

 


$$\begin{aligned} g_u &= \\ g_d &= \\ g_{avg} &= \\ p_u &= \\ p_d &= \\ p_{avg} &= \end{aligned}$$

NAND2

 

$$\begin{aligned} g_u &= \\ g_d &= \\ g_{avg} &= \\ p_u &= \\ p_d &= \\ p_{avg} &= \end{aligned}$$

NOR2

 

$$\begin{aligned} g_u &= \\ g_d &= \\ g_{avg} &= \\ p_u &= \\ p_d &= \\ p_{avg} &= \end{aligned}$$


11/1/2006

VLSI Design I; A. Milenkovic


9
 
## Pseudo-nMOS Gates

- Design for unit current on output to compare with unit inverter.
- pMOS fights nMOS




Inverter

 


$$\begin{aligned} g_u &= 4/3 \\ g_d &= 4/9 \\ g_{avg} &= 8/9 \\ p_u &= \\ p_d &= \\ p_{avg} &= \end{aligned}$$

NAND2

 

$$\begin{aligned} g_u &= 8/3 \\ g_d &= 8/9 \\ g_{avg} &= 16/9 \\ p_u &= \\ p_d &= \\ p_{avg} &= \end{aligned}$$

NOR2

 

$$\begin{aligned} g_u &= 4/3 \\ g_d &= 4/9 \\ g_{avg} &= 8/9 \\ p_u &= \\ p_d &= \\ p_{avg} &= \end{aligned}$$


11/1/2006

VLSI Design I; A. Milenkovic


10
 
## Pseudo-nMOS Gates


- Design for unit current on output to compare with unit inverter.
- pMOS fights nMOS




Inverter

 

NAND2

 

NOR2

 

11/1/2006


VLSI Design I; A. Milenkovic

11

## Pseudo-nMOS Design

- Ex: Design a k-input AND gate using pseudo-nMOS. Estimate the delay driving a fanout of H

- $G =$
- $F =$
- $P =$
- $N =$
- $D =$

 

11/1/2006


VLSI Design I; A. Milenkovic

12
 
## Pseudo-nMOS Design

- Ex: Design a k-input AND gate using pseudo-nMOS. Estimate the delay driving a fanout of H

- $G = 1 * 8/9 = 8/9$
- $F = GBH = 8H/9$
- $P = 1 + (4+8k)/9 = (8k+13)/9$
- $N = 2$
- $D = NF^{1/N} + P = \frac{4\sqrt{2H}}{3} + \frac{8k+13}{9}$




11/1/2006

VLSI Design I; A. Milenkovic

13
 
## Pseudo-nMOS Power

- Pseudo-nMOS draws power whenever  $Y = 0$ 
  - Called static power  $P = I \cdot V_{DD}$
  - A few mA / gate \* 1M gates would be a problem
  - This is why nMOS went extinct!
- Use pseudo-nMOS sparingly for wide NORs
- Turn off pMOS when not in use




11/1/2006

VLSI Design I; A. Milenkovic

14
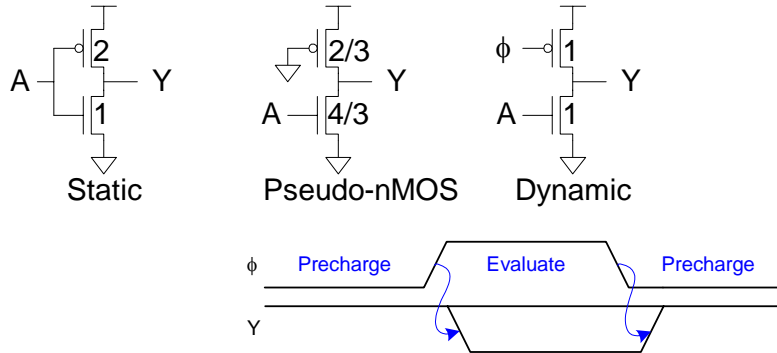
## Dynamic Logic

- *Dynamic gates* uses a clocked pMOS pullup
- Two modes: *precharge* and *evaluate*




11/1/2006

VLSI Design I; A. Milenkovic

15
 
## The Foot

- What if pulldown network is ON during precharge?
- Use series evaluation transistor to prevent fight.




11/1/2006

VLSI Design I; A. Milenkovic

16



## Logical Effort

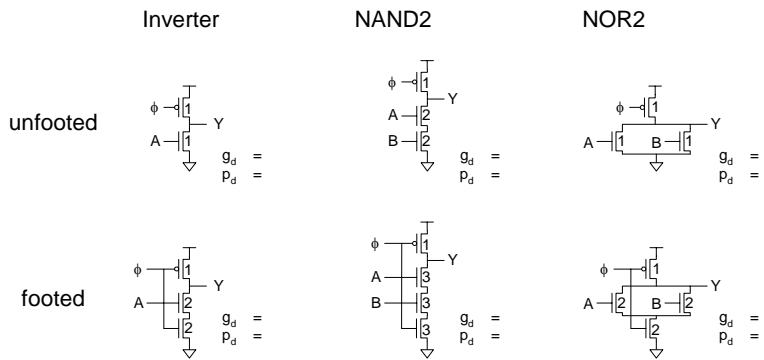


11/1/2006

VLSI Design I; A. Milenkovic

17

## Logical Effort

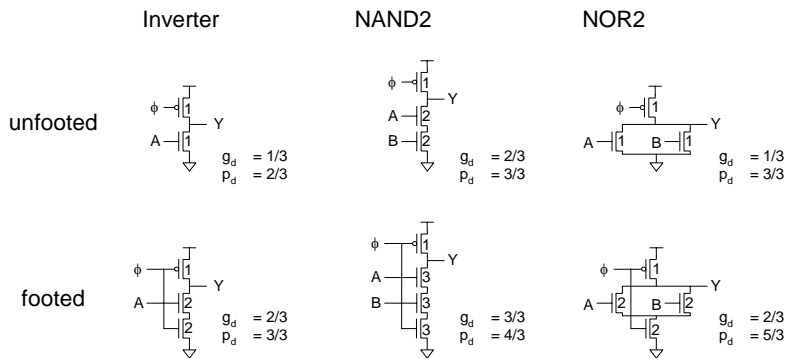

11/1/2006


VLSI Design I; A. Milenkovic

18
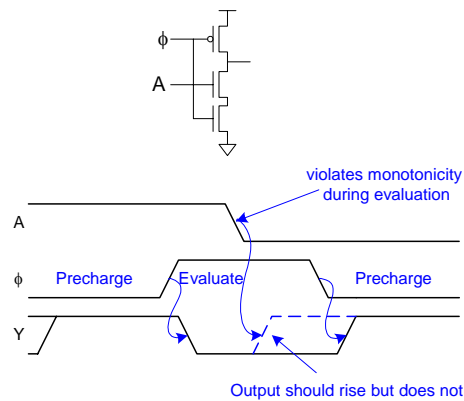
## Monotonicity

- Dynamic gates require *monotonically rising* inputs during evaluation

- 0 -> 0
- 0 -> 1
- 1 -> 1
- But not 1 -> 0




11/1/2006

VLSI Design I; A. Milenkovic

19
 
## Monotonicity Woes

- But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!




11/1/2006

VLSI Design I; A. Milenkovic

20
 
## Monotonicity Woes

- But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!




11/1/2006

VLSI Design I; A. Milenkovic

21
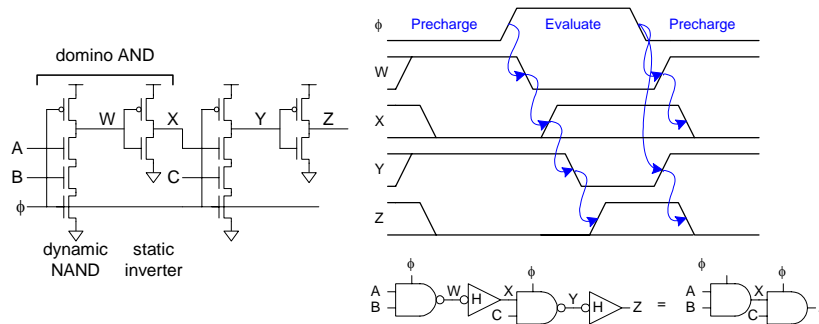
## Domino Gates

- Follow dynamic stage with inverting static gate
  - Dynamic / static pair is called domino gate
  - Produces monotonic outputs




11/1/2006

VLSI Design I; A. Milenkovic

22
 
## Domino Optimizations

- Each domino gate triggers next one, like a string of dominos toppling over
- Gates evaluate sequentially but precharge in parallel
- Thus evaluation is more critical than precharge
- HI-skewed static stages can perform logic



11/1/2006


VLSI Design I; A. Milenkovic

23

## Dual-Rail Domino

- Domino only performs noninverting functions:
  - AND, OR but not NAND, NOR, or XOR
- Dual-rail domino solves this problem
  - Takes true and complementary inputs
  - Produces true and complementary outputs

sig_h	sig_l	Meaning
0	0	Precharged
0	1	'0'
1	0	'1'
1	1	invalid

 

11/1/2006

VLSI Design I; A. Milenkovic

24

### Example: AND/NAND

- Given  $A_h, A_l, B_h, B_l$
- Compute  $Y_h = A * B, Y_l = \sim(A * B)$


11/1/2006

VLSI Design I; A. Milenkovic

25
 
### Example: AND/NAND

- Given  $A_h, A_l, B_h, B_l$
- Compute  $Y_h = A * B, Y_l = \sim(A * B)$
- Pulldown networks are conduction complements



11/1/2006


VLSI Design I; A. Milenkovic

26


 
## Charge Sharing

- Dynamic gates suffer from charge sharing




11/1/2006

VLSI Design I; A. Milenkovic

29
 
## Charge Sharing

- Dynamic gates suffer from charge sharing



$$V_x = V_Y =$$



11/1/2006

VLSI Design I; A. Milenkovic

30
  
## Charge Sharing

- Dynamic gates suffer from charge sharing



$$V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$$


11/1/2006

VLSI Design I; A. Milenkovic

31
 
## Secondary Precharge

- Solution: add secondary precharge transistors
  - Typically need to precharge every other node
- Big load capacitance  $C_Y$  helps as well



11/1/2006

VLSI Design I; A. Milenkovic

32



## Noise Sensitivity

---

- Dynamic gates are very sensitive to noise
  - Inputs:  $V_{IH} \approx V_{tn}$
  - Outputs: floating output susceptible noise
- Noise sources
  - Capacitive crosstalk
  - Charge sharing
  - Power supply noise
  - Feedthrough noise
  - And more!


## Domino Summary

---


- Domino logic is attractive for high-speed circuits
  - 1.5 – 2x faster than static CMOS
  - But many challenges:
    - Monotonicity
    - Leakage
    - Charge sharing
    - Noise
- Widely used in high-performance microprocessors
 
## NMOS Transistors in Series/Parallel

- Primary inputs drive both gate and source/drain terminals
- NMOS switch closes when the gate input is high



$X = Y$  if A and B

 

$X = Y$  if A or B

- Remember –  
**NMOS transistors pass a strong 0 but a weak 1**


11/1/2006

VLSI Design I; A. Milenkovic


35
 
## PMOS Transistors in Series/Parallel

- Primary inputs drive both gate and source/drain terminals
- PMOS switch closes when the gate input is low



 $X = Y$  if  $\overline{A}$  and  $\overline{B} = \overline{A + B}$



$X = Y$  if  $\overline{A}$  or  $\overline{B} = \overline{A \cdot B}$


- Remember –  
**PMOS transistors pass a strong 1 but a weak 0**

11/1/2006

VLSI Design I; A. Milenkovic

36

## Pass Transistor (PT) Logic

 


- Gate is static – a low-impedance path exists to both supply rails under all circumstances
- **N** transistors instead of **2N**
- No static power consumption
- Ratioless
- Bidirectional (versus unidirectional)

11/1/2006

VLSI Design I; A. Milenkovic

37

## VTC of PT AND Gate

 


Pure PT logic is not **regenerative** - the signal gradually degrades after passing through a number of PTs (can fix with static CMOS inverter insertion)

11/1/2006

VLSI Design I; A. Milenkovic

38

## NMOS Only PT Driving an Inverter

 


- $V_x$  does not pull up to  $V_{DD}$ , but  $V_{DD} - V_{Tn}$
- Threshold voltage drop causes static power consumption ( $M_2$  may be weakly conducting forming a path from  $V_{DD}$  to GND)
- Notice  $V_{Tn}$  increases of pass transistor due to **body effect** ( $V_{SB}$ )

11/1/2006

VLSI Design I; A. Milenkovic

39
 
## Voltage Swing of PT Driving an Inverter



- **Body effect** – large  $V_{SB}$  at  $x$  - when pulling high (B is tied to GND and S charged up close to  $V_{DD}$ )
- So the voltage drop is even worse


$$V_x = V_{DD} - (V_{Tn0} + \gamma(\sqrt{|2\phi_f| + V_x} - \sqrt{|2\phi_f|}))$$

11/1/2006

VLSI Design I; A. Milenkovic

40

## Cascaded NMOS Only PTs

 

Swing on  $y = V_{DD} - V_{Tn1} - V_{Tn2}$

Swing on  $y = V_{DD} - V_{Tn1}$


- Pass transistor gates should **never** be cascaded as on the left
- Logic on the right suffers from static power dissipation and reduced noise margins

11/1/2006

VLSI Design I; A. Milenkovic

41

## Solution 1: Level Restorer

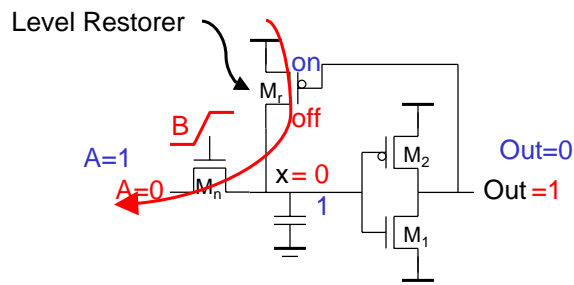


- Full swing on  $x$  (due to Level Restorer) so no static power consumption by inverter
- No static backward current path through Level Restorer and PT since Restorer is only active when  $A$  is high
- For correct operation  $M_r$  must be sized correctly (**ratioed**)

11/1/2006

VLSI Design I; A. Milenkovic

42
 
## Transient Level Restorer Circuit Response



- Restorer has speed and power impacts: increases the capacitance at x, slowing down the gate; increases  $t_r$  (but decreases  $t_f$ )


11/1/2006

VLSI Design I; A. Milenkovic

43
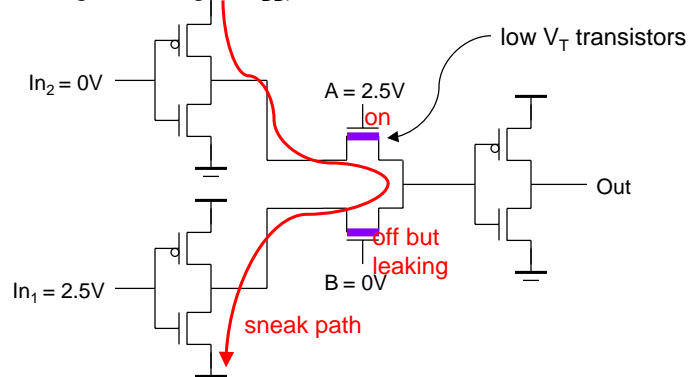
## Solution 2: Multiple $V_T$ Transistors

- Technology solution: Use (near) zero  $V_T$  devices for the NMOS PTs to eliminate *most* of the threshold drop (body effect still in force preventing full swing to  $V_{DD}$ )



- Impacts static power consumption due to subthreshold currents flowing through the PTs (even if  $V_{GS}$  is below  $V_T$ )




11/1/2006

VLSI Design I; A. Milenkovic

44

### Solution 3: Transmission Gates (TGs)

- Most widely used solution

   

- Full swing bidirectional switch controlled by the gate signal C,  $A = B$  if  $C = 1$




11/1/2006

VLSI Design I; A. Milenkovic

45

### Solution 3: Transmission Gates (TGs)

- Most widely used solution

   


- Full swing bidirectional switch controlled by the gate signal C,  $A = B$  if  $C = 1$

11/1/2006

VLSI Design I; A. Milenkovic

46

## Resistance of TG

 



11/1/2006

VLSI Design I; A. Milenkovic

47
  
## Pass Transistor Circuits

- Use pass transistors like switches to do logic
- Inputs drive diffusion terminals as well as gates
- CMOS + Transmission Gates:
  - 2-input multiplexer
  - Gates should be restoring




11/1/2006

VLSI Design I; A. Milenkovic

48



## TG Multiplexer

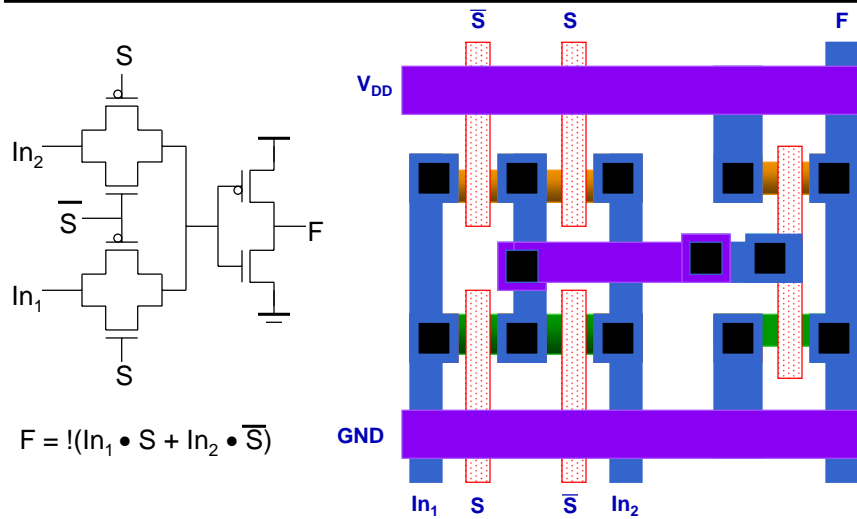


11/1/2006

VLSI Design I; A. Milenkovic

49

## Transmission Gate XOR

 


11/1/2006

VLSI Design I; A. Milenkovic

50

## Transmission Gate XOR

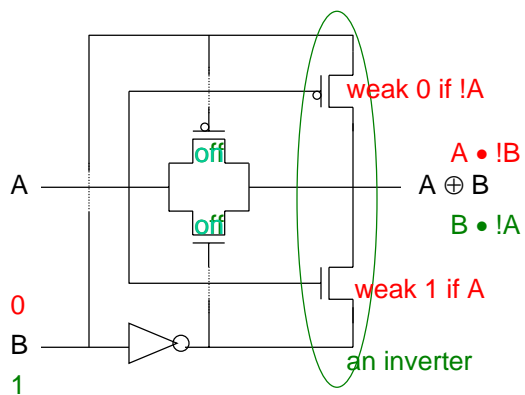


11/1/2006

VLSI Design I; A. Milenkovic

51

## TG Full Adder

 


11/1/2006

VLSI Design I; A. Milenkovic

52

## Differential TG Logic (DPL)

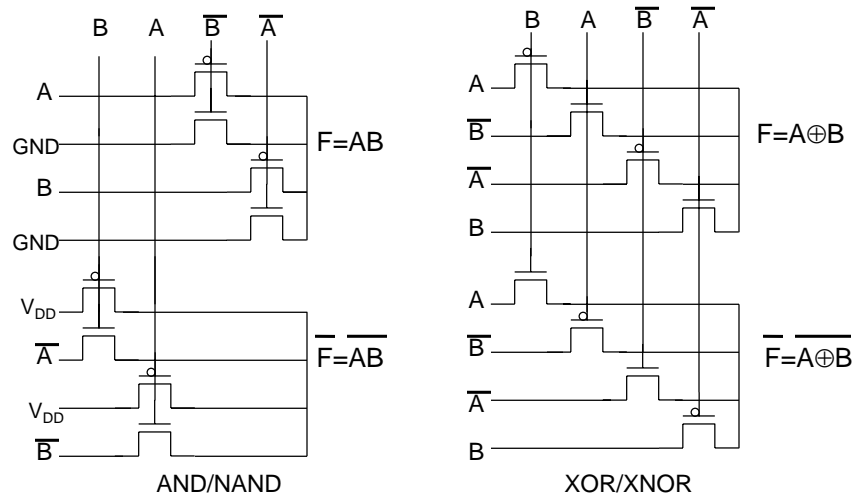


11/1/2006

VLSI Design I; A. Milenkovic

53
 
## CPL

- **Complementary Pass-transistor Logic**
  - Dual-rail form of pass transistor logic
  - Avoids need for ratioed feedback
  - Optional cross-coupling for rail-to-rail swing




11/1/2006

VLSI Design I; A. Milenkovic

54

## Differential PT Logic (CPL)

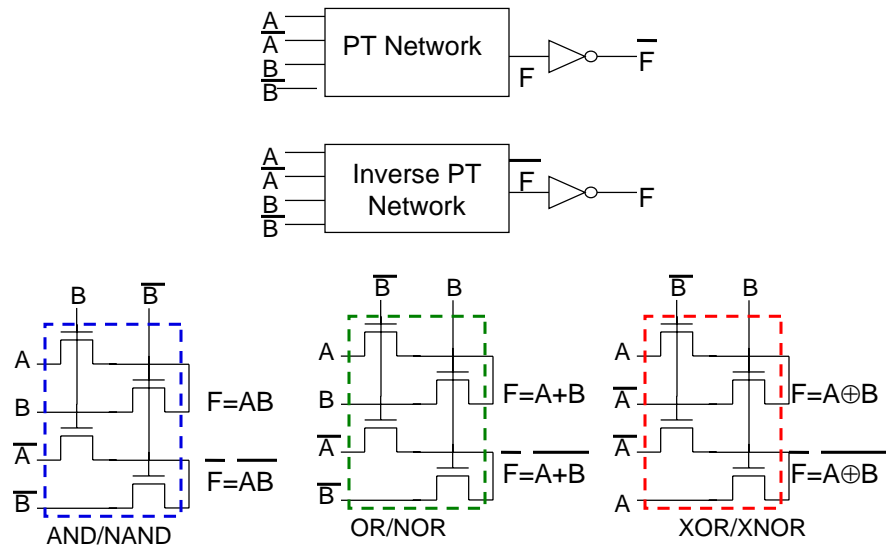

11/1/2006

VLSI Design I; A. Milenkovic

55

## CPL Properties


- **Differential** so complementary data inputs and outputs are always available (so don't need extra inverters)
- Still static, since the output defining nodes are always tied to  $V_{DD}$  or GND through a low resistance path
- Design is **modular**; all gates use the same topology, only the inputs are permuted.
- Simple XOR makes it attractive for structures like **adders**
- Fast (assuming number of transistors in series is small)
- Additional routing overhead for complementary signals
- Still have static power dissipation problems

11/1/2006

VLSI Design I; A. Milenkovic

56

## CPL Full Adder

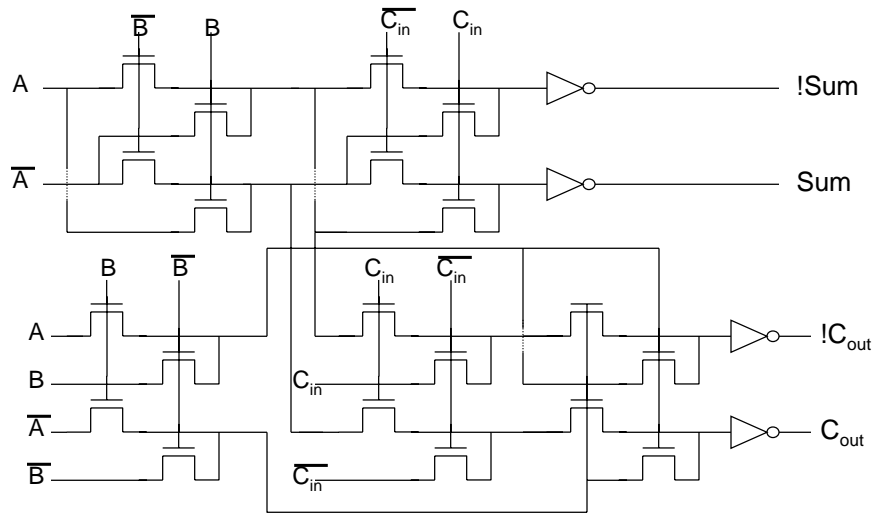


11/1/2006

VLSI Design I; A. Milenkovic

57

## CPL Full Adder

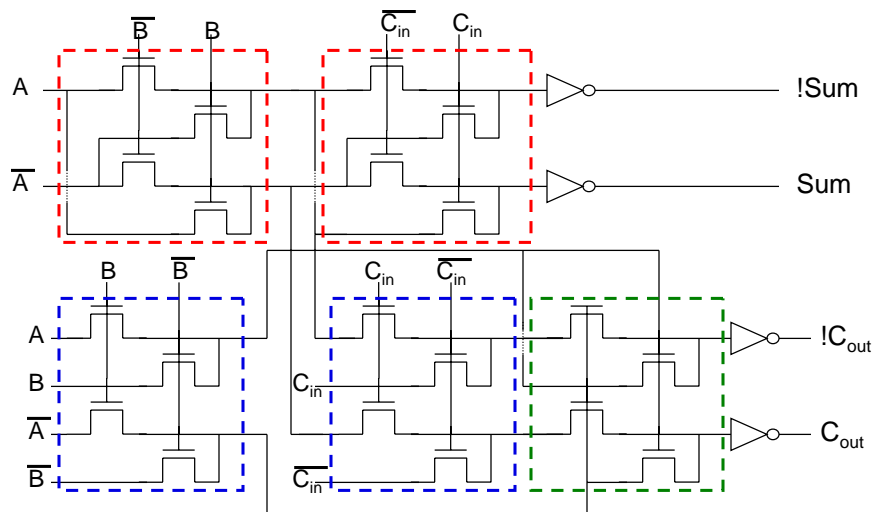

11/1/2006

VLSI Design I; A. Milenkovic

58