 

**CPE/EE 427, CPE 527
VLSI Design I
Designing for Speed**

Department of Electrical and Computer Engineering
University of Alabama in Huntsville

Cray was a legend in computers ... said that he liked to hire inexperienced engineers right out of school, because they do not usually know what's supposed to be impossible.

The Soul of a New Machine, Kidder, pg. 77

Review: CMOS Inverter: Dynamic



$$t_{pHL} = f(R_n, C_L)$$

$$t_{pHL} = 0.69 R_{eqn} C_L$$

$$t_{pHL} = 0.69 (3/4 (C_L V_{DD}) / I_{DSATn})$$

$$= 0.52 C_L / (W/L_n k'_n V_{DSATn})$$

10/4/2006

VLSI Design I; A. Milenkovic

3

Review: Designing Inverters for Performance


- **Reduce C_L**
 - internal diffusion capacitance of the gate itself
 - interconnect capacitance
 - fanout
- **Increase W/L ratio** of the transistor
 - the most powerful and effective performance optimization tool in the hands of the designer
 - watch out for self-loading!
- **Increase V_{DD}**
 - only minimal improvement in performance at the cost of increased energy dissipation
- **Slope engineering** - keeping signal rise and fall times smaller than or equal to the gate propagation delays and of approximately equal values
 - good for performance
 - good for power consumption

10/4/2006

VLSI Design I; A. Milenkovic

4

Switch Delay Model

 


10/4/2006

VLSI Design I; A. Milenkovic

5

Input Pattern Effects on Delay

 


- Delay is dependent on the **pattern** of inputs
- Low to high transition
 - both inputs go low
 - delay is $0.69 R_p / 2 C_L$ since two p-resistors are on in parallel
 - one input goes low
 - delay is $0.69 R_p C_L$
- High to low transition
 - both inputs go high
 - delay is $0.69 2R_n C_L$
- Adding transistors in series (without sizing) slows down the circuit

10/4/2006

VLSI Design I; A. Milenkovic

6

Delay Dependence on Input Patterns

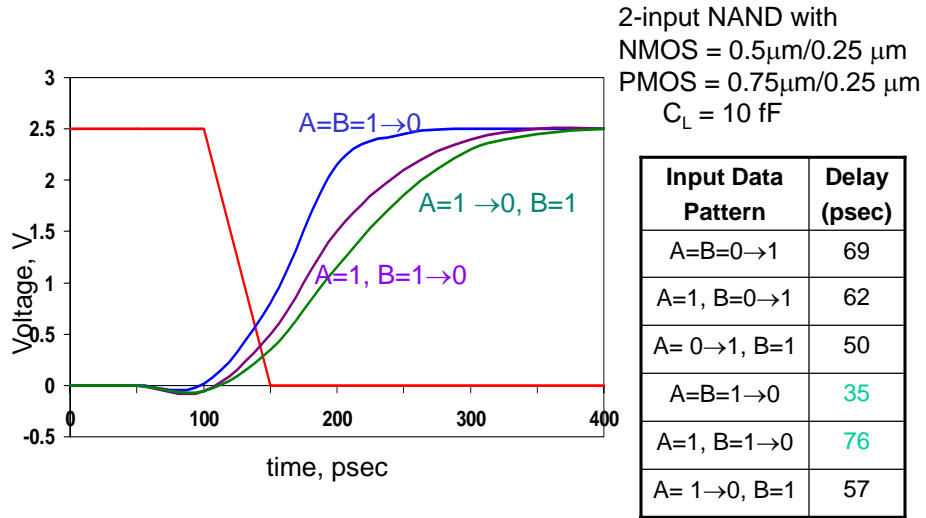


10/4/2006

VLSI Design I; A. Milenkovic

7

Transistor Sizing

 


10/4/2006

VLSI Design I; A. Milenkovic

8

Transistor Sizing a Complex CMOS Gate

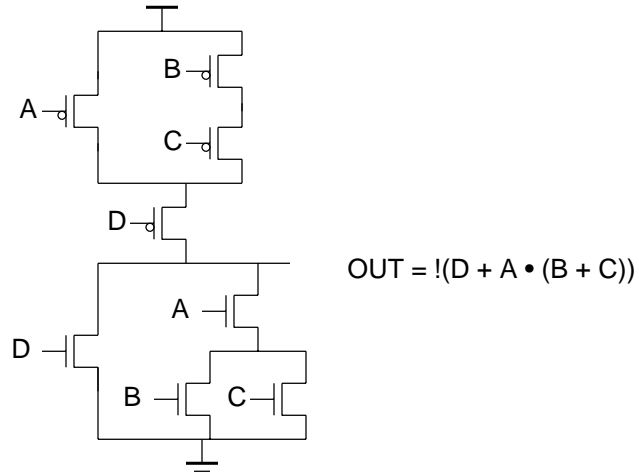


10/4/2006

VLSI Design I; A. Milenkovic

9

Transistor Sizing a Complex CMOS Gate

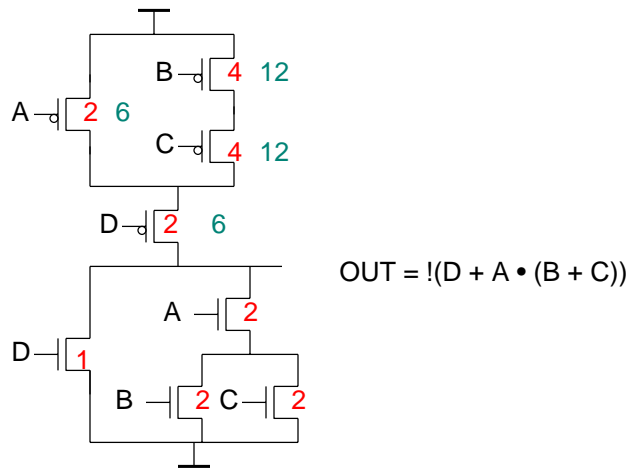


10/4/2006

VLSI Design I; A. Milenkovic

10

Fan-In Considerations

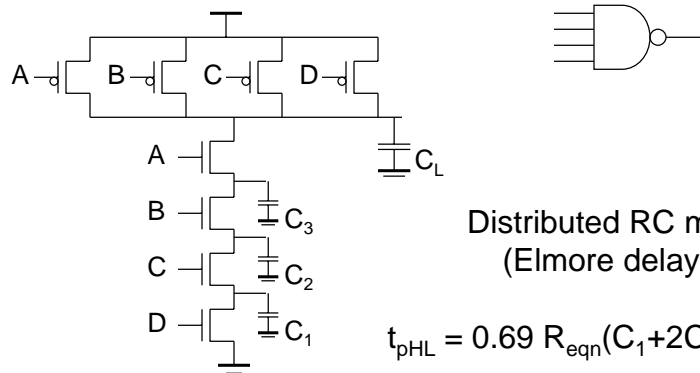

Distributed RC model
(Elmore delay)

$$t_{pHL} = 0.69 R_{eqn}(C_1 + 2C_2 + 3C_3 + 4C_L)$$


Propagation delay deteriorates rapidly as a function of fan-in – **quadratically** in the worst case.

10/4/2006

VLSI Design I; A. Milenkovic

11

t_p as a Function of Fan-In

 

Gates with a fan-in greater than 4 should be avoided.

10/4/2006


VLSI Design I; A. Milenkovic

12

Fast Complex Gates: Design Technique 1

- Transistor sizing
 - as long as fan-out capacitance dominates
- Progressive sizing

Distributed RC line

 

$$M1 > M2 > M3 > \dots > MN$$

The fet closest to the output should be the smallest.

Can reduce delay by more than 20%; decreasing gains as technology shrinks


10/4/2006

VLSI Design I; A. Milenkovic

13

Fast Complex Gates: Design Technique 2

 - Input re-ordering
 - when not all inputs arrive at the same time




10/4/2006

VLSI Design I; A. Milenkovic

14

Fast Complex Gates: Design Technique 2

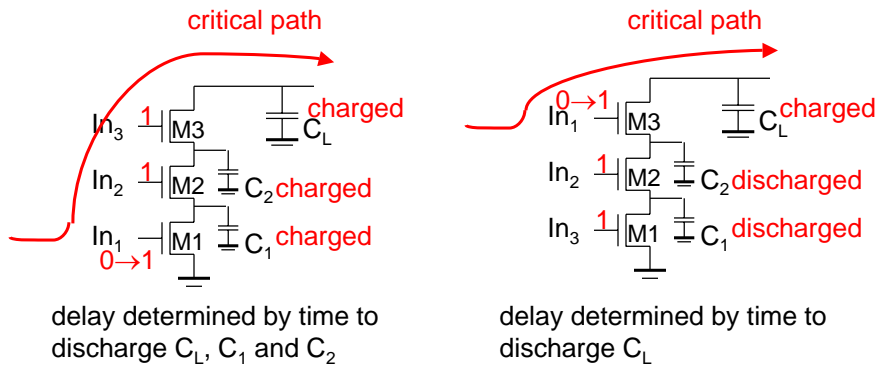- Input re-ordering
 - when not all inputs arrive at the same time




10/4/2006

VLSI Design I; A. Milenkovic

15

Sizing and Ordering Effects

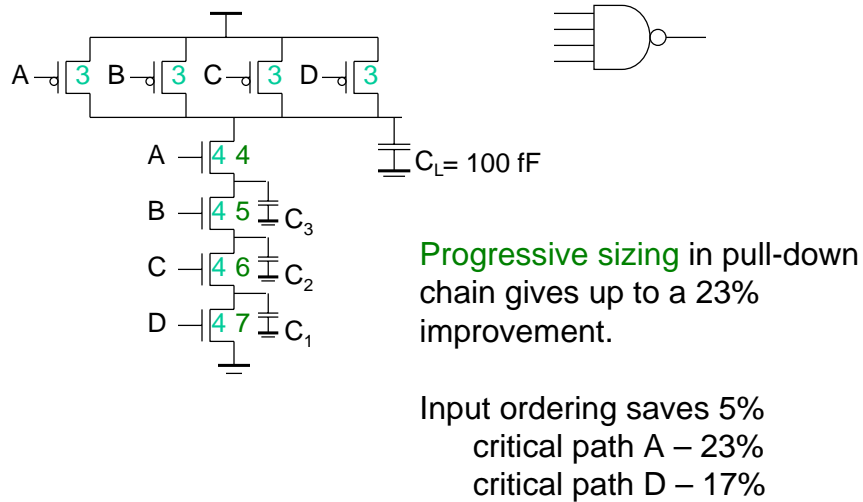

10/4/2006


VLSI Design I; A. Milenkovic

16

Fast Complex Gates: Design Technique 3

- Alternative logic structures

$$F = ABCDEFGH$$

 


10/4/2006

VLSI Design I; A. Milenkovic

17

Fast Complex Gates: Design Technique 4

 - Isolating fan-in from fan-out using buffer insertion



- Real lesson is that optimizing the propagation delay of a gate in isolation is misguided.

10/4/2006

VLSI Design I; A. Milenkovic

18

Fast Networks: Design Technique 5 - Logical Effort

- The optimum fan-out for a chain of N inverters driving a load C_L is

$$f = \sqrt[N]{C_L/C_{in}}$$

- so, if we can, keep the fan-out per stage around 4.

- Can the same approach (**logical effort**) be used for any combinational circuit?

- For a complex gate, we expand the inverter equation

$$t_p = t_{p0} (1 + C_{ext}/\gamma C_g) = t_{p0} (1 + f/\gamma)$$

to

$$t_p = t_{p0} (p + g f/\gamma)$$

- t_{p0} is the intrinsic delay of an inverter
- f is the effective fan-out (C_{ext}/C_g) – also called the **electrical effort**
- p is the ratio of the intrinsic (unloaded) delay of the complex gate and a simple inverter (a function of the gate topology and layout style)
- g is the **logical effort**

10/4/2006

VLSI Design I; A. Milenkovic

19

Intrinsic Delay Term, p

- The more involved the structure of the complex gate, the higher the intrinsic delay compared to an inverter

Gate Type	p
Inverter	1
n-input NAND	n
n-input NOR	n
n-way mux	2n
XOR, XNOR	$n 2^{n-1}$

Ignoring second order effects such as internal node capacitances

10/4/2006

VLSI Design I; A. Milenkovic

20

Logical Effort Term, g

- g represents the fact that, for a given load, complex gates have to work harder than an inverter to produce a similar (speed) response
 - the logical effort of a gate tells how much worse it is at producing an output current than an inverter (how much more input capacitance a gate presents to deliver it same output current)

Gate Type	g (for 1 to 4 input gates)			
	1	2	3	4
Inverter	1			
NAND		4/3	5/3	(n+2)/3
NOR		5/3	7/3	(2n+1)/3
mux		2	2	2
XOR		4	12	


10/4/2006

VLSI Design I; A. Milenkovic

21

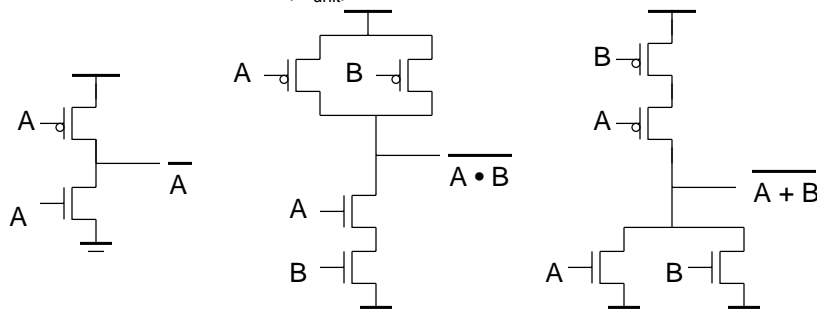Example of Logical Effort

- Assuming a pmos/nmos ratio of 2, the input capacitance of a minimum-sized inverter is three times the gate capacitance of a minimum-sized nmos (C_{unit})




10/4/2006

VLSI Design I; A. Milenkovic

22

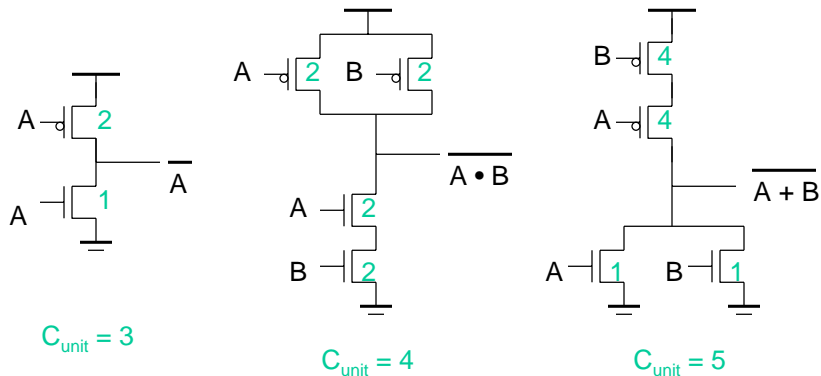Example of Logical Effort

- Assuming a pmos/nmos ratio of 2, the input capacitance of a minimum-sized inverter is three times the gate capacitance of a minimum-sized nmos (C_{unit})




10/4/2006

VLSI Design I; A. Milenkovic

23

Delay as a Function of Fan-Out

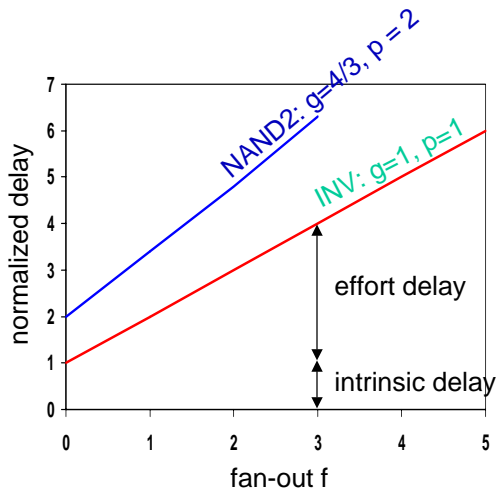

- The slope of the line is the logical effort of the gate
- The y-axis intercept is the intrinsic delay
- Can adjust the delay by adjusting the effective fan-out (by sizing) or by choosing a gate with a different logical effort
- Gate effort: $h = fg$

10/4/2006

VLSI Design I; A. Milenkovic

24

Path Delay of Complex Logic Gate Network


- Total path delay through a combinational logic block

$$t_p = \sum t_{p,j} = t_{p0} \sum (p_j + (f_j g_j)/\gamma)$$

- So, the minimum delay through the path determines that **each stage should bear the same gate effort**

$$f_1 g_1 = f_2 g_2 = \dots = f_N g_N$$

 - Consider optimizing the delay through the logic network



how do we determine a, b, and c sizes?

10/4/2006

VLSI Design I; A. Milenkovic

25

Path Delay Equation Derivation

- The **path logical effort**, $G = \prod g_i$
- And the **path effective fan-out** (path electrical effort) is $F = C_L/C_{g1}$
- The **branching effort** accounts for fan-out to other gates in the network

$$b = (C_{on-path} + C_{off-path})/C_{on-path}$$

- The **path branching effort** is then $B = \prod b_i$
- And the **total path effort** is then $H = GFB$

- So, the minimum delay through the path is

$$D = t_{p0} (\sum p_j + (N \sqrt{H})/\gamma)$$

10/4/2006


VLSI Design I; A. Milenkovic

26

Path Delay of Complex Logic Gates, con't

- For gate i in the chain, its size is determined by
 
$$s_i = (g_1 s_1) / g_i \prod_{j=1}^{i-1} (f_j / b_j)$$



- For this network

- $F = C_L / C_{g1} = 5$
- $G = 1 \times 5/3 \times 5/3 \times 1 = 25/9$
- $B = 1$ (no branching)
- $H = GFB = 125/9$, so the optimal stage effort is $\sqrt[4]{H} = 1.93$
 - Fan-out factors are $f_1=1.93$, $f_2=1.93 \times 3/5 = 1.16$, $f_3 = 1.16$, $f_4 = 1.93$
- So the gate sizes are $a = f_1 g_1 / g_2 = 1.16$, $b = f_1 f_2 g_1 / g_3 = 1.34$ and $c = f_1 f_2 f_3 g_1 / g_4 = 2.60$

10/4/2006

VLSI Design I; A. Milenkovic

27

Fast Complex Gates: Design Technique 6

- Reducing the voltage swing

$$\begin{aligned} t_{pHL} &= 0.69 (3/4 (C_L V_{DD}) / I_{DSATn}) \\ &= 0.69 (3/4 (C_L V_{swing}) / I_{DSATn}) \end{aligned}$$

- linear reduction in delay
- also reduces power consumption
- requires use of "sense amplifiers" on the receiving end to restore the signal level (will look at their design when covering memory design)

10/4/2006

VLSI Design I; A. Milenkovic



28

TG Logic Performance

- Effective resistance of the TG is modeled as a parallel connection of $R_p (= (V_{DD} - V_{out})/(-I_{Dp}))$ and

$$R_n (= (V_{DD} - V_{out})/I_{Dn})$$

$$W/L_p = 0.50/0.25$$

  

$$W/L_n = 0.50/0.25$$


- So, the assumption that the TG switch has a constant resistive value, R_{eq} , is acceptable

10/4/2006

VLSI Design I; A. Milenkovic

29

Delay of a TG Chain

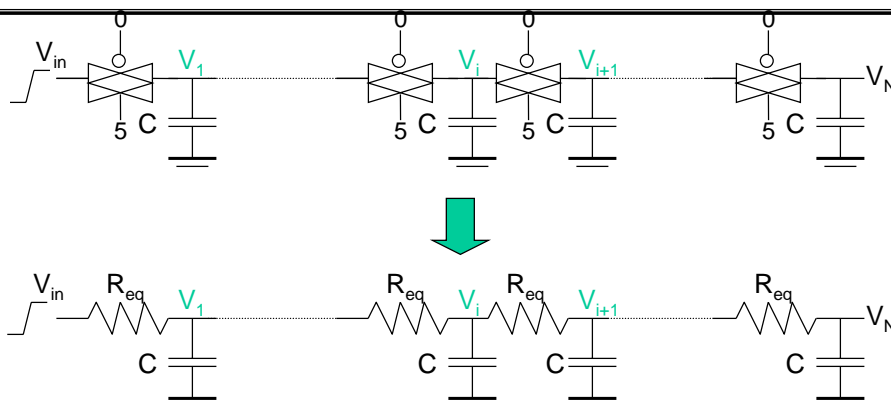

- Delay of the RC chain (N TG's in series) is

$$t_p(V_n) = 0.69 \sum_{k=1}^N kCR_{eq} = 0.69 CR_{eq} (N(N+1))/2 \approx 0.35 CR_{eq} N^2$$


10/4/2006

VLSI Design I; A. Milenkovic

30

TG Delay Optimization

 - Can speed it up by inserting buffers every M switches



- Delay of buffered chain (M TG's between buffer)

$$t_p = 0.69 \lfloor N/M CR_{eq} (M(M+1))/2 \rfloor + (N/M - 1) t_{pbuf}$$

$$M_{opt} = 1.7 \sqrt{t_{pbuf}/CR_{eq}} \approx 3 \text{ or } 4$$