
**CPE/EE 427, CPE 527
VLSI Design I
Logical Effort**

Department of Electrical and Computer Engineering
University of Alabama in Huntsville


Aleksandar Milenkovic (www.ece.uah.edu/~milenka)

Outline

- Introduction
- Delay in a Logic Gate
- Multistage Logic Networks
- Choosing the Best Number of Stages
- Example
- Summary

Introduction


- Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries

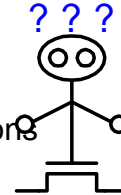

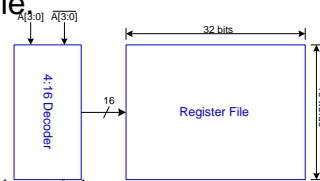Example

- Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs $A[3:0]$
 - Each input may drive 10 unit-sized transistors
- Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?



Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$$\tau = 3RC$$

≈ 12 ps in 180 nm process

40 ps in 0.6 μm process

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. *stage effort*)
 - Again has two components

9/27/2006

VLSI Design I; A. Milenkovic

7

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. *stage effort*)
 - Again has two components
- g : *logical effort*
 - Measures relative ability of gate to deliver current
 - $g \equiv 1$ for inverter

9/27/2006

VLSI Design I; A. Milenkovic

8

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. stage effort)
 - Again has two components
- h : *electrical effort* = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout

9/27/2006

VLSI Design I; A. Milenkovic

9

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Parasitic delay p
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance

9/27/2006


VLSI Design I; A. Milenkovic

10

Delay Plots

$$d = f + p$$

$$= gh + p$$

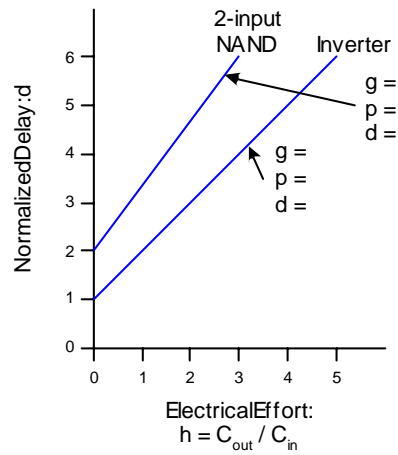

9/27/2006

VLSI Design I; A. Milenkovic


11

Delay Plots

$$d = f + p$$

$$= gh + p$$

- What about NOR2?

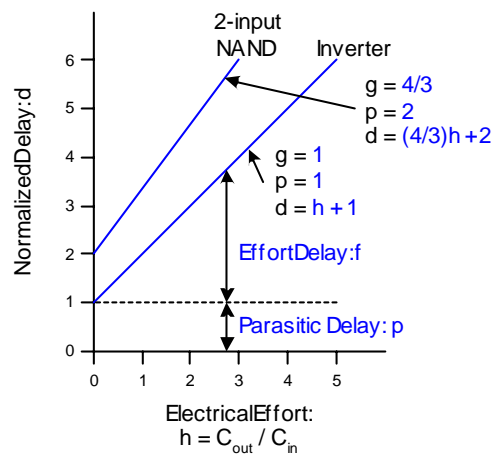


9/27/2006

VLSI Design I; A. Milenkovic

12

Computing Logical Effort

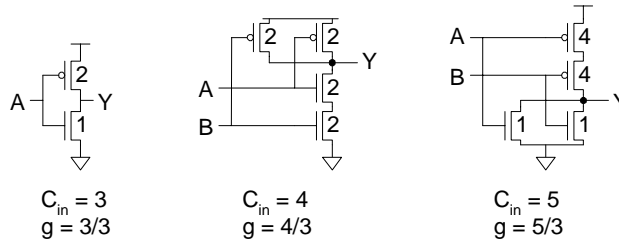- DEF: Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths



9/27/2006

VLSI Design I; A. Milenkovic

13

Catalog of Gates

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	(n+2)/3
NOR		5/3	7/3	9/3	(2n+1)/3
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

9/27/2006

VLSI Design I; A. Milenkovic

14

Catalog of Gates

- Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	


9/27/2006

VLSI Design I; A. Milenkovic

15

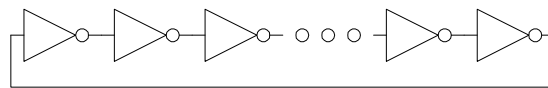Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$

Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$

Frequency: $f_{osc} =$


9/27/2006

VLSI Design I; A. Milenkovic

16

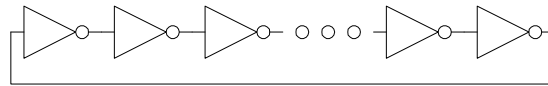Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g = 1$

Electrical Effort: $h = 1$

Parasitic Delay: $p = 1$

Stage Delay: $d = 2$

Frequency: $f_{osc} = 1/(2*N*d) = 1/4N$

31 stage ring oscillator in
0.6 μm process has
frequency of ~ 200 MHz


9/27/2006

VLSI Design I; A. Milenkovic

17

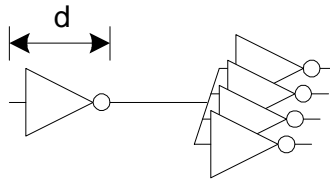Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$

Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$


9/27/2006

VLSI Design I; A. Milenkovic

18

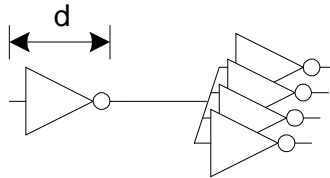Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$

Electrical Effort: $h = 4$

Parasitic Delay: $p = 1$

Stage Delay: $d = 5$

The FO4 delay is about

200 ps in 0.6 μm process

60 ps in a 180 nm process

$f/3$ ns in an f μm process

9/27/2006

VLSI Design I; A. Milenkovic

19

Multistage Logic Networks

- Logical effort generalizes to multistage networks
- Path Logical Effort


$$G = \prod g_i$$

- Path Electrical Effort

$$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$$

- Path Effort

$$F = \prod f_i = \prod g_i h_i$$

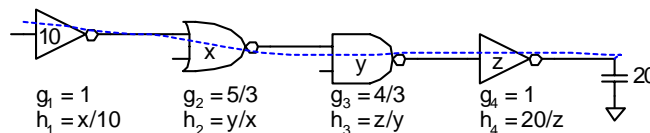

9/27/2006

VLSI Design I; A. Milenkovic

20

Multistage Logic Networks

- Logical effort generalizes to multistage networks

- Path Logical Effort

$$G = \prod g_i$$

- Path Electrical Effort

$$H = \frac{C_{out-path}}{C_{in-path}}$$

- Path Effort

$$F = \prod f_i = \prod g_i h_i$$

- Can we write $F = GH$?

9/27/2006

VLSI Design I; A. Milenkovic

21

Paths that Branch

- No! Consider paths that branch:

$$G =$$


$$H =$$

$$GH =$$

$$h_1 =$$

$$h_2 =$$

$$F = GH?$$

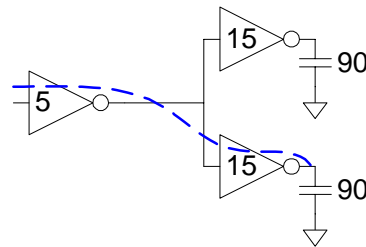

9/27/2006

VLSI Design I; A. Milenkovic

22

Paths that Branch

- No! Consider paths that branch:

$$G = 1$$


$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

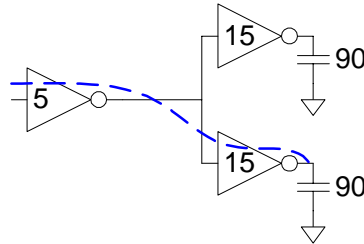

9/27/2006

VLSI Design I; A. Milenkovic

23

Branching Effort

- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$

9/27/2006

VLSI Design I; A. Milenkovic

24

Multistage Delays

- Path Effort Delay $D_F = \sum f_i$
- Path Parasitic Delay $P = \sum p_i$
- Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

Gate Sizes

- How wide should the gates be for least delay?

$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$
$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.


9/27/2006

VLSI Design I; A. Milenkovic

27

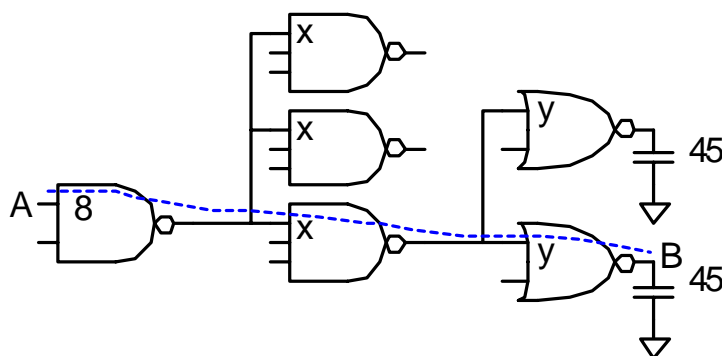Example: 3-stage path

- Select gate sizes x and y for least delay from A to B




9/27/2006

VLSI Design I; A. Milenkovic

28

Example: 3-stage path

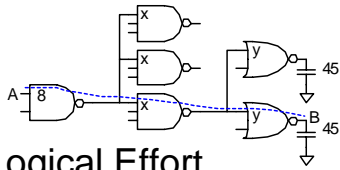


Logical Effort $G =$
 Electrical Effort $H =$
 Branching Effort $B =$
 Path Effort $F =$
 Best Stage Effort $f =$
 Parasitic Delay $P =$
 Delay $D =$

9/27/2006

VLSI Design I; A. Milenkovic

29

Example: 3-stage path

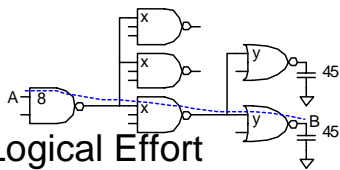

Logical Effort $G = (4/3) * (5/3) * (5/3) = 100/27$
 Electrical Effort $H = 45/8$
 Branching Effort $B = 3 * 2 = 6$
 Path Effort $F = GBH = 125$
 Best Stage Effort $f = \sqrt[3]{F} = 5$
 Parasitic Delay $P = 2 + 3 + 2 = 7$
 Delay $D = 3 * 5 + 7 = 22 = 4.4 FO4$

9/27/2006

VLSI Design I; A. Milenkovic


30

Example: 3-stage path

- Work backward for sizes

y =

x =

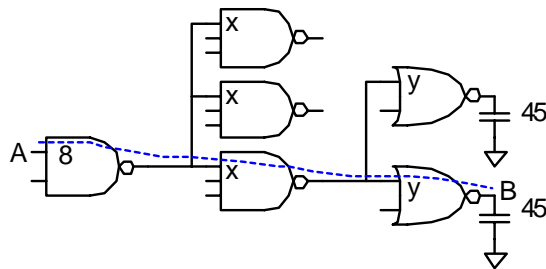

9/27/2006

VLSI Design I; A. Milenkovic


31

Example: 3-stage path

- Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$

$$x = (15 * 2) * (5/3) / 5 = 10$$

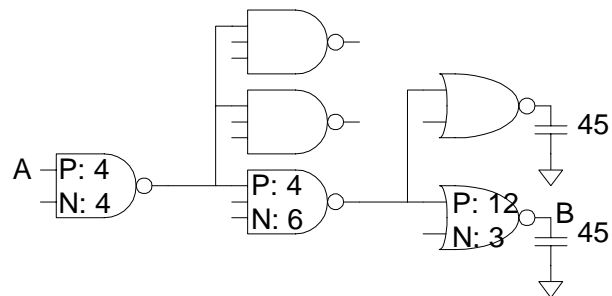

9/27/2006


VLSI Design I; A. Milenkovic

32

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

D =

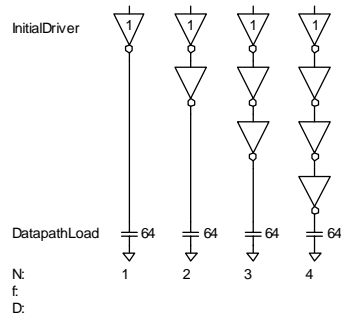

9/27/2006

VLSI Design I; A. Milenkovic


33

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

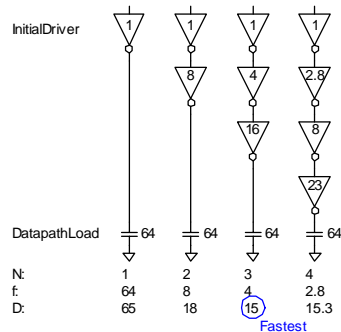


9/27/2006

VLSI Design I; A. Milenkovic

34

Derivation

- Consider adding inverters to end of path
 - How many give least delay?
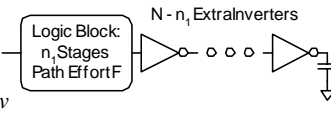
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$


The diagram shows a logic block labeled 'Logic Block: n₁ Stages Path Effort F' connected to a chain of 'N - n₁ Extra Inverters'. The chain starts with an inverter, followed by three small circles representing intermediate inverters, and ends with another inverter connected to ground.

$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{\frac{1}{N}}$


$$p_{inv} + \rho(1 - \ln \rho) = 0$$

Best Stage Effort

- $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

Sensitivity Analysis

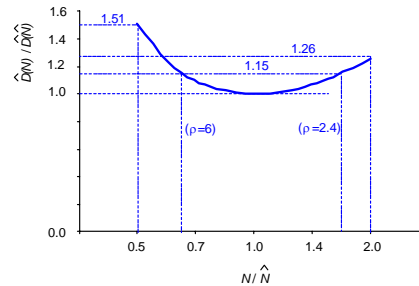- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$

9/27/2006

VLSI Design I; A. Milenkovic


37

Example, Revisited

- Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- Decoder specifications:

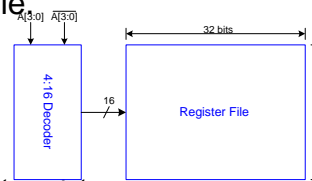- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors



- Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

9/27/2006

VLSI Design I; A. Milenkovic

38

Number of Stages

- Decoder effort is mainly electrical and branching

Electrical Effort: $H =$

Branching Effort: $B =$

- If we neglect logical effort (assume $G = 1$)

Path Effort: $F =$

Number of Stages: $N =$

9/27/2006

VLSI Design I; A. Milenkovic

39

Number of Stages

- Decoder effort is mainly electrical and branching

Electrical Effort: $H = (32 \cdot 3) / 10 = 9.6$

Branching Effort: $B = 8$

- If we neglect logical effort (assume $G = 1$)

Path Effort: $F = GBH = 76.8$

Number of Stages: $N = \log_4 F = 3.1$

- Try a 3-stage design

9/27/2006

VLSI Design I; A. Milenkovic

40

Gate Sizes & Delay


Logical Effort: $G =$

Path Effort: $F =$

Stage Effort: $\hat{f} =$

Path Delay: $D =$

Gate sizes: $z =$ $y =$

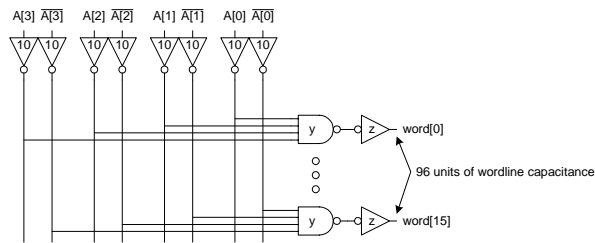

9/27/2006

VLSI Design I; A. Milenkovic

41

Gate Sizes & Delay


Logical Effort: $G = 1 * 6/3 * 1 = 2$

Path Effort: $F = GBH = 154$

Stage Effort: $\hat{f} = F^{1/3} = 5.36$

Path Delay: $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

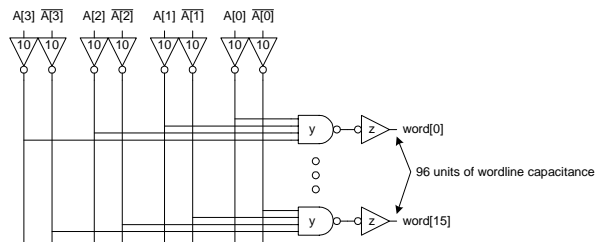Gate sizes: $z = 96 * 1/5.36 = 18$ $y = 18 * 2/5.36 = 6.7$



9/27/2006

VLSI Design I; A. Milenkovic

42

Comparison

- Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

9/27/2006

VLSI Design I; A. Milenkovic

43

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

9/27/2006

VLSI Design I; A. Milenkovic

44

Method of Logical Effort

- 1) Compute path effort
 - 2) Estimate best number of stages
 - 3) Sketch path with N stages
 - 4) Estimate least delay
 - 5) Determine best stage effort
 - 6) Find gate sizes
- $$F = GBH$$
- $$N = \log_4 F$$
- $$D = NF^{\frac{1}{N}} + P$$
- $$\hat{f} = F^{\frac{1}{N}}$$
- $$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

9/27/2006

VLSI Design I; A. Milenkovic

45

Limits of Logical Effort

- Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- Simplistic delay model
 - Neglects input rise time effects
- Interconnect
 - Iteration required in designs with wire
- Maximum speed only
 - Not minimum area/power for constrained delay

9/27/2006

VLSI Design I; A. Milenkovic

46

Summary

- Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits
 - But requires practice to master