

CPE/EE 427, CPE 527
VLSI Design I
L06: Complementary CMOS Logic Gates





Department of Electrical and Computer Engineering
 University of Alabama in Huntsville

Aleksandar Milenkovic (www.ece.uah.edu/~milenka)
www.ece.uah.edu/~milenka/cpe527-05F

Course Administration


- Instructor: Aleksandar Milenkovic
milenka@ece.uah.edu
www.ece.uah.edu/~milenka
 EB 217-L
 Mon. 5:30 PM – 6:30 PM,
 Wen. 12:30 – 13:30 PM
- URL: <http://www.ece.uah.edu/~milenka/cpe527-05F>
- TA: Joel Wilder
- Labs: Lab#2 posted (due 9/23/05)
- Text: CMOS VLSI Design, 3rd ed., Weste, Harris
 Introduction, Design Metrics, IC Fabrication (Read Chapter 1); IC Fabrication (Chapter 3)
- Review: Introduction, Design Metrics, IC Fabrication (Read Chapter 1); IC Fabrication (Chapter 3)
- Today: MOS Non-ideal IV, CMOS Inverter (Chapter 2)

9/14/2005 VLSI Design I; A. Milenkovic 2

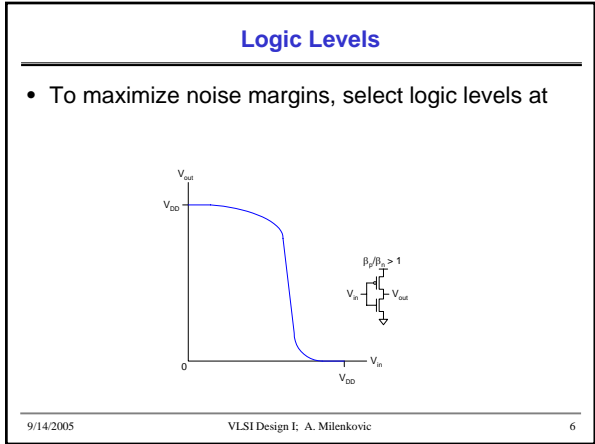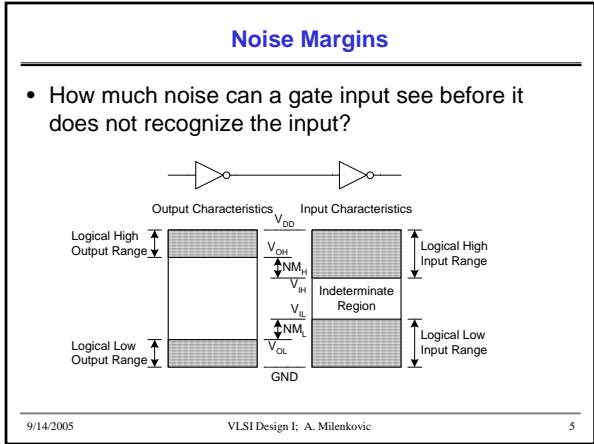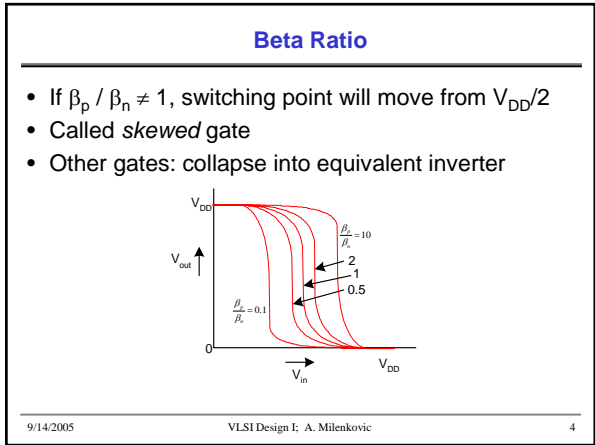 


Logic Levels

 
- To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristic



 CMOS Inverter: Switch Model of Dynamic Behavior



 CMOS Inverter: Switch Model of Dynamic Behavior



Gate response time is determined by the time to charge C_L through R_p (discharge C_L through R_n)

Relative Transistor Sizing

- When designing static CMOS circuits, balance the driving strengths of the transistors by making the PMOS section wider than the NMOS section to
 - maximize the noise margins and
 - obtain symmetrical characteristics

Switching Threshold

- V_M where $V_{in} = V_{out}$ (both PMOS and NMOS in saturation since $V_{DS} = V_{GS}$)
 - $V_M \approx rV_{DD}/(1+r)$ where $r = k_p V_{DSATp}/k_n V_{DSATn}$
- Switching threshold set by the ratio r , which compares the **relative driving strengths** of the PMOS and NMOS transistors
- Want $V_M = V_{DD}/2$ (to have comparable high and low noise margins), so want $r \approx 1$

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k_p V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)}$$

Switch Threshold Example

- In our generic 0.25 micron CMOS process, using the process parameters from slide L03.25, a $V_{DD} = 2.5V$, and a minimum size NMOS device ($(W/L)_n$ of 1.5)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

$$\frac{(W/L)_p}{(W/L)_n} =$$

Switch Threshold Example

- In our generic 0.25 micron CMOS process, using the process parameters, a $V_{DD} = 2.5V$, and a minimum size NMOS device ($(W/L)_n$ of 1.5)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6} \cdot 0.63}{-30 \times 10^{-6} \cdot -1.0} \times \frac{(1.25 - 0.43 - 0.63/2)}{(1.25 - 0.4 - 1.0/2)} = 3.5$$

$$(W/L)_p = 3.5 \times 1.5 = 5.25 \text{ for a } V_M \text{ of } 1.25V$$

9/14/2005 VLSI Design I: A. Milenkovic 13

Simulated Inverter V_M

- V_M is relatively insensitive to variations in device ratio
 - setting the ratio to 3, 2.5 and 2 gives V_M 's of 1.22V, 1.18V, and 1.13V
- Increasing the width of the PMOS moves V_M towards V_{DD}
- Increasing the width of the NMOS moves V_M toward GND

Note: x-axis is semilog

9/14/2005 VLSI Design I: A. Milenkovic 14

Noise Margins Determining V_{IH} and V_{IL}

By definition, V_{IH} and V_{IL} are where $dV_{out}/dV_{in} = -1$ (= gain)

$$NM_H = V_{DD} - V_{IH}$$

$$NM_L = V_{IL} - GND$$

Approximating:

$$V_{IH} = V_M - V_M/g$$

$$V_{IL} = V_M + (V_{DD} - V_M)/g$$

So high gain in the transition region is very desirable

A piece-wise linear approximation of VTC

9/14/2005 VLSI Design I: A. Milenkovic 15

CMOS Inverter VTC from Simulation

0.25um, $(W/L)_p/(W/L)_n = 3.4$
 $(W/L)_n = 1.5$ (min size)
 $V_{DD} = 2.5V$

$V_M \approx 1.25V$, $g = -27.5$

$V_{IL} = 1.2V$, $V_{IH} = 1.3V$
 $NM_L = NM_H = 1.2$
 (actual values are
 $V_{IL} = 1.03V$, $V_{IH} = 1.45V$
 $NM_L = 1.03V$ & $NM_H = 1.05V$)

Output resistance
 low-output = $2.4k\Omega$
 high-output = $3.3k\Omega$

9/14/2005 VLSI Design I: A. Milenkovic 16

Gain Determinates

Gain is a strong function of the slopes of the currents in the saturation region, for $V_{in} = V_M$

$$g \approx \frac{(1+r)}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$


Determined by technology parameters, especially channel length modulation (λ). Only designer influence through supply voltage and V_M (transistor sizing).

9/14/2005 VLSI Design I: A. Milenkovic 17

Impact of Process Variation on VTC Curve




process variations (mostly) cause a shift in the switching threshold

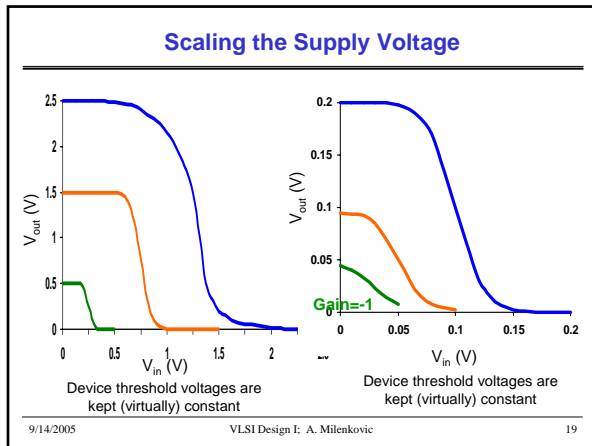9/14/2005 VLSI Design I: A. Milenkovic 18




Static CMOS Logic

- ### CMOS Circuit Styles
- **Static complementary CMOS** - except during switching, output connected to either VDD or GND via a low-resistance path
 - high noise margins
 - full rail to rail swing
 - VOH and VOL are at VDD and GND, respectively
 - low output impedance, high input impedance
 - no steady state path between VDD and GND (no static power consumption)
 - delay a function of load capacitance and transistor resistance
 - comparable rise and fall times (under the appropriate transistor sizing conditions)
 - **Dynamic CMOS** - relies on temporary storage of signal values on the capacitance of high-impedance circuit nodes
 - simpler, faster gates
 - increased sensitivity to noise
- 9/14/2005 VLSI Design I: A. Milenkovic 21

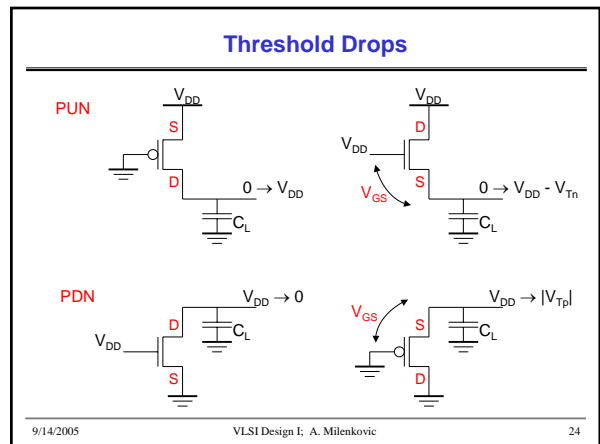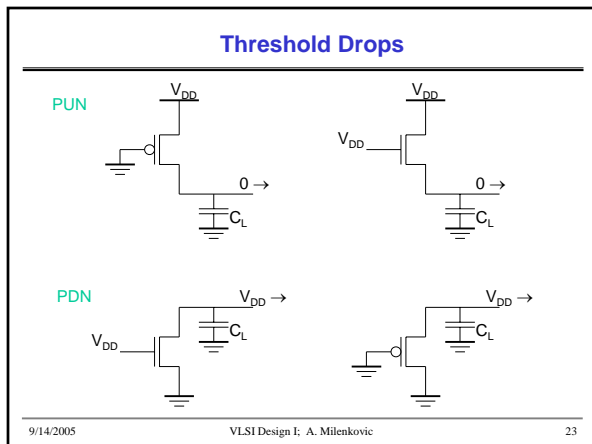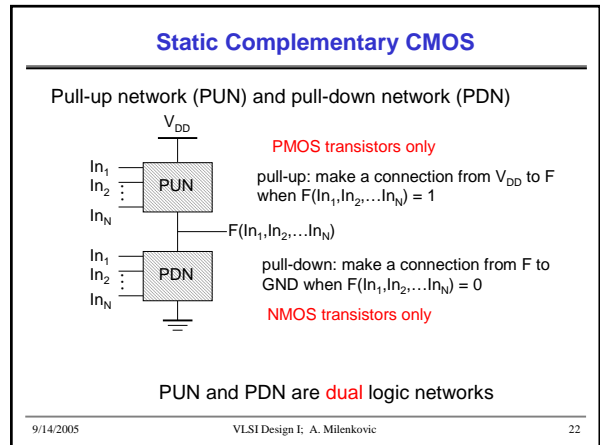


Construction of PDN

 - NMOS devices in **series** implement a NAND function



 - NMOS devices in **parallel** implement a NOR function



9/14/2005

VLSI Design I; A. Milenkovic

25

Dual PUN and PDN

- PUN and PDN are dual networks

– DeMorgan's theorems

$$\overline{A + B} = \overline{A} \cdot \overline{B} \quad [!(A + B) = !A \cdot !B \text{ or } !(A | B) = !A \& !B]$$

$$\overline{A \cdot B} = \overline{A} + \overline{B} \quad [!(A \cdot B) = !A + !B \text{ or } !(A \& B) = !A | !B]$$

– a **parallel** connection of transistors in the PUN corresponds to a **series** connection of the PDN


- Complementary gate is naturally **inverting** (NAND, NOR, AOI, OAI)
- Number of transistors for an N-input logic gate is **2N**

9/14/2005


VLSI Design I; A. Milenkovic

26

CMOS NAND

 

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0


 


9/14/2005

VLSI Design I; A. Milenkovic

27

CMOS NAND

  


9/14/2005

VLSI Design I; A. Milenkovic

28

CMOS NOR

 

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0





9/14/2005

VLSI Design I; A. Milenkovic

29

CMOS NOR

  

9/14/2005

VLSI Design I; A. Milenkovic

30

Complex CMOS Gate

$OUT = !(D + A \cdot (B + C))$

9/14/2005 VLSI Design I: A. Milenkovic 31

Complex CMOS Gate

$OUT = !(D + A \cdot (B + C))$

9/14/2005 VLSI Design I: A. Milenkovic 32

XNOR/XOR Implementation

XNOR

$A \oplus B$

XOR

$A \oplus B$

$A \oplus B$

$A \oplus B$

- How many transistors in each?
- Can you create the stick transistor layout for the lower left circuit?

9/14/2005 VLSI Design I: A. Milenkovic 33

Combinational Logic Cells

- CMOS logic cells
 - AND-OR-INVERT (AOI)
 - OR-AND-INVERT (OAI)
- Example: AOI221

$Z = (A \cdot B + C \cdot D + E)'$

$Z = AOI221(A, B, C, D, E)$

Exercise: Construct this logic cell?
- Example: OAI321

$Z = [(A+B+C) \cdot (D+E) \cdot F]'$

$Z = OAI321(A, B, C, D, E, F)$

Exercise: Construct this logic cell?

9/14/2005 VLSI Design I: A. Milenkovic 34

AOI221

9/14/2005 VLSI Design I: A. Milenkovic 35

Standard Cell Layout Methodology

Routing channel







signals

V_{DD}

GND

What logic function is this?

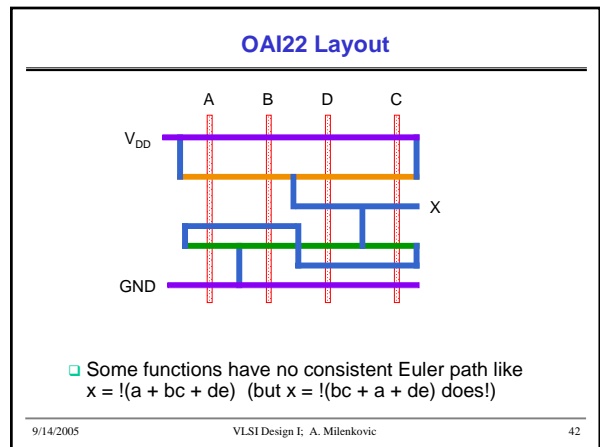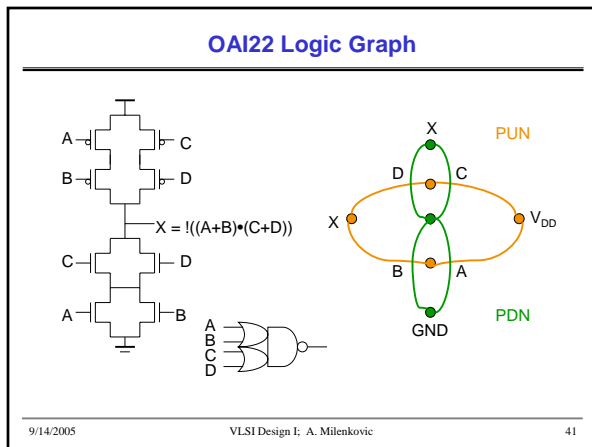 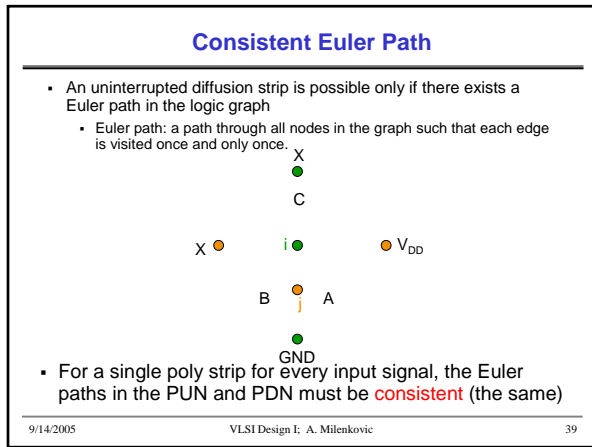 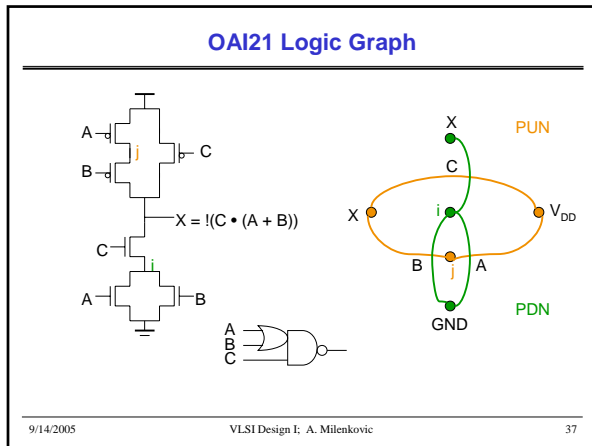9/14/2005 VLSI Design I: A. Milenkovic 36



Combinational Logic Cells (cont'd)

- The AOI family of cells with 3 index numbers or less
 - $X = \{AOI, OAI, AO, OA\}$; $a, b, c = \{2, 3\}$


Cell Type	Cells	Number of Unique Cells
Xa1	X21, X31	2
Xa11	X211, X311	2
Xab	X22, X33, X32	3
Xab1	X221, X321, X331	3
Xabc	X222, X333, X332, X322	4
Total		14

9/14/2005

VLSI Design I; A. Milenkovic

43

VTC is Data-Dependent

 

- The threshold voltage of M_2 is higher than M_1 due to the body effect (γ)

$$V_{Tn1} = V_{Tn0}$$

$$V_{Tn2} = V_{Tn0} + \gamma(\sqrt{|2\phi_F|} + V_{in}) - \sqrt{|2\phi_F|}$$


since V_{SB} of M_2 is not zero (when $V_B = 0$) due to the presence of C_{int} .

9/14/2005

VLSI Design I; A. Milenkovic

44

Static CMOS Full Adder Circuit

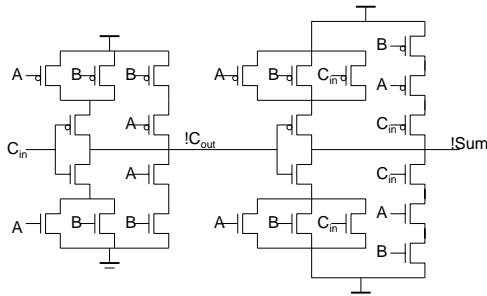


9/14/2005

VLSI Design I; A. Milenkovic

45

Static CMOS Full Adder Circuit
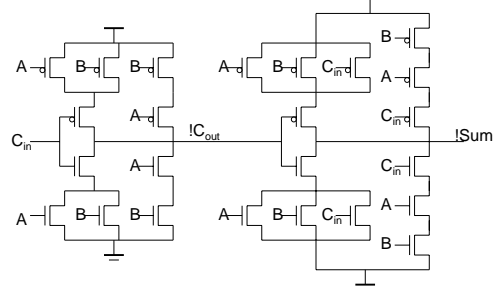
$$!C_{out} = !C_{in} \& (!A \mid !B) \mid (!A \& !B) \quad !Sum = C_{out} \& (!A \mid !B \mid !C_{in}) \mid (!A \& !B \& !C_{in})$$



$$C_{out} = C_{in} \& (A \mid B) \mid (A \& B) \quad Sum = !C_{out} \& (A \mid B \mid C_{in}) \mid (A \& B \& C_{in})$$

9/14/2005

VLSI Design I; A. Milenkovic

46