
CPE/EE 427, CPE 527
VLSI Design I
L15: Power and
Designing for Low Power

Department of Electrical and Computer Engineering
University of Alabama in Huntsville


Aleksandar Milenkovic (www.ece.uah.edu/~milenska)
www.ece.uah.edu/~milenska/cpe527-05F

Why Power Matters

- Packaging costs
- Power supply rail design
- Chip and system cooling costs
- Noise immunity and system reliability
- Battery life (in portable systems)
- Environmental concerns
 - Office equipment accounted for 5% of total US commercial energy usage in 1993
 - Energy Star compliant systems

Why worry about power? -- Power Dissipation

 Lead microprocessors power continues to increase



Power delivery and dissipation will be prohibitive

10/18/2005

VLSI Design I; A. Milenkovic

Source: Borkar, De Intel®

3

Problem Illustration

***What happens
when the
CPU cooler is
removed?***





www.tomshardware.de
www.tomshardware.com

10/18/2005

VLSI Design I; A. Milenkovic

4

  Why worry about power ? – Battery Size/Weight




Expected battery lifetime increase
over the next 5 years: **30 to 40%**

From Rabaey, 1995

Why worry about power? -- Standby Power

Year	2002	2005	2008	2011	2014
Power supply V_{dd} (V)	1.5	1.2	0.9	0.7	0.6
Threshold V_T (V)	0.4	0.4	0.35	0.3	0.25

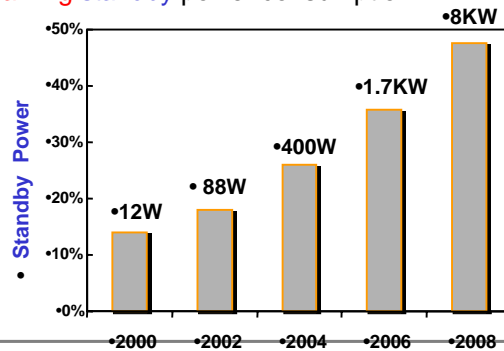- Drain leakage will increase as V_T decreases to maintain noise margins and meet frequency demands, leading to excessive **battery draining standby** power consumption.



...and phones leaky!



Source: Borkar, De Intel®

Power and Energy Figures of Merit


- **Power** consumption in **Watts**
 - determines battery life in hours
- **Peak power**
 - determines power ground wiring designs
 - sets packaging limits
 - impacts signal noise margin and reliability analysis
- **Energy** efficiency in **Joules**
 - rate at which power is consumed over time
- **Energy = power * delay**
 - **Joules = Watts * seconds**
 - lower energy number means less power to perform a computation at the same frequency

10/18/2005

VLSI Design I; A. Milenkovic

7

Power versus Energy

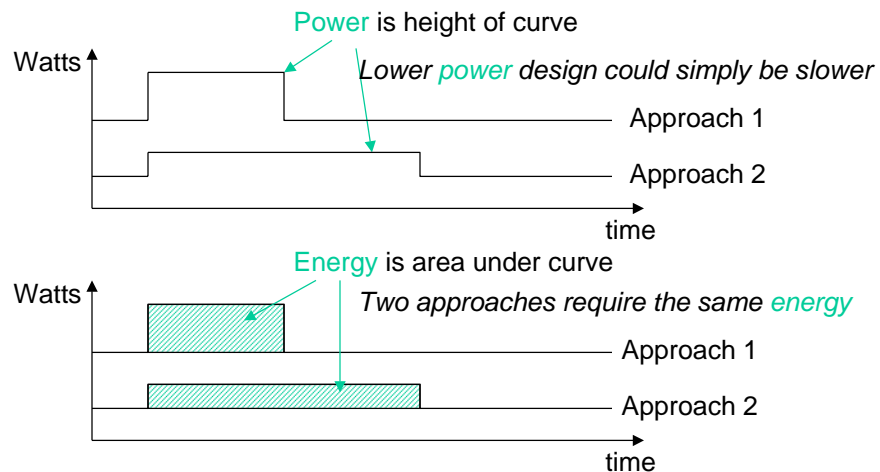

10/18/2005

VLSI Design I; A. Milenkovic


8

PDP and EDP

- Power-delay product (**PDP**) = $P_{av} * t_p = (C_L V_{DD}^2)/2$
 - PDP is the average **energy** consumed per switching event (Watts * sec = Joule)
 - **lower** power design could simply be a **slower** design

- Energy-delay product (**EDP**) = $PDP * t_p = P_{av} * t_p^2$

 - EDP is the average **energy** consumed multiplied by the computation time required
- takes into account that one can **trade** increased delay for lower energy/operation (e.g., via supply voltage scaling that increases delay, but decreases energy consumption)



- allows one to understand tradeoffs better


10/18/2005

VLSI Design I; A. Milenkovic

9

Understanding Tradeoffs

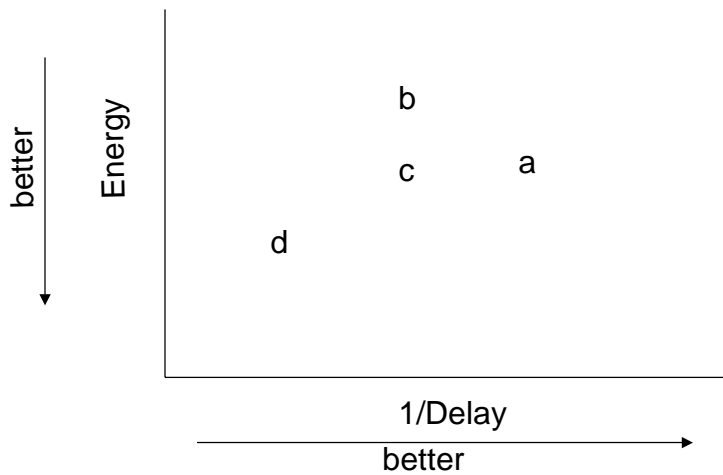Which design is the “best” (fastest, coolest, both) ?




10/18/2005

VLSI Design I; A. Milenkovic

10

Understanding Tradeoffs

 Which design is the "best" (fastest, coolest, both) ?



10/18/2005

VLSI Design I; A. Milenkovic

11

CMOS Energy & Power Equations

$$E = C_L V_{DD}^2 P_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} P_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

$$f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f_{clock}$$

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

Dynamic
power

Short-circuit
power


Leakage
power

10/18/2005

VLSI Design I; A. Milenkovic

12

Dynamic Power Consumption

 

$$\text{Energy/transition} = C_L * V_{DD}^2 * P_{0 \rightarrow 1}$$

$$P_{\text{dyn}} = \text{Energy/transition} * f = C_L * V_{DD}^2 * P_{0 \rightarrow 1} * f$$

$$P_{\text{dyn}} = C_{\text{EFF}} * V_{DD}^2 * f \quad \text{where } C_{\text{EFF}} = P_{0 \rightarrow 1} C_L$$

Not a function of transistor sizes!

Data dependent - a function of **switching activity!**

10/18/2005

VLSI Design I; A. Milenkovic

13

Pop Quiz

- Consider a 0.25 micron chip, 500 MHz clock, average load cap of 15fF/gate (fanout of 4), 2.5V supply.
 - Dynamic Power consumption per gate is ??
- With 1 million gates (assuming each transitions every clock)
 - Dynamic Power of entire chip = ??.

10/18/2005

VLSI Design I; A. Milenkovic

14

Lowering Dynamic Power

Capacitance:
Function of fan-out,
wire length, transistor
sizes

Supply Voltage:
Has been dropping
with successive
generations

$$P_{\text{dyn}} = C_L V_{\text{DD}}^2 P_{0 \rightarrow 1} f$$

Activity factor:
How often, on average,
do wires switch?


Clock frequency:
Increasing...

10/18/2005

VLSI Design I; A. Milenkovic

15

Short Circuit Power Consumption

 

Finite slope of the input signal causes a direct current path between V_{DD} and GND for a short period of time during switching when both the NMOS and PMOS transistors are conducting.

10/18/2005

VLSI Design I; A. Milenkovic

16

Short Circuit Currents Determinates

$$E_{sc} = t_{sc} V_{DD} I_{peak} P_{0 \rightarrow 1}$$

$$P_{sc} = t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1}$$


- Duration and slope of the input signal, t_{sc}
- I_{peak} determined by
 - the saturation current of the P and N transistors which depend on their sizes, process technology, temperature, etc.
 - strong function of the ratio between input and output slopes
 - a function of C_L

10/18/2005

VLSI Design I; A. Milenkovic


17

Impact of C_L on P_{sc}

 

Large capacitive load

 Output fall time significantly larger than input rise time.



Small capacitive load


Output fall time substantially smaller than the input rise time.

10/18/2005

VLSI Design I; A. Milenkovic

18

I_{peak} as a Function of C_L

 

When load capacitance is small, I_{peak} is large.

Short circuit dissipation is minimized by matching the rise/fall times of the input and output signals - **slope engineering**.


500 psec input slope

10/18/2005

VLSI Design I; A. Milenkovic

19

P_{sc} as a Function of Rise/Fall Times

 

When load capacitance is small ($t_{\text{sin}}/t_{\text{sout}} > 2$ for $V_{\text{DD}} > 2\text{V}$) the power is dominated by P_{sc}

If $V_{\text{DD}} < V_{\text{Tn}} + |V_{\text{Tp}}|$ then P_{sc} is eliminated since both devices are never on at the same time.


$W/L_p = 1.125 \mu\text{m}/0.25 \mu\text{m}$ normalized wrt zero input
 $W/L_n = 0.375 \mu\text{m}/0.25 \mu\text{m}$ rise-time dissipation
 $C_L = 30 \text{ fF}$

10/18/2005

VLSI Design I; A. Milenkovic

20

Leakage (Static) Power Consumption

 

Sub-threshold current is the dominant factor.

All increase **exponentially** with temperature!


10/18/2005

VLSI Design I; A. Milenkovic

21

Leakage as a Function of V_T

 - Continued scaling of supply voltage and the subsequent scaling of threshold voltage will make subthreshold conduction a dominant component of power dissipation.



- An 90mV/decade V_T roll-off - so each 255mV increase in V_T gives 3 orders of magnitude reduction in leakage (but adversely affects performance)

10/18/2005

VLSI Design I; A. Milenkovic

22

TSMC Processes Leakage and V_T

	CL018 G	CL018 LP	CL018 ULP	CL018 HS	CL015 HS	CL013 HS
V_{dd}	1.8 V	1.8 V	1.8 V	2 V	1.5 V	1.2 V
T_{ox} (effective)	42 Å	42 Å	42 Å	42 Å	29 Å	24 Å
L_{gate}	0.16 μm	0.16 μm	0.18 μm	0.13 μm	0.11 μm	0.08 μm
I_{DSat} (n/p) ($\mu\text{A}/\mu\text{m}$)	600/260	500/180	320/130	780/360	860/370	920/400
I_{off} (leakage) ($\text{pA}/\mu\text{m}$)	20	1.60	0.15	300	1,800	13,000
V_{Tn}	0.42 V	0.63 V	0.73 V	0.40 V	0.29 V	0.25 V
FET Perf. (GHz)	30	22	14	43	52	80


From MPR, 2000

10/18/2005

VLSI Design I; A. Milenkovic

23

Exponential Increase in Leakage Currents

 

From De, 1999

10/18/2005

VLSI Design I; A. Milenkovic

24

Review: Energy & Power Equations

$$E = C_L V_{DD}^2 P_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} P_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

$$f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f_{clock}$$

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

Dynamic power
(~90% today and decreasing relatively)

Short-circuit power
(~8% today and decreasing absolutely)

Leakage power
(~2% today and increasing)

10/18/2005

VLSI Design I; A. Milenkovic

25

Power and Energy Design Space

	Constant Throughput/Latency	Variable Throughput/Latency	
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced V_{dd} Sizing Multi V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- V_T	Sleep Transistors Multi- V_{dd} Variable V_T	+ Variable V_T


10/18/2005

VLSI Design I; A. Milenkovic

26

Dynamic Power as a Function of Device Size

- Device sizing affects dynamic energy consumption
 - gain is largest for networks with large overall effective fan-outs ($F = C_L/C_{g,1}$)
- The optimal gate sizing factor (f) for dynamic energy is smaller than the one for performance, especially for large F 's
 - e.g., for $F=20$,
 $f_{opt}(energy) = 3.53$ while
 $f_{opt}(performance) = 4.47$
- If energy is a concern avoid oversizing beyond the optimal

 

10/18/2005

VLSI Design I; A. Milenkovic

From Nikolic, UCB

27

Dynamic Power Consumption is Data Dependent

- Switching activity, $P_{0 \rightarrow 1}$, has two components
 - A static component – function of the logic topology
 - A dynamic component – function of the timing behavior (glitching)

Static transition probability

$$P_{0 \rightarrow 1} = P_{out=0} \times P_{out=1}$$

$$= P_0 \times (1 - P_0)$$

2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

With input signal probabilities

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

NOR static transition probability

$$= 3/4 \times 1/4 = 3/16$$


10/18/2005

VLSI Design I; A. Milenkovic

28

NOR Gate Transition Probabilities

 - Switching activity is a strong function of the input signal statistics
 - P_A and P_B are the probabilities that inputs A and B are one



$$P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - (1 - P_A)(1 - P_B)) (1 - P_A)(1 - P_B)$$


10/18/2005

VLSI Design I; A. Milenkovic

29

Transition Probabilities for Some Basic Gates

	$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$
NOR	$(1 - (1 - P_A)(1 - P_B)) \times (1 - P_A)(1 - P_B)$
OR	$(1 - P_A)(1 - P_B) \times (1 - (1 - P_A)(1 - P_B))$
NAND	$P_A P_B \times (1 - P_A P_B)$
AND	$(1 - P_A P_B) \times P_A P_B$
XOR	$(1 - (P_A + P_B - 2P_A P_B)) \times (P_A + P_B - 2P_A P_B)$

 

For X: $P_{0 \rightarrow 1} =$

For Z: $P_{0 \rightarrow 1} =$


10/18/2005

VLSI Design I; A. Milenkovic

30

Transition Probabilities for Some Basic Gates

	$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$
NOR	$(1 - (1 - P_A)(1 - P_B)) \times (1 - P_A)(1 - P_B)$
OR	$(1 - P_A)(1 - P_B) \times (1 - (1 - P_A)(1 - P_B))$
NAND	$P_A P_B \times (1 - P_A P_B)$
AND	$(1 - P_A P_B) \times P_A P_B$
XOR	$(1 - (P_A + P_B - 2P_A P_B)) \times (P_A + P_B - 2P_A P_B)$

 

For X: $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_A) P_A$
 $= 0.5 \times 0.5 = 0.25$

For Z: $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_X P_B) P_X P_B$
 $= (1 - (0.5 \times 0.5)) \times (0.5 \times 0.5) = 3/16$


10/18/2005

VLSI Design I; A. Milenkovic

31

Inter-signal Correlations

 - Determining switching activity is complicated by the fact that signals exhibit correlation in space and time
 - reconvergent fan-out



Reconvergent fan-out

$$P(Z=1) = P(B=1) \& P(X=1 \mid B=1)$$

- Have to use **conditional probabilities**

10/18/2005

VLSI Design I; A. Milenkovic


32

Inter-signal Correlations

- Determining switching activity is complicated by the fact that signals exhibit correlation in space and time

– reconvergent fan-out
 
$$(1-0.5)(1-0.5) \times (1-(1-0.5)(1-0.5)) = 3/16$$



Reconvergent

$$P(Z=1) = P(B=1) * P(X=1 | B=1)$$

$$= 0.5 * 1 = 0.5$$

$$P(Z=0) = 1 - P(B=1) * P(X=1 | B=1) = 0.5$$

$$P(0 \rightarrow 1) = 0.5 * 0.5 = 0.25$$

$$P(Z=1) = P(B=1) \& P(X=1 | B=1)$$

- Have to use **conditional probabilities**

10/18/2005



VLSI Design I; A. Milenkovic

33

Logic Restructuring

Logic restructuring: changing the topology of a logic network to reduce transitions
  
$$\text{AND: } P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_A P_B) \times P_A P_B$$



- Chain implementation has a lower overall switching activity than the tree implementation for random inputs



Ignores glitching effects

10/18/2005

VLSI Design I; A. Milenkovic

34

Input Ordering

  



Beneficial to postpone the introduction of signals with a **high** transition rate (signals with signal probability close to 0.5)

10/18/2005

VLSI Design I; A. Milenkovic

35

Input Ordering

  

Beneficial to postpone the introduction of signals with a **high** transition rate (signals with signal probability close to 0.5)



10/18/2005

VLSI Design I; A. Milenkovic

36

Glitching in Static CMOS Networks

  - Gates have a nonzero propagation delay resulting in spurious transitions or **glitches** (dynamic hazards)
 - glitch: node exhibits multiple transitions in a single cycle before settling to the correct logic value





10/18/2005

VLSI Design I; A. Milenkovic

37

Glitching in Static CMOS Networks

  - Gates have a nonzero propagation delay resulting in spurious transitions or **glitches** (dynamic hazards)
 - glitch: node exhibits multiple transitions in a single cycle before settling to the correct logic value




10/18/2005

VLSI Design I; A. Milenkovic


38

Glitching in an RCA

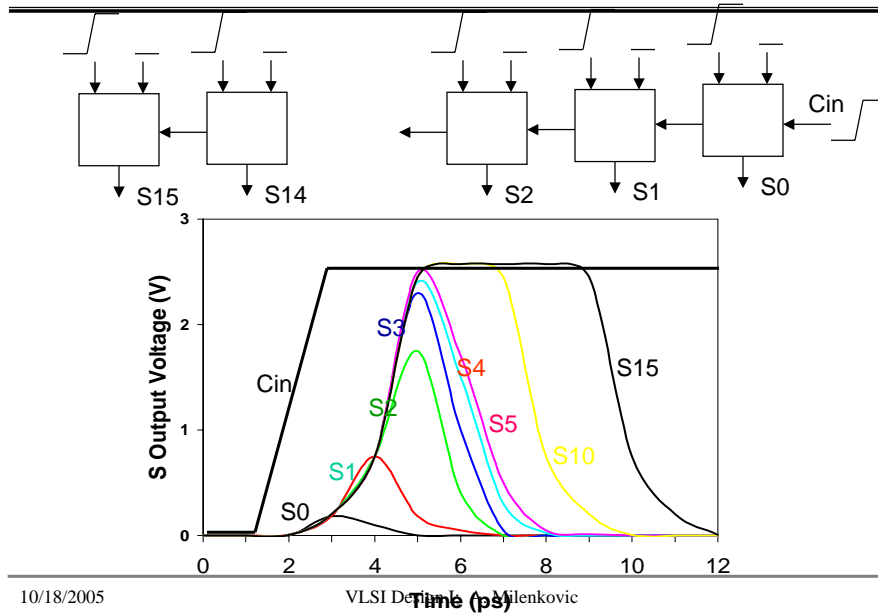

Balanced Delay Paths to Reduce Glitching

 Glitching is due to a mismatch in the path lengths in the logic network; if all input signals of a gate change simultaneously, no glitching occurs



So equalize the lengths of timing paths through logic

Power and Energy Design Space

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced V_{dd} Sizing Multi- V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- V_T	Sleep Transistors Multi- V_{dd} Variable V_T	+ Variable V_T


10/18/2005

VLSI Design I; A. Milenkovic

41

Dynamic Power as a Function of V_{DD}

 - Decreasing the V_{DD} **decreases** dynamic energy consumption (quadratically)
- But, **increases** gate delay (decreases performance)



- Determine the critical path(s) at **design time** and use high V_{DD} for the transistors on those paths for speed. Use a lower V_{DD} on the other gates, especially those that drive large capacitances (as this yields the largest energy benefits).


10/18/2005

VLSI Design I; A. Milenkovic

42

Multiple V_{DD} Considerations

- How many V_{DD} ? – Two is becoming common
 - Many chips already have two supplies (one for core and one for I/O)
- When combining multiple supplies, **level converters** are required whenever a module at the lower supply drives a gate at the higher supply (step-up)
 - If a gate supplied with V_{DDL} drives a gate at V_{DDH} , the PMOS never turns off
 - The cross-coupled PMOS transistors do the level conversion
 - The NMOS transistor operate on a reduced supply
 - Level converters are not needed for a step-down change in voltage
 - Overhead of level converters can be mitigated by doing conversions at register boundaries and embedding the level conversion inside the flipflop

 


10/18/2005

VLSI Design I; A. Milenkovic

43

Dual-Supply Inside a Logic Block

 - Minimum energy consumption is achieved if **all** logic paths are critical (have the same delay)
- Clustered voltage-scaling
 - Each path starts with V_{DDH} and switches to V_{DDL} (gray logic gates) when delay **slack** is available
 - Level conversion is done in the flipflops at the end of the paths



10/18/2005

VLSI Design I; A. Milenkovic

44

Power and Energy Design Space

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced V_{dd} Sizing Multi- V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- V_T	Sleep Transistors Multi- V_{dd} Variable V_T	+ Variable V_T

10/18/2005

VLSI Design I; A. Milenkovic


45

Stack Effect

- Leakage is a function of the circuit topology and the value of the inputs

$$V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

 where V_{T0} is the threshold voltage at $V_{SB} = 0$; V_{SB} is the source-bulk (substrate) voltage; γ is the **body-effect coefficient**



A	B	V_x	I_{SUB}
0	0	$V_T \ln(1+n)$	$V_{GS}=V_{BS}= -V_x$
0	1	0	$V_{GS}=V_{BS}=0$
1	0	$V_{DD}-V_T$	$V_{GS}=V_{BS}=0$
1	1	0	$V_{SG}=V_{SB}=0$

- Leakage is least when $A = B = 0$
- Leakage reduction due to stacked transistors is called the **stack effect**

10/18/2005

VLSI Design I; A. Milenkovic

46

Short Channel Factors and Stack Effect

- In short-channel devices, the subthreshold leakage current depends on V_{GS} , V_{BS} and V_{DS} . The V_T of a short-channel device decreases with increasing V_{DS} due to **DIBL** (drain-induced barrier lowering).
 - Typical values for DIBL are 20 to 150mV change in V_T per voltage change in V_{DS} so the stack effect is even more significant for short-channel devices.
 - V_X reduces the drain-source voltage of the top nfet, increasing its V_T and lowering its leakage
- For our 0.25 micron technology, V_X settles to $\sim 100\text{mV}$ in steady state so $V_{BS} = -100\text{mV}$ and $V_{DS} = V_{DD} - 100\text{mV}$ which is 20 times smaller than the leakage of a device with $V_{BS} = 0\text{mV}$ and $V_{DS} = V_{DD}$


10/18/2005

VLSI Design I; A. Milenkovic

47

Leakage as a Function of Design Time V_T

- Reducing the V_T **increases** the subthreshold leakage current (exponentially)
 - 90mV reduction in V_T increases leakage by an order of magnitude
- But, reducing V_T **decreases** gate delay (increases performance)
- Determine the critical path(s) at **design time** and use low V_T devices on the transistors on those paths for speed. Use a high V_T on the other logic for leakage control.
 - A careful assignment of V_T 's can reduce the leakage by as much as 80%

 


10/18/2005

VLSI Design I; A. Milenkovic

48

Dual-Thresholds Inside a Logic Block

 - Minimum energy consumption is achieved if **all** logic paths are critical (have the same delay)
- Use lower threshold on timing-critical paths
 - Assignment can be done on a per gate or transistor basis; no clustering of the logic is needed
 - No level converters are needed




10/18/2005

VLSI Design I; A. Milenkovic

49

Variable V_T (ABB) at Run Time

- $V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$
 - For an n-channel device, the substrate is normally tied to ground ($V_{SB} = 0$)
 - A negative bias on V_{SB} causes V_T to increase
 - Adjusting the substrate bias at **run time** is called **adaptive body-biasing (ABB)**
 - Requires a dual well fab process

 

10/18/2005

VLSI Design I; A. Milenkovic

50