



Verilog Tutorial

Aleksandar Milenković

The LaCASA Laboratory
Electrical and Computer Engineering Department
The University of Alabama in Huntsville
Email: milenka@ece.uah.edu
Web: <http://www.ece.uah.edu/~milenka>
<http://www.ece.uah.edu/~lacasa>



Outline

- Introduction
- Verilog (with focus on synthesis)
 - Continuous Assignments (`assign`)
 - Hierarchy
 - Always Blocks





Introduction

- Verilog is a Hardware Description Language (HDL)
- Developed by Phil Moorby at Gateway Design Automation in 1984; acquired by Cadence in 1989
- Allow description of a digital system at
 - Behavioral Level – describes how the outputs are computed as functions of the inputs
 - Structural Level – describes how a module is composed of simpler modules of basic primitives (gates or transistors)
- Design styles: Top-Down vs. Bottom-Up



Continuous Assignments

- Describe inputs & outputs
- Assign statement
 - Left-hand side is updated any time the right-hand side changes (a or b)
- Implies combinational logic

```

module mux2_4 (input [3:0] d0, d1,
              input s,
              output [3:0] y);
    assign y = s ? d1 : d0;
endmodule

```

```

module and8 (input [7:0] a,
            output y);
    assign y = &a;
endmodule

```

```

module adder (a, b, y);
    input [31:0] a;
    input [31:0] b;
    output [31:0] y;

    assign y = a + b;
endmodule

```

```

module invA4 (input [3:0] a,
            output [3:0] y);
    assign y = ~a;
endmodule

```

```

module fa (input a, b, cin,
          output s, cout);
    assign s = a ^ b ^ cin;
    assign cout = (a & b) | (cin & (a | b));
endmodule

```





Hierarchy

- Structural design style
- Mux4 out of Mux2s
- Try Dec4to16 using Dec2to4s?

```

module mux2_4 (input [3:0] d0, d1,
              input s,
              output [3:0] y);

    assign y = s ? d1 : d0;
endmodule

```

```

module mux4_4 (input [3:0] d0, d1, d2, d3,
              input [1:0] s,
              output [3:0] y);

    wire [3:0] mol, moh;
    mux2_4 lowmux(d0, d1, s[0], mol);
    mux2_4 highmux(d2, d3, s[0], moh);
    mux2_4 finalmux(mol, moh, s[1], y);
endmodule

```



... and more

```

module tristate_4 (input [3:0] a,
                 input en,
                 output [3:0] y);

    assign y = en ? a : 4'bz;
endmodule

```

```

// mux2 using tristate
module mux2_4 (input [3:0] d0, d1,
              input s,
              output [3:0] y);

    tristate(d0, ~s, y);
    tristate(d1, s, y);
endmodule

```

```

// demonstrate selection of ranges on a bus
module mux2_8 (input [7:0] d0, d1,
              input s,
              output [7:0] y);

    mux2_4 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);
    mux2_4 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
endmodule

```

```

// demonstrate signal concatenation
module mul (input [7:0] a, b,
           output [7:0] upper, lower);

    assign {upper, lower} = a * b;
endmodule

```

```

// demonstrate sign extension
module (input [7:0] a,
       output [15:0] y);

    assign y = {{16{a[7]}}, a[7:0]};
endmodule

```



Always Blocks

- **Always** blocks are reevaluated only when signals in the header (called a *sensitivity list*) change
- Depending on the form, can imply either sequential or combinational circuits



Combinational Logic

```
module mux2( input d0, d1, s,
             output y);

    reg y;

    always @(s or d0 or d1)
    begin : MUX
        case(s)
            1'b0 : y = d0;
            1'b1 : y = d1;
        endcase
    end
endmodule
```

```
module mux2( input d0, d1, s,
             output y);

    reg y;

    always @(*)
    begin : MUX
        case(s)
            1'b0 : y = d0;
            1'b1 : y = d1;
        endcase
    end
endmodule
```

Warning: All the signals on the left side of assignments in always blocks must be declared as `reg`. However, declaring a signal as `reg` does not mean the signal is actually a register.



Tri-State

```

module three_st (T, I, O);
  input T, I;
  output O;
  reg O;

  always @(T or I)
  begin
    if (~T)
      O = I;
    else
      O = 1'bZ;
    end
  endmodule


```

```

module three_st (T, I, O);
  input T, I;
  output O;

  assign O = (~T) ? I : 1'bZ;
endmodule

```

 

9

Registers

D-FF with Positive Clock

```

module flop (C, D, Q);
  input C, D;
  output Q;
  reg Q;

  always @(posedge C)
  begin
    Q = D;
  end
endmodule

```



D-FF with Negative-edge Clock and Async. Clear

```

module flop (C, D, CLR, Q);
  input C, D, CLR;
  output Q;
  reg Q;

  always @(negedge C or posedge CLR)
  begin
    if (CLR)
      Q = 1'b0;
    else
      Q = D;
    end
  end
endmodule

```

  

10


DFFs

D-FF with Positive-Edge Clock and Synchronous Set

```

module flop (C, D, S, Q);
input C, D, S;
output Q;
reg Q;

 always @(posedge C)
begin
if (S)
Q = 1'b1;
else
Q = D;
end
endmodule
    
```




D-FF with Positive-Edge Clock and Clock Enable

```

module flop (C, D, CE, Q);
input C, D, CE;
output Q;
reg Q;

 always @(posedge C)
begin
if (CE)
Q = D;
end
endmodule
    
```




Latches

Latch with Positive Gate

```

module latch (G, D, Q);
input G, D;
output Q;
reg Q;

 always @(G or D)
begin
if (G)
Q = D;
end
endmodule
    
```




Latch with Positive Gate and Asynchronous Clear

```

module latch (G, D, CLR, Q);
input G, D, CLR;
output Q;
reg Q;

 always @(G or D or CLR)
begin
if (CLR)
Q = 1'b0;
else if (G)
Q = D;
end
endmodule
    
```





4-bit Latch


4-bit Latch with Positive Gate Inverted Gate and Asynchronous Preset

```

module latch (G, D, PRE, Q);
  input G, PRE;
  input [3:0] D;
  output [3:0] Q;
  reg [3:0] Q;

  always @(G or D or PRE)
  begin
    if (PRE)
      Q = 4'b1111;
    else if (~G)
      Q = D;
    end
  end
endmodule

```

 

4-bit Register


4-bit Register Positive-Edge Clock, Asynchronous Set and Clock Enable

```

module flop (C, D, CE, PRE, Q);
  input C, CE, PRE;
  input [3:0] D;
  output [3:0] Q;
  reg [3:0] Q;

  always @(posedge C or posedge PRE)
  begin
    if (PRE)
      Q = 4'b1111;
    else
      if (CE)
        Q = D;
    end
  end
endmodule

```

 

Counters

?

```
module counter (C, CLR, Q);
input C, CLR;
output [3:0] Q;
reg [3:0] tmp;

always @(posedge C or posedge CLR)
begin
if (CLR)
tmp = 4'b0000;
else
tmp = tmp + 1'b1;
end
assign Q = tmp;
endmodule
```

??

```
module counter (C, CLR, Q);
input C, CLR;
output [3:0] Q;
reg [3:0] tmp;

always @(posedge C or posedge CLR)
begin
if (CLR)
tmp = 4'b0000;
else
tmp = tmp + 1'b1;
end
assign Q = tmp;
endmodule
```



Memories

```
module ram (input clk,
input [5:0] addr,
input wrb,
input [15:0] din,
output [15:0] dout);

reg [15:0] mem[63:0]; // memory

always @(posedge clk)
begin
if (~wrb)
mem[addr] <= din;
end

assign dout = mem[addr];
endmodule
```



Blocking and Non-blocking Assignments

- Blocking assignments (use =)
 - A group of blocking assignments inside a begin-end block is evaluated sequentially
- Non-blocking assignments (use <=)
 - A group of non-blocking assignments are evaluated in parallel; all of the statements are evaluated before any of the left sides are updated.



Shift Register

```
module shiftreg (input clk,
                 input sin,
                 output reg [3:0] q);
    always @(posedge clk)
    begin
        q[0] <= sin;
        q[1] <= q[0];
        q[2] <= q[1];
        q[3] <= q[2];
        // could be replaced by
        // q <= {q[2:0], sin}
    end
endmodule
```

```
// this is incorrect shift register
module shiftreg (input clk,
                 input sin,
                 output reg [3:0] q);

    always @(posedge clk)
    begin
        q[0] = sin;
        q[1] = q[0];
        q[2] = q[1];
        q[3] = q[2];
    end
endmodule
```



State Machine

- Identify 3 portions
 - State register
 - Next state logic
 - Output logic
- State register
 - Resets asynchronously to the initial state
 - Otherwise advances to the next state
- Next logic
 - Computes the next state as a function of the current state and inputs
- Output logic
 - Computes the output as a function of the current state and the inputs

 


FIG A.5 History FSM state transition diagram



State Machine Description

```

module hFSM (input clk, reset, a,
             output x, y);
    reg[2:0] state, nextstate;
    parameter S0 = 3'b000;
    parameter S1 = 3'b010;
    parameter S2 = 3'b011;
    parameter S3 = 3'b100;
    parameter S4 = 3'b101;

    always @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    always @(*)
        case (state)
            S0: if (a) nextstate <= S3;
                else nextstate <= S1;
            S1: if (a) nextstate <= S3;
                else nextstate <= S2;
            S2: if (a) nextstate <= S3;
                else nextstate <= S2;
            S3: if (a) nextstate <= S4;
                else nextstate <= S1;
            S4: if (a) nextstate <= S4;
                else nextstate <= S1;
            default: nextstate <= S0;
        endcase
endmodule
    
```

```

//output logic
assign x = (state[1] & ~a) |
           (state[2] & a);
assign y = (state[1] & state[0] & ~a)
           | (state[2] & state[0] & a);
endmodule
    
```

