


CPE 626
Advanced VLSI Design
Lecture 3: VHDL Recapitulation

Aleksandar Milenkovic

<http://www.ece.uah.edu/~milenska>
<http://www.ece.uah.edu/~milenska/cpe626-04F/>
milenska@ece.uah.edu

Assistant Professor
 Electrical and Computer Engineering Dept.
 University of Alabama in Huntsville




Advanced VLSI Design

Outline

- ✿ Introduction to VHDL
- ✿ Modeling of Combinational Networks
- ✿ Modeling of FFs
- ✿ Delays
- ✿ Modeling of FSMs
- ✿ Wait Statements
- ✿ VHDL Data Types
- ✿ VHDL Operators
- ✿ Functions, Procedures, Packages

© A. Milenkovic 2




Advanced VLSI Design

Intro to VHDL

- ✿ Technology trends
 - ✿ 1 billion transistor chip running at 20 GHz in 2007
- ✿ Need for Hardware Description Languages
 - ✿ Systems become more complex
 - ✿ Design at the gate and flipflop level becomes very tedious and time consuming
- ✿ HDLs allow
 - ✿ Design and debugging at a higher level before conversion to the gate and flip-flop level
 - ✿ Tools for synthesis do the conversion
- ✿ VHDL, Verilog
- ✿ VHDL – VHSIC Hardware Description Language

© A. Milenkovic 3




Advanced VLSI Design

Intro to VHDL


- ✿ Developed originally by DARPA
 - ✿ for specifying digital systems
- ✿ International IEEE standard (IEEE 1076-1993)
- ✿ Hardware Description, Simulation, Synthesis
- ✿ Provides a mechanism for digital design and reusable design documentation
- ✿ Support different description levels
 - ✿ Structural (specifying interconnections of the gates),
 - ✿ Dataflow (specifying logic equations), and
 - ✿ Behavioral (specifying behavior)

© A. Milenkovic 4



Advanced VLSI Design

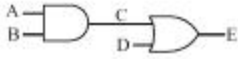
VHDL Description of Combinational Networks



```


Concurrent Statements
C <= A and B after 5 ns;
E <= C or D after 5 ns;
If delay is not specified, "delta" delay is assumed
C <= A and B;
E <= C or D;
Order of concurrent statements is not important
E <= C or D;
C <= A and B;
This statement executes repeatedly
CLK <= not CLK after 10 ns;
This statement causes a simulation error
CLK <= not CLK;
    
```

© A. Milenkovic 5



Advanced VLSI Design

Entity-Architecture Pair

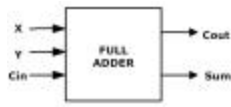

Full Adder Example


```

entity FullAdder is
port (X, Y, Cin: in bit; -- Inputs
      Cout, Sum: out bit); -- Outputs
end FullAdder;

architecture Equations of FullAdder is
begin
Sum <= X xor Y xor Cin after 10 ns;
Cout <= (X and Y) or (X and Cin) or (Y and Cin) after 10 ns;
end Equations;
    
```

© A. Milenkovic 6


VHDL Program Structure

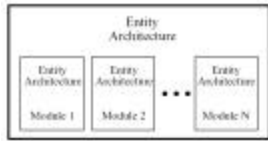

```
entity entity-name is
[port(interface-signal-declaration);]
end [entity] [entity-name];

architecture architecture-name of entity-name is
[declarations]
begin
architecture body [architecture-name];
end [architecture] [architecture-name];
```

4-bit Adder

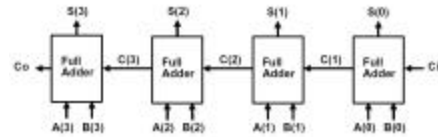

```
entity Adder4 is
port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;
```

4-bit Adder (cont'd)

```
entity Adder4 is
port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;
```

```
architecture Structure of Adder4 is
component FullAdder
port (X, Y, Cin: in bit; -- Inputs
Cout, Sum: out bit); -- Outputs
end component;
signal C: bit_vector(3 downto 1);
begin --instantiate four copies of the FullAdder
FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
end Structure;
```

4-bit Adder - Simulation

```
list A B Co C Ci S -- put these signals on the output list
force A 1111 -- set the A inputs to 1111
force B 0011 -- set the B inputs to 0011
force Ci 1 -- set the Ci to 1
run 50 -- run the simulation for 50 ns
force Ci 0
force A 0101
force B 1110
run 50
```


ns	delta	a	b	co	c	ci	s
0	ns	0100	0000	0	010	0	0000
0	ns	1111	0001	0	010	1	0000
10	ns	1111	0001	0	010	1	1111
20	ns	1111	0001	0	010	1	1101
30	ns	1111	0001	0	110	1	1001
40	ns	1111	0001	1	110	1	0001
50	ns	0101	1110	1	110	0	0101
60	ns	0101	1110	1	110	0	0101
70	ns	0101	1110	1	110	0	0111
80	ns	0101	1110	1	110	0	0011

Modeling Flip-Flops Using VHDL Processes

```
General form of process
process(sensitivity-list)
begin
sequential-statements
end process;
```

- Whenever one of the signals in the sensitivity list changes, the sequential statements are executed in sequence one time

D Flip-flop Model

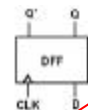


```
entity DFF is
port (D, CLK: in bit;
Q: out bit; QN: out bit := '1');
-- initialize QN to '1' since bit signals are initialized to '0' by default
end DFF;

architecture SIMPLE of DFF is
begin
process (CLK) -- process is executed when CLK changes
begin
if CLK = '1' then -- rising edge of clock
Q <= D after 10 ns;
QN <= not D after 10 ns;
end if;
end process;
end SIMPLE;
```

Advanced VLSI Design

JK Flip-Flop Model

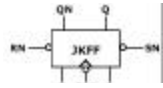

```

entity JKFF is
  port (SN, RN, J, K, CLK: in bit;
        Q: inout bit; QN: out bit := '1'); -- see Note 1
end JKFF;

architecture JKFF1 of JKFF is
begin
  process (SN, RN, CLK) -- see Note 2
  begin
    if RN = '0' then Q <= '0' after 10 ns; -- RN=D will clear the FF
    elsif SN = '0' then Q <= '1' after 10 ns; -- SN=D will set the FF
    elsif CLK = '0' and CLK'event then -- see Note 3
      Q <= (J and not Q) or (not K and Q) after 10 ns; -- see Note 4
    end if;
  end process;
  QN <= not Q; -- see Note 5
end JKFF1;
  
```

© A. Milenkovic

13

Advanced VLSI Design

Concurrent Statements vs. Process

A, B, C, D are integers
A=1, B=2, C=3, D=0
D changes to 4 at time 10

```

A <= B; -- statement 1
B <= C; -- statement 2
C <= D; -- statement 3
  
```

```

process (B, C, D)
begin
  A <= B; -- statement 1
  B <= C; -- statement 2
  C <= D; -- statement 3
end process;
  
```

Simulation Results

time	delta	A	B	C	D
0	+0	0	1	2	0
10	+0	1	2	3	4
10	+1	1	2	4	4
10	+2	1	4	4	4
10	+3	4	4	4	4


(stat. 3 exe.)
(stat. 2 exe.)
(stat. 1 exe.)
(no exec.)

© A. Milenkovic

14

Advanced VLSI Design

Using Nested IFs:

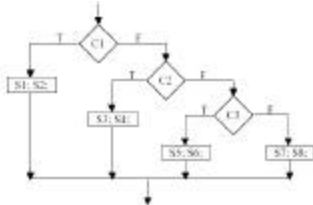

```

if (C1) then S1; S2;
else if (C2) then S3; S4;
else if (C3) then S5; S6;
else S7; S8;
end if;


if (C1) then S1; S2;
elsif (C2) then S3; S4;
elsif (C3) then S5; S6;
else S7; S8;
end if;
  
```

© A. Milenkovic

15

Advanced VLSI Design

VHDL Models for a MUX

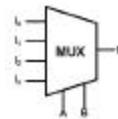

```

F <= (not A and not B and 10) or
(not A and B and 11) or
(A and not B and 12) or
(A and B and 13);
  
```

MUX model using a conditional signal assignment statement:

```

F <= 10 when Sel = 0
else 11 when Sel = 1
else 12 when Sel = 2
else 13;
  
```

Sel represents the integer equivalent of a 2-bit binary number with bits A and B

If a MUX model is used inside a process, the MUX can be modeled using a CASE statement (cannot use a concurrent statement):

```

case Sel is
  when 0 => F <= 10;
  when 1 => F <= 11;
  when 2 => F <= 12;
  when 3 => F <= 13;
end case;

The case statement has the general form:

case expression is
  when choice1 => sequential_statements1;
  when choice2 => sequential_statements2;
  ...
  [when others => sequential_statements];
end case;
  
```

© A. Milenkovic

16

Advanced VLSI Design

MUX Models (1)

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
  port (
    A : in std_logic_vector(15 downto 0);
    SEL : in std_logic_vector( 3 downto 0);
    Y : out std_logic);
end SELECTOR;

architecture RTL1 of SELECTOR is
begin
  p0 : process (A, SEL)
  begin
    if (SEL = "0000") then Y <= A(0);
    elsif (SEL = "0001") then Y <= A(1);
    elsif (SEL = "0010") then Y <= A(2);
    elsif (SEL = "0011") then Y <= A(3);
    elsif (SEL = "0100") then Y <= A(4);
    elsif (SEL = "0101") then Y <= A(5);
    elsif (SEL = "0110") then Y <= A(6);
    elsif (SEL = "0111") then Y <= A(7);
    elsif (SEL = "1000") then Y <= A(8);
    elsif (SEL = "1001") then Y <= A(9);
    elsif (SEL = "1010") then Y <= A(10);
    elsif (SEL = "1011") then Y <= A(11);
    elsif (SEL = "1100") then Y <= A(12);
    elsif (SEL = "1101") then Y <= A(13);
    elsif (SEL = "1110") then Y <= A(14);
    else Y <= A(15);
    end if;
  end process;
end RTL1;
  
```

© A. Milenkovic

17

Advanced VLSI Design

MUX Models (2)

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
  port (
    A : in std_logic_vector(15 downto 0);
    SEL : in std_logic_vector( 3 downto 0);
    Y : out std_logic);
end SELECTOR;

architecture RTL3 of SELECTOR is
begin
  with SEL select
    Y <= A(0) when "0000",
    A(1) when "0001",
    A(2) when "0010",
    A(3) when "0011",
    A(4) when "0100",
    A(5) when "0101",
    A(6) when "0110",
    A(7) when "0111",
    A(8) when "1000",
    A(9) when "1001",
    A(10) when "1010",
    A(11) when "1011",
    A(12) when "1100",
    A(13) when "1101",
    A(14) when "1110",
    A(15) when others;
end RTL3;
  
```

© A. Milenkovic

18

MUX Models (3)

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
port (
    A : in std_logic_vector(15
downto 0);
    SEL : in std_logic_vector( 3
downto 0);
    Y : out std_logic);
end SELECTOR;

architecture RTL2 of SELECTOR is
begin
    p1 : process (A, SEL)
    begin
        case SEL is
            when '0000' => Y <= A(0);
            when '0001' => Y <= A(1);
            when '0010' => Y <= A(2);
            when '0011' => Y <= A(3);
            when '0100' => Y <= A(4);
            when '0101' => Y <= A(5);
            when '0110' => Y <= A(6);
            when '0111' => Y <= A(7);
            when '1000' => Y <= A(8);
            when '1001' => Y <= A(9);
            when '1010' => Y <= A(10);
            when '1011' => Y <= A(11);
            when '1100' => Y <= A(12);
            when '1101' => Y <= A(13);
            when '1110' => Y <= A(14);
            when others => Y <= A(15);
        end case;
    end process;
end RTL2;
    
```

MUX Models (4)


```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
port (
    A : in std_logic_vector(15
downto 0);
    SEL : in std_logic_vector( 3
downto 0);
    Y : out std_logic);
end SELECTOR;

architecture RTL4 of SELECTOR is
begin
    Y <= A(conv_integer(SEL));
end RTL4;
    
```


Compilation and Simulation of VHDL Code

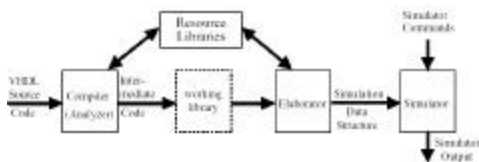- ❑ Compiler (Analyzer) – checks the VHDL source code
 - ❑ does it conforms with VHDL syntax and semantic rules
 - ❑ are references to libraries correct
- ❑ Intermediate form used by a simulator or by a synthesizer
- ❑ Elaboration




Timing Model

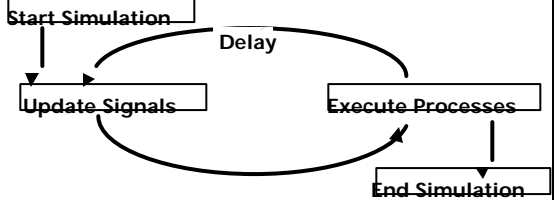- ❑ VHDL uses the following simulation cycle to model the stimulus and response nature of digital hardware




Delay Types

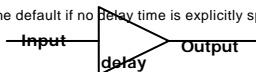- ❑ All VHDL signal assignment statements prescribe an amount of time that must transpire before the signal assumes its new value
- ❑ This prescribed delay can be in one of three forms:
 - ❑ Transport -- prescribes propagation delay only
 - ❑ Inertial -- prescribes propagation delay and minimum input pulse width
 - ❑ Delta -- the default if no delay time is explicitly specified



Transport Delay

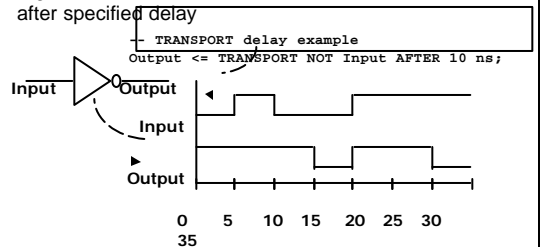- ❑ Transport delay must be explicitly specified
 - ❑ i.e. keyword "TRANSPORT" must be used
- ❑ Signal will assume its new value after specified delay




Inertial Delay

- Provides for specification propagation delay and input pulse width, i.e. 'inertia' of output:

```
target <= [REJECT time_expression] INERTIAL waveform;
```

- Inertial delay is default and REJECT is optional:
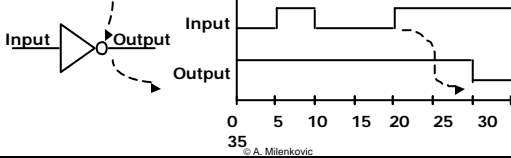
```
Output <= NOT Input AFTER 10 ns;
-- Propagation delay and minimum pulse width are 10ns
```



Inertial Delay (cont.)

- Example of gate with 'inertia' smaller than propagation delay
 - e.g. Inverter with propagation delay of 10ns which suppresses pulses shorter than 5ns

```
Output <= REJECT 5ns INERTIAL NOT Input AFTER 10ns;
```



- Note: the REJECT feature is new to VHDL 1076-1993

Delta Delay


- Default signal assignment propagation delay if no delay is explicitly prescribed
 - VHDL signal assignments do not take place immediately
 - Delta is an infinitesimal VHDL time unit so that all signal assignments can result in signals assuming their values at a future time

```
E.g. Output <= NOT Input;
-- Output assumes new value in one delta cycle
```

- Supports a model of concurrent VHDL process execution
 - Order in which processes are executed by simulator does not affect simulation output


Simulation Example
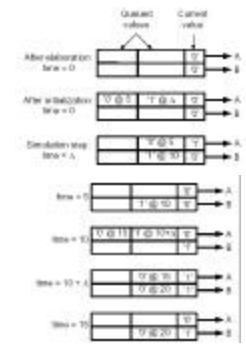
```
entity simulation_example is
end simulation_example;
architecture test of simulation_example is
    signal A,B: bit;
begin
    P1: process(B)
    begin
        A <= '1';
        A <= transport '0' after 5 ns;
    end process P1;
    P2: process(A)
    begin
        if A = '1' then B <= not B after 10 ns; end if;
    end process P2;
end test;
```



Modeling a Sequential Machine

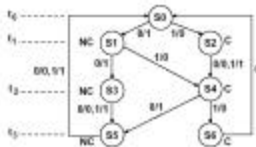Mealy Machine for 8421 BCD to 8421 BCD + 3 bit serial converter



PS	NS		Z	
	X=0	X=1	X=0	X=1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S6	S6	1	0
S5	S0	S0	0	1
S6	S0	-	1	-

How to model this in VHDL?

Modeling a Sequential Machine

```
entity SM is
end entity SM;
architecture Behavioral of SM is
    signal state: integer := 0;
    signal Z: integer := 0;
begin
    process(SM)
    begin
        if state = 0 then
            Z <= 1;
            state <= 1;
        elsif state = 1 then
            Z <= 1;
            state <= 2;
        elsif state = 2 then
            Z <= 0;
            state <= 4;
        elsif state = 3 then
            Z <= 0;
            state <= 5;
        elsif state = 4 then
            Z <= 1;
            state <= 6;
        elsif state = 5 then
            Z <= 0;
            state <= 0;
        elsif state = 6 then
            Z <= 1;
            state <= 0;
        end if;
    end process;
end Behavioral;
```

state	Z	next state
0	1	1
1	1	2
2	0	4
3	0	5
4	1	6
5	0	0
6	1	0



Behavioral VHDL Model

```

entity SM1_2 is
  port(CLK: IN std_logic; Z: out std_logic);
  and SM1_2;
architecture Structure of SM1_2 is
  signal State, NextState: integer := 0;
  process(State,Z)
  begin
    case State is
      when 0 =>
        if CLK'event then
          if State = 0 then NextState := 1; end if;
          if State = 1 then NextState := 2; end if;
          if State = 2 then NextState := 3; end if;
          if State = 3 then NextState := 4; end if;
          if State = 4 then NextState := 5; end if;
          if State = 5 then NextState := 6; end if;
          if State = 6 then NextState := 7; end if;
          if State = 7 then NextState := 8; end if;
          if State = 8 then NextState := 9; end if;
          if State = 9 then NextState := 0; end if;
        end if;
      when 1 to 9 =>
        NextState := State;
      when others => null;
    end case;
  end process;
  process(CLK)
  begin
    if CLK'event then
      State <= NextState;
    end if;
  end process;
end Structure;

```

State	Next State	Z
0	1	0
1	2	0
2	3	0
3	4	0
4	5	0
5	6	0
6	7	0
7	8	0
8	9	0
9	0	1

- Two processes:
- the first represents the combinational network;
 - the second represents the state register



Simulation of the VHDL Model


Simulation command file:

```

wave CLK X State NextState Z
force CLK 0 0, 1 100 -repeat 200
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
run 1600

```

Waveforms:

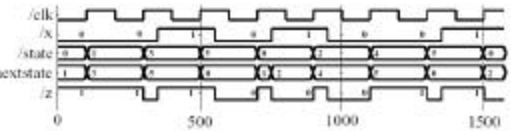

Dataflow VHDL Model

```

-- The following is a description of the sequential machine of
-- Figure 3-17 in terms of its next state equations.
-- The following state assignment was used:
-- S0->0; S1->4; S2->5; S3->7; S4->6; S5->3; S6->2
entity SM1_2 is
  port(CLK: in std_logic;
        Z: out std_logic);
  and SM1_2;
architecture Equations_1 of SM1_2 is
  signal Q1,Q2,Q3: bit;
  begin
    process(CLK)
    begin
      if CLK='1' then
        Q1 <= not Q2 after 10 ns;
        Q2 <= Q1 after 10 ns;
        Q3 <= (Q1 and Q2 and Q3) or (not X and Q1 and not Q3) or
              (X and not Q1 and not Q2) after 10 ns;
      end if;
    end process;
    Z <= (not X and not Q3) or (X and Q3) after 20 ns;
  end Equations_1;
end SM1_2;

```




Structural Model

```

library BITLIB;
use BITLIB.bit_pack.all;

entity SM1_2 is
  port(CLK: in std_logic;
        Z: out std_logic);
  and SM1_2;
architecture Structure of SM1_2 is
  signal A1,A2,A3,A5,A6,D3: bit:=0;
  signal Q1,Q2,Q3: bit:=0;
  signal Q1N,Q2N,Q3N,XN: bit:=1;
  begin
    I1: Inverter port map (X,XN);
    G1: NAND1 port map (Q1,Q2,Q1,A1);
    G2: NAND1 port map (Q1,Q2N,XN,A2);
    G3: NAND1 port map (X,Q1N,Q2N,A3);
    G4: NAND1 port map (A1,A2,A3,D3);
    FF1: DFF port map (Q2N,CLK,Q1,Q1N);
    FF2: DFF port map (Q3,CLK,Q2,Q2N);
    FF3: DFF port map (D3,CLK,Q3,Q3N);
    G5: NAND1 port map (X,Q3,A5);
    G6: NAND1 port map (XN,Q3N,A6);
    G7: NAND1 port map (A5,A6,Z);
  end Structure;

```

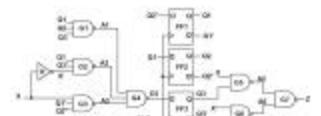

Package bit_pack is a part of library BITLIB – includes gates, flip-flops, counters (See Appendix B for details)



Simulation of the Structural Model


Simulation command file:

```

wave CLK X Q1 Q2 Q3 Z
force CLK 0 0, 1 100 -repeat 200
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
run 1600

```

Waveforms:

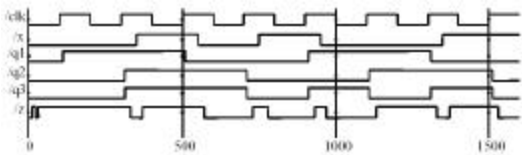

Wait Statements

- ... an alternative to a sensitivity list
 - Note: a process cannot have both wait statement(s) and a sensitivity list
- Generic form of a process with wait statement(s)

How wait statements work?

```

process
begin
  sequential-statements
  wait statement
  sequential-statements
  wait-statement
  ...
end process;

```

- Execute seq. statement until a wait statement is encountered.
- Wait until the specified condition is satisfied.
- Then execute the next set of sequential statements until the next wait statement is encountered.
- ...
- When the end of the process is reached start over again at the beginning.



Forms of Wait Statements


wait on sensitivity-list;
wait for time-expression;
wait until boolean-expression;

- ❑ Wait on
 - ⌚ until one of the signals in the sensitivity list changes
- ❑ Wait for
 - ⌚ waits until the time specified by the time expression has elapsed
 - ⌚ What is this:
wait for 0 ns;
- ❑ Wait until
 - ⌚ the boolean expression is evaluated whenever one of the signals in the expression changes, and the process continues execution when the expression evaluates to TRUE



Using Wait Statements (1)


```
library IEEE;
use IEEE.Std_logic_1164.all;
entity SM1_2 is port(X, CLK: in bit; Z: out bit); end SM1_2;
architecture Table of SM1_2 is signal State, NextState: bit;
begin
  process
  begin
    case State is
      when 0 =>
        if X='0' then Z<='1'; NextState<='1'; end if;
        if X='1' then Z<='0'; NextState<='2'; end if;
      when 1 =>
        if X='0' then Z<='1'; NextState<='3'; end if;
        if X='1' then Z<='0'; NextState<='4'; end if;
      when 2 =>
        if X='0' then Z<='0'; NextState<='4'; end if;
        if X='1' then Z<='1'; NextState<='4'; end if;
      when 3 =>
        if X='0' then Z<='0'; NextState<='5'; end if;
        if X='1' then Z<='1'; NextState<='5'; end if;
      when 4 =>
        if X='0' then Z<='1'; NextState<='5'; end if;
        if X='1' then Z<='0'; NextState<='6'; end if;
      when 5 =>
        if X='0' then Z<='0'; NextState<='6'; end if;
        if X='1' then Z<='1'; NextState<='6'; end if;
    end case;
  end process;
end SM1_2;
```

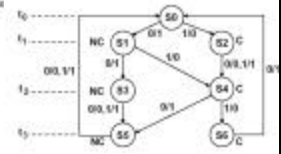

Using Wait Statements (2)

```
when 5 =>
  if X='0' then Z<='1'; NextState<='6'; end if;
  when others => null; -- should not occur
end case;

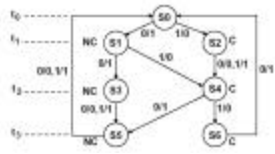wait on CLK, X;
if rising_edge(CLK) then
  State <= NextState;
  wait for 0 ns; -- wait for State to be updated
end if;
end process;
end Table;
```



Problem #1

- ❑ Using the labels, list the order in which the following signal assignments are evaluated if in2 changes from a '0' to a '1'. Assume in1 has been a '1' and in2 has been a '0' for a long time, and then at time t in2 changes from a '0' to a '1'.

```
entity not_another_prob is
  port (in1, in2: in bit;
        a: out bit);
end not_another_prob;

architecture oh_behave of not_another_prob is
  signal b, c, d, e, f: bit;
begin
  L1: d <= not(in1);
  L2: c <= not(in2);
  L3: f <= (d and in2);
  L4: e <= (c and in1);
  L5: a <= not b;
  L6: b <= e or f;
end oh_behave;
```



Problem #2

- ❑ Under what conditions do the two assignments below result in the same behavior? Different behavior? Draw waveforms to support your answers.

```
out <= reject 5 ns inertial (not a) after 20 ns;
out <= transport (not a) after 20 ns;
```



Variables

- ❑ What are they for: Local storage in processes, procedures, and functions
- ❑ Declaring variables

```
variable list_of_variable_names : type_name
[ := initial value ];
```

Variables must be declared within the process in which they are used and are local to the process
Note: exception to this is SHARED variables

Signals

- ✦ Signals must be declared outside a process
- ✦ Declaration form

```
signal list_of_signal_names : type_name
[ := initial value ];
```

- Declared in an architecture can be used anywhere within that architecture

Constants

- ✦ Declaration form

```
constant constant_name : type_name := constant_value;
constant delay1 : time := 5 ns;
```

- Constants declared at the start of an architecture can be used anywhere within that architecture
- Constants declared within a process are local to that process

Variables vs. Signals

- ✦ Variable assignment statements
 - ✦ expression is evaluated and the variable is instantaneously updated (no delay, not even delta delay)

```
variable_name := expression;
```

- Signal assignment statement

```
signal_name <= expression [after delay];
```

- expression is evaluated and the signal is scheduled to change after delay; if no delay is specified the signal is scheduled to be updated after a delta delay

Variables vs. Signals (cont'd)

Process Using Variables

```
entity dummy is
end dummy;

architecture var of dummy is
    signal trigger, sum: integer=0;
begin
    process
        variable var1: integer=1;
        variable var2: integer=2;
        variable var3: integer=3;
    begin
        wait on trigger;
        var1 := var2 + var3;
        var2 := var1;
        var3 := var2;
        sum := var1 + var2 + var3;
    end process;
end var;
```

Sum = ?

Process Using Signals

```
entity dummy is
end dummy;

architecture sig of dummy is
    signal trigger, sum: integer=0;
    signal sig1: integer=1;
    signal sig2: integer=2;
    signal sig3: integer=3;
begin
    process
        begin
            wait on trigger;
            sig1 <= sig2 + sig3;
            sig2 <= sig1;
            sig3 <= sig2;
            sum <= sig1 + sig2 + sig3;
        end process;
    end sig;
```

Sum = ?

Predefined VHDL Types

- ✦ Variables, signals, and constants can have any one of the predefined VHDL types or they can have a user-defined type
- ✦ Predefined Types
 - ✦ bit – {‘0’, ‘1’}
 - ✦ boolean – {TRUE, FALSE}
 - ✦ integer – $[-2^{31} - 1 .. 2^{31} - 1]$
 - ✦ real – floating point number in range $-1.0E38$ to $+1.0E38$
 - ✦ character – legal VHDL characters including lower- uppercase letters, digits, special characters, ...
 - ✦ time – an integer with units fs, ps, ns, us, ms, sec, min, or hr

User Defined Type

- ✦ Common user-defined type is enumerated

```
type state_type is (S0, S1, S2, S3, S4, S5);
signal state : state_type := S1;
```

- If no initialization, the default initialization is the leftmost element in the enumeration list (S0 in this example)
- VHDL is strongly typed language => signals and variables of different types cannot be mixed in the same assignment statement, and no automatic type conversion is performed

Arrays

Example

```
type SHORT_WORD is array (15 downto 0) of bit;
signal DATA_WORD : SHORT_WORD;
variable ALT_WORD : SHORT_WORD := "01010101010101";
constant ONE_WORD : SHORT_WORD := (others => '1');
```

- ALT_WORD(0) – rightmost bit
- ALT_WORD(5 downto 0) – low order 6 bits
- General form

```
type arrayTypeName is array index_range of element_type;
signal arrayName : arrayTypeName (:=InitialValues);
```

Arrays (cont'd)

Multidimensional arrays

```
type matrix4x3 is array (1 to 4, 1 to 3) of integer;
variable matrixA: matrix4x3 :=
((1,2,3), (4,5,6), (7,8,9), (10,11,12));
```

- matrixA(3, 2) = ?
 - Unconstrained array type
- ```
type intvec is array (natural range<>) of integer;
type matrix is array (natural range<>, natural range<>) of integer;
```
- range must be specified when the array object is declared

```
signal intvec5 : intvec(1 to 5) := (3,2,6,8,1);
```

### Sequential Machine Model Using State Table

```
entity SM1_2 is
port (X, CLK: in bit;
 Z: out bit);
end SM1_2;

architecture Table of SM1_2 is
type StateTable is array (integer range<>, bit range<>) of integer;
type OutTable is array (integer range<>, bit range<>) of bit;
signal State, NextState: integer := 0;
constant ST: StateTable (0 to 4, '0' to '1') :=
((1,2), (3,4), (4,4), (3,5), (5,6), (6,0), (0,0));
constant OT: OutTable (0 to 4, '0' to '1') :=
((1,'0'), (1,'0'), (0,'1'), (0,'1'), (1,'1'), (1,'0'));
begin
NextState <= ST(State,X); -- read next state from state table
Z <= OT(State,X); -- read output from output table
process(CLK)
begin
if CLK = '1' then -- rising edge of CLK
State <= NextState;
end if;
end process;
end Table;
```

| PS | NS  |     | Z   |     |
|----|-----|-----|-----|-----|
|    | X=0 | X=1 | X=0 | X=1 |
| 00 | 01  | 02  | 1   | 0   |
| 01 | 03  | 04  | 1   | 0   |
| 02 | 04  | 04  | 0   | 1   |
| 03 | 05  | 05  | 0   | 1   |
| 04 | 05  | 06  | 1   | 0   |
| 05 | 00  | 00  | 0   | 1   |
| 06 | 00  | -   | 1   | -   |

### Predefined Unconstrained Array Types

Bit\_vector, string

```
type bit_vector is array (natural range<>) of bit;
type string is array (positive range<>) of character;
constant string1: string(1 to 29) := "This string is 29 characters."
constant A : bit_vector(0 to 5) := "10101";
-- ('1', '0', '1', '0', '1');
```

- Subtypes
  - include a subset of the values specified by the type

```
subtype SHORT_WORD is : bit_vector(15 to 0);
```
- POSITIVE, NATURAL – predefined subtypes of type integer

### VHDL Operators

- Binary logical operators: and or nand nor xor xnor
- Relational: = /= < <= > >=
- Shift: sll srl sla sra rol ror
- Adding: + - & (concatenation)
- Unary sign: + -
- Multiplying: \* / mod rem
- Miscellaneous: not abs \*\*

- Class 7 has the highest precedence (applied first), followed by class 6, then class 5, etc

### Example of VHDL Operators

```
In the following expression, A, B, C, and D are bit_vectors:
(A & not B or C ror 2 and D) = "110010"

The operators would be applied in the order:
not, &, ror, or, and, =

If A = "110", B = "111", C = "01000", and D = "111011", the computation would proceed as follows:
not B = "000" (bit-by-bit complement)
A & not B = "110000" (concatenation)
C ror 2 = "000110" (rotate right 2 places)
[A & not B] or [C ror 2] = "110110" (bit-by-bit or)
[A & not B or C ror 2] and D = "110010" (bit-by-bit and)
[(A & not B or C ror 2) and D] = "110010" = TRUE
(the parentheses force the equality test to be done last and the result is TRUE)
```



### Example of Shift Operators (cont'd)

The shift operators can be applied to any bit\_vector or boolean\_vector. In the following examples, A is a bit\_vector equal to "10010101":

- A sll 2 is "01010100" (shift left logical, filled with '0')
- A srl 3 is "00010010" (shift right logical, filled with '0')
- A sla 3 is "10101111" (shift left arithmetic, filled with right bit)
- A sra 2 is "11100101" (shift right arithmetic, filled with left bit)
- A rol 3 is "10101100" (rotate left)
- A ror 5 is "10101100" (rotate right)



### VHDL Functions

Functions execute a sequential algorithm and return a single value to calling program

```
function rotate_right (reg: bit_vector)
return bit_vector is
begin
return reg ror 1;
end rotate_right;
```

- A = "10010101"
- B <- rotate\_right(A);

General form

```
function function-name (formal-parameter-list)
return return-type is
[declarations]
begin
sequential statements -- must include return return-value;
end function-name;
```



### For Loops

General form of a for loop:

```
[loop-label:] for loop-index in range loop
sequential statements
end loop [loop-label];
```

Exit statement has the form:

```
exit; -- OR
exit when condition;
```

#### For Loop Example:

-- compare two 8-character strings and return TRUE if equal

```
function comp_string(string1, string2: string(1 to 8))
return boolean is
variable B: boolean;
begin
loopex: for j in 1 to 8 loop
B := string1(j) = string2(j);
exit when B=FALSE;
end loop loopex;
return B;
end comp_string;
```



### Add Function

-- This function adds 2 4-bit vectors and a carry. -- It returns a 5-bit sum

```
function add4 (A,B: bit_vector(3 downto 0); carry: bit)
return bit_vector is
variable cout: bit;
variable cin: bit := carry;
variable Sum: bit_vector(4 downto 0):="00000";
begin
loop1: for i in 0 to 3 loop
cout := (A(i) and B(i)) or (A(i) and cin) or (B(i) and cin);
Sum(i) := A(i) xor B(i) xor cin;
cin := cout;
end loop loop1;
Sum(4) := cout;
return Sum;
end add4;
```

Example function call:

```
Sum1 <- add4(A1, B1, cin);
```



### VHDL Procedures

- Facilitate decomposition of VHDL code into modules
- Procedures can return any number of values using output parameters

```
procedure procedure_name (formal-parameter-list) is
[declarations]
begin
Sequential-statements
end procedure_name;

procedure_name (actual-parameter-list);
```



### Procedure for Adding Bit\_vectors

-- This procedure adds two n-bit bit\_vectors and a carry and -- returns an n-bit sum and a carry. Add1 and Add2 are assumed -- to be of the same length and dimensioned n-1 downto 0.

```
procedure Addvec
(Add1,Add2: in bit_vector;
Cin: in bit;
signal Sum: out bit_vector;
signal Cout: out bit;
n: in positive) is
variable C: bit;
begin
C := Cin;
for i in 0 to n-1 loop
Sum(i) <- Add1(i) xor Add2(i) xor C;
C := (Add1(i) and Add2(i)) or (Add1(i) and C) or (Add2(i) and C);
end loop;
Cout <= C;
end Addvec;
```

Example procedure call:

```
Addvec(A1, B1, Cin, Sum1, Cout, 4);
```



### Parameters for Subprogram Calls

| Mode            | Class                 | Actual Parameter |               |
|-----------------|-----------------------|------------------|---------------|
|                 |                       | Procedure Call   | Function Call |
| in <sup>1</sup> | constant <sup>2</sup> | expression       | expression    |
|                 | signal                | signal           | signal        |
|                 | variable              | n/a              | n/a           |
| out/inout       | signal                | signal           | n/a           |
|                 | variable <sup>3</sup> | variable         | n/a           |

<sup>1</sup> default mode for functions    <sup>2</sup> default for in mode    <sup>3</sup> default for out/inout mode



### Packages and Libraries

- Provide a convenient way of referencing frequently used functions and components

- Package declaration

```
package package-name is
 package declarations
end [package][(package-name)];
```

- Package body [optional]

```
package body package-name is
 package body declarations
end [package body][(package name)];
```



### Library BITLIB – bit\_pack package

```
package bit_pack is
 function add4 (reg1,reg2: bit_vector; downto 0; carry: bit)
 return bit_vector;
 function bitand_4sig(signal: clocked)
 return boolean;
 function rising_4sig(signal: clocked)
 return boolean;
 function not241sec3: bit_vector;
 return integer;
 function int2vec(int1: integer)
 return bit_vector;
 procedure add2vec:
 [A01,A032] in bit_vector;
 On: in bit;
 signal sum: out bit_vector;
 signal cout: out bit;
 s: in natural;
 component j0f
 generic: DELAY time := 10 ns;
 port: S0, S1, L0, C0: in bit; Q, Q0: in out bit;
 end component;
 component j0f
 generic: DELAY time := 10 ns;
 port: S0, S1, L0, C0: in bit; Q, Q0: out bit;
 end component;
 --
 -- [other component declarations go here]
 --
end bit_pack;
```



### Library BITLIB – bit\_pack package

```
package body bit_pack is
 -- This function adds 2 4-bit numbers, returns a 5-bit sum
 function add4 (reg1,reg2: bit_vector; downto 0; carry: bit)
 return bit_vector is
 variable cout: bit := 0;
 variable cin: bit := carry;
 variable retvec: bit_vector(4 downto 0) := "00000";
 begin
 for i in 0 to 3 loop
 cout := (reg1(i) and reg2(i) or (reg1(i) and cin) or
 (reg2(i) and cin) or cin) and not cin;
 cin := cout;
 end loop i;
 retvec(4) := cout;
 return retvec;
end add4;
-- Package for filling edge
function filling_4sig(signal: clocked)
return boolean is
begin
 return cout'event and cout = '1';
end filling_4sig;
-- other functions and procedure declarations go here
end bit_pack;
```



## CPE 626: Advanced VLSI Design VHDL Recap (Part II)

Department of Electrical and  
Computer Engineering  
University of Alabama in Huntsville



### Additional Topics in VHDL

- Attributes
- Transport and Inertial Delays
- Operator Overloading
- Multivalued Logic and Signal Resolution
- IEEE 1164 Standard Logic
- Generics
- Generate Statements
- Synthesis of VHDL Code
- Synthesis Examples
- Files and Text IO

## Signal Attributes

Attributes associated with signals that return a value

| Attribute     | Returns                                                             |
|---------------|---------------------------------------------------------------------|
| S'EVENT       | True if an event occurred during the current delta, else false      |
| S'ACTIVE      | True if a transaction occurred during the current delta, else false |
| S'LAST_EVENT  | Time elapsed since the previous event on S                          |
| S'LAST_VALUE  | Value of S before the previous event on S                           |
| S'LAST_ACTIVE | Time elapsed since previous transaction on S                        |

A'event – true if a change in S has just occurred

A'active – true if A has just been reevaluated, even if A does not change

## Review: Signal Attributes (cont'd)

Attributes that create a signal

| Attribute           | Creates                                                                     |
|---------------------|-----------------------------------------------------------------------------|
| S'DELAYED [(time)]* | signal same as S delayed by specified time                                  |
| S'STABLE [(time)]*  | Boolean signal that is true if S had no events for the specified time       |
| S'QUBET [(time)]*   | Boolean signal that is true if S had no transactions for the specified time |
| S'TRANSACTION       | signal of type BIT that changes for every transaction on S                  |

\* Delta is used if no time is specified

## Array Attributes


Type RGN is array (0 to 15, 7 downto 0) of bit;  
Signal RGN3 : RGN;

| Attribute          | Returns                          | Examples                                                              |
|--------------------|----------------------------------|-----------------------------------------------------------------------|
| A'LEFT(N)          | left bound of Nth index range    | RGN1'LEFT(1) = 0<br>RGN1'LEFT(2) = 7                                  |
| A'RIGHT(N)         | right bound of Nth index range   | RGN1'RIGHT(1) = 15<br>RGN1'RIGHT(2) = 8                               |
| A'HIGH(N)          | highest bound of Nth index range | RGN1'HIGH(1) = 8<br>RGN1'HIGH(2) = 7                                  |
| A'LOW(N)           | lowest bound of Nth index range  | RGN1'LOW(1) = 0<br>RGN1'LOW(2) = 8                                    |
| A'RANGE(N)         | Nth index range                  | RGN1'RANGE(1) = 0 to 15<br>RGN1'RANGE(2) = 7 downto 0                 |
| A'REVERSE_RANGE(N) | Nth index range, reversed        | RGN1'REVERSE_RANGE(1) = 15 downto 0<br>RGN1'REVERSE_RANGE(2) = 8 to 7 |
| A'LENGTH(N)        | size of Nth index range          | RGN1'LENGTH(1) = 16<br>RGN1'LENGTH(2) = 8                             |

A can be either an array name or an array type.

Array attributes work with signals, variables, and constants.

## Transport and Inertial Delay

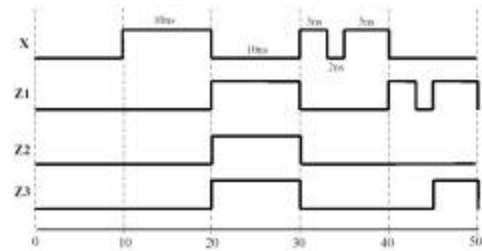

Z1 <= transport X after 10 ns; -- transport delay  
Z2 <= X after 10 ns; -- inertial delay  
Z3 <= reject 4 ns X after 10 ns; -- delay with specified rejection pulse width

## Review: Operator Overloading

- ❑ Operators +, - operate on integers
- ❑ Write procedures for bit vector addition/subtraction
  - ❑ addvec, subvec
- ❑ Operator overloading allows using + operator to implicitly call an appropriate addition function
- ❑ How does it work?
  - ❑ When compiler encounters a function declaration in which the function name is an operator enclosed in double quotes, the compiler treats the function as an operator overloading (“+”)
  - ❑ when a “+” operator is encountered, the compiler automatically checks the types of operands and calls appropriate functions

## VHDL Package with Overloaded Operators

-- This package provides two overloaded functions for the plus operator  
package bit\_overload is  
function "+" (A00: bit\_vector) return bit\_vector;  
function "+" (A00: bit\_vector; A02: integer) return bit\_vector;  
end bit\_overload;

```
library IEEE;
use IEEE.Std_Logic_1164;
package body bit_overload is
-- This function returns a bit_vector sum of two bit_vector operands.
-- The add is performed bit by bit with an internal carry.
function "+" (A00: bit_vector) return bit_vector is
variable sum: bit_vector(A00'length-1 downto 0);
variable c: bit := '0'; -- no carry in
alias n1: bit_vector(A00'length-1 downto 0) is A00;
alias n2: bit_vector(A02'length-1 downto 0) is A02;
begin
```

```
for i in sum'range loop
sum(i) := n1(i) xor n2(i) xor c;
c := (n1(i) and n2(i) or (n1(i) and c) or (n2(i) and c));
end loop; return sum;
end "+";
```

```
-- This function returns a bit_vector sum of a bit_vector and an integer.
-- using the previous function after the integer is converted.
function "+" (A01: bit_vector; A02: integer) return bit_vector is
begin
return (A01 + int2vec(A02, A01'length));
end "+";
end bit_overload;
```

Advanced VLSI Design

## Multivalued Logic

- Bit (0, 1)
- Tristate buffers and buses => high impedance state 'Z'
- Unknown state 'X'
  - e. g., a gate is driven by 'Z', output is unknown
  - a signal is simultaneously driven by '0' and '1'

© A. Milenkovic 73

Advanced VLSI Design

## Tristate Buffers

```

use WORK_Fourpack.all;
entity t_buf_comp is
port (a,b,c,d : in X01Z; -- signals are
 f : out X01Z; -- 4-valued)
and t_buf_comp;
architecture t_buf_comp of t_buf_comp is
begin
 f <= a when b = '1' else 'Z';
 f <= c when d = '1' else 'Z';
end t_buf_comp;

entity t_buf_drv of t_buf_comp is
begin
 buf1 : process (a,b)
 begin
 if (b='1') then f<=a;
 else
 f<='Z'; --"drive" the output high Z when not enabled
 end if;
 end process buf1;
 buf2 : process (c,d)
 begin
 if (d='1') then f<=c;
 else
 f<='Z'; --"drive" the output high Z when not enabled
 end if;
 end process buf2;
end t_buf_drv;

```

Resolution function to determine the actual value of f since it is driven from two different sources

© A. Milenkovic 74

Advanced VLSI Design

## Signal Resolution

- VHDL signals may either be resolved or unresolved
- Resolved signals have an associated resolution function
- Bit type is unresolved –
  - there is no resolution function
  - if you drive a bit signal to two different values in two concurrent statements, the compiler will generate an error

© A. Milenkovic 75

Advanced VLSI Design

## Signal Resolution (cont'd)

```

signal R : X01Z := 'Z'; ...
R <= transport '0' after 2 ns, 'Z' after 6 ns;

```

| Time | s(0) | s(1) | s(2) | R   |
|------|------|------|------|-----|
| 0    | 'Z'  | 'Z'  | 'Z'  | 'Z' |
| 2    | '0'  | 'Z'  | 'Z'  | '0' |
| 4    | '0'  | '1'  | 'Z'  | '0' |
| 6    | 'Z'  | '1'  | 'Z'  | '1' |
| 8    | 'Z'  | '1'  | '1'  | '1' |
| 10   | 'Z'  | '1'  | '0'  | '0' |

© A. Milenkovic 76

Advanced VLSI Design

## Resolution Function for X01Z

```

package Fourpack is
type u_x01z is ('0','1','Z'); -- u_x01z is unresolved
type u_x01z_vector is array (natural range <>) of u_x01z;
function resolve4 (a : u_x01z_vector) return u_x01z;
subtype x01z is resolved u_x01z;
-- x01z is a resolved subtype which uses the resolution function resolve4
type x01z_vector is array (natural range <>) of x01z;
end Fourpack;

package body Fourpack is
type x01z_table is array (u_x01z,u_x01z) of u_x01z;
constant resolution_table : x01z_table := (
('0','0','0'),
('0','1','0'),
('0','Z','0'),
('1','0','0'),
('1','1','1'),
('1','Z','X'),
('Z','0','X'),
('Z','1','X'),
('Z','Z','Z'));
function resolve4 (a : u_x01z_vector) return u_x01z is
variable result : u_x01z := 'Z';
begin
 if (a'length = 1) then
 return a(0);
 else
 for i in a'range loop
 result := resolution_table(result,a(i));
 end loop;
 return result;
 end resolve4;
end Fourpack;

```

Define AND and OR for 4-valued inputs?

© A. Milenkovic 77

Advanced VLSI Design

## AND and OR Functions Using X01Z

| AND | 'X' | '0' | '1' | 'Z' |
|-----|-----|-----|-----|-----|
| 'X' | 'X' | '0' | 'X' | 'X' |
| '0' | '0' | '0' | '0' | '0' |
| '1' | 'X' | '0' | '1' | 'X' |
| Z   | X   | 0   | X   | X   |

| OR  | 'X' | '0' | '1' | 'Z' |
|-----|-----|-----|-----|-----|
| 'X' | 'X' | 'X' | '1' | 'X' |
| '0' | 'X' | '0' | '1' | 'X' |
| '1' | '1' | '1' | '1' | '1' |
| Z   | X   | X   | 1   | X   |

© A. Milenkovic 78



### IEEE 1164 Standard Logic

#### 9-valued logic system

- ⊛ 'U' – Uninitialized
- ⊛ 'X' – Forcing Unknown
- ⊛ '0' – Forcing 0
- ⊛ '1' – Forcing 1
- ⊛ 'Z' – High impedance
- ⊛ 'W' – Weak unknown
- ⊛ 'L' – Weak 0
- ⊛ 'H' – Weak 1
- ⊛ '-' – Don't care

If forcing and weak signal are tied together, the forcing signal dominates.

Useful in modeling the internal operation of certain types of ICs.

In this course we use a subset of the IEEE values: X10Z



### Resolution Function for IEEE 9-valued

```
CONSTANT resolution_table : std_logic_table := (
-- | U X 0 1 Z W L H -
| 'U' 'U' 'U' 'U' 'U' 'U' 'U' 'U' 'U' -- U
| 'X' 'X' 'X' 'X' 'X' 'X' 'X' 'X' 'X' -- X
| '0' '0' '0' '0' '0' '0' '0' '0' '0' -- 0
| '1' '1' '1' '1' '1' '1' '1' '1' '1' -- 1
| 'Z' 'Z' 'Z' 'Z' 'Z' 'Z' 'Z' 'Z' 'Z' -- Z
| 'W' 'W' 'W' 'W' 'W' 'W' 'W' 'W' 'W' -- W
| 'L' 'L' 'L' 'L' 'L' 'L' 'L' 'L' 'L' -- L
| 'H' 'H' 'H' 'H' 'H' 'H' 'H' 'H' 'H' -- H
| '-' '-' '-' '-' '-' '-' '-' '-' '-' -- -
);
```



### AND Table for IEEE 9-valued

```
CONSTANT and_table : std_logic_table := (
-- | U X 0 1 Z W L H -
| 'U' 'X' '0' 'X' 'X' 'X' '0' 'X' 'X' -- X
| 'X' '0' '0' '0' '0' '0' '0' '0' '0' -- 0
| '0' '0' '0' '0' '0' '0' '0' '0' '0' -- 0
| '1' 'X' '0' '1' 'X' 'X' '0' '1' '1' -- 1
| 'X' '0' '0' 'X' 'X' 'X' '0' 'X' 'X' -- Z
| '0' 'X' '0' 'X' 'X' 'X' '0' 'X' 'X' -- W
| '1' '0' '0' '0' '0' '0' '0' '0' '0' -- L
| 'X' '0' '0' '1' 'X' 'X' '0' '1' '1' -- H
| '1' 'X' '0' 'X' 'X' 'X' '0' 'X' 'X' -- -
);
```



### AND Function for std\_logic\_vectors

```
function 'and' (l1 : std_logic; r1 : std_logic) return LOGIC is
begin
return (and_table(l1, r1));
end 'and';

function 'and' (l : std_logic_vector; r : std_logic_vector) return std_logic_vector is
alias lv : std_logic_vector (1 to l'LENGTH) is l;
alias rv : std_logic_vector (1 to r'LENGTH) is r;
variable result : std_logic_vector (1 to l'LENGTH);
begin
if (l'LENGTH /= r'LENGTH) then
assert FALSE
report "Arguments of overloaded 'and' operator are not of the same length"
severity FAILURE;
else
for i in result'RANGE loop
result(i) := and_table(lv(i), rv(i));
end loop;
return result;
end 'and';
```



### Generics

- ⊛ Used to specify parameters for a component in such a way that the parameter values must be specified when the component is instantiated
- ⊛ Example: rise/fall time modeling

```
entity NAND2 is
generic (Trise, Tfall: time; load: natural);
port (a,b : in bit; c : out bit);
end NAND2;

architecture behavior of NAND2 is
signal rand_value : bit;
begin
rand_value <= a nand b;
c <= rand_value after (Trise + 3 ns * load) when rand_value = '1'
else rand_value after (Tfall + 2 ns * load);
end behavior;
```



### Rise/Fall Time Modeling Using Generics

```
entity NAND2 is
generic (Trise, Tfall: time; load: natural);
port (a,b : in bit; c : out bit);
end NAND2;

architecture behavior of NAND2 is
signal rand_value : bit;
begin
rand_value <= a nand b;
c <= rand_value after (Trise + 3 ns * load) when rand_value = '1'
else rand_value after (Tfall + 2 ns * load);
end behavior;


entity NAND2_test is
port (in1, in2, in3, in4 : in bit;
out1, out2 : out bit);
end NAND2_test;

architecture behavior of NAND2_test is
component NAND2 is
generic (Trise: time := 3 ns; Tfall: time := 2 ns;
load: natural := 1);
port (a,b : in bit;
c : out bit);
end component;
begin
U1: NAND2 generic map (2 ns, 1 ns, 2) port map (in1, in2, out1);
U2: NAND2 port map (in3, in4, out2);
end behavior;
```


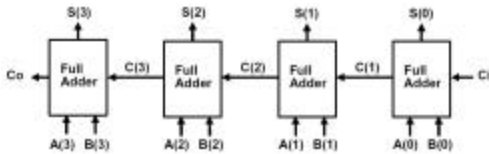
## Generate Statements

- ✦ Provides an easy way of instantiating components when we have an iterative array of identical components
- ✦ Example: 4-bit RCA



© A. Milenkovic

85



## 4-bit Adder

```
entity Adder4 is
 port {A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
 S: out bit_vector(3 downto 0); Co: out bit}; -- Outputs
end Adder4;

architecture Structure of Adder4 is
 component FullAdder
 port {X, Y, Cin: in bit; -- Inputs
 Cout, Sum: out bit}; -- Outputs
 end component;
 signal C: bit_vector(3 downto 1);
begin
 --instantiate four copies of the FullAdder
 FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
 FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
 FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
 FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
end Structure;
```

© A. Milenkovic

86



## 4-bit Adder using Generate

```
entity Adder4 is
 port {A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
 S: out bit_vector(3 downto 0); Co: out bit}; -- Outputs
end Adder4;

architecture Structure of Adder4 is
 component FullAdder
 port {X, Y, Cin: in bit; -- Inputs
 Cout, Sum: out bit}; -- Outputs
 end component;
 signal C: bit_vector(4 downto 0);
begin
 C(0) <= Ci;
 -- generate four copies of the FullAdder
 FullAdd4: for i in 0 to 3 generate
 begin
 FAx: FullAdder port map (A(i), B(i), C(i), C(i+1), S(i));
 end generate FullAdd4;
 Co <= C(4);
end Structure;
```

© A. Milenkovic

87



## Files

- ✦ File input/output in VHDL
- ✦ Used in test benches
  - Source of test data
  - Storage for test results
- ✦ VHDL provides a standard TEXTIO package
  - read/write lines of text

© A. Milenkovic

88



## Files

## File Declaration

**file** file-name: file-type [open mode] is "file-pathname";

## Example:

```
file test_data: text open read_mode is "c:\test\test.dat"
```

> declares a file named test\_data of type text which is opened in the read mode. The physical location of the file is in the test1 directory on the c: drive.

## Modes for Opening a File

**read\_mode** file elements can be read using a read procedure

**write\_mode** new empty file is created; elements can be written using a write procedure

**append\_mode** allows writing to an existing file

© A. Milenkovic

89



## Standard TEXTIO Package

- ✦ Contains declarations and procedures for working with files composed of lines of text
- ✦ Defines a file type named text:
 

```
type text is file of string;
```
- ✦ Contains procedures for reading lines of text from a file of type text and for writing lines of text to a file

© A. Milenkovic

90



### Reading TEXTIO file

- ❏ **Readline** reads a line of text and places it in a buffer with an associated pointer
- ❏ Pointer to the buffer must be of type line, which is declared in the textio package as:
  - type line is access string;
- ❏ When a variable of type line is declared, it creates a pointer to a string
- ❏ Code
 

```
variable buff: line;
...
readline (test_data, buff);
```

  - ❏ reads a line of text from test\_data and places it in a buffer which is pointed to by buff

### Extracting Data from the Line Buffer

- ❏ To extract data from the line buffer, call a read procedure one or more times
- ❏ For example, if bv4 is a bit\_vector of length four, the call
 

```
read(buff, bv4)
```

  - ❏ extracts a 4-bit vector from the buffer, sets bv4 equal to this vector, and adjusts the pointer buff to point to the next character in the buffer. Another call to read will then extract the next data object from the line buffer.

### Extracting Data from the Line Buffer (cont'd)

- ❏ TEXTIO provides overloaded read procedures to read data of types bit, bit\_vector, boolean, character, integer, real, string, and time from buffer
- ❏ Read forms
  - read(pointer, value)
  - read(pointer, value, good)
  - ❏ good is boolean that returns TRUE if the read is successful and FALSE if it is not
  - ❏ type and size of value determines which of the read procedures is called
  - ❏ character, strings, and bit\_vectors within files of type text are not delimited by quotes

### Writing to TEXTIO files

- ❏ Call one or more write procedures to write data to a line buffer and then call writeline to write the line to a file
 

```
variable buffw : line;
variable int1 : integer;
variable bv8 : bit_vector(7 downto 0);
...
write(buffw, int1, right, 6); --right just., 6 ch. wide
write(buffw, bv8, right, 10);
writeln(buffw, output_file);
```

  - ❏ Write parameters: 1) buffer pointer of type line, 2) a value of any acceptable type, 3) justification (left or right), and 4) field width (number of characters)

### An Example

- ❏ Procedure to read data from a file and store the data in a memory array
- ❏ Format of the data in the file
  - ❏ address N comments  
byte1 byte2 ... byteN comments
  - address - 4 hex digits
  - N - indicates the number of bytes of code
  - bytei - 2 hex digits
  - each byte is separated by one space
  - the last byte must be followed by a space
  - anything following the last state will not be read and will be treated as a comment

### An Example (cont'd)

- ❏ Code sequence: an example
 

```
12AC 7 (7 hex bytes follow)
AE 03 B6 91 C7 00 0C (LDX imm, LDA dir, STA ext)
005B 2 (2 bytes follow)
01 FC_
```
- ❏ TEXTIO does not include read procedure for hex numbers
  - ❏ we will read each hex value as a string of characters and then convert the string to an integer
- ❏ How to implement conversion?
  - table lookup - constant named lookup is an array of integers indexed by characters in the range '0' to 'F'
  - this range includes the 23 ASCII characters: '0', '1', ... '9', ':', ';', '<', '=', '>', '?', '@', ... 'F'
  - corresponding values: 0, 1, ... 9, -1, -1, -1, -1, -1, -1, 10, 11, 12, 13, 14, 15



## Advanced VLSI Design

### VHDL Code to Fill Memory Array

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all; -- CONV_STD_LOGIC_VECTOR(int, size)
use std.textio.all;

entity testfill is
end testfill;

architecture fillem of testfill is
 type RAMType is array (0 to 8191) of std_logic_vector(7 downto 0);
 signal mem: RAMType := (others => (others => '0'));

 procedure fill_memory(signal mem: inout RAMType) is
 type HexTable is array(character range <>) of integer;
 -- valid hex chars: 0, 1, ..., A, B, C, D, E, F [upper-case only]
 constant lookup : HexTable('0' to 'F') :=
 (0, 1, 2, 3, 4, 5, 6, 7, 8, 9, -1, -1, -1, -1,
 -1, -1, -1, -1, 10, 11, 12, 13, 14, 15);
 file infile: text open read_mode is "mem1.txt"; -- open file for reading
 -- file infile: text is in "mem1.txt"; -- VHDL 93 version
 variable buff: line;
 variable addr_s: string(8 downto 1);
 variable data_s : string(3 downto 1); -- data_s(1) has a space
 variable addr1, byte_cnt: integer; variable data: integer range 255 downto 0;

```

© A. Milenkovic 97

## Advanced VLSI Design

### VHDL Code to Fill Memory Array (cont'd)

```

begin
while (not eof(infile)) loop
 readline(infile, buff);
 read(buff, addr_s); -- read addr hexnum
 read(buff, byte_cnt); -- read number of bytes to read
 addr1 := lookup(addr_s(4))*4096 + lookup(addr_s(3))*256
 + lookup(addr_s(2))*16 + lookup(addr_s(1));
 readline(infile, buff);
 for i in 1 to byte_cnt loop
 read(buff, data_s); -- read 2 digit hex data and a space
 data := lookup(data_s(3))*16 + lookup(data_s(2));
 mem(addr1) <= CONV_STD_LOGIC_VECTOR(data, 8);
 addr1 := addr1 + 1;
 end loop;
end fill_memory;

begin
testbench: process
begin
fill_memory(mem);
-- insert code that uses memory data
end process;
end fillem;

```

© A. Milenkovic 98

## Advanced VLSI Design

### Synthesis of VHDL Code

- ❑ Synthesizer
  - ❏ take a VHDL code as an input
  - ❏ synthesize the logic: output may be a logic schematic with an associated wirelist
- ❑ Synthesizers accept a subset of VHDL as input
- ❑ Efficient implementation?
- ❑ Context
  - ...
  - A <= B and C; wait until clk'event and clk = '1';
  - A <= B and C;

Implies CM for A      Implies a register or flip-flop

© A. Milenkovic 99

## Advanced VLSI Design

### Synthesis of VHDL Code (cont'd)

- ❑ When use integers specify the range
  - ❏ if not specified, the synthesizer may infer 32-bit register
- ❑ When integer range is specified, most synthesizers will implement integer addition and subtraction using binary adders with appropriate number of bits
- ❑ General rule: when a signal is assigned a value, it will hold that value until it is assigned new value

© A. Milenkovic 100

## Advanced VLSI Design

### Unintentional Latch Creation

```

entity latch_example is
port(a: in integer range 0 to 3;
 b: out bit);
end latch_example;

architecture test1 of latch_example is
begin
process(a)
begin
case a is
when 0 => b <= '1';
when 1 => b <= '0';
when 2 => b <= '1';
when others => null;
end case;
end process;
end test1;

```

What if a = 3?  
The previous value of b should be held in the latch, so G should be 0 when a = 3.

© A. Milenkovic 101

## Advanced VLSI Design

### If Statements

```

if A = '1' then NextState <= 3;
end if;

What if A /= 1?
Retain the previous value for NextState?
Synthesizer might interpret this to mean that NextState is unknown!

if A = '1' then NextState <= 3;
else NextState <= 2;
end if;

```


© A. Milenkovic 102

### Synthesis of an If Statement

```
entity if_example is
 port(a,b: in bit;
 c,d,e: in bit; vector Z: downto 0);
 Z: out bit_vector(2 downto 0);
end if_example;


architecture test1 of if_example is
begin
 process(a,b)
 begin
 if a = '1' then Z <= c;
 elsif b = '1' then Z <= d;
 else Z <= e;
 end if;
 end process;
end test1;
```

Synthesized code before optimization

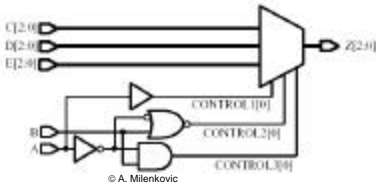

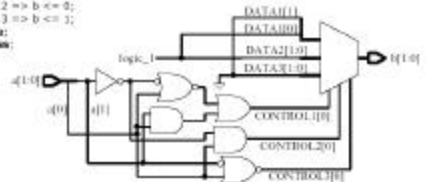
### Synthesis of a Case Statement

```
entity case_example is
 port(a: in integer range 0 to 3;
 b: out integer range 0 to 3);
end case_example;
architecture test1 of case_example is
begin
 process(a)
 begin
 case a is
 when 0 => b <= 1;
 when 1 => b <= 2;
 when 2 => b <= 0;
 when 3 => b <= 3;
 end case;
 end process;
end test1;
```


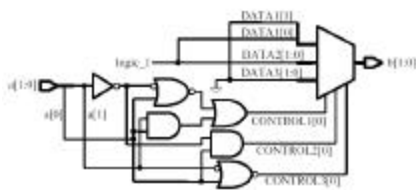
### Case Statement: Before and After Optimization



### Standard VHDL Synthesis Package

- ❑ Every VHDL synthesis tool provides its own package of functions for operations commonly used in hardware models
- ❑ IEEE is developing a standard synthesis package, which includes functions for arithmetic operations on bit\_vectors and std\_logic\_vectors
  - ❑ numeric\_bit package defines operations on bit\_vectors
    - type unsigned is array (natural range<>) of bit;
    - type signed is array (natural range<>) of bit;
  - ❑ package include overloaded versions of arithmetic, relational, logical, and shifting operations, and conversion functions
  - ❑ numeric\_std package defines similar operations on std\_logic\_vectors

### Numeric\_bit, Numeric\_std

- ❖ Overloaded operators
  - ❑ Unary: abs, -
  - ❑ Arithmetic: +, -, \*, /, rem, mod
  - ❑ Relational: >, <, >=, <=, =, /=
  - ❑ Logical: not, and, or, nand, nor, xor, xnor
  - ❑ Shifting: shift\_left, shift\_right, rotate\_left, rotate\_right, sll, srl, rol, ror

### Numeric\_bit, Numeric\_std (cont'd)

If the left and right signed operands are of different lengths, the shortest operand will be sign-extended before performing an arithmetic operation. For unsigned operands, the shortest operand will be extended by filling in 0's on the left. Examples:

```
signed: "01101" + "11011" becomes "01101" + "11011" = "01000"
unsigned: "01101" + "10111" becomes "01101" + "01011" = "11000"
```

When addition is performed on unsigned or signed operands, the final carry is discarded and overflow is ignored. If a carry is needed, an extra bit can be added to one of the operands. Examples:



### Numeric\_bit, Numeric\_std (cont'd)

```

constant A: unsigned(3 downto 0) := "1101";
constant B: signed(3 downto 0) := "1011";
variable Sums: unsigned(4 downto 0);
variable Sums: signed(4 downto 0);
variable Overflow: boolean

Sum0 := '0' & A + unsigned("0101");
-- result is "10010" (sum = 2, carry = 1)
Sums := B(3) & B + signed("1101");
-- result is "11000" (sum = -8, carry = 1)
Overflow := Sums(4) /= Sums(3) -- Overflow is false

```

In the above example, the notation unsigned["0101"] is a type qualification which assigns the type unsigned to the bit vector "0101".



### Synthesis Examples (1)

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity example1 is
port (signal clock: in bit;
 signal A, B: in signed(3 downto 0);
 signal pr: out boolean;
 signal acc: inout signed(3 downto 0) := "0000";
 signal count: inout unsigned(2 downto 0) := "000");
end example1;

architecture rtl of example1 is
begin
 pr <= (A >= B); -- 4-bit comparator
 process
 begin
 wait until clock'event and clock = '1';
 acc <= acc + B; -- 4-bit register and 4-bit adder
 count <= count + 1; -- 4-bit counter
 end process;
end;

```



### Synthesis Examples (2a)

- Mealy machine: BCD to BCD+3 Converter

```

entity SM1_2 is
port(X, CLK: in bit; Z: out bit);
end SM1_2;

architecture Table of SM1_2 is
 subtype s_type is integer range 0 to 7;
 signal State, NextState: s_type; -- state assignment
 constant S0: s_type := 0;
 constant S1: s_type := 4;
 constant S2: s_type := 3;
 constant S3: s_type := 7;
 constant S4: s_type := 6;
 constant S5: s_type := 3;
 constant S6: s_type := 2;
begin
 process(State,X) -- Combinational Network
 begin
 Z <= '0'; NextState <= S0; -- added to avoid latch
 case State is
 when S0 =>
 if X='0' then Z <='1'; NextState <= S1;
 else Z <='0'; NextState <= S2; end if;
 when S1 =>
 if X='0' then Z <='1'; NextState <= S3;
 else Z <='0'; NextState <= S4; end if;
 when S2 =>
 if X='0' then Z <='0'; NextState <= S4;
 else Z <='1'; NextState <= S4; end if;
 end case;
 end process;
end;

```



### Synthesis Examples (2b)

- Mealy machine: BCD to BCD+3 Converter

```


when S3 =>
 if X='0' then Z <='0'; NextState <= S5;
 else Z <='1'; NextState <= S5; end if;
when S4 =>
 if X='0' then Z <='1'; NextState <= S5;
 else Z <='0'; NextState <= S5; end if;
when S5 =>
 if X='0' then Z <='0'; NextState <= S0;
 else Z <='1'; NextState <= S0; end if;
when S6 =>
 if X='0' then Z <='1'; NextState <= S0; end if;
when others => null;
end case;
end process;

process(CLK) -- State Register
begin
 if CLK='1' and CLK'event then -- rising edge of clock
 State <= NextState;
 end if;
end process;
end Table;

```



### Synthesis Examples (2c)

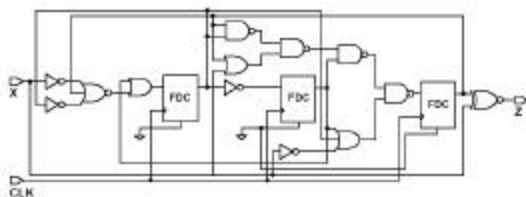

3 FF, 13 gates



### Writing Test Benches

- MUX 16 to 1
  - 16 data inputs
  - 4 selection inputs

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
port(
 A: in std_logic_vector(15 downto 0);
 SEL: in std_logic_vector(3 downto 0);
 Y: out std_logic);
end SELECTOR;

architecture RTL of SELECTOR is
begin
 Y <= A(conv_integer(SEL));
end RTL;

```



## Assert Statement

- Checks to see if a certain condition is true, and if not causes an error message to be displayed

```
assert boolean-expression
report string-expression
severity severity-level;
```

- Four possible severity levels
  - NOTE
  - WARNING
  - ERROR
  - FAILURE
- Action taken for a severity level depends on the simulator



## Writing Test Benches

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity TBSELECTOR is
end TBSELECTOR;

architecture BEH of TBSELECTOR is
component SELECTOR
port(
 A: in std_logic_vector(15 downto 0);
 SEL: in std_logic_vector(3 downto 0);
 Y: out std_logic);
end component;
signal TA : std_logic_vector(15 downto 0);
signal TSEL : std_logic_vector(3 downto 0);
signal TY, Y : std_logic;
constant PERIOD : time := 50 ns;
constant STROBE : time := 45 ns;
```



## Writing Test Benches

```
begin
P0: process
variable cnt : std_logic_vector(4 downto 0);
begin
for j in 0 to 31 loop
cnt := conv_std_logic_vector(j, 5);
TSEL <= cnt(3 downto 0);
Y <= cnt(4);
A <= (A'range => not cnt(4));
A(conv_integer(cnt(3 downto 0))) <= cnt(4);
wait for PERIOD;
end loop;
wait;
end process;
```



## Writing Test Benches

```
begin
check: process
variable err_cnt : integer := 0;
begin
wait for STROBE;
for j in 0 to 31 loop
assert FALSE report "comparing" severity NOTE;
if (Y /= TY) then
assert FALSE report "not compared" severity WARNING;
err_cnt := err_cnt + 1;
end if;
wait for PERIOD;
end loop;
assert (err_cnt = 0) report "test failed" severity ERROR;
assert (err_cnt /= 0) report "test passed" severity NOTE;
wait;
end process;
sel1: SELECTOR port map (A => TA, SEL = TSEL, Y => TY);
end BEH;
```



## Things to Remember

- Attributes associated to signals
  - allow checking for setup, hold times, and other timing specifications
- Attributes associated to arrays
  - allow us to write procedures that do not depend on the manner in which arrays are indexed
- Inertial and transport delays
  - allow modeling of different delay types that occur in real systems
- Operator overloading
  - allow us to extend the definition of VHDL operators so that they can be used with different types of operands



## Things to Remember (cont'd)

- Multivalued logic and the associated resolution functions
  - allow us to model tri-state buses, and systems where a signal is driven by more than one source
- Generics
  - allow us to specify parameter values for a component when the component is instantiated
- Generate statements
  - efficient way to describe systems with iterative structure
- TEXTIO
  - convenient way for file input/output