


CPE 626
Advanced VLSI Design
Lecture 4: VHDL Recapitulation (Part 2)

Aleksandar Milenkovic

<http://www.ece.uah.edu/~milenka>
<http://www.ece.uah.edu/~milenka/cpe626-04F/>
milenka@ece.uah.edu

Assistant Professor
 Electrical and Computer Engineering Dept.
 University of Alabama in Huntsville




Advanced VLSI Design

Outline

- ✦ Introduction to VHDL
- ✦ Modeling of Combinational Networks
- ✦ Modeling of FFs
- ✦ Delays
- ✦ Modeling of FSMs
- ✦ Wait Statements
- ✦ VHDL Data Types
- ✦ VHDL Operators
- ✦ Functions, Procedures, Packages

© A. Milenkovic 2



Advanced VLSI Design


Variables

- ✦ What are they for:
Local storage in processes, procedures, and functions
- ✦ Declaring variables


```
variable list_of_variable_names : type_name
[ := initial value ];
```

Variables must be declared within the process in which they are used and are local to the process
Note: exception to this is SHARED variables

© A. Milenkovic 3



Advanced VLSI Design

Signals

- ✦ Signals must be declared outside a process
- ✦ Declaration form


```
signal list_of_signal_names : type_name
[ := initial value ];
```
- Declared in an architecture can be used anywhere within that architecture

© A. Milenkovic 4



Advanced VLSI Design

Constants

- ✦ Declaration form


```
constant constant_name : type_name := constant_value;
constant delay1 : time := 5 ns;
```
- Constants declared at the start of an architecture can be used anywhere within that architecture
- Constants declared within a process are local to that process

© A. Milenkovic 5



Advanced VLSI Design

Variables vs. Signals

- ✦ Variable assignment statements
 - ✦ expression is evaluated and the variable is instantaneously updated (no delay, not even delta delay)
 - ```
variable_name := expression;
```
- Signal assignment statement
 

```
signal_name <= expression [after delay];
```

  - expression is evaluated and the signal is scheduled to change after delay; if no delay is specified the signal is scheduled to be updated after a delta delay

© A. Milenkovic 6

### Variables vs. Signals (cont'd)

#### Process Using Variables

```
entity dummy is
end dummy;

architecture var of dummy is
 signal trigger, sum: integer:=0;
begin
 process
 variable var1: integer:=1;
 variable var2: integer:=2;
 variable var3: integer:=3;
 begin
 wait on trigger;
 var1 := var2 + var3;
 var2 := var1;
 var3 := var2;
 sum += var1 + var2 + var3;
 end process;
end var;

Sum = ?
```

#### Process Using Signals

```
entity dummy is
end dummy;

architecture sig of dummy is
 signal trigger, sum: integer:=0;
 signal sig1: integer:=2;
 signal sig2: integer:=4;
 signal sig3: integer:=3;
begin
 process
 begin
 wait on trigger;
 sig1 <= sig2 + sig3;
 sig2 <= sig1;
 sig3 <= sig2;
 sum += sig1 + sig2 + sig3;
 end process;
end sig;

Sum = ?
```

### Predefined VHDL Types

- ❖ Variables, signals, and constants can have any one of the predefined VHDL types or they can have a user-defined type
- ❖ Predefined Types
  - ⌘ bit – {'0', '1'}
  - ⌘ boolean – {TRUE, FALSE}
  - ⌘ integer – [ $-2^{31} - 1.. 2^{31} - 1$ ]
  - ⌘ real – floating point number in range  $-1.0E38$  to  $+1.0E38$
  - ⌘ character – legal VHDL characters including lower- uppercase letters, digits, special characters, ...
  - ⌘ time – an integer with units fs, ps, ns, us, ms, sec, min, or hr

### User Defined Type

- ❖ Common user-defined type is *enumerated*

```
type state_type is (S0, S1, S2, S3, S4, S5);
signal state : state_type := S1;
```

- If no initialization, the default initialization is the leftmost element in the enumeration list (S0 in this example)
- VHDL is strongly typed language => signals and variables of different types cannot be mixed in the same assignment statement, and no automatic type conversion is performed

### Arrays

- ❖ Example

```
type SHORT_WORD is array (15 downto 0) of bit;
signal DATA_WORD : SHORT_WORD;
variable ALT_WORD : SHORT_WORD := "0101010101010101";
constant ONE_WORD : SHORT_WORD := (others => '1');
```

- ALT\_WORD(0) – rightmost bit
- ALT\_WORD(5 downto 0) – low order 6 bits
- General form

```
type arrayTypeName is array index_range of element_type;
signal arrayName : arrayTypeName [:=InitialValues];
```

### Arrays (cont'd)

- ❖ Multidimensional arrays

```
type matrix4x3 is array (1 to 4, 1 to 3) of integer;
variable matrixA: matrix4x3 :=
((1,2,3), (4,5,6), (7,8,9), (10,11,12));
```

- matrixA(3,2) = ?
  - Unconstrained array type
- ```
type intvec is array (natural range<>) of integer;
type matrix is array (natural range<>, natural range<>) of integer;
```
- range must be specified when the array object is declared

```
signal intvec5 : intvec(1 to 5) := (3,2,6,8,1);
```

Sequential Machine Model Using State Table

```
entity SM1_2 is
    port (X, CLK: in bit;
          Z: out bit);
end SM1_2;

architecture Table of SM1_2 is
    type StateTab is array (integer range <>, bit range <>) of integer;
    type OutTab is array (integer range <>, bit range <>) of bit;
    signal State, NextState: integer := 0;
    constant ST: StateTab (0 to 5, '0' to '1') :=
        ((1,1), (1,0), (1,1), (1,0), (1,0), (1,0));
    constant OT: OutTab (0 to 5, '0' to '1') :=
        ((1,'0'), (1,'0'), (1,'1'), (0,'1'), (0,'1'), (1,'0'));
begin
    NextState <= ST(State,X); -- concurrent statements
    Z <= OT(State,X); -- read next state from state table
    process(CLK) -- read output from output table
    begin
        if CLK = '1' then -- rising edge of CLK
            State <= NextState;
        end if;
    end process;
end Table;
```

PS	NS		Z	
	X=0	X=1	X=0	X=1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S5	1	0
S5	S0	S0	0	1
S6	S0	-	1	-



Predefined Unconstrained Array Types

Bit_vector, string

```

type bit_vector is array (natural range <>) of bit;
type string is array (positive range <>) of character;
constant string1: string(1 to 29) := "This string is 29 characters.";
constant A : bit_vector(0 to 5) := "10101";
-- ('1', '0', '1', '0', '1');

```

- Subtypes
 - include a subset of the values specified by the type


```
subtype SHORT_WORD is : bit_vector(15 to 0);
```
- POSITIVE, NATURAL – predefined subtypes of type integer



VHDL Operators

- Binary logical operators: and or nand nor xor xnor
- Relational: = /= < <= > >=
- Shift: sll srl sla sra rol ror
- Adding: + - & (concatenation)
- Unary sign: + -
- Multiplying: * / mod rem
- Miscellaneous: not abs **
- Class 7 has the highest precedence (applied first), followed by class 6, then class 5, etc



Example of VHDL Operators

In the following expression, A, B, C, and D are bit_vectors:

```
(A & not B or C ror 2 and D) = "110010"
```

The operators would be applied in the order:

```
not, &, ror, or, and, =
```

If A = "110", B = "111", C = "011000", and D = "111011", the computation would proceed as follows:

```

not B = "000" (bit-by-bit complement)
A & not B = "110000" (concatenation)
C ror 2 = "000110" (rotate right 2 places)
(A & not B) or (C ror 2) = "110110" (bit-by-bit or)
(A & not B or C ror 2) and D = "110010" (bit-by-bit and)
[(A & not B or C ror 2) and D] = "110010" = TRUE
(the parentheses force the equality test to be done last and the result is TRUE)

```



Example of Shift Operators (cont'd)

The shift operators can be applied to any bit_vector or boolean_vector. In the following examples, A is a bit_vector equal to "10010101":

```

A sll 2 is "01010100" (shift left logical, filled with '0')
A srl 3 is "00010010" (shift right logical, filled with '0')
A sla 3 is "10101111" (shift left arithmetic, filled with right bit)
A sra 2 is "11100101" (shift right arithmetic, filled with left bit)
A rol 3 is "10101100" (rotate left)
A ror 5 is "10101100" (rotate right)

```



VHDL Functions

- Functions execute a sequential algorithm and return a single value to calling program

```

function rotate_right (reg: bit_vector)
return bit_vector is
begin
return reg ror 1;
end rotate_right;

```

- A = "10010101"
- B <- rotate_right(A);

- General form

```

function function-name (formal-parameter-list)
return return-type is
[declarations]
begin
sequential statements; -- must include return return-value;
end function-name;

```



For Loops

General form of a for loop:

```

[loop-label:] for loop-index in range loop
sequential statements
end loop [loop-label];

```

Exit statement has the form:
exit; -- OR
exit when condition;

For Loop Example:

```

-- compare two 8-character strings and return TRUE if equal
function comp_string(string1, string2: string(1 to 8))
return boolean is
variable B: boolean;
begin
loopex: for j in 1 to 8 loop
B := string1(j) = string2(j);
exit when B=FALSE;
end loop loopex;
return B;
end comp_string;

```

Add Function

```
-- This function adds 2 4-bit vectors and a carry.
-- It returns a 5-bit sum
function add4 (A,B: bit_vector(3 downto 0); carry: bit)
return bit_vector is
variable cout: bit;
variable cin: bit := carry;
variable Sum: bit_vector(4 downto 0):="00000";
begin
loop1: for i in 0 to 3 loop
cout := (A(i) and B(i)) or (A(i) and cin) or (B(i) and cin);
Sum(i) := A(i) xor B(i) xor cin;
cin := cout;
end loop loop1;
Sum(4):= cout;
return Sum;
end add4;
```

```
Example function call:
Sum1 <= add4(A1, B1, cin);
```

VHDL Procedures

- Facilitate decomposition of VHDL code into modules
- Procedures can return any number of values using output parameters

```
procedure procedure_name (formal-parameter-list) is
[declarations]
begin
Sequential-statements
end procedure_name;

procedure_name (actual-parameter-list);
```

Procedure for Adding Bit_vectors

-- This procedure adds two n-bit bit_vectors and a carry and -- returns an n-bit sum and a carry. Add1 and Add2 are assumed -- to be of the same length and dimensioned n-1 downto 0.

```
procedure Addvec
(Add1,Add2: in bit_vector;
Cin: in bit;
signal Sum: out bit_vector;
signal Cout: out bit;
n: in positive) is
variable C: bit;
begin
C := Cin;
for i in 0 to n-1 loop
Sum(i) <= Add1(i) xor Add2(i) xor C;
C := (Add1(i) and Add2(i)) or (Add1(i) and C) or (Add2(i) and C);
end loop;
Cout <= C;
end Addvec;
```

```
Example procedure call:
Addvec(A1, B1, Cin, Sum1, Cout, 4);
```

Parameters for Subprogram Calls

Mode	Class	Actual Parameter	
		Procedure Call	Function Call
in ¹	constant ²	expression	expression
	signal	signal	signal
	variable	variable	n/a
out/inout	signal	signal	n/a
	variable ³	variable	n/a

¹ default mode for functions; ² default for in mode; ³ default for out/inout mode

Packages and Libraries

- Provide a convenient way of referencing frequently used functions and components

- Package declaration

```
package package-name is
package declarations
end [package][package-name];
```

- Package body [optional]

```
package body package-name is
package body declarations
end [package body][package name];
```

Library BITLIB – bit_pack package

```
package bit_pack is
function add4 (sig1,sig2: bit_vector(3 downto 0); carry: bit)
return bit_vector;
function bin2sig(sig: signal (clocked))
return Boolean;
function sig2bin(sig: signal (clocked))
return Boolean;
function not2sig(sig: bit_vector)
return integer;
function int2vec(int1,ABloc: integer)
return bit_vector;
procedure addvec
(sig1,sig2: in bit_vector;
Cin: in bit;
signal sum: out bit_vector;
signal cout: out bit;
n: in natural);
component bitF
generic(DelayTime: = 10 ns);
port(SN, PN, Z, CK: in bit; Q, QN: inout bit);
end component;
component bit
generic(DelayTime: = 10 ns);
port(D, CLK: in bit; Q: out bit);
end component;
component bit2
generic(DelayTime: = 10 ns);
port(A, B: in bit; Z: out bit);
end component;
component bit3
generic(DelayTime: = 10 ns);
port(A, B, C: in bit; Z: out bit);
end component;
component bit4
generic(DelayTime: = 10 ns);
port(A, B, C, D: in bit; Z: out bit);
end component;
component bit5
generic(DelayTime: = 10 ns);
port(A, B, C, D, E: in bit; Z: out bit);
end component;
component bit6
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F: in bit; Z: out bit);
end component;
component bit7
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G: in bit; Z: out bit);
end component;
component bit8
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H: in bit; Z: out bit);
end component;
component bit9
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I: in bit; Z: out bit);
end component;
component bit10
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J: in bit; Z: out bit);
end component;
component bit11
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K: in bit; Z: out bit);
end component;
component bit12
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L: in bit; Z: out bit);
end component;
component bit13
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L, M: in bit; Z: out bit);
end component;
component bit14
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L, M, N: in bit; Z: out bit);
end component;
component bit15
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L, M, N, O: in bit; Z: out bit);
end component;
component bit16
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P: in bit; Z: out bit);
end component;
component bit17
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q: in bit; Z: out bit);
end component;
component bit18
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q, R: in bit; Z: out bit);
end component;
component bit19
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q, R, S: in bit; Z: out bit);
end component;
component bit20
generic(DelayTime: = 10 ns);
port(A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q, R, S, T: in bit; Z: out bit);
end component;
end bit_pack;
```



Library BITLIB – bit_pack package

```

package library BIT_PACK_LIB
-- This function adds 2 4-bit numbers, returns a 5-bit sum
function add4 (reg1,reg2: BIT_VECTOR(3 downto 0); carry: BIT)
return BIT_VECTOR(4);
variable cout: BIT:= '0';
variable cin: BIT:= carry;
variable result: BIT_VECTOR(4 downto 0);
begin
for i in 0 to 3 loop
cout := (reg1(i) and reg2(i)) or (reg1(i) and cin) or
reg2(i) and cin;
result(i) := reg1(i) xor reg2(i) xor cin;
cin := cout;
end loop;
return result;
end add4;
-- Function for falling edge
function falling_edge(signal:clock:BIT)
return Boolean;
begin
return (clock'event and clock = '0')
and falling_edges;
-- other functions and procedure declarations optional
end BIT_PACK;

```



CPE 626: Advanced VLSI Design VHDL Recap (Part II)

Department of Electrical and
Computer Engineering
University of Alabama in Huntsville



Additional Topics in VHDL

- ✿ Attributes
- ✿ Transport and Inertial Delays
- ✿ Operator Overloading
- ✿ Multivalued Logic and Signal Resolution
- ✿ IEEE 1164 Standard Logic
- ✿ Generics
- ✿ Generate Statements
- ✿ Synthesis of VHDL Code
- ✿ Synthesis Examples
- ✿ Files and Text IO



Signal Attributes

Attributes associated with signals
that return a value

Attribute	Returns
S'EVENT	True if an event occurred during the current delta, else false
S'ACTIVE	True if a transaction occurred during the current delta, else false
S'LAST_EVENT	Time elapsed since the previous event on S
S'LAST_VALUE	Value of S before the previous event on S
S'LAST_ACTIVE	Time elapsed since previous transaction on S

A'event – true if a change in S has just occurred

A'active – true if A has just been reevaluated, even if A does not change



Review: Signal Attributes (cont'd)

Attributes that create a signal

Attribute	Creates
S'DELAYED [(time)]*	signal same as S delayed by specified time
S'STABLE [(time)]*	Boolean signal that is true if S had no events for the specified time
S'QUEUE [(time)]*	Boolean signal that is true if S had no transactions for the specified time
S'TRANSACTION	signal of type BIT that changes for every transaction on S

*.Delta is used if no time is specified



Array Attributes

Type RDN is array (0 to 15, 7 downto 0) of bit;
Signal RDN2 is RDN;


Attribute	Returns	Examples
A'LEFT(N)	left bound of Nth index range	RDN1'LEFT(1) = 0 RDN1'LEFT(2) = 7
A'RIGHT(N)	right bound of Nth index range	RDN1'RIGHT(1) = 15 RDN1'RIGHT(2) = 8
A'HIGH(N)	largest bound of Nth index range	RDN1'HIGH(1) = 15 RDN1'HIGH(2) = 7
A'LOW(N)	smallest bound of Nth index range	RDN1'LOW(1) = 0 RDN1'LOW(2) = 8
A'RANGE(N)	Nth index range	RDN1'RANGE(1) = 0 to 15 RDN1'RANGE(2) = 7 downto 0
A'REVERSE_RANGE(N)	Nth index range (reversed)	RDN1'REVERSE_RANGE(1) = 15 downto 0 RDN1'REVERSE_RANGE(2) = 0 to 7
A'LENGTH(N)	size of Nth index range	RDN1'LENGTH(1) = 16 RDN1'LENGTH(2) = 8

A can be either an array name or an array type.

Array attributes work with signals, variables, and constants.



Transport and Inertial Delay

 

Z1 <= transport X after 10 ns; -- transport delay
 Z2 <= X after 10 ns; -- inertial delay
 Z3 <= reject 4 ns X after 10 ns; -- delay with specified rejection pulse width



Review: Operator Overloading

- ❑ Operators +, - operate on integers
- ❑ Write procedures for bit vector addition/subtraction
 - ❖ addvec, subvec
- ❑ Operator overloading allows using + operator to implicitly call an appropriate addition function
- ❑ How does it work?
 - ❖ When compiler encounters a function declaration in which the function name is an operator enclosed in double quotes, the compiler treats the function as an operator overloading (“+”)
 - ❖ when a “+” operator is encountered, the compiler automatically checks the types of operands and calls appropriate functions



VHDL Package with Overloaded Operators

```

-- This package provides two overloaded functions for the plus operator
package bit_overload is
  function "+" (A00: bit_vector) return bit_vector;
  function "+" (A00: bit_vector; A01: integer) return bit_vector;
and bit_overload;

library IEEE;
use IEEE.std_logic_1164.all;

package body bit_overload is
  -- This function returns a bit_vector sum of two bit_vector operands.
  -- The add is performed bit by bit with an internal carry
  function "+" (A00: bit_vector) return bit_vector is
    variable sum: bit_vector(A00'length-1 downto 0);
    variable c: bit := '0'; -- no carry in
    alias n1: bit_vector(A00'length-1 downto 0) is A00;
    alias n2: bit_vector(A00'length-1 downto 0) is A00;
  begin
    for i in sum'range loop
      sum(i) := n1(i) xor n2(i) xor c;
      c := (n1(i) and n2(i) or (n1(i) and c) or (n2(i) and c));
    end loop; return (sum);
  end "+";


  -- This function returns a bit_vector sum of a bit_vector and an integer
  -- using the previous function after the integer is overloaded.
  function "+" (A00: bit_vector; A01: integer) return bit_vector is
  begin
    return (A00 + intvec(A01, A00'length));
  end "+";
end bit_overload;

```



Multivalued Logic

 - ❖ Bit (0, 1)
- ❖ Tristate buffers and buses => high impedance state 'Z'
- ❖ Unknown state 'X'
 - ❖ e. g., a gate is driven by 'Z', output is unknown
 - ❖ a signal is simultaneously driven by '0' and '1'




Tristate Buffers

```

use WORK.Fourpack.all;
entity t_buf_4pack is
  port (a,b,c,d : in STD_ULOGI; -- signals are
        F : out STD_ULOGI; -- 4-voltes)
  and t_buf_4pack;
architecture t_buf_4pack of t_buf_4pack is
  f <= a when b = '1' else 'Z';
  f <= c when d = '1' else 'Z';
end t_buf_4pack;

architecture t_buf_4pack of t_buf_4pack is
  begin
    process (a,b)
    begin
      if (b='1') then f<=a;
      else f<='Z'; --"drive" the output high Z when not enabled
      end if;
    end process buf1;
    process (c,d)
    begin
      if (d='1') then f<=c;
      else f<='Z'; --"drive" the output high Z when not enabled
      end if;
    end process buf2;
  end t_buf_4pack;

```

 

Resolution function to determine the actual value of f since it is driven from two different sources




Signal Resolution

- ❖ VHDL signals may either be resolved or unresolved
- ❖ Resolved signals have an associated resolution function
- ❖ Bit type is unresolved –
 - ❖ there is no resolution function
 - ❖ if you drive a bit signal to two different values in two concurrent statements, the compiler will generate an error

Signal Resolution (cont'd)
 
```
signal R : X01Z := 'Z'; ...
R <= transport '0' after 2 ns, 'Z' after 6 ns;
```



Resolution Function for X01Z

```
package Four000 is
  type u_x01z is ('X','0','1','Z');
  type u_x01z_vector is array (natural range <>) of u_x01z;
  function resolved (s : u_x01z_vector) return u_x01z;
  subtype x01z is resolved u_x01z;
  -- x01z is a resolved subtype which uses the resolution function implied
  type x01z_vector is array (natural range <>) of x01z;
end Four000;

package body Four000 is
  constant resolution_table : x01z_table := (
    ['X','0','1','Z'],
    ['X','0','1','Z'],
    ['X','0','1','Z'],
    ['X','0','1','Z']);
  function resolved (s : u_x01z_vector) return u_x01z is
  variable result : u_x01z := 'Z';
  begin
    if (s'length = 1) then
      return s(0);
    else
      for i in s'range loop
        result := resolution_table(s(i),result);
      end loop;
    end if;
    return result;
  end resolved;
end Four000;
```

Define AND and OR for 4-valued inputs?

AND and OR Functions Using X01Z

AND	'X'	'0'	'1'	'Z'
'X'	'X'	'0'	'1'	'X'
'0'	'0'	'0'	'0'	'0'
'1'	'X'	'0'	'1'	'X'
'Z'	'X'	'0'	'1'	'X'

OR	'X'	'0'	'1'	'Z'
'X'	'X'	'X'	'1'	'X'
'0'	'X'	'0'	'1'	'X'
'1'	'1'	'1'	'1'	'1'
'Z'	'X'	'X'	'1'	'X'

IEEE 1164 Standard Logic

9-valued logic system

- ⊛ 'U' – Uninitialized
- ⊛ 'X' – Forcing Unknown
- ⊛ '0' – Forcing 0
- ⊛ '1' – Forcing 1
- ⊛ 'Z' – High impedance
- ⊛ 'W' – Weak unknown
- ⊛ 'L' – Weak 0
- ⊛ 'H' – Weak 1
- ⊛ '-' – Don't care

If forcing and weak signal are tied together, the forcing signal dominates.

Useful in modeling the internal operation of certain types of ICs.

In this course we use a subset of the IEEE values: X10Z

Resolution Function for IEEE 9-valued

```
CONSTANT resolution_table : stdlogic_table := (
  -- | U X 0 1 Z W L H -
  ['U','U','U','U','U','U','U','U','U'], -- U
  ['X','X','X','X','X','X','X','X','X'], -- X
  ['0','0','0','0','0','0','0','0','0'], -- 0
  ['1','1','1','1','1','1','1','1','1'], -- 1
  ['Z','Z','Z','Z','Z','Z','Z','Z','Z'], -- Z
  ['W','W','W','W','W','W','W','W','W'], -- W
  ['L','L','L','L','L','L','L','L','L'], -- L
  ['H','H','H','H','H','H','H','H','H'], -- H
  ['-','-','-','-','-','-','-','-','-'], -- -
);
```

AND Table for IEEE 9-valued

```
CONSTANT and_table : stdlogic_table := (
  -- | U X 0 1 Z W L H -
  ['U','U','U','U','U','U','U','U','U'], -- U
  ['X','X','X','X','X','X','X','X','X'], -- X
  ['0','0','0','0','0','0','0','0','0'], -- 0
  ['1','1','1','1','1','1','1','1','1'], -- 1
  ['Z','Z','Z','Z','Z','Z','Z','Z','Z'], -- Z
  ['W','W','W','W','W','W','W','W','W'], -- W
  ['L','L','L','L','L','L','L','L','L'], -- L
  ['H','H','H','H','H','H','H','H','H'], -- H
  ['-','-','-','-','-','-','-','-','-'], -- -
);
```

AND Function for std_logic_vectors

```
function "and" ( l : std_logic; r : std_logic ) return UNDEF is
begin
    return (and_table(), 0);
end "and";

function "and" ( l : std_logic_vector; return std_logic_vector is
alias lv : std_logic_vector ( 1 to l'LENGTH ) is l;
alias rv : std_logic_vector ( 1 to r'LENGTH ) is r;
variable result : std_logic_vector ( 1 to l'LENGTH );
begin
    if ( l'LENGTH /= r'LENGTH ) then
        assert FALSE
        report "arguments of overloaded 'and' operator are not of the same length"
        severity FAILURE;
    else
        for i in result'RANGE loop
            result(i) := and_table (lv(i), rv(i));
        end loop;
    end if;
    return result;
end "and";
```

Generics

- Used to specify parameters for a component in such a way that the parameter values must be specified when the component is instantiated
- Example: rise/fall time modeling

```
entity NAND2 is
generic (Trise, Tfall: time; load: natural);
port (A,B : in bit; C: out bit);
end NAND2;

architecture behavior of NAND2 is
signal rand_value : bit;
begin
    rand_value <= a nand b;
    c <= rand_value after (Trise + 3 ns * load) when rand_value = '1'
    else rand_value after (Tfall + 2 ns * load);
end behavior;
```

Rise/Fall Time Modeling Using Generics

```
entity NAND2 is
generic (Trise, Tfall: time; load: natural);
port (a,b : in bit; c: out bit);
end NAND2;


architecture behavior of NAND2 is
signal rand_value : bit;
begin
    rand_value <= a nand b;
    c <= rand_value after (Trise + 3 ns * load) when rand_value = '1'
    else rand_value after (Tfall + 2 ns * load);
end behavior;

entity NAND2_test is
port (in1, in2, in3, in4 : in bit;
      out1, out2 : out bit);
end NAND2_test;

architecture behavior of NAND2_test is
component NAND2 is
generic (Trise: time := 3 ns; Tfall: time := 2 ns;
        load: natural := 1);
port (a,b : in bit;
      c: out bit);
end component;
begin
    U1: NAND2 generic map (2 ns, 1 ns, 2) port map (in1, in2, out1);
    U2: NAND2 port map (in3, in4, out2);
end behavior;
```

Generate Statements

 - Provides an easy way of instantiating components when we have an iterative array of identical components
- Example: 4-bit RCA



4-bit Adder

```
entity Adder4 is
port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
      S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;

architecture Structure of Adder4 is
component FullAdder
port (X, Y, Cin: in bit; -- Inputs
      Cout, Sum: out bit); -- Outputs
end component;
signal C: bit_vector(3 downto 1);
begin
    -- instantiate four copies of the FullAdder
    FAD: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
    FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
    FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
    FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
end Structure;
```

4-bit Adder using Generate

```
entity Adder4 is
port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
      S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;

architecture Structure of Adder4 is
component FullAdder
port (X, Y, Cin: in bit; -- Inputs
      Cout, Sum: out bit); -- Outputs
end component;
signal C: bit_vector(4 downto 0);
begin
    C(0) <= Ci;
    -- generate four copies of the FullAdder
    FullAdd4: for i in 0 to 3 generate
    begin
        FAi: FullAdder port map (A(i), B(i), C(i), C(i+1), S(i));
    end generate FullAdd4;
    Co <= C(4);
end Structure;
```




Files

- ❖ File input/output in VHDL
- ❖ Used in test benches
 - ⌘ Source of test data
 - ⌘ Storage for test results
- ❖ VHDL provides a standard TEXTIO package
 - ⌘ read/write lines of text



Files

File Declaration

file file-name: file-type [open mode] is "file-pathname";

Example:

```
file test_data: text open read_mode is "c:\test\test.dat"
```

> declares a file named test_data of type text which is opened in the read mode. The physical location of the file is in the test1 directory on the c: drive.

Modes for Opening a File

read_mode file elements can be read using a read procedure

write_mode new empty file is created; elements can be written using a write procedure

append_mode allows writing to an existing file



Standard TEXTIO Package

- ❖ Contains declarations and procedures for working with files composed of lines of text
- ❖ Defines a file type named text:


```
type text is file of string;
```
- ❖ Contains procedures for reading lines of text from a file of type text and for writing lines of text to a file



Reading TEXTIO file

- ❖ **Readline** reads a line of text and places it in a buffer with an associated pointer
- ❖ Pointer to the buffer must be of type line, which is declared in the textio package as:
 - type line is access string;
- ❖ When a variable of type line is declared, it creates a pointer to a string
- ❖ Code


```
variable buff: line;
...
readline (test_data, buff);
```

 - ⌘ reads a line of text from test_data and places it in a buffer which is pointed to by buff



Extracting Data from the Line Buffer

- ❖ To extract data from the line buffer, call a read procedure one or more times
- ❖ For example, if bv4 is a bit_vector of length four, the call


```
read(buff, bv4)
```

 - ⌘ extracts a 4-bit vector from the buffer, sets bv4 equal to this vector, and adjusts the pointer buff to point to the next character in the buffer. Another call to read will then extract the next data object from the line buffer.



Extracting Data from the Line Buffer (cont'd)

- ❖ TEXTIO provides overloaded read procedures to read data of types bit, bit_vector, boolean, character, integer, real, string, and time from buffer
- ❖ Read forms
 - read(pointer, value)
 - read(pointer, value, good)
 - ⌘ good is boolean that returns TRUE if the read is successful and FALSE if it is not
 - ⌘ type and size of value determines which of the read procedures is called
 - ⌘ character, strings, and bit_vectors within files of type text are not delimited by quotes



Writing to TEXTIO files

- Call one or more write procedures to write data to a line buffer and then call writeline to write the line to a file

```
variable buffw : line;
variable intl : integer;
variable bv8 : bit_vector(7 downto 0);
...
write(buffw, intl, right, 6); --right just., 6 ch. wide
write(buffw, bv8, right, 10);
writeln(buffw, output_file);
```

- Write parameters: 1) buffer pointer of type line, 2) a value of any acceptable type, 3) justification (left or right), and 4) field width (number of characters)



An Example

- Procedure to read data from a file and store the data in a memory array
- Format of the data in the file

- address N comments
 - byte1 byte2 ... byteN comments
 - address - 4 hex digits
 - N - indicates the number of bytes of code
 - bytei - 2 hex digits
 - each byte is separated by one space
 - the last byte must be followed by a space
 - anything following the last state will not be read and will be treated as a comment



An Example (cont'd)

- Code sequence: an example
 - 12AC 7 (7 hex bytes follow)
 - AE 03 B6 91 C7 00 0C (LDX imm, LDA dir, STA ext)
 - 005B 2 (2 bytes follow)
 - 01 FC_
- TEXTIO does not include read procedure for hex numbers
 - we will read each hex value as a string of characters and then convert the string to an integer
- How to implement conversion?
 - table lookup - constant named lookup is an array of integers indexed by characters in the range '0' to 'F'
 - this range includes the 23 ASCII characters: '0', '1', ... '9', '-', '.', ':', '<', '=', '>', '?', '@', 'A', ... 'F'
 - corresponding values: 0, 1, ... 9, -1, -1, -1, -1, -1, -1, -1, 10, 11, 12, 13, 14, 15



VHDL Code to Fill Memory Array

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all; -- CONV_STB_LOGIC_VECTOR(int, size)
use std.textio.all;

entity testfill is
end testfill;

architecture filmem of testfill is
type RAMType is array (0 to 8191) of std_logic_vector(7 downto 0);
signal mem : RAMType := (others => (others => '0'));

procedure fill_memory(signal mem : inout RAMType) is
type HexTable is array(character range <>) of integer;
-- valid hex chars: 0, 1, ..., A, B, C, D, E, F [upper-case only]
constant lookup : HexTable('0' to 'F') :=
(0, 1, 2, 3, 4, 5, 6, 7, 8, 9, -1, -1, -1,
-1, -1, -1, -1, 10, 11, 12, 13, 14, 15);
file infile : text open read_mode is "mem1.txt"; -- open file for reading
-- file infile: text is in "mem1.txt"; -- VHDL '97 version
variable buff : line;
variable addr_s : string(4 downto 1);
variable data_s : string(3 downto 1); -- data_s[1] has a space
variable addr1, byte_cnt : integer; variable data : integer range 255 downto 0;
```



VHDL Code to Fill Memory Array (cont'd)

```
begin
while (not endfile(infile)) loop
readline(infile, buff);
read(buff, addr_s); -- read addr hexnum
read(buff, byte_cnt); -- read number of bytes to read
addr1 := lookup(addr_s(4))*4096 + lookup(addr_s(3))*256
+ lookup(addr_s(2))*16 + lookup(addr_s(1));
readline(infile, buff);
for i in 1 to byte_cnt loop
read(buff, data_s); -- read 3 digit hex data and a space
data := lookup(data_s(3))*16 + lookup(data_s(2));
mem(addr1) <= CONV_STB_LOGIC_VECTOR(data, 8);
addr1 := addr1 + 1;
end loop;
end while;
end fill_memory;

begin
testbench: process
begin
fill_memory(mem);
-- insert code that uses memory data
end process;
end filmem;
```



Synthesis of VHDL Code

- Synthesizer
 - take a VHDL code as an input
 - synthesize the logic: output may be a logic schematic with an associated wirelist
- Synthesizers accept a subset of VHDL as input
- Efficient implementation?
- Context

```
...
A <= B and C; wait until clk'event and clk = '1';
A <= B and C;
```

Implies CM for A

Implies a register or flip-flop



Synthesis of VHDL Code (cont'd)

- When use integers specify the range
 - if not specified, the synthesizer may infer 32-bit register
- When integer range is specified, most synthesizers will implement integer addition and subtraction using binary adders with appropriate number of bits
- General rule: when a signal is assigned a value, it will hold that value until it is assigned new value




Unintentional Latch Creation

```

entity latch_example is
  port(a: in integer range 0 to 3;
        b: out bit);
end latch_example;

architecture test of latch_example is
  process(s)
  begin
    case a is
      when 0 => b <= '1';
      when 1 => b <= '0';
      when 2 => b <= '1';
      when others => null;
    end case;
  end process;
end test;

```

 

What if a = 3?

The previous value of b should be held in the latch, so G should be 0 when a = 3.



If Statements

```

if A = '1' then NextState <= 3;
end if;

```

What if A /= 1?

Retain the previous value for NextState?

Synthesizer might interpret this to mean that NextState is unknown!

```

if A = '1' then NextState <= 3;
else NextState <= 2;
end if;

```



Synthesis of an If Statement


```

entity f_example is
  port(a,b: in bit;
        C,D,E: in bit_vector(2 downto 0);
        Z: out bit_vector(2 downto 0));
end f_example;

architecture test of f_example is
  process(A,B)
  begin
    if A = '1' then Z <= C;
    elsif B = '0' then Z <= D;
    else Z <= E;
  end if;
end process;
end test;

```

Synthesized code before optimization

 


Synthesis of a Case Statement

```


entity case_example is
  port(a: in integer range 0 to 3;
        b: out integer range 0 to 3);
end case_example;

architecture test of case_example is
  process(a)
  begin
    case a is
      when 0 => b <= 1;
      when 1 => b <= 2;
      when 2 => b <= 0;
      when 3 => b <= 3;
    end case;
  end process;
end test;

```

 

 Case Statement: Before and After Optimization





Standard VHDL Synthesis Package

- ❑ Every VHDL synthesis tool provides its own package of functions for operations commonly used in hardware models
- ❑ IEEE is developing a standard synthesis package, which includes functions for arithmetic operations on bit_vectors and std_logic_vectors
 - ❑ numeric_bit package defines operations on bit_vectors
 - type unsigned is array (natural range<>) of bit;
 - type signed is array (natural range<>) of bit;
 - ❑ package include overloaded versions of arithmetic, relational, logical, and shifting operations, and conversion functions
 - ❑ numeric_std package defines similar operations on std_logic_vectors



Numeric_bit, Numeric_std

- ❖ Overloaded operators
 - ❑ Unary: abs, -
 - ❑ Arithmetic: +, -, *, /, rem, mod
 - ❑ Relational: >, <, >=, <=, =, /=
 - ❑ Logical: not, and, or, nand, nor, xor, xnor
 - ❑ Shifting: shift_left, shift_right, rotate_left, rotate_right, sll, srl, rol, ror



Numeric_bit, Numeric_std (cont'd)

If the left and right signed operands are of different lengths, the shortest operand will be sign-extended before performing an arithmetic operation. For unsigned operands, the shortest operand will be extended by filling in 0's on the left. Examples:

```

unsigned:  "01111" + "1011"  becomes "01101" + "11011" = "01000"
signed:    "01111" + "1011"  becomes "01101" + "01011" = "11000"

```

When addition is performed on unsigned or signed operands, the final carry is discarded and overflow is ignored. If a carry is needed, an extra bit can be added to one of the operands. Examples:



Numeric_bit, Numeric_std (cont'd)

```

constant A: unsigned(3 downto 0) := "1101";
constant B: signed(3 downto 0) := "1011";
variable Sums: signed(4 downto 0);
variable Overflow: boolean
-----
Sums := 0' & A + unsigned("0101");
-- result is "10010" (sum = 2, carry = 1)
Sums := B(3) & B + signed("1101");
-- result is "11000" (sum = -8, carry = 1)
Overflow := Sums(4) /= Sums(3)  -- Overflow is false

```

In the above example, the notation unsigned("0101") is a type qualification which assigns the type unsigned to the bit vector "0101".



Synthesis Examples (1)

```

library IEEE;
use IEEE std_logic_1164.all;
use IEEE std_logic_arith.all;

entity example1 is
port (signal clock: in bit;
      signal A, B: in signed(3 downto 0);
      signal go: out boolean;
      signal acc: inout signed(3 downto 0) := "0000";
      signal count: inout unsigned(2 downto 0) := "000");
end example1;

architecture ex1 of example1 is
begin
  go <= (A >= B);  -- 4-bit comparator
  process
  begin
    wait until clock'event and clock = '1';
    acc <= acc + B;  -- 4-bit register and 4-bit adder
    count <= count + 1;  -- 4-bit counter
  end process;
end;

```



Synthesis Examples (2a)

- ❖ Mealy machine: BCD to BCD+3 Converter

```

entity SM1_2 is
port(X, CLK: in bit; Z: out bit);
end SM1_2;

architecture Table of SM1_2 is
  subtype s_type is integer range 0 to 7;
  signal State, NextState: s_type;
  constant S0: s_type := 0;  -- state assignment
  constant S1: s_type := 4;
  constant S2: s_type := 5;
  constant S3: s_type := 7;
  constant S4: s_type := 6;
  constant S5: s_type := 3;
  constant S6: s_type := 2;
begin
  process(State,X)  -- Combinational Network
  begin
    Z <= '0'; NextState <= S0;  -- added to avoid latch
  case State is
  when S0 =>
    if X='0' then Z<='1'; NextState<=S1;
    else Z<='0'; NextState<=S2; end if;
  when S1 =>
    if X='0' then Z<='1'; NextState<=S3;
    else Z<='0'; NextState<=S4; end if;
  when S2 =>
    if X='0' then Z<='0'; NextState<=S4;
    else Z<='1'; NextState<=S4; end if;
  end case;
end process;

```


Synthesis Examples (2b)

- Mealy machine: BCD to BCD+3 Converter

```

when S3 =>
  if X='0' then Z<='0'; NextState<=S3;
  else Z<='1'; NextState<=S0; end if;
when S4 =>
  if X='0' then Z<='1'; NextState<=S3;
  else Z<='0'; NextState<=S5; end if;
when S5 =>
  if X='0' then Z<='0'; NextState<=S0;
  else Z<='1'; NextState<=S0; end if;
when S6 =>
  if X='0' then Z<='1'; NextState<=S0; end if;
when others => null;
end case;
end process;
process(CLK) -- Static Register
begin
  if CLK='1' and CLK'event then -- rising edge of clock
    State <= NextState;
  end if;
end process;
end Table;
    
```

Synthesis Examples (2c)

 

3 FF, 13 gates

Writing Test Benches

- MUX 16 to 1
- 16 data inputs
- 4 selection inputs

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
  port(
    A: in std_logic_vector(15 downto 0);
    SEL: in std_logic_vector(3 downto 0);
    Y: out std_logic);
end SELECTOR;

architecture RTL of SELECTOR is
begin
  Y <= A(conv_integer(SEL));
end RTL;
    
```

Assert Statement

- Checks to see if a certain condition is true, and if not causes an error message to be displayed

```

assert boolean-expression
  report string-expression
  severity severity-level;
    
```

- Four possible severity levels
 - NOTE
 - WARNING
 - ERROR
 - FAILURE
- Action taken for a severity level depends on the simulator

Writing Test Benches

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity TBSELECTOR is
end TBSELECTOR;

architecture BEH of TBSELECTOR is
  component SELECTOR
  port(
    A: in std_logic_vector(15 downto 0);
    SEL: in std_logic_vector(3 downto 0);
    Y: out std_logic);
  end component;
  signal TA : std_logic_vector(15 downto 0);
  signal TSEL : std_logic_vector(3 downto 0);
  signal TY, Y : std_logic;
  constant PERIOD : time := 50 ns;
  constant STROBE : time := 45 ns;
    
```

Writing Test Benches

```

begin
P0: process
  variable cnt : std_logic_vector(4 downto 0);
  begin
    for j in 0 to 31 loop
      cnt := conv_std_logic_vector(j, 5);
      TSEL <= cnt(3 downto 0);
      Y <= cnt(4);
      A <= (A'range => not cnt(4));
      A(conv_integer(cnt(3 downto 0))) <= cnt(4);
      wait for PERIOD;
    end loop;
  wait;
end process;
    
```



Writing Test Benches

```

begin
check: process
variable err_cnt : integer := 0;
begin
wait for STROBE;
for j in 0 to 31 loop
assert FALSE report "comparing" severity NOTE;
if (Y /= TY) then
assert FALSE report "not compared" severity WARNING;
err_cnt := err_cnt + 1;
end if;
wait for PERIOD;
end loop;
assert (err_cnt = 0) report "test failed" severity ERROR;
assert (err_cnt /= 0) report "test passed" severity NOTE;
wait;
end process;
sell: SELECTOR port map (A => TA, SEL = TSEL, Y => TY);
end BEH;

```



Things to Remember

- ❑ Attributes associated to signals
 - ⌚ allow checking for setup, hold times, and other timing specifications
- ❑ Attributes associated to arrays
 - ⌚ allow us to write procedures that do not depend on the manner in which arrays are indexed
- ❑ Inertial and transport delays
 - ⌚ allow modeling of different delay types that occur in real systems
- ❑ Operator overloading
 - ⌚ allow us to extend the definition of VHDL operators so that they can be used with different types of operands



Things to Remember (cont'd)

- ❑ Multivalued logic and the associated resolution functions
 - ⌚ allow us to model tri-state buses, and systems where a signal is driven by more than one source
- ❑ Generics
 - ⌚ allow us to specify parameter values for a component when the component is instantiated
- ❑ Generate statements
 - ⌚ efficient way to describe systems with iterative structure
- ❑ TEXTIO
 - ⌚ convenient way for file input/output