

**CPE 626**  
**Advanced VLSI Design**  
**Lecture 6: VHDL Synthesis**

Aleksandar Milenkovic

<http://www.ece.uah.edu/~milenska>  
<http://www.ece.uah.edu/~milenska/cpe626-04F/>  
[milenka@ece.uah.edu](mailto:milenka@ece.uah.edu)

Assistant Professor  
 Electrical and Computer Engineering Dept.  
 University of Alabama in Huntsville

---

---

---

---

---


---

---

---

---

---



**Advanced VLSI Design**

**Register File: An Example**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following lines to use the declarations that are
-- provided for instantiating Xilinx primitive components.
--library UNISIM;
--use UNISIM.VComponents.all;

entity regfile is
  Port ( clk : in std_logic;
        din : in std_logic_vector(15 downto 0);
        rdA : in std_logic;
        rdB : in std_logic;
        wr : in std_logic;
        rdA_A : in std_logic_vector(3 downto 0);
        rdA_B : in std_logic_vector(3 downto 0);
        wrA : in std_logic_vector(3 downto 0);
        doutA : out std_logic_vector(15 downto 0);
        doutB : out std_logic_vector(15 downto 0));
end regfile;
  
```

© A. Milenkovic 2

---

---

---

---

---

---

---

---

---

---



**Advanced VLSI Design**

**Register File: An Example (cont'd)**

```

architecture Behavioral of regfile is
  type memory_array is array(15 downto 0) of std_logic_vector(15 downto 0);
  signal rfile : memory_array := (others => (others => '0'));

begin
  process(clk)
  begin
    if (clk'event and clk='1') then
      if (wr = '1') then
        rfile(conv_integer(wrA)) <= din;
      end if;
    end if;
  end process;

  doutA <= rfile(conv_integer(rdA_A)) when rdA = '1' else (others => 'Z');
  doutB <= rfile(conv_integer(rdA_B)) when rdB = '1' else (others => 'Z');

end Behavioral;
  
```

© A. Milenkovic 3

---

---

---

---

---

---

---


---

---

---



### RTL Schematic

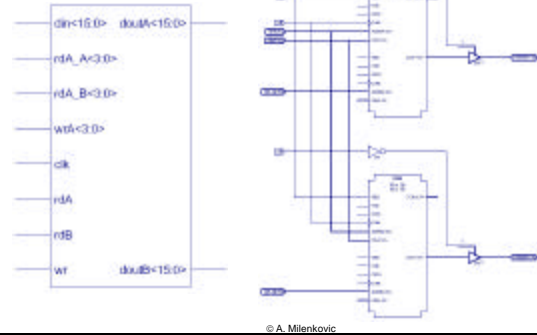


---

---

---

---

---

---

---

---

---

---



### Testbench: An Example

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY regfile_tbench_vhd_tb IS
END regfile_tbench_vhd_tb;

ARCHITECTURE behavior OF regfile_tbench_vhd_tb IS

    COMPONENT regfile
    PORT(
        clk : IN std_logic;
        din : IN std_logic_vector(15 downto 0);
        rdA : IN std_logic;
        rdB : IN std_logic;
        wr : IN std_logic;
        rdA_A : IN std_logic_vector(3 downto 0);
        rdA_B : IN std_logic_vector(3 downto 0);
        wrA : IN std_logic_vector(3 downto 0);
        doutA : OUT std_logic_vector(15 downto 0);
        doutB : OUT std_logic_vector(15 downto 0)
    );
END COMPONENT;

    SIGNAL clk : std_logic := '0';
    SIGNAL din : std_logic_vector(15 downto 0);
    SIGNAL rdA : std_logic;
    SIGNAL rdB : std_logic;
    SIGNAL wr : std_logic;
    SIGNAL rdA_A : std_logic_vector(3 downto 0);
    SIGNAL rdA_B : std_logic_vector(3 downto 0);
    SIGNAL wrA : std_logic_vector(3 downto 0);
    SIGNAL doutA : std_logic_vector(15 downto 0);
    SIGNAL doutB : std_logic_vector(15 downto 0);

```

© A. Milenkovic 5

---

---

---

---

---

---

---

---

---

---



### Testbench: An Example

```

BEGIN
    uut : regfile PORT MAP(
        clk => clk,
        din => din,
        rdA => rdA,
        rdB => rdB,
        wr => wr,
        rdA_A => rdA_A,
        rdA_B => rdA_B,
        wrA => wrA,
        doutA => doutA,
        doutB => doutB
    );

    tb : PROCESS
    BEGIN
        din <= "1111111111111111";
        wr <= '0' after 0 ns, '1' after 200 ns, '0' after 350 ns;
        wrA <= "0000" after 0 ns, "0001" after 500 ns;
        rdA <= '1';
        rdB <= '1';
        rdA_A <= "0000" after 0 ns, "0001" after 600 ns;
        rdA_B <= "0000" after 0 ns, "0001" after 600 ns;
        wait; -- will wait forever
    END PROCESS;
END;

-- *** Test Bench - User Defined Section *** -- *** End Test Bench - User Defined Section ***
clk <= not clk after 100 ns;

```

© A. Milenkovic 6

---

---

---

---

---

---

---

---

---

---





## Schematic Capture

- ✿ RTL code
- ✿ Carefully Select Design Hierarchy
- ✿ Architectural Wizards (Clocking, RocketIO)
- ✿ Core Generator

---

---

---

---

---

---

---

---



## Core Generator

- ✿ Design tool that delivers parameterized cores optimized for Xilinx FPGAs
  - ✎ E.g., adders, multipliers, filters, FIFOs, memories ...
- ✿ Core Generator outputs
  - ✎ \*.EDN file => EDIF (Electronic Data Interchange Format) netlist file; it includes information required to implement the module in a Xilinx FPGA
  - ✎ \*.VHO => VHDL template file; used as a model for instantiating a module in a VHDL design
  - ✎ \*.VHD => VHDL wrapper file; provides support for functional simulation

---

---

---

---

---

---

---

---



## Functional Simulation

- ✿ Verify the syntax and functionality
  - ✎ Separate simulation for each module => easier to debug
  - ✎ When each module behaves as expected, create a test bench for entire design

---

---

---

---

---

---

---

---



### Coding for Synthesis

---

---

---

---

---

---

---

---



### Avoid Ports Declared as Buffers

```

Entity alu is
port(
  A : in STD_LOGIC_VECTOR(3 downto 0);
  B : in STD_LOGIC_VECTOR(3 downto 0);
  CLK : in STD_LOGIC;
  C : out STD_LOGIC_VECTOR(3 downto 0)
);
end alu;
architecture BEHAVIORAL of alu is
  -- dummy signal
  signal C_INT : STD_LOGIC_VECTOR(3 downto 0);
begin
  C <= C_INT;
  process begin
    if (CLK'event and CLK='1') then
      C_INT <= UNSIGNED(A) + UNSIGNED(B) +
        UNSIGNED(C_INT);
    end if;
  end process;
end BEHAVIORAL;

Entity alu is
port(
  A : in STD_LOGIC_VECTOR(3 downto 0);
  B : in STD_LOGIC_VECTOR(3 downto 0);
  CLK : in STD_LOGIC;
  C : buffer STD_LOGIC_VECTOR(3 downto 0) );
end alu;
architecture BEHAVIORAL of alu is
begin
  process begin
    if (CLK'event and CLK='1') then
      C <= UNSIGNED(A) + UNSIGNED(B) +
        UNSIGNED(C);
    end if;
  end process;
end BEHAVIORAL;

```



---

---

---

---

---

---

---

---




### Signals vs. Variables for Synthesis

```

-- XOR_VAR.VHD
Library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity xor_var is
port (
  A, B, C: in STD_LOGIC;
  X, Y: out STD_LOGIC
);
end xor_var;
architecture VAR_ARCH of xor_var is
begin
  VAR:process (A,B,C)
  variable D: STD_LOGIC;
  begin
    D := A;
    X <= C xor D;
    D := B;
    Y <= C xor D;
  end process;
end VAR_ARCH;

```

 

---

---

---

---

---

---

---

---




### Signals vs. Variables for Synthesis

```

-- XOR_SIG.VHD
Library IEEE;
use IEEE.std_logic_1164.all;
entity xor_sig is
port (
  A, B, C: in STD_LOGIC;
  X, Y: out STD_LOGIC
);
end xor_sig;
architecture SIG_ARCH of xor_sig is
signal D: STD_LOGIC;
begin
  SIG:process (A,B,C)
  begin
    D <= A; -- ignored !!
    X <= C xor D;
    D <= B; -- overrides !!
    Y <= C xor D;
  end process;
end SIG_ARCH;

```

 


---

---

---

---

---

---

---

---



### Guidelines for synthesis

- ⚙️ VHDL/Verilog are not originally planned as languages for synthesis
  - ⚙️ Many HDL simulation constructs are not supported in synthesis
- ⚙️ Omit "wait for XX" statements
- ⚙️ Omit delay statements "... after XX;"
- ⚙️ Omit initial values
- ⚙️ Order and grouping of arithmetic statement can influence synthesis

---

---

---

---

---

---

---

---



### If Statement vs. Case Statement

- ⚙️ If statement generally produces priority-encoded logic
  - ⚙️ can contain a set of different expressions
- ⚙️ Case statement generally creates balanced logic
  - ⚙️ evaluated against a common controlling expression
- ⚙️ In general, use the Case statement for complex decoding and use the If statement for speed critical paths

---

---

---

---

---

---

---

---





### Resource Sharing: VHDL Example

```

-- RES_SHARING.VHD
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;
entity res_sharing is
port (
  A1,B1,C1,D1 : in STD_LOGIC_VECTOR (7 downto 0);
  COND_1 : in STD_LOGIC;
  Z1 : out STD_LOGIC_VECTOR (7 downto 0));
end res_sharing;
architecture BEHAV of res_sharing is
begin
  P1: process (A1,B1,C1,D1,COND_1)
  begin
    if (COND_1='1') then
      Z1 <= A1 + B1;
    else
      Z1 <= C1 + D1;
    end if;
  end process; -- end P1
end BEHAV;

```

---

---

---

---

---

---

---


---

---

---



### Implementation: W/O Resource Sharing

 


---

---

---

---

---

---

---

---

---

---