

CPE 626 Advanced VLSI Design Lecture 7: VHDL Synthesis

Aleksandar Milenkovic


<http://www.ece.uah.edu/~milenka>
<http://www.ece.uah.edu/~milenka/cpe626-04F/>
milenka@ece.uah.edu

Assistant Professor
Electrical and Computer Engineering Dept.
University of Alabama in Huntsville



Advanced VLSI Design

Design Flow Overview

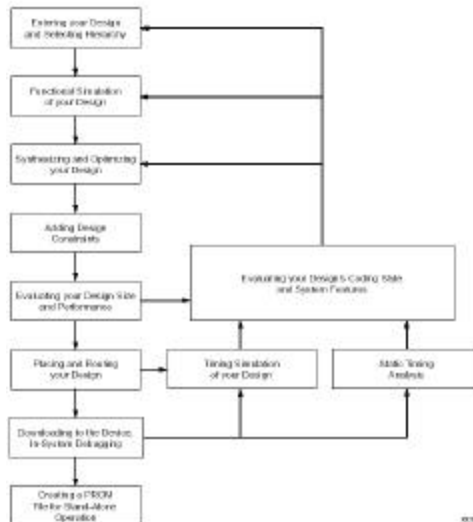



Schematic Capture

- RTL code
- Carefully Select Design Hierarchy
- Architectural Wizards (Clocking, RocketIO)
- Core Generator



Core Generator

- Design tool that delivers parameterized cores optimized for Xilinx FPGAs
 - ▣ E.g., adders, multipliers, filters, FIFOs, memories
 - ...
- Core Generator outputs
 - ▣ *.EDN file => EDIF (Electronic Data Interchange Format) netlist file; it includes information required to implement the module in a Xilinx FPGA
 - ▣ *.VHO => VHDL template file; used as a model for instantiating a module in a VHDL design
 - ▣ *.VHD => VHDL wrapper file; provides support for functional simulation



Functional Simulation

- Verify the syntax and functionality
 - ▣ Separate simulation for each module => easier to debug
 - ▣ When each module behaves as expected, create a test bench for entire design



Coding for Synthesis



Avoid Ports Declared as Buffers

```

Entity alu is
port(
  A : in STD_LOGIC_VECTOR(3 downto 0);
  B : in STD_LOGIC_VECTOR(3 downto 0);
  CLK : in STD_LOGIC;
  C : out STD_LOGIC_VECTOR(3 downto 0)
);
end alu;
architecture BEHAVIORAL of alu is
-- dummy signal
  signal C_INT : STD_LOGIC_VECTOR(3 downto 0);
begin
  C <= C_INT;
  process begin
    if (CLK'event and CLK='1') then
      C_INT <= UNSIGNED(A) + UNSIGNED(B) +
        UNSIGNED(C_INT);
    end if;
  end process;
end BEHAVIORAL;

```

```

Entity alu is
port(
  A : in STD_LOGIC_VECTOR(3 downto 0);
  B : in STD_LOGIC_VECTOR(3 downto 0);
  CLK : in STD_LOGIC;
  C : buffer STD_LOGIC_VECTOR(3 downto 0) );
end alu;
architecture BEHAVIORAL of alu is
begin
  process begin
    if (CLK'event and CLK='1') then
      C <= UNSIGNED(A) + UNSIGNED(B) +
        UNSIGNED(C);
    end if;
  end process;
end BEHAVIORAL;

```




Signals vs. Variables for Synthesis

```

-- XOR_VAR.VHD
Library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity xor_var is
port (
  A, B, C: in STD_LOGIC;
  X, Y: out STD_LOGIC
);
end xor_var;
architecture VAR_ARCH of xor_var is
begin
  VAR:process (A,B,C)
    variable D: STD_LOGIC;
  begin
    D := A;
    X <= C xor D;
    D := B;
    Y <= C xor D;
  end process;
end VAR_ARCH;


```

 



Signals vs. Variables for Synthesis
 
```
-- XOR_SIG.VHD
Library IEEE;
use IEEE.std_logic_1164.all;
entity xor_sig is
port (
  A, B, C: in STD_LOGIC;
  X, Y: out STD_LOGIC
);
end xor_sig;
architecture SIG_ARCH of xor_sig is
  signal D: STD_LOGIC;
begin
  SIG:process (A,B,C)
  begin
    D <= A; -- ignored !!
    X <= C xor D;
    D <= B; -- overrides !!
    Y <= C xor D;
  end process;
end SIG_ARCH;
```



Guidelines for synthesis

- VHDL/Verilog are not originally planned as languages for synthesis
 - ▣ Many HDL simulation constructs are not supported in synthesis
- Omit “wait for XX” statements
- Omit delay statements “ ... after XX;”
- Omit initial values
- Order and grouping of arithmetic statement can influence synthesis



If Statement vs. Case Statement

- If statement generally produces priority-encoded logic
 - ▣ can contain a set of different expressions
- Case statement generally creates balanced logic
 - ▣ evaluated against a common controlling expression
- In general, use the Case statement for complex decoding and use the If statement for speed critical paths




MUX 4-1 Synthesis

```
-- IF_EX.VHD
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity if_ex is
port (
    SEL: in STD_LOGIC_VECTOR(1 downto 0);
    A,B,C,D: in STD_LOGIC;
    MUX_OUT: out STD_LOGIC);
end if_ex;
architecture BEHAV of if_ex is
begin
    IF_PRO: process (SEL,A,B,C,D)
    begin
        if (SEL="00") then MUX_OUT <= A;
        elsif (SEL="01") then MUX_OUT <= B;
        elsif (SEL="10") then MUX_OUT <= C;
        elsif (SEL="11") then MUX_OUT <= D;
        else MUX_OUT <= '0';
        end if;
    end process; --END IF_PRO
end BEHAV;
```

```
-- CASE_EX.VHD
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity case_ex is
port (
    SEL : in STD_LOGIC_VECTOR(1 downto 0);
    A,B,C,D: in STD_LOGIC;
    MUX_OUT: out STD_LOGIC);
end case_ex;
architecture BEHAV of case_ex is
begin
    CASE_PRO: process (SEL,A,B,C,D)
    begin
        case SEL is
            when "00" => MUX_OUT <= A;
            when "01" => MUX_OUT <= B;
            when "10" => MUX_OUT <= C;
            when "11" => MUX_OUT <= D;
            when others => MUX_OUT <= '0';
        end case;
    end process; --End CASE_PRO
end BEHAV;
```



MUX 4-1 Implementation

 

Resource Sharing

- An optimization that uses a single functional block (adder, multiplier, shifter, ...) to implement several HDL operators
- Pros: less gates, simpler routing
- Cons: adds extra logic levels => increase delay (avoid sharing on the critical path)



Resource Sharing: VHDL Example


```

-- RES_SHARING.VHD
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;
entity res_sharing is
port (
  A1,B1,C1,D1 : in STD_LOGIC_VECTOR (7 downto 0);
  COND_1 : in STD_LOGIC;
  Z1 : out STD_LOGIC_VECTOR (7 downto 0));
end res_sharing;
architecture BEHAV of res_sharing is
begin
  P1: process (A1,B1,C1,D1,COND_1)
  begin
    if (COND_1='1') then
      Z1 <= A1 + B1;
    else
      Z1 <= C1 + D1;
    end if;
  end process; -- end P1
end BEHAV;


```



Implementation: W/WO Resource Sharing

 

Enabled

 

Disabled



Registers: Asynchronous Preset/Set

```

-- FF_EXAMPLE.VHD
-- Example of Implementing Registers
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity ff_example is
port ( RESET, SET, CLOCK, ENABLE: in STD_LOGIC;
      D_IN: in STD_LOGIC_VECTOR (7 downto 0);
      A_Q_OUT: out STD_LOGIC_VECTOR (7 downto 0);
      B_Q_OUT: out STD_LOGIC_VECTOR (7 downto 0);
      C_Q_OUT: out STD_LOGIC_VECTOR (7 downto 0);
      D_Q_OUT: out STD_LOGIC_VECTOR (7 downto 0);
      E_Q_OUT: out STD_LOGIC_VECTOR (7 downto 0));
end ff_example;
architecture BEHAV of ff_example is
begin
  -- D flip-flop
  FF: process (CLOCK)
  begin
    if (CLOCK'event and CLOCK='1') then
      A_Q_OUT <= D_IN;
    end if;
  end process; -- End FF

  -- Flip-flop with asynchronous reset
  FF_ASYNC_RESET: process (RESET, CLOCK)
  begin
    if (RESET = '1') then
      B_Q_OUT <= "00000000";
    elsif (CLOCK'event and CLOCK='1') then
      B_Q_OUT <= D_IN;
    end if;
  end process;

  -- Flip-flop with asynchronous set
  FF_ASYNC_SET: process (SET, CLOCK)
  begin
    if (SET = '1') then
      C_Q_OUT <= "11111111";
    elsif (CLOCK'event and CLOCK = '1') then
      C_Q_OUT <= D_IN;
    end if;
  end process; -- End FF_ASYNC_SET
end architecture BEHAV;

```



Registers: Asynchronous Preset/Set

```

-- Flip-flop with asynchronous reset
-- and clock enable
FF_CLOCK_ENABLE: process (ENABLE, RESET,
                          CLOCK)
begin
  if (RESET = '1') then
    D_Q_OUT <= "00000000";
  elsif (CLOCK'event and CLOCK='1') then
    if (ENABLE = '1') then
      D_Q_OUT <= D_IN;
    end if;
  end process; -- End FF_CLOCK_ENABLE

  -- Flip-flop with asynchronous reset
  -- asynchronous set and clock enable
  FF_ASR_CLOCK_ENABLE: process (ENABLE,
                                RESET, SET, CLOCK)
  begin
    if (RESET = '1') then
      E_Q_OUT <= "00000000";
    elsif (SET = '1') then
      E_Q_OUT <= "11111111";
    elsif (CLOCK'event and CLOCK='1') then
      if (ENABLE = '1') then
        E_Q_OUT <= D_IN;
      end if;
    end if;
  end process; -- End FF_ASR_CLOCK_ENABLE
end BEHAV;

```



Use Clock_Enable instead gated Clock


```

-- Better implementation is to use --
-- clock enable rather than gated clock --
-----
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity gate_clock is
  port (IN1,IN2,DATA,CLK,LOAD: in
        STD_LOGIC;
        OUT1: out STD_LOGIC);
end gate_clock;
architecture BEHAVIORAL of gate_clock is
  signal GATECLK: STD_LOGIC;
begin
  GATECLK <= (IN1 and IN2 and CLK);
  GATE_PR: process (GATECLK,DATA,LOAD)
  begin
    if (GATECLK'event and GATECLK='1')
      if (LOAD = '1') then
        OUT1 <= DATA;
      end if;
    end if;
  end process; -- End GATE_PR
end BEHAVIORAL;

```

⚙️ This implementation introduces

 - ❑ Glitches
- ❑ Clock delays
- ❑ Clock skew





Use Clock Enable Instead Gated Clocks

```


-- CLOCK_ENABLE.VHD
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity clock_enable is
  port (IN1,IN2,DATA,CLOCK,LOAD: in STD_LOGIC;
        DOUT: out STD_LOGIC);
end clock_enable;
architecture BEHAV of clock_enable is
  signal ENABLE: STD_LOGIC;
begin
  ENABLE <= IN1 and IN2 and LOAD;
  EN_PR: process (ENABLE,DATA,CLOCK)
  begin
    if (CLOCK'event and CLOCK='1') then
      if (ENABLE = '1') then
        DOUT <= DATA;
      end if;
    end if;
  end process; -- End EN_PR
end BEHAV;

```

 

 

 HDL Coding Techniques for Common Building Blocks



Advanced VLSI Design

Multiplication in FPGAs

 <http://www.andraka.com/multipli.htm>



Multiplier

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity mult is
  port(
    A : in std_logic_vector(17 downto 0);
    B : in std_logic_vector(17 downto 0);
    RES : out std_logic_vector(35 downto 0)
  );
end mult;

architecture archi of mult is
begin
  RES <= A * B;
end archi;
```

- Device utilization summary:

Selected Device : 3s50tq144-5

Number of Slices:	19 out of 768	2%
Number of 4 input LUTs:	36 out of 1536	2%
Number of bonded IOBs:	72 out of 97	74%
Number of MULT18X18s:	3 out of 4	75%

- Delay = 14.975ns (Levels of Logic = 25)



Inferring Pipelined Multiplier

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity multpipe is
  generic(
    A_port_size : integer := 18;
    B_port_size : integer := 18
  );
  port(
    clk : in std_logic;
    A : in unsigned (A_port_size-1 downto 0);
    B : in unsigned (B_port_size-1 downto 0);
    MULT : out unsigned ( (A_port_size+B_port_size-1) downto 0));
end multpipe;
```



Inferring Pipelined Multiplier (cont'd)

```

architecture Behavioral of multpipe is
    signal a_in, b_in : unsigned (A_port_size-1 downto 0);
    signal mult_res : unsigned ( (A_port_size+B_port_size-1) downto 0);
    signal pipe_1,
           pipe_2,
           pipe_3 : unsigned ((A_port_size+B_port_size-1) downto 0);
begin
    mult_res <= a_in * b_in;


    process (clk)
    begin
        if (clk'event and clk='1') then
            a_in <= A; b_in <= B;
            pipe_1 <= mult_res;
            pipe_2 <= pipe_1;
            pipe_3 <= pipe_2;
            MULT <= pipe_3;
        end if;
    end process;
end Behavioral;

```

=> Four pipeline stages



Pipelined Multiplier: RTL Schematic

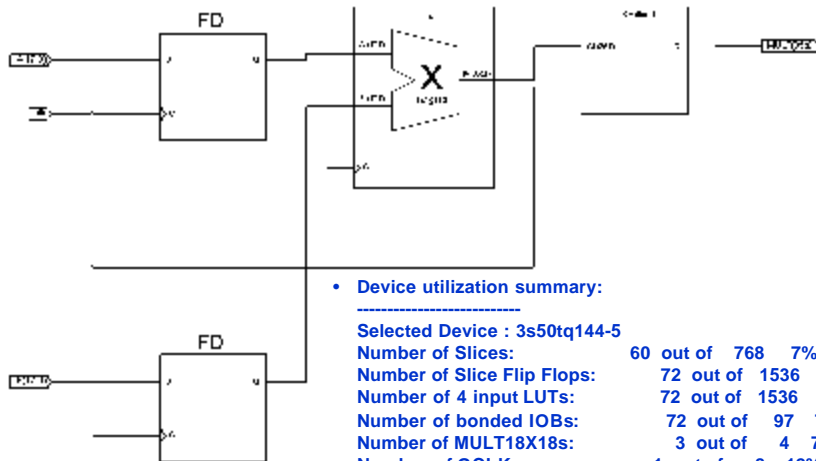

• Device utilization summary:

Selected Device : 3s50tq144-5

Number of Slices:	60 out of 768	7%
Number of Slice Flip Flops:	72 out of 1536	4%
Number of 4 input LUTs:	72 out of 1536	4%
Number of bonded IOBs:	72 out of 97	74%
Number of MULT18X18s:	3 out of 4	75%
Number of GCLKs:	1 out of 8	12%

• Delay: 9.824ns (Levels of Logic = 23)



Inferring PM: Alternative Description #1

```
architecture beh of mult is
    signal a_in, b_in : unsigned (A_port_size-1 downto 0);
    signal mult_res : unsigned ((A_port_size+B_port_size-1) downto 0);
    signal pipe_2,
           pipe_3 : unsigned ((A_port_size+B_port_size-1) downto 0);
begin
    process (clk)
    begin
        if (clk'event and clk='1') then
            a_in <= A; b_in <= B;
            mult_res <= a_in * b_in;
            pipe_2 <= mult_res;
            pipe_3 <= pipe_2;
            MULT <= pipe_3;
        end if;
    end process;
end beh;
```



Inferring PM: Alternative Description #2

```
architecture beh of mult is
    signal a_in, b_in : unsigned (A_port_size-1 downto 0);
    signal mult_res : unsigned ((A_port_size+B_port_size-1) downto 0);
    type pipe_reg_type is array (2 downto 0) of unsigned
        ((A_port_size+B_port_size-1) downto 0);
    signal pipe_regs : pipe_reg_type;
begin
    mult_res <= a_in * b_in;
    process (clk)
    begin
        if (clk'event and clk='1') then
            a_in <= A; b_in <= B;
            pipe_regs <= mult_res & pipe_regs(2 downto 1);
            MULT <= pipe_regs(0);
        end if;
    end process;
end beh;
```



RAMs/ROMs


- XST offers an automatic RAM recognition
 - ▣ Keep you HDL code technology independent
- XST can infer distributed or Block RAM
- Parameters
 - ▣ Synchronous write, Write enable, RAM enable, Asynchronous or synchronous read, Reset of the data output latches, Data output reset, Single, dual or multiple-port read, Single-port write



Dual-port Block RAM

- Only XST supports RAM inference
- Infers Dual Port Block Ram
 
```
entity dpblockram is
port (clk : in std_logic;
      we  : in std_logic;
      a   : in std_logic_vector(4 downto 0);
      dpra : in std_logic_vector(4 downto 0);
      di  : in std_logic_vector(3 downto 0);
      spo : out std_logic_vector(3 downto 0);
      dpo : out std_logic_vector(3 downto 0));
end dpblockram;
```





Dual-port Block RAM


```
architecture syn of dpblockram is
  type ram_type is array (31 downto 0) of std_logic_vector (3 downto 0);
  signal RAM : ram_type;
  signal read_a : std_logic_vector(4 downto 0);
  signal read_dpra : std_logic_vector(4 downto 0);
begin
  process (clk)
  begin
    if (clk'event and clk = '1') then
      if (we = '1') then
        RAM(conv_integer(a)) <= di;
      end if;
      read_a <= a;
      read_dpra <= dpra;
    end if;
  end process;

  spo <= RAM(conv_integer(read_a));
  dpo <= RAM(conv_integer(read_dpra));
end syn;
```



Dual-port Distributed RAM
 
```
entity dpdistram is
port (clk : in std_logic;
      we : in std_logic;
      a : in std_logic_vector(4 downto 0);
      dpra : in std_logic_vector(4 downto 0);
      di : in std_logic_vector(3 downto 0);
      spo : out std_logic_vector(3 downto 0);
      dpo : out std_logic_vector(3 downto 0));
end dpdistram;
```





Dual-port Distributed RAM

```
architecture syn of dpdistram is
type ram_type is array (31 downto 0) of std_logic_vector (3 downto 0);
signal RAM : ram_type;

begin
process (clk)
begin
if (clk'event and clk = '1') then
if (we = '1') then
RAM(conv_integer(a)) <= di;
end if;
end if;
end process;
spo <= RAM(conv_integer(a));
dpo <= RAM(conv_integer(dpra));
end syn;
```



Dual-port RAM with Enable on Each Port

Write VHDL description.

