



CPE 626 The SystemC Language

Aleksandar Milenkovic

E-mail: milenka@ece.uah.edu

Web: <http://www.ece.uah.edu/~milenka>

Outline

- Introduction
- Data Types
- Modeling Combinational Logic
- Modeling Synchronous Logic
- Misc

Introduction

- What is SystemC?
- Why SystemC?
- Design Methodology
- Capabilities
- SystemC RTL

What is SystemC

An extension of C++
enabling modeling of hardware descriptions

- SystemC adds a class library to C++
- Mechanisms to model system architecture
 - Concurrency – multiple processes executed concurrently
 - Timed events
 - Reactive behavior
- Constructs to describe hardware
 - Signals
 - Modules
 - Ports
 - Processes
- Simulation kernel

©A. Milenkovic

4

What is SystemC


- Provides methodology for describing
 - System level design
 - Software algorithms
 - Hardware architecture
- Design Flow
 - Create a system level model
 - Explore various algorithms
 - Simulate to validate model and optimize design
 - Create executable specifications
 - Hardware team and software team use the same specification

Test input files

©A. Milenkovic

5

C++/SystemC Development Environment

 


©A. Milenkovic

6

Why SystemC?

 - Designs become
 - Bigger in size
 - Faster in speed
 - Larger in complexity
- Design description on higher levels of abstraction enables
 - Faster simulation
 - Hardware/software co-simulation
 - Architectural Exploration



©A. Milenkovic

7

Why SystemC?


SystemC describes overall system

- System level design
- Describing hardware architectures
- Describing software algorithms
- Verification
- IP exchange

©A. Milenkovic

8


Non-SystemC Design Methodology

 

©A. Milenkovic

9


SystemC Design Methodology

 

©A. Milenkovic

10

System Level Design Process

 

©A. Milenkovic

11

SystemC Capabilities

- Modules
 - SC_MODULE class
- Processes
 - SC_METHOD, SC_THREAD
- Ports: input, output, inout
- Signals
 - resolved, unresolved
 - updates after a delta delay
- Rich set of data types
 - 2-value, 4-value logic
 - fixed, arbitrary size
- Clocks
 - built-in notion of clocks
- Event-base simulation
- Multiple abstraction levels
- Communication protocols
- Debugging support
- Waveform tracing
 - VCD: Value Change Dump (IEEE Std. 1364)
 - WIF: Waveform Interch. F.
 - ISDB: Integrated Signal Data Base
- RTL synthesis flow
- System and RTL modeling
- Software and Hardware

©A. Milenkovic

12

SystemC Half Adder

```
// File half_adder.h
#include "systemc.h"

SC_MODULE(half_adder) {
    sc_in<bool> a, b;
    sc_out<bool> sum, carry;

    void prc_half_adder();
}

SC_CTOR(half_adder) {
    SC_METHOD(prc_half_adder);
    sensitive << a << b;
}
};

// File half_adder.cpp
#include "half_adder.h"

void half_adder::prc_half_adder() {
    sum = a ^ b;
    carry = a & b;
}
```

©A. Milenkovic

13

SystemC Decoder 2/4

```
// File decoder2by4.h
#include "systemc.h"

SC_MODULE(decoder2by4) {
    sc_in<bool> enable;
    sc_in<sc_uint<2>> select;
    sc_out<sc_uint<4>> z;

    void prc_decoder2by4();
}

SC_CTOR(decoder2by4) {
    SC_METHOD(prc_decoder2by4);
    sensitive(enable, select);
}
};

// File decoder2by4.cpp
#include "decoder2by4.h"

void decoder2by4::prc_decoder2by4()
{
    if (enable) {
        switch(select.read()) {
            case 0: z=0x0; break;
            case 1: z=0x0B; break;
            case 2: z=0x0B; break;
            case 3: z=0x7; break;
        }
    } else
        z=0xF;
}
```

Note: Stream vs. Function notation

```
sensitive << a << b; // Stream notation style
sensitive(a, b); // Function notation style
```

©A. Milenkovic

14

Hierarchy: Building a full adder

```
// File full_adder.h
#include "systemc.h"

SC_MODULE(full_adder) {
    sc_in<bool> a,b,carry_in;
    sc_out<bool> sum,carry_out;
    sc_signal<bool> c1, s1, c2;
    void prc_or();
    half_adder *hal_ptr, *ha2_ptr;

    SC_CTOR(full_adder) {
        hal_ptr = new half_adder("hal");
        hal_ptr->a(a); hal_ptr->b(b);
        hal_ptr->sum(s1);
        hal_ptr->>carry(c1);
        ha2_ptr = new half_adder("ha2");
        (*ha2_ptr)(s1, carry_in,sum,c2);
        SC_METHOD(prc_or);
        sensitive << c1 << c2;
    }
};

// a destructor
~full_adder() {
    delete hal_ptr;
    delete ha2_ptr;
}

// File: full_adder.cpp
#include "full_adder.h"

void full_adder::prc_or(){
    carry_out = c1 | c2;
}
```

©A. Milenkovic

15

Verifying the Functionality: Driver

```
// File driver.h
#include "systemc.h"

SC_MODULE(driver) {
    sc_out<bool> d_a,d_b,d_cin;

    void prc_driver();

    SC_CTOR(driver) {
        SC_THREAD(prc_driver);
    }
};

// File: driver.cpp
#include "driver.h"

void driver::prc_driver(){
    sc_uint<3> pattern;
    pattern=0;

    while(1) {
        d_a=pattern[0];
        d_b=pattern[1];
        d_cin=pattern[2];
        wait(5, SC_NS);
        pattern++;
    }
}
```

©A. Milenkovic

16

Verifying the Functionality: Monitor

```
// File monitor.h
#include "systemc.h"

SC_MODULE(monitor) {
    sc_in<bool> m_a,m_b,m_cin,
                m_sum, m_cout;

    void prc_monitor();

    SC_CTOR(monitor) {
        SC_THREAD(prc_monitor);
        sensitive << m_a<<m_b<<m_cin,
                m_sum, m_cout;
    }
};

// File: monitor.cpp
#include "monitor.h"

void monitor::prc_monitor(){
    cout << "At time " <<
        sc_time_stamp() << ":";
    cout << "(a,b,carry_in): ";
    cout << m_a << m_b << m_cin;
    cout << "(sum,carry_out): ";
    cout << m_sum << m_cout << endl;
}
```

©A. Milenkovic

17

Verifying the Functionality: Main

```
// File full_adder_main.cpp
#include "driver.h"
#include "monitor.h"
#include "full_adder.h"

int sc_main(int argc, char * argv[]) {
    sc_signal<bool> t_a, t_b, t_cin, t_sum, t_cout;

    full_adder f1("FullAdderWithHalfAdders");
    f1 << t_a << t_b << t_cin << t_sum << t_cout;

    driver d1("GenWaveforms");
    d1.d_a(t_a);
    d1.d_b(t_b);
    d1.d_cin(t_cin);

    monitor m1("MonitorWaveforms");
    m1 << t_a << t_b << t_cin << t_sum << t_cout;

    sc_start(100, SC_NS);
    return(0);
}
```

©A. Milenkovic

18

Modeling Combinational Logic

```
// File: bist_cell.h
#include "systemc.h"
SC_MODULE(bist_cell) {
    sc_in<bool> b0,b1,d0,d1;
    sc_out<bool> z;
    void prc_bist_cell();
    SC_CTOR(bist_cell) {
        SC_METHOD(prc_bist_cell);
        sensitive <>b0<>b1<>d0<>d1;
    }
}

// File: bist_cell.cpp
#include "bist_cell.h"

void bist_cell::prc_bist_cell(){
    z = !(!(d0&b1)&!(b0&d1))|!
        (!(d0&b1)|!(b0&d1));
}
```

➤ Use SC_METHOD process with an event sensitivity list

©A. Milenkovic

19

Modeling Combinational Logic: Local Variables

```
// File: bist_cell.cpp
#include "bist_cell.h"

void bist_cell::prc_bist_cell(){
    z = !(!(d0&b1)&!(b0&d1))|!
        !(d0&b1)&!(b0&d1));
}

➤ Local variables in the process (s1, s2, s3)
do not synthesize to wires
➤ Hold temporary values (improve readability)
➤ Are assigned values instantaneously
(no delta delay) –
one variable can represent many wires (s2)
    • signals and ports are updated
        after a delta delay
➤ Simulation is likely faster with local variables
```

```
// File: bist_cell.cpp
#include "bist_cell.h"

void bist_cell::prc_bist_cell(){
    bool s1, s2, s3;
    s1 = !(b0&d1);
    s2 = !(d0&b1);
    s3 = !(s2|s1);
    s2 = s2&s1;
    z = !(s2|s3);
}
```

©A. Milenkovic

20

Modeling Combinational Logic: Reading and Writing Ports and Signals

```
// File: xor_gates.h
#include "systemc.h"
SC_MODULE(xor_gates) {
    sc_in<sc_uint<4>> bre, sty;
    sc_out<sc_uint<4>> tap;
    void prc_xor_gates();
    SC_CTOR(xor_gates) {
        SC_METHOD(prc_xor_gates);
        sensitive <> bre <> sty;
    }
}

// File: xor_gates.cpp
#include "xor_gates.h"

void bist_cell::prc_xor_gates(){
    tap = bre ^ sty;
}
```

➤ Use read() and write() methods for reading and writing values from and to a port or signal

```
// File: xor_gates.cpp
#include "xor_gates.h"

void bist_cell::prc_xor_gates(){
    tap = bre.read() ^ sty.read();
}
```

©A. Milenkovic

21

Modeling Combinational Logic: Logical Operators

```
// File: xor_gates.h
#include "systemc.h"
const int SIZE=4;

SC_MODULE(xor_gates) {
    sc_in<sc_uint<SIZE> > bre, sty;
    sc_out <sc_uint<SIZE> > tap;
    void prc_xor_gates();
    SC_CTOR(xor_gates) {
        SC_METHOD(prc_xor_gates);
        sensitive << bre << sty;
    }
}

// File: xor_gates.cpp
#include "xor_gates.h"

void bist_cell:::prc_xor_gates(){
    tap = bre.read() ^ sty.read();
}
```

- ^ - xor
- & - and
- | - or

©A. Milenkovic

22

Modeling Combinational Logic: Arithmetic Operations

```
sc_uint<4> write_addr;
sc_int<5> read_addr;

read_addr = write_addr + read_addr;
```

- Note: all fixed precision integer type calculations occur on a 64-bit representation and appropriate truncation occurs depending on the target result size
- E.g.:
 - write_addr is zero-extended to 64-bit
 - read_addr is sign-extended to 64-bit
 - + is performed on 64-bit data
 - result is truncated to 5-bit result and assigned back to read_addr

©A. Milenkovic

23

Modeling Combinational Logic: Unsigned Arithmetic

```
// File: u_adder.h
#include "systemc.h"

SC_MODULE(u_adder) {
    sc_in<sc_uint<4> > a, b;
    sc_out <sc_uint<5> > sum;
    void prc_u_adder();
    SC_CTOR(u_adder) {
        SC_METHOD(prc_u_adder);
        sensitive << a << b;
    }
};

// File: u_adder.cpp
#include "u_adder.h"

void u_adder :::prc_u_adder(){
    sum = a.read() + b.read();
}
```

©A. Milenkovic

24

Modeling Combinational Logic: Signed Arithmetic

```
// File: s_adder.h
#include "systemc.h"

SC_MODULE(s_adder) {
    sc_in<sc_int<4>> a, b;
    sc_out <sc_int<5>> sum;

    void prc_s_adder();
}

SC_CTOR(s_adder) {
    SC_METHOD(prc_s_adder);
    sensitive << a << b;
}
}

// File: s_adder.cpp
#include "s_adder.h"

void s_adder ::prc_s_adder(){
    sum = a.read() + b.read();
}
```

©A. Milenkovic

25

Modeling Combinational Logic: Signed Arithmetic (2)

```
// File: s_adder_c.h
#include "systemc.h"

SC_MODULE(s_adder_c) {
    sc_in<sc_int<4>> a, b;
    sc_out <sc_int<4>> sum;
    sc_out <bool> carry_out;

    void prc_s_adder_c();
}

SC_CTOR(s_adder_c) {
    SC_METHOD(prc_s_adder_c);
    sensitive << a << b;
}
}

// File: s_adder.cpp
#include "s_adder_c.h"

void s_adder_c::prc_s_adder_c(){
    sc_int<5> temp;

    temp = a.read() + b.read();
    sum = temp.range(3,0);
    carry_out = temp[4];
}
```

©A. Milenkovic

26

Modeling Combinational Logic: Relational Operators

```
// File: gt.h
#include "systemc.h"
const WIDTH=8;

SC_MODULE(gt) {
    sc_in<sc_int<4>> a, b;
    sc_out <bool> z;
    void prc_gt();
}

SC_CTOR(gt) {
    SC_METHOD(prc_gt);
    sensitive << a << b;
}

// File: gt.cpp
#include "gt.h"
void gt::prc_gt(){
    sc_int<WIDTH> atemp, btemp;

    atemp = a.read();
    btemp = b.read();
    z = sc_uint<WIDTH>(atemp.range(WIDTH/2-1,0)) >
        sc_uint<WIDTH>(btemp.range(WIDTH-1,WIDTH/2));
}
```

©A. Milenkovic

27

Modeling Combinational Logic: Vector and Ranges

```
// Bit or range select of a port  
// or a signal is not allowed  
  
sc_in<sc_uint<4> > data;  
sc_signal<sc_bv<6> > counter;  
sc_uint<4> temp;  
sc_uint<6> cnt_temp;  
bool mode, preset;  
  
mode = data[2]; // not allowed  
//instead  
temp = data.read();  
mode = temp[2];  
  
counter[4] = preset; // not allowed  
cnt_temp = counter;  
cnt_temp[4] = preset;  
counter = cnt_temp;
```

©A. Milenkovic

28

Multiple Processes and Delta Delay

```
// File: mult_proc.h  
#include "systemc.h"  
  
SC_MODULE(mult_proc) {  
    sc_in<bool> in;  
    sc_out<bool> out;  
  
    sc_signal<bool> c1, c2;  
    void mult_proc1();  
    void mult_proc2();  
    void mult_proc3();  
  
    SC_CTOR(mult_proc) {  
        SC_METHOD(mult_proc1);  
        sensitive << in;  
        SC_METHOD(mult_proc2);  
        sensitive << c1;  
        SC_METHOD(mult_proc3);  
        sensitive << c2;  
    }  
};
```

```
// File: mult_proc.cpp  
#include "mult_proc.h"  
  
void mult_proc::mult_proc1(){  
    c1 = !in;  
}  
  
void mult_proc::mult_proc2(){  
    c2 = !c1;  
}  
  
void mult_proc::mult_proc3(){  
    out = !c2;  
}
```

©A. Milenkovic

30

If Statement

```
// File: simple_alu.h
#include "systemc.h"
const int WS=4;

SC_MODULE(simple_alu) {
    sc_in<sc_uint<WS>> a, b;
    sc_in<bool> ctrl;
    sc_out< sc_uint<WS>> z;

    void prc_simple_alu();
}

SC_CTOR(simple_alu)
{
    SC_METHOD(prc_simple_alu);
    sensitive << a << b << ctrl;
}
};
```

```
// File: simple_alu.cpp
#include "simple_alu.h"

void
simple_alu::prc_simple_alu(){
    if(ctrl)
        z = a.read() & b.read();
    else
        z = a.read() | b.read();
}
```

©A. Milenkovic

31

If Statement: Priority encoder

```
// File: priority.h
#include "systemc.h"
const int IS=4;
const int OS=3;

SC_MODULE(priority) {
    sc_in<sc_uint<IS>> sel;
    sc_out< sc_uint<OS>> z;

    void prc_priority();
}

SC_CTOR(priority)
{
    SC_METHOD(prc_priority);
    sensitive << sel;
}
};
```

```
// File: priority.cpp
#include "priority.h"

void priority::prc_priority(){
    sc_uint<IS> tsel;

    tsel = sel.read();

    if(tsel[0]) z = 0;
    else if (tsel[1]) z = 1;
    else if (tsel[2]) z = 2;
    else if (tsel[3]) z = 3;
    else z = 7;
}
```

©A. Milenkovic

32

Switch Statement: ALU

```
// File: alu.h
#include "systemc.h"
const int WORD=4;
enum op_type {add, sub, mul, div};

SC_MODULE(alu) {
    sc_in<sc_uint<WORD>> a, b;
    sc_in<op_type> op;
    sc_out< sc_uint<WORD>> z;

    void prc_alu();
}

SC_CTOR(alu)
{
    SC_METHOD(prc_alu);
    sensitive << a << b << op;
}
};
```

```
// File: alu.cpp
#include "alu.h"

void priority::prc_alu(){
    sc_uint<WORD> ta, tb;

    ta = a.read();
    tb = b.read();
    switch (op) {
        case add: z = ta+tb; break;
        case sub: z = ta-tb; break;
        case mul: z = ta*tb; break;
        case div: z = ta/tb; break;
    }
}
```

©A. Milenkovic

33

Loops

- C++ loops: for, do-while, while
- SystemC RTL supports only for loops
- For loop iteration must be a compile time constant

©A. Milenkovic

34

Loops: An Example

```
// File: demux.h
#include "systemc.h"
const int IW=2;
const int OW=4;

SC_MODULE(demux) {
    sc_in<sc_uint<IW> > a;
    sc_out<sc_uint<OW> > z;

    void prc_demux();
}

SC_CTOR(demux) {
    SC_METHOD(prc_demux);
    sensitive << a;
}
```



```
// File: demux.cpp
#include "demux.h"

void priority::prc_demux(){
    sc_uint<3> j;
    sc_uint<OW> temp;

    for(j=0; j<OW; j++)
        if(a==j) temp[j] = 1;
        else temp[j] = 0;
}
```

©A. Milenkovic

35

Methods

- Methods other than SC_METHOD processes can be used in a SystemC RTL

©A. Milenkovic

36

Methods

```
// File: oddls.h
#include "systemc.h"
const int SIZE = 6;

SC_MODULE(oddls) {
    sc_in<sc_uint<SIZE>> data_in;
    sc_out<bool> is_odd;

    bool isOdd(sc_uint<SIZE> abus);
    void prc_oddls();

    SC_CTOR(oddls) {
        SC_METHOD(prc_oddls);
        sensitive << data_in;
    }
};
```

```
// File: oddls.cpp
#include "oddls.h"

void oddls::prc_oddls(){
    is_odd = isodd(data_in);
}

bool oddls::isOdd
(sc_uint<SIZE> abus) {
    bool result;
    int i;

    for(i=0; i<SIZE; i++)
        result = result ^ abus[i];
    return(result);
}
```

©A. Milenkovic

37

Modeling Synchronous Logic: Flip-flops

```
// File: dff.h
#include "systemc.h"

SC_MODULE(dff) {
    sc_in<bool> d, clk;
    sc_out<bool> q;

    void prc_dff();

    SC_CTOR(dff) {
        SC_METHOD(prc_dff);
        sensitive_pos << clk;
    }
};
```

```
// File: dff.cpp
#include "dff.h"

void dff::prc_dff(){
    q = d;
}
```

©A. Milenkovic

38

Registers

```
// File: reg.h
#include "systemc.h"
const int WIDTH = 4;

SC_MODULE(reg) {
    sc_in<sc_uint<WIDTH>> cstate;
    sc_in<bool> clock;
    sc_out<sc_uint<WIDTH>> nstate;

    void prc_reg();

    SC_CTOR(dff) {
        SC_METHOD(prc_dff);
        sensitive_neg << clock;
    }
};
```

```
// File: reg.cpp
#include "reg.h"

void reg::prc_reg(){
    cstate = nstate;
}
```

©A. Milenkovic

39

Sequence Detector: "101"

```
// File: sdet.h
#include "systemc.h"

SC_MODULE(sdet) {
    sc_in<bool> clk, data;
    sc_out<bool> sfound;

    sc_signal<bool> first, second,
                    third;
    // synchronous logic process
    void prc_sdet();
    // comb logic process
    void prc_out();
}

SC_CTOR(sdet) {
    SC_METHOD(prc_sdet);
    sensitive_pos << clk;
    SC_METHOD(prc_out);
    sensitive << first << second
        << third;
}
```

```
// File: sdet.cpp
#include "sdet.h"

void sdet::prc_sdet(){
    first = data;
    second = first;
    third = second
}

void sdet::prc_out(){
    sfound = first &
        (!second) & third;
}
```

©A. Milenkovic

40

Counter: Up-down, Async Negative Clear

```
// File: cnt4.h
#include "systemc.h"
const int CSIZE = 4;
SC_MODULE(cnt4) {
    sc_in<bool> mclk, cl, updown;
    sc_out<sc_uint<CSIZE> > dout;

    void prc_cnt4();

    SC_CTOR(cnt4) {
        SC_METHOD(prc_cnt4);
        sensitive_pos << mclk;
        sensitive_neg << cl;
    }
};
```

```
// File: cnt4.cpp
#include "cnt4.h"

void sdet::prc_cnt4(){
    if(!clear)
        data_out = 0;
    else
        if(updown)
            dout=dout.read()+1;
        else
            dout=dout.read()-1;
}
```

©A. Milenkovic

41