 


**CPE/EE 422/522  
Advanced Logic Design  
L17**

Electrical and Computer Engineering  
University of Alabama in Huntsville


**Networks for Arithmetic Operations**

**Case Study: Serial Parallel Multiplier**




Note: we use unsigned binary numbers

**Block Diagram of a Binary Multiplier**

 


Ad – add signal // adder outputs are stored into the ACC  
Sh – shift signal // shift all 9 bits to right  
Ld – load signal // load multiplier into the 4 lower bits of the ACC  
and clear the upper 5 bits

**Multiplication Example**

 

dividing line between product and multiplier

## State Graph for Binary Multiplier

 

23/07/2003

UAH-CPE/EE 422/522 ©AM

5

## Behavioral VHDL Model

```

library BITLIB;
use BITLIB.bit_pack.all;
entity mult4x4 is
    port (Clk, St: in bit;
          Mplier, Mrand: in bit_vector(3 downto 0);
          Done: out bit);
end mult4x4;

architecture behave1 of mult4x4 is
    signal State: integer range 0 to 9; -- accumulator
    signal ACC: bit_vector(8 downto 0); -- M is bit 0 of ACC
    alias M: bit is ACC(0);
begin
    process
    begin
        wait until Clk = '1'; -- executes on rising edge of clock
        case State is
            when 0 => -- initial State
                if St = '1' then
                    ACC(8 downto 4) <= '00000'; -- Begin cycle
                    ACC(3 downto 0) <= Mplier; -- load the multiplier
                    State <= 1;
                end if;
            -- ... (rest of the process code)
        end case;
    end process;
end behave1;
    
```

23/07/2003

UAH-CPE/EE 422/522 ©AM

6

## Behavioral VHDL Model (cont'd)

```

when 1 | 3 | 5 | 7 => -- "add/shift" State
    if M = '1' then -- Add multiplicand
        ACC(8 downto 4) <= add94(ACC(7 downto 4), Mrand, '0');
        State <= State + 1;
    else
        ACC <= '0' & ACC(8 downto 3); -- Shift accumulator right
        State <= State + 2;
    end if;
when 2 | 4 | 6 | 8 => -- "shift" State
    ACC <= '0' & ACC(8 downto 1); -- Right shift
    State <= State + 1;
when 9 => -- End of cycle
    State <= 0;
end case;
end process;
Done <= '1' when State = 9 else '0';
end behave1;
    
```

23/07/2003

UAH-CPE/EE 422/522 ©AM

7

## Multiplier Control with Counter


- Current design: control part generates the control signals (shift/add) and counts the number of steps
- If the number of bits is large (e.g., 64), the control network can be divided into a counter and a shift/add control

23/07/2003

UAH-CPE/EE 422/522 ©AM

8
 
## Multiplier Control with Counter (cont'd)



Add-shifts control: tests  $S_t$  and  $M$  and generates the proper sequence of add and shift signals


Counter control: counter generates a completion signal  $K$  that stops the multiplier after the proper number of shifts have been completed

23/07/2003

UAH-CPE/EE 422/522 ©AM

9
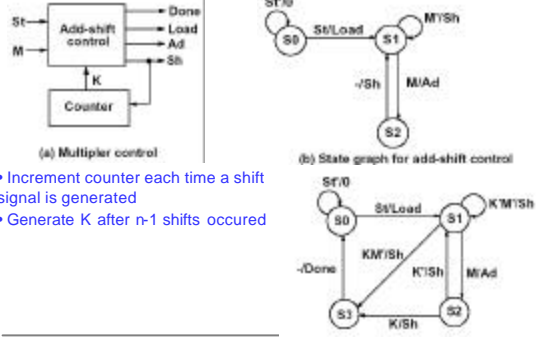
## Multiplier Control with Counter (cont'd)



- Increment counter each time a shift signal is generated
- Generate  $K$  after  $n-1$  shifts occurred

23/07/2003

UAH-CPE/EE 422/522 ©AM

10

## Operation of a Multiplier Using Counter

Time	State	Counter	Product Register	$S_t$	$M$	$K$	Load	Ad	Sh	Done
t0	S0	00	00000000	0	0	0	0	0	0	0
t1	S0	00	00000000	1	0	0	1	0	0	0
t2	S1	00	00000101	0	1	0	0	1	0	0
t3	S2	00	01101101	0	1	0	0	0	1	0
t4	S1	01	001101101	0	1	0	0	1	0	0
t5	S2	01	100111101	0	1	0	0	0	1	0
t6	S1	10	010011110	0	0	0	0	0	1	0
t7	S1	11	001001110	0	1	1	0	1	0	0
t8	S2	11	100011111	0	1	1	0	0	1	0
t9	S3	00	010001111	0	1	0	0	0	0	1

23/07/2003

UAH-CPE/EE 422/522 ©AM

11

## Array Multiplier

$X_3$	$X_2$	$X_1$	$X_0$	Multiplier				
$Y_3$	$Y_2$	$Y_1$	$Y_0$					
$X_3Y_0$	$X_2Y_0$	$X_1Y_0$	$X_0Y_0$	partial product 0				
$X_3Y_1$	$X_2Y_1$	$X_1Y_1$	$X_0Y_1$	partial product 1				
$C_{12}$	$C_{11}$	$C_{10}$		1st row carries				
$X_3Y_2$	$X_2Y_2$	$X_1Y_2$	$X_0Y_2$	partial product 2				
$C_{22}$	$C_{21}$	$C_{20}$		2nd row carries				
$X_3Y_3$	$X_2Y_3$	$X_1Y_3$	$X_0Y_3$	partial product 3				
$C_{32}$	$C_{31}$	$C_{30}$		3rd row carries				
$C_{33}$	$S_{32}$	$S_{31}$	$S_{30}$	3rd row sums				
$P_7$	$P_6$	$P_5$	$P_4$	$P_3$	$P_2$	$P_1$	$P_0$	final product:

- What do we need to realize Array Multiplier?


- AND gates = ?
- FA = ?
- HA = ?

23/07/2003

UAH-CPE/EE 422/522 ©AM

12

## Array Multiplier (cont'd)

 

23/07/2003

UAH-CPE/EE 422/522 ©AM

13

## Array Multiplier (cont'd)

- Complexity of the N-bit array multiplier
  - number of AND gates = ?
  - number of HA = ?
  - number of FA = ?
- Delay
  - $t_g$  – longest AND gate delay
  - $t_{ad}$  – longest possible delay through an adder

23/07/2003

UAH-CPE/EE 422/522 ©AM

14

## Multiplication of Signed Binary Numbers

- How to multiply signed binary numbers?
- Procedure
  - Complement the multiplier if negative
  - Complement the multiplicand if negative
  - Multiply two positive binary numbers
  - Complement the product if it should be negative
- Simple but requires more hardware and time than other available methods

23/07/2003

UAH-CPE/EE 422/522 ©AM

15

## Multiplication of Signed Binary Numbers


- Four cases
    - Multiplicand is positive, multiplier is positive
    - Multiplicand is negative, multiplier is positive
    - Multiplicand is positive, multiplier is negative
    - Multiplier is negative, multiplicand is negative
  - Examples
    - $0111 \times 0101 = ?$
    - $1101 \times 0101 = ?$
    - $0101 \times 1101 = ?$
    - $1011 \times 1101 = ?$
- Preserve the sign of the partial product at each step
  - If multiplier is negative, complement the multiplicand before adding it in at the last step

23/07/2003

UAH-CPE/EE 422/522 ©AM

16

## 2's Complement Multiplier

 


23/07/2003

UAH-CPE/EE 422/522 ©AM

17
 
## State Graph for 2's Complement Multiplier




23/07/2003

UAH-CPE/EE 422/522 ©AM

18

## Faster Multiplier

 


- Move wires from the adder outputs one position to the right => add and shift can occur at the same clock cycle

23/07/2003

UAH-CPE/EE 422/522 ©AM

19

## State Graph for Faster Multiplier

 

23/07/2003

UAH-CPE/EE 422/522 ©AM

20

## Behavioral Model for Faster Multiplier

```

library IEEE;
use IEEE.Bit_Pack.all;

entity mul2C is
    port (CLK, St: in bit;
          Mplier_M operand: in bit_vector(3 downto 0);
          Product: out bit_vector(6 downto 0);
          Done: out bit);
end mul2C;

architecture behav of mul2C is
    signal State: integer range 0 to 5;
    signal A, B: bit_vector(3 downto 0);
    alias M: bit is Moperand;

    process
        variable addout: bit_vector(4 downto 0);
    begin
        wait until CLK = '1';
        case State is
            when 0 => -- Initial State
                if St = '1' then
                    A <= "0000"; -- Begin cycle
                    B <= Mplier; -- load the multiplier
                    State <= 1;
                end if;
        end case;
    end process;
end behav;

```

23/07/2003

UAH-CPE/EE 422/522 ©AM

21

## Behavioral Model for Faster Multiplier

```

when 1 | 2 | 3 => -- "add/shift" State
    if M = '1' then
        addout := add4(A_M operand, '0'); -- Add multiplicand to A and shift
        A <= M operand(3) & addout(3 downto 1);
        B <= addout(0) & B(3 downto 1);
    else
        A <= A(3) & A(3 downto 1); -- Arithmetic right shift
        B <= A(0) & B(3 downto 1);
    end if;
    State <= State + 1; -- add complement if sign bit
when 4 => -- of multiplier is 1
    if M = '1' then
        addout := add4(A, not M operand, '1');
        A <= not M operand(3) & addout(3 downto 1);
        B <= addout(0) & B(3 downto 1);
    else
        A <= A(3) & A(3 downto 1); -- Arithmetic right shift
        B <= A(0) & B(3 downto 1);
    end if;
    State <= 5; wait for 0 ns;
    Done <= '1'; Product <= A(2 downto 0) & B;
when 5 => -- output product
    State <= 0;
    Done <= '0';
end if;
end case;
end process;
end behav;

```

23/07/2003

UAH-CPE/EE 422/522 ©AM

22

## Command File and Simulation

```

-- command file to test signed multiplier
test CLK: St State A B Done Product
force st 1 2, 0 22
force clk 1 0, 0 10 - repeat 20
-- (3/0 - 3/0)
force M operand 0101
force Mplier 1101
run 120

```

ns	delta	CLK	St	State	A	B	Done	Product
0	+1	1	0	0	0000	0000	0	0000000
2	+0	1	1	0	0000	0000	0	0000000
10	+0	0	1	0	0000	0000	0	0000000
20	+1	1	1	1	0000	1101	0	0000000
22	+0	1	0	1	0000	1101	0	0000000
30	+0	0	0	1	0000	1101	0	0000000
40	+1	1	0	2	0010	1110	0	0000000
50	+0	0	0	2	0010	1110	0	0000000
60	+1	1	0	3	0001	0111	0	0000000
70	+0	0	0	3	0001	0111	0	0000000
80	+1	1	0	4	0011	0011	0	0000000
90	+0	0	0	4	0011	0011	0	0000000
100	+1	1	0	5	1111	0001	1	1110001
110	+0	0	0	5	1111	0001	1	1110001
120	+1	1	0	6	1111	0001	0	1110001

23/07/2003

UAH-CPE/EE 422/522 ©AM

23

## Test Bench for Signed Multiplier

```

library IEEE;
use IEEE.Bit_Pack.all;

entity testmul is
    port (CLK, St: in bit;
          Mplier_M operand: in bit_vector(3 downto 0);
          Product: out bit_vector(6 downto 0);
          Done: out bit);
end testmul;

component mul2C
    port (CLK, St: in bit;
          Mplier_M operand: in bit_vector(3 downto 0);
          Product: out bit_vector(6 downto 0);
          Done: out bit);
end component;

constant N: integer := 11;
constant Moperand: bit_vector := "11011", "1001", "0101", "1101", "0111", "1001", "0111",
    "1001", "0000", "1111", "1011";
constant Mplier: bit_vector := "10101", "0001", "1101", "1101", "0111", "0111", "1000",
    "1001", "1101", "1111", "0000";

signal CLK, St, Done: bit;
signal Mplier, Moperand: bit_vector(3 downto 0);
signal Product: bit_vector(6 downto 0);

begin
    CLK <= not CLK after 10 ns;
    process
        begin
            for i in 1 to N loop
                Moperand <= Moperand(i); Mplier <= Mplier(i); St <= '1';
                wait until rising_edge(CLK); St <= '1'; wait until falling_edge(Done);
            end loop;
        end process;
    end;
end testmul;

```

23/07/2003

UAH-CPE/EE 422/522 ©AM

24

## Hardware Testing and Design for Testability

- Testing during design process
  - use VHDL test benches to verify that the overall design and algorithms used are correct
  - verify timing and logic after the synthesis
- Post-fabrication testing
  - when a digital system is manufactured, test to verify that it is free from manufacturing defects
  - today, cost of testing is major component of the manufacturing cost
  - efficient techniques are needed to test and design digital systems so that they are easy to test

23/07/2003

UAH-CPE/EE 422/522 ©AM

25

## Testing Combinational Logic

- Common types of errors
  - short circuit
  - open circuit
- If the input to a gate is shorted to ground, the input acts as if it is stuck at logic 0
  - s-a-0 (stuck-at-0) faults
- If the input to a gate is shorted to positive supply voltage, the input acts as if it is stuck at logic 1
  - s-a-1 (stuck-at-1) faults


23/07/2003

UAH-CPE/EE 422/522 ©AM

26
 
## Stuck-at Faults

- How many single stuck-at faults —
  - $2(n + 1)$  — where n is the number of inputs




- We will assume
    - that there is only one stuck-at-fault active at a time in the whole circuit
- “SSF” — single stuck-at fault

23/07/2003

UAH-CPE/EE 422/522 ©AM

27

## Stuck-at Faults for AND and OR gates

 


23/07/2003

UAH-CPE/EE 422/522 ©AM


28

## Testing an AND-OR Network

 

BRUTE-FORCE testing:  
apply  $2^8=512$  different input combinations and check the output

a	b	c	d	e	f	g	h	i	Faults Tested
1	1	1	0	X	X	X	X	X	a0, b0, c0, p0
0	X	X	1	1	0	X	X		q0, e0, r0, q0
0	X	X	0	X	X	1	1		g0, h0, i0, r0
0	1	1	0	1	1	0	1		s1, d1, q1, p1, q1, r1
1	0	1	1	0	1	0	1		b1, e1, h1, p1, q1, r1
1	1	0	1	1	0	1	0		c1, f1, i1, p1, q1, r1

 


23/07/2003

UAH-CPE/EE 422/522 ©AM

29
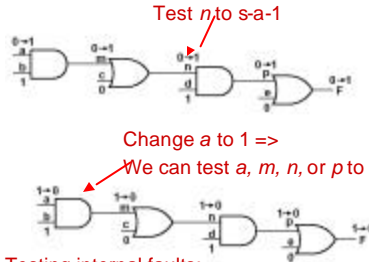
## Path Detection & Sensitization: Small Example



$n=0 \Rightarrow$   
 $m=0, c=0 \Rightarrow$   
 $a=0, b=1, c=0$   
 $d=1, e=0$

Testing internal faults:  
choose a set of inputs that will excite the fault and then propagate the fault to the network output


23/07/2003

UAH-CPE/EE 422/522 ©AM

30
 
## An Example

- What is a minimum set of test vectors to test the network below for all stuck-at-1 and stuck-at-0 faults?




- E.g., start with A-a-p-v-f path, determine the test vector to test s-a-0
- determine the list of faults covered
- select an untested fault, determine the required ABCD inputs
- determine the additional faults tested
- repeat the process until all faults are covered

23/07/2003

UAH-CPE/EE 422/522 ©AM

31

## An Example (cont'd)

 

- Step 1: A-a-p-v-f-F, s-a-0  
- ABCD: 1101 (+)
- Step 2: s-a-0 for c  
- C=1, p=0, w=1 => ABCD=1011 (\*)
- Step 3: s-a-0 for q  
- C=1, D=1, t=0, s=1 => ABCD=1111 (#)
- Step 4: s-a-1 for a  
- A=0, B=1, C=0, D=1 => ABCD=0101 (&)
- Step 5: s-a-1 for d (%)  
- D=0, C=0, t=1 => ABCD = 1100

	U	T
a	+	&
b	+	+
c	+	&
d	+	%
p	+	+
q	#	+
r	+	#
s	#	+
t	-	#
u	+	#
v	+	&
w	+	#
f	+	#

23/07/2003

UAH-CPE/EE 422/522 ©AM

32



## Testing Sequential Logic

- In general, much more difficult than testing combinational logic since we must use sequences of inputs
  - typically we can observe inputs and outputs, not the state of flip-flops
  - assume the reset input, so we can reset the network to the initial state
- Test procedure
  - reset the network to the initial state
  - apply a test sequence and observe the output sequence
  - if the output is correct, repeat the test for another sequence
- How many test sequences do we have?
  - how do we test that the initial state of the network under test is equivalent to the initial state of the correct network?
  - what is the sequence length?


23/07/2003

UAH-CPE/EE 422/522 ©AM

33
 
## Testing Sequential Logic (cont'd)

- In practice, if the network has  $N$  or fewer states, then apply only input sequences of length less than or equal to  $2N-1$
- Example
  - consider a network which includes 5 inputs, 1 output, and 4 states
  - total number of test sequences:  $(2^5)^7 = 2^{35} \Rightarrow$  infeasible (!)
  - derive a small set of test sequences that will adequately test a SN




23/07/2003

UAH-CPE/EE 422/522 ©AM

34
 
## Testing Sequential Logic (cont'd)

- Consider input sequence
  - $X = 010110011$
  - Output sequence  $Z = 001011110$
  - If we change the network  $S3 \rightarrow S0 \Rightarrow S3 \rightarrow S3$ , the output sequence will be the same
- Find distinguishing sequence
  - an input sequence that will distinguish each state from the other states



Input sequence:  $X=11$


- $S0: Z = 01$
- $S1: Z = 11$
- $S2: Z = 10$
- $S3: Z = 00$

23/07/2003

UAH-CPE/EE 422/522 ©AM

35

## Testing Sequential Logic (cont'd)

 

Q(i)Z	State	Next State	Output
00	S0	S0	0
01	S1	S0	0
10	S1	S2	1
11	S1	S3	1

Verify each entry in the table using the following sequences:

Input	Output	Transition Verified
0111	0110	(S0 to S0)
0111	0111	(S0 to S1)
11011	0101	(S1 to S0)
01111	0110	(S1 to S2)
11011	01100	(S2 to S3)
01111	01100	(S2 to S0)
0110011	011110	(S3 to S2)
110111	011010	(S3 to S0)


23/07/2003

UAH-CPE/EE 422/522 ©AM

36
 
## Testing Sequential Logic (cont'd)

- Implementation of the FSM
  - $S_0=00, S_1=10, S_2=01, S_3=11$
- Test a for s-a-1
  - to do this Q1Q2 must be 10  
=> go to the state S1 and then set X to 0 (R10)
  - in normal operation, the next state will be S0; if a is s-a-1 then next state is S2
  - distinguish the state (S0 or S2); apply sequence 11
  - Final sequence: R1011  
Normal output: 0101  
Faulty output: 0110



23/07/2003

UAH-CPE/EE 422/522 ©AM

37

## Scan Testing

- Testing of sequential networks is greatly simplified if we can observe the state of all the flip-flops instead of just observing the network outputs
  - Connect the output of each flip-flop to one of the IC pins?
  - Arrange flip-flops to form a shift register => shift out the state of flip-flops bit by bit using a single serial output pin => Scan path testing


23/07/2003

UAH-CPE/EE 422/522 ©AM

38
 
## Scan Path Testing

- Sequential network is separated into a combinational logic part and a state register composed of flip-flops



- Two ports FFs (2 D inputs and 2 clock inputs)
  - D1 is stored in the FF on C1 pulse
  - D2 is stored in the FF on C2 pulse
  - Q of each FF is connected to D2 of the next FF to form a shift register


23/07/2003

UAH-CPE/EE 422/522 ©AM

39
 
## Scan Path Testing

- Normal operation
  - system clock  $SCK = C1$
  - inputs:  $X_1, X_2, \dots, X_N$
  - outputs:  $Z_1, Z_2, \dots, Z_N$
- Testing
  - FFs are set to a specified state using the SDI and TCK
  - test vector is applied  $X_1, X_2, \dots, X_N$
  - outputs  $Z_1, Z_2, \dots, Z_N$  are verified
  - SCK is pulsed to take the network to the next state
  - next state is verified by pulsing the TCK to shift the state code out of the scan register via SDO



23/07/2003

UAH-CPE/EE 422/522 ©AM


40

## Scan Path Testing: An Example

- SQ:  $X_1X_2, Q_1Q_2Q_3, Z_1Z_2$

One row of the state transition table:

$Q_1Q_2Q_3$	$Q_1^+Q_2^+Q_3^+$	$Z_1Z_2$
$X_1X_2 = 00\ 01\ 11\ 10$	$00\ 01\ 11\ 10$	$00\ 01\ 11\ 10$
101	010 110 011 111	10 11 00 01

 


23/07/2003

UAH-CPE/EE 422/522 ©AM

41

## Scan Chain

 


23/07/2003

UAH-CPE/EE 422/522 ©AM

42

## Scan Test with Multiple ICs

 

23/07/2003

UAH-CPE/EE 422/522 ©AM

43

## Boundary Scan

- PCB testing has become more difficult
  - ICs have become more complex, with more and more pins
  - PCBs have become more denser with multiple layers and fine traces
  - Bed-of-nails testing
    - use sharp probes to contact the traces on the board
    - test data are applied to and read from various ICs
    - => not practical for high-density PCBs with fine traces and complex ICs
- Boundary scan test methodology:
  - introduced to facilitate the testing of complex PC boards
  - developed by JTAG (Joint Task Action Group)
  - adopted as ANSI/IEEE Standard 1149.1 – “Standard Test Access Port and Boundary Scan Architecture”
  - IC manufacturers make ICs that conform the standard
  - ICs can be linked together on a PCB, so that they can be tested using only a few pins on the PCB edge connector


23/07/2003

UAH-CPE/EE 422/522 ©AM

44
 
## Boundary Scan Register

- Boundary Scan Register (BSR) – cells of the BSR are placed between input or output pins and the internal core logic
- Four or five pins of the IC are devoted to the test-access-port (TAP)



Boundary scan cells

TAP pins


- TDI – Test data input (data are shifted serially into the BSR)
- TCK – Test clock
- TMS – Test mode select
- TDO – Test data output (serial output from BSR)
- TRST – Test reset (resets the TAP controller and test logic – optional pin)

23/07/2003

UAH-CPE/EE 422/522 ©AM

45

## PCB with Boundary Scan ICs

 


- BSRs in the ICs are linked together serially in a single chain with input TDI and output TDO.
- TCK, TMS, TRST are connected in parallel to all of the ICs.

23/07/2003

UAH-CPE/EE 422/522 ©AM

46

## Boundary Scan Cell

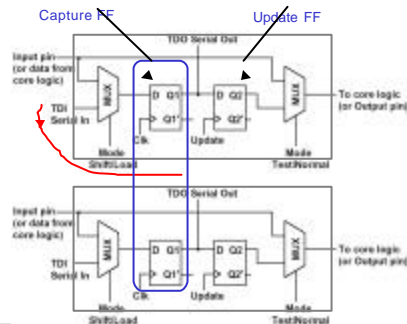


23/07/2003

UAH-CPE/EE 422/522 ©AM

47

## Basic Boundary Scan Architecture

 


- BSR1 – shift register, which consists of the Q1 flip-flops in the boundary scan cells
- BSR2 – represents the Q2 flip-flops; can be parallel loaded from BSR1 when an update signal is received
- TDI can be shifted into the BSR1, through a bypass register, or into the ISR

23/07/2003


UAH-CPE/EE 422/522 ©AM

48

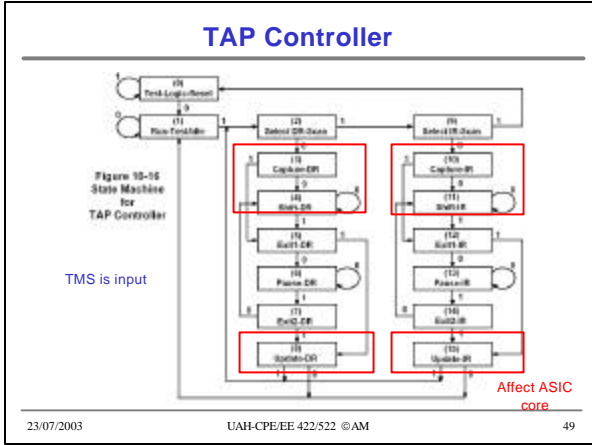

- ### TAP Controller: How it Works (I)
- TAP Controller
    - 16 state FSM
    - Change states depending on TMS and TCK
    - Output: signals to control the test data registers and instruction register (including serial shift clocks and update clocks)
  - Test-logic-reset is the initial state; on a low TMS go to Run-Test/Idle state
  - TMS: 1100 => Shift-IR
  - In Shift-IR command is shifted in through TDI port
  - ...
- 23/07/2003 UAH-CPE/EE 422/522 ©AM 50

- ### Instructions in the IEEE Standard
- BYPASS: allows the TDI serial data to go through 1-bit bypass register on the IC instead of through the BSR1. In this way one or more ICs on the PCB may be bypassed.
  - SAMPLE/RELOAD: used to scan the BSR without interfering with the normal operation of the core logic. Data is transferred to or from the core logic from or to the IC pins without interference. Samples of this data can be taken and scanned out through the BSR. Test data can be shifted into the BSR.
  - EXTEST: allows board-level interconnect testing and testing of clusters of components which do not incorporate the boundary scan test features. Test data is shifted into the BSR and then it goes to the output pins. Data from the input pins is captured by the BSR.
  - INTTEST (optional): this instruction allows testing of the core logic by shifting test data into the boundary-scan register. Data shifted into the BSR takes the place of data from the input pins, and output data from the core logic is loaded into the BSR.
  - RUNBIST (optional): this instruction causes special built-in self-test (BIST) logic within the IC to execute.
- 23/07/2003 UAH-CPE/EE 422/522 ©AM 51

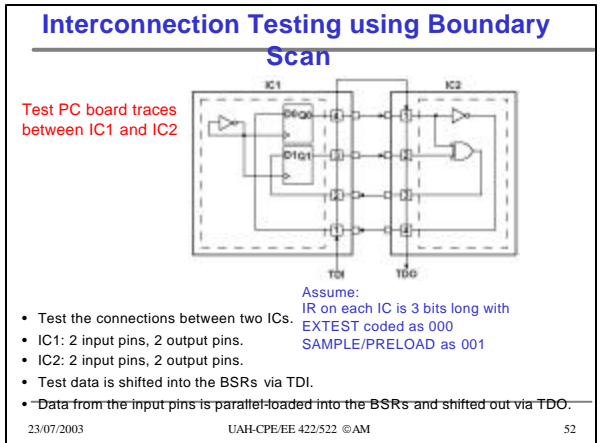

## Steps Required to Test Connections

- 1. Reset the TAP state machine to the Test-Logic-Reset state by inputting a sequence of five 1's on TMS. The TAP controller is designed so that a sequence of five 1's will always reset it regardless of the present state. Alternatively, TRST could be asserted if it is available.
- 2. Scan in the SAMPLE/PRELOAD instruction to both ICs using the sequences for TMS and TDI given below.
  - State: 0 1 2 9 10 11 11 11 11 11 11 12 15 2
  - TMS: 0 1 1 0 0 0 0 0 0 0 1 1 1
  - TDI: ---- - 1 0 0 1 0 0 - -
- The TMS sequence 01100 takes the TAP controller to the Shift-IR state. In this state, copies of the SAMPLE/PRELOAD instruction (code 001) are shifted into the instruction registers on both ICs. In the Update-IR state, the instructions are loaded into the instruction decode registers. Then the TAP controller goes back to the Select DR-scan state.

23/07/2003


UAH-CPE/EE 422/522 ©AM

53

## Steps Required to Test Connections (cont'd)

 - 3. Preload the first set of test data into the ICs using the sequences for TMS and TDI given below.
  - State: 2 3 4 4 4 4 4 4 4 5 8 2
  - TMS: 0 0 0 0 0 0 0 0 1 1 1
  - TDI: -- 0 1 0 0 1 0 0 --

Data is shifted into BSR1 in the Shift-DR state, and it is transferred to BSR2 in the Update-DR state. The result is as follo



23/07/2003

UAH-CPE/EE 422/522 ©AM

54

## Steps Required to Test Connections (cont'd)

- 4. Scan in the EXTEST instruction to both ICs using the following sequences:

State: 2 9 10 11 11 11 11 11 11 12 15 2  
 TMS: 1 0 0 0 0 0 0 0 1 1 1  
 TDI: --- 0 0 0 0 0 0 - -

The EXTEST instruction (000) is scanned into the instruction register in state Shift-IR and loaded into the instruction decode register in state Update-IR. At this point, the preloaded test data goes to the output pins, and it is transmitted to the adjacent IC input pins via the printed circuit board traces.

23/07/2003


UAH-CPE/EE 422/522 ©AM

55

## Steps Required to Test Connections (cont'd)

 - 5. Capture the test results from the IC inputs. Scan this data out to TDO and scan the second set of test data in using the following sequences:
  - State: 2 3 4 4 4 4 4 4 4 5 8 2
  - TMS: 0 0 0 0 0 0 0 0 1 1 1
  - TDI: -- 1 0 0 0 1 0 0 --
  - TDO: -- x x 1 0 x x 1 0 --

The data from the input pins is loaded into BSR1 in state Capture-DR. At this time, if no faults have been detected, the BSRs should be configured as shown below, where the X's indicate captured data which is not relevant to the test.



The test results are then shifted out of BSR1 in state Shift-DR as the new test data is shifted in. The new data is loaded into BSR2 in the Update-IR state.

23/07/2003

UAH-CPE/EE 422/522 ©AM

56


## Steps Required to Test Connections (cont'd)

- 6. Capture the test results from the IC inputs. Scan this data out to TDO and scan all 0's in using the following sequences:  
 State: 2 3 4 4 4 4 4 4 4 5 8 2 9 0  
 TMS: 0 0 0 0 0 0 0 0 0 1 1 1 1 1  
 TDI: -- 0 0 0 0 0 0 0 0 ----  
 TDO: -- x x 0 1 x x 0 1 ----

The data from the input pins is loaded into BSR1 in state Capture-DR. Then it is shifted out in state Shift-DR as all 0's are shifted in. The 0's are loaded into BSR2 in the Update-IR state. The controller then returns to the Test-Logic-Reset state and normal operation of the ICs can then occur. The interconnection test passes if the observed TDO sequences match the ones given above.
 
## Built-In Self-Test


- Add logic to the IC so that it can test itself
  - Built-In Self-Test – BIST
- Using BIST
  - when test mode is selected by the test-select signal, an on-chip test generator applies test patterns to the circuit under test
  - the resulting outputs are observed by the response monitor, which produces an error signal if an incorrect output is detected




## Self-Test Circuit for RAM


 
## Linear Feedback Shift Registers (LFSR)


 
## Self-Test Circuit for RAM with Signature Regs



MISR – Multiple Input  
Signature Register

E.g. for MISR –form a check-  
sum by adding up all data bytes  
stored in the RAM