

CPE/EE 422/522 Advanced Logic Design L05

Electrical and Computer Engineering
University of Alabama in Huntsville

Outline


- What we know
 - Combinational Networks
 - Sequential Networks:
 - Basic Building Blocks, Mealy & Moore Machines, Max Frequency, Setup & Hold Times, Synchronous Design
- What we do not know
 - Equivalent states and reduction of state tables
 - Hardware Description Languages

11/06/2003

UAH-CPE/EE 422/522 ©AM

2

Review: Mealy Sequential Networks

 


- (1) X inputs are changed to a new value
- (2) After a delay, the Z outputs and next state appear at the output of CM
- (3) The next state is clocked into the state register and the state changes

11/06/2003

UAH-CPE/EE 422/522 ©AM

3

 Review: General Model of Moore Sequential Machine



$$\begin{aligned}
 X &= x_1 x_2 \dots x_n & Q(t^+) &= G(X(t), Q(t)) \\
 Q &= Q_1 Q_2 \dots Q_k & Z(t) &= F(Q(t)) \\
 Z &= z_1 z_2 \dots z_m
 \end{aligned}$$

11/06/2003

UAH-CPE/EE 422/522 ©AM

4

Intro to VHDL

- Technology trends
 - 1 billion transistor chip running at 20 GHz in 2007
- Need for Hardware Description Languages
 - Systems become more complex
 - Design at the gate and flip-flop level becomes very tedious and time consuming
- HDLs allow
 - Design and debugging at a higher level before conversion to the gate and flip-flop level
 - Tools for synthesis do the conversion
- VHDL, Verilog
- VHDL – VHSIC Hardware Description Language

11/06/2003

UAH-CPE/EE 422/522 ©AM

5

Intro to VHDL


- Developed originally by DARPA
 - for specifying digital systems
- International IEEE standard (IEEE 1076-1993)
- Hardware Description, Simulation, Synthesis
- Provides a mechanism for digital design and reusable design documentation
- Support different description levels
 - Structural (specifying interconnections of the gates),
 - Dataflow (specifying logic equations), and
 - Behavioral (specifying behavior)
- **Top-down, Technology-Dependent**

11/06/2003

UAH-CPE/EE 422/522 ©AM

6

 VHDL Description of Combinational Networks



Concurrent Statements

```
C <= A and B after 5 ns;
E <= C or D after 5 ns;
```

If delay is not specified, "delta" delay is assumed

```
C <= A and B;
E <= C or D;
```

Order of concurrent statements is not important

```
E <= C or D;
C <= A and B;
```

This statement executes repeatedly

```
CLK <= not CLK after 10 ns;
```

This statement causes a simulation error

```
CLK <= not CLK;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

7

Entity-Architecture Pair

Full Adder Example



```
entity FullAdder is
  port (X, Y, Cin: in bit; -- Inputs
        Cout, Sum: out bit); -- Outputs
end FullAdder;


architecture Equations of FullAdder is
begin
  -- Concurrent Assignments
  Sum <= X xor Y xor Cin after 10 ns;
  Cout <= (X and Y) or (X and Cin) or (Y and Cin) after 10 ns;
end Equations;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

8

VHDL Program Structure

 

```
entity entity-name is
  [port(interface-signal-declaration);]
end [entity] [entity-name];


architecture architecture-name of entity-name is
  [declarations]
begin
  architecture body [architecture-name];
end [architecture] [architecture-name];
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

9

4-bit Adder

 

```
entity Adder4 is
  port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
        S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

10

4-bit Adder (cont'd)

```
entity Adder4 is
  port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
        S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;
```

```
architecture Structure of Adder4 is
  component FullAdder
  port (X, Y, Cin: in bit; -- Inputs
        Cout, Sum: out bit); -- Outputs
  end component;
  signal C: bit_vector(3 downto 1);
begin
  --instantiate four copies of the FullAdder
  FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
  FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
  FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
  FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
end Structure;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

11

4-bit Adder - Simulation

```
list A B Co C Ci S -- put these signals on the output list
force A 1111 -- set the A inputs to 1111
force B 0001 -- set the B inputs to 0001
force Ci 1 -- set the Ci to 1
run 50 -- run the simulation for 50 ns
force Ci 0
force A 0101
force B 1110
run 50

ns delta a b co c ci s
0 +0 0000 0000 0 000 0 0000
0 +1 1111 0001 0 000 1 0000
10 +0 1111 0001 0 001 1 1111
20 +0 1111 0001 0 011 1 1101
30 +0 1111 0001 0 111 1 1001
40 +0 1111 0001 1 111 1 0001
50 +0 0101 1110 1 111 0 0001
60 +0 0101 1110 1 110 0 0101
70 +0 0101 1110 1 100 0 0111
80 +0 0101 1110 1 100 0 0011
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

12

Modeling Flip-Flops Using VHDL Processes

General form of process

```

process(sensitivity-list)
begin
    sequential-statements
end process;
    
```

- Whenever one of the signals in the sensitivity list changes, the sequential statements are executed in sequence one time

Concurrent Statements vs. Process

A, B, C, D are integers
 A=1, B=2, C=3, D=0
 D changes to 4 at time 10

```

A <= B; -- statement 1
B <= C; -- statement 2
C <= D; -- statement 3
    
```

```

process (B, C, D)
begin
    A <= B; -- statement 1
    B <= C; -- statement 2
    C <= D; -- statement 3
end process;
    
```

Simulation Results

time	delta	A	B	C	D
0	+0	1	2	3	0
10	+1	2	3	4	0
10	+2	3	4	4	4
10	+3	4	4	4	4

D Flip-flop Model




Bit values are enclosed in single quotes

```

entity DFF is
    port (D, CLK: in bit;
          Q: out bit; QN: out bit := '1');
    -- initialize QN to '1' since bit signals are initialized to '0' by default.
end DFF;

architecture SIMPLE of DFF is
begin
    process (CLK) -- process is executed when CLK changes
    begin
        if CLK = '1' then -- rising edge of clock
            Q <= D after 10 ns;
            QN <= not D after 10 ns;
        end if;
    end process;
end SIMPLE;
    
```

JK Flip-Flop Model

 


```

entity JKFF is
    port (SN, RN, J, K, CLK: in bit; -- inputs
          Q: inout bit; QN: out bit := '1'); -- see Note 1
end JKFF;

architecture JKFF of JKFF is
begin
    process (SN, RN, CLK) -- see Note 2
    begin
        if RN = '0' then Q <= '0' after 10 ns; -- RN=0 will clear the FF
        elsif SN = '0' then Q <= '1' after 10 ns; -- SN=0 will set the FF
        elsif CLK = '0' and CLK event then -- see Note 3
            Q <= (J and not Q) or (not K and Q) after 10 ns; -- see Note 4
        end if;
    end process;
    QN <= not Q; -- see Note 5
end JKFF;
    
```

JK Flip-Flop Model

- Note 1: Q is declared as **inout** (rather than **out**) because it appears on both the left and right sides of an assignment within the architecture.
- Note 2: The flip-flop can change state in response to changes in SN, RN, and CLK, so these 3 signals are in the sensitivity list.
- Note 3: The condition (CLK = '0' and CLK'event) is TRUE only if CLK has just changed from '1' to '0'.
- Note 4: Characteristic equation which describes behavior of JK flip-flop.
- Note 5: Every time Q changes, QN will be updated. If the statement were placed within the process, the old value of Q would be used instead of the new value.

 


```

entity JKFF is
    port (SN, RN, J, K, CLK: in bit; -- inputs
          Q: inout bit; QN: out bit := '1'); -- see Note 1
end JKFF;

architecture JKFF of JKFF is
begin
    process (SN, RN, CLK) -- see Note 2
    begin
        if SN = '0' then Q <= '0' after 10 ns; -- SN=0 will clear the FF
        elsif RN = '0' then Q <= '1' after 10 ns; -- SN=0 will set the FF
        elsif CLK = '0' and CLK'event then -- see Note 3
            Q <= (J and not Q) or (not K and Q) after 10 ns; -- see Note 4
        end if;
    end process;
    QN <= not Q; -- see Note 5
end JKFF;
    
```

Using Nested IFs and ELSEIFs

 


```

if (C1) then S1; S2;
else if (C2) then S3; S4;
else if (C3) then S5; S6;
else S7; S8;
end if;

if (C1) then S1; S2;
elsif (C2) then S3; S4;
elsif (C3) then S5; S6;
else S7; S8;
end if;
    
```

VHDL Models for a MUX

 

F <= (not A and not B and 0) or
(not A and B and 1) or
(A and not B and 2) or
(A and B and 3);

MUX model using a conditional signal assignment statement:

```
F <= 0 when Sel = 0
     1 when Sel = 1
     2 when Sel = 2
     3;
```

Sel represents the integer equivalent of a 2-bit binary number with bits A and B

If a MUX model is used inside a process, the MUX can be modeled using a CASE statement (cannot use a concurrent statement):

```
case Sel is
  when 0 => F <= 0;
  when 1 => F <= 1;
  when 2 => F <= 2;
  when 3 => F <= 3;
end case;
```

The case statement has the general form:

```
case expression is
  when choice1 => sequential_statements1;
  when choice2 => sequential_statements2;
  ...
  when others => sequential_statements3;
end case;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

19

MUX Models (1)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
  port (
    A : in std_logic_vector(15 downto 0);
    SEL : in std_logic_vector(3 downto 0);
    Y : out std_logic;
  end SELECTOR;
```

```
architecture RTL1 of SELECTOR is
  begin
    p0 : process (A, SEL)
    begin
      if (SEL = "0000") then Y <= A(0);
      elsif (SEL = "0001") then Y <= A(1);
      elsif (SEL = "0010") then Y <= A(2);
      elsif (SEL = "0011") then Y <= A(3);
      elsif (SEL = "0100") then Y <= A(4);
      elsif (SEL = "0101") then Y <= A(5);
      elsif (SEL = "0110") then Y <= A(6);
      elsif (SEL = "0111") then Y <= A(7);
      elsif (SEL = "1000") then Y <= A(8);
      elsif (SEL = "1001") then Y <= A(9);
      elsif (SEL = "1010") then Y <= A(10);
      elsif (SEL = "1011") then Y <= A(11);
      elsif (SEL = "1100") then Y <= A(12);
      elsif (SEL = "1101") then Y <= A(13);
      elsif (SEL = "1110") then Y <= A(14);
      else Y <= A(15);
      end if;
    end process;
  end RTL1;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

20

MUX Models (2)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
  port (
    A : in std_logic_vector(15 downto 0);
    SEL : in std_logic_vector(3 downto 0);
    Y : out std_logic;
  end SELECTOR;
```

```
architecture RTL3 of SELECTOR is
  begin
    with SEL select
      Y <= A(0) when "0000",
         A(1) when "0001",
         A(2) when "0010",
         A(3) when "0011",
         A(4) when "0100",
         A(5) when "0101",
         A(6) when "0110",
         A(7) when "0111",
         A(8) when "1000",
         A(9) when "1001",
         A(10) when "1010",
         A(11) when "1011",
         A(12) when "1100",
         A(13) when "1101",
         A(14) when "1110",
         A(15) when others;
  end RTL3;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

21

MUX Models (3)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
  port (
    A : in std_logic_vector(15 downto 0);
    SEL : in std_logic_vector(3 downto 0);
    Y : out std_logic;
  end SELECTOR;
```

```
architecture RTL2 of SELECTOR is
  begin
    p1 : process (A, SEL)
    begin
      case Sel is
        when "0000" => Y <= A(0);
        when "0001" => Y <= A(1);
        when "0010" => Y <= A(2);
        when "0011" => Y <= A(3);
        when "0100" => Y <= A(4);
        when "0101" => Y <= A(5);
        when "0110" => Y <= A(6);
        when "0111" => Y <= A(7);
        when "1000" => Y <= A(8);
        when "1001" => Y <= A(9);
        when "1010" => Y <= A(10);
        when "1011" => Y <= A(11);
        when "1100" => Y <= A(12);
        when "1101" => Y <= A(13);
        when "1110" => Y <= A(14);
        when others => Y <= A(15);
      end case;
    end process;
  end RTL2;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

22

MUX Models (4)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
  port (
    A : in std_logic_vector(15 downto 0);
    SEL : in std_logic_vector(3 downto 0);
    Y : out std_logic;
  end SELECTOR;
```

```
architecture RTL4 of SELECTOR is
  begin
    Y <= A(conv_integer(SEL));
  end RTL4;
```


11/06/2003

UAH-CPE/EE 422/522 ©AM

23

Compilation and Simulation of VHDL Code

 - Compiler (Analyzer) – checks the VHDL source code
 - does it conform with VHDL syntax and semantic rules
 - are references to libraries correct
- Intermediate form used by a simulator or by a synthesizer
- Elaboration
 - create ports, allocate memory storage, create interconnections, ...
 - establish mechanism for executing of VHDL processes




11/06/2003

UAH-CPE/EE 422/522 ©AM

24

Timing Model

 - VHDL uses the following simulation cycle to model the stimulus and response nature of digital hardware




11/06/2003

UAH-CPE/EE 422/522 ©AM

25

Delay Types

 - All VHDL signal assignment statements prescribe an amount of time that must transpire before the signal assumes its new value
- This prescribed delay can be in one of three forms:
 - Transport – prescribes propagation delay only
 - Inertial – prescribes propagation delay and minimum input pulse width
 - Delta – the default if no delay time is explicitly specified




11/06/2003

UAH-CPE/EE 422/522 ©AM

26

Transport Delay

 - Transport delay must be explicitly specified
 - I.e. keyword "TRANSPORT" must be used
- Signal will assume its new value after specified delay



11/06/2003

UAH-CPE/EE 422/522 ©AM

27


Inertial Delay

- Provides for specification propagation delay and input pulse width, i.e. 'inertia' of output:

```
target <= [REJECT time_expression] INERTIAL waveform;
```

- Inertial delay is default and REJECT is optional:
 
```
Output <= NOT Input AFTER 10 ns;
-- Propagation delay and minimum pulse width are 10ns
```



11/06/2003


UAH-CPE/EE 422/522 ©AM

28

Inertial Delay (cont.)

 - Example of gate with 'inertia' smaller than propagation delay
 - e.g. Inverter with propagation delay of 10ns which suppresses pulses shorter than 5ns

```
Output <= REJECT 5ns INERTIAL NOT Input AFTER 10ns;
```



- Note: the REJECT feature is new to VHDL-1076-1993

11/06/2003

UAH-CPE/EE 422/522 ©AM

29

Delta Delay

- Default signal assignment propagation delay if no delay is explicitly prescribed
 - VHDL signal assignments do not take place immediately
 - Delta is an infinitesimal VHDL time unit so that all signal assignments can result in signals assuming their values at a future time

```
E.g. Output <= NOT Input;
-- Output assumes new value in one delta cycle
```

- Supports a model of concurrent VHDL process execution
 - Order in which processes are executed by simulator does not affect simulation output

11/06/2003

UAH-CPE/EE 422/522 ©AM

30


Simulation Example

```

entity simulation_example is
end simulation_example;

architecture test1 of simulation_example is
    signal A,S,Q;
begin
    F1: process(Z)
    begin
        A <= '1';
        A <= transport '0' after 5 ns;
    end process F1;

     F2: process(A)
    begin
        if A = '1' then Q <= not Q after 10 ns; end if;
    end process F2;
end test1;
    
```



11/06/2003

UAH-CPE/EE 422/522 ©AM

31

Problem #1

- Using the labels, list the order in which the following signal assignments are evaluated if in2 changes from a '0' to a '1'. Assume in1 has been a '1' and in2 has been a '0' for a long time, and then at time t in2 changes from a '0' to a '1'.

```

entity not_another_prob is
    port (in1, in2: in bit;
          a: out bit);
end not_another_prob;

architecture oh_behave of not_another_prob is
    signal b, c, d, e, f: bit;
begin
    L1: d <= not(in1);
    L2: c <= not(in2);
    L3: f <= (d and in2);
    L4: e <= (c and in1);
    L5: a <= not b;
    L6: b <= e or f;
end oh_behave;
    
```

11/06/2003

UAH-CPE/EE 422/522 ©AM

32

Problem #2

- Under what conditions do the two assignments below result in the same behavior? Different behavior? Draw waveforms to support your answers.

```

out <= reject 5 ns inertial (not a) after 20 ns;
out <= transport (not a) after 20 ns;
    
```


11/06/2003

UAH-CPE/EE 422/522 ©AM

33

Modeling a Sequential Machine

 Mealy Machine for
8421 BCD to 8421 BCD + 3 bit serial converter



PS	NS		Z	
	X=0	X=1	X=0	X=1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S9	S9	0	1
S6	S9	-	1	-

How to model this in VHDL?

11/06/2003

UAH-CPE/EE 422/522 ©AM

34

Behavioral VHDL Model

```

entity DFF_2 is
    port (CLK: in bit;
          D: in bit;
          Q: out bit);
end DFF_2;

architecture F1 of DFF_2 is
    signal Q0, nextstate: bit;
begin
    process(D,CLK)
    begin
        if CLK'event and CLK = '1' then
            nextstate <= D;
        else
            nextstate <= Q0;
        end if;
        Q <= nextstate;
    end process;
end F1;
    
```



Two processes:

- the first represents the combinational network;
- the second represents the state register

11/06/2003

UAH-CPE/EE 422/522 ©AM

35


Simulation of the VHDL Model

Simulation command file:

```

wave CLK X State NextState Z
force CLK 0 0, 1 100 -repeat 200
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
run 1600
    
```

Waveforms:

 

11/06/2003

UAH-CPE/EE 422/522 ©AM

36

Dataflow VHDL Model

-- The following is a description of the sequential machine of
 -- Figure 1-17 in terms of its next state equations.
 -- The following state assignment was used:
 -- S0-->0; S1-->4; S2-->5; S3-->7; S4-->6; S5-->3; S6-->2

```
entity SM1_2 is
    port(X,CLK: in bit;
         Z: out bit);
end SM1_2;

architecture Equations1_4 of SM1_2 is
    signal Q1,Q2,Q3: bit;
begin
    process(CLK)
    begin
        if CLK='1' then -- rising edge of clock
            Q1<=not Q2 after 10 ns;
            Q2<=Q1 after 10 ns;
            Q3<=(Q1 and Q2 and Q3) or (not X and Q1 and not Q3) or
                (X and not Q1 and not Q2) after 10 ns;
        end if;
        Z<=(not X and not Q3) or (X and Q3) after 20 ns;
    end process;
end Equations1_4;
```

11/06/2003

UAH-CPE/EE 422/522 ©AM


37

Structural Model

```
library BITLIB;
use BITLIB.all; pack all;

entity SM1_2 is
    port(X,CLK: in bit;
         Z: out bit);
end SM1_2;

architecture Structure of SM1_2 is
    signal A1,A2,A3,A5,A6,D3: bit:= '0';
    signal Q1,Q2,Q3: bit:= '0';
    signal Q1N,Q2N,Q3N,XN: bit:= '1';
begin
    I1: Inverter port map (X,XN);
    G1: NAND3 port map (Q1,Q2,Q3,A1);
    G2: NAND3 port map (Q1,Q2N,Q3N,A2);
    G3: NAND3 port map (X,Q1N,Q2N,A3);
    G4: NAND3 port map (A1,A2,A3,D3);
    FF1: DFF port map (Q2N,CLK,Q1,Q1N);
    FF2: DFF port map (Q1,CLK,Q2,Q2N);
    FF3: DFF port map (D3,CLK,Q3,Q3N);
    G5: NAND2 port map (X,Q3,A5);
    G6: NAND2 port map (XN,Q3N,A6);
    G7: NAND2 port map (A5,A6,Z);
end Structure;
```

 

Package bit_pack is a part of library BITLIB – includes gates, flip-flops, counters (See Appendix B for details)

11/06/2003

UAH-CPE/EE 422/522 ©AM


38

Simulation of the Structural Model

Simulation command file:

```
wave CLK X Q1 Q2 Q3 Z
force CLK 0 0, 1 100 -repeat 200
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
run 1600
```

Waveforms:

 

11/06/2003

UAH-CPE/EE 422/522 ©AM

39

Wait Statements

- ... an alternative to a sensitivity list
 - Note: a process cannot have both wait statement(s) and a sensitivity list
- Generic form of a process with wait statement(s)

```
process
begin
    sequential-statements
    wait statement
    sequential-statements
    wait-statement
    ...
end process;
```

How wait statements work?

- Execute seq. statement until a wait statement is encountered.
- Wait until the specified condition is satisfied.
- Then execute the next set of sequential statements until the next wait statement is encountered.
- ...
- When the end of the process is reached start over again at the beginning.

11/06/2003

UAH-CPE/EE 422/522 ©AM

40

Forms of Wait Statements

```
wait on sensitivity-list;
wait for time-expression;
wait until boolean-expression;
```

- Wait on
 - until one of the signals in the sensitivity list changes
- Wait for
 - waits until the time specified by the time expression has elapsed
 - What is this: wait for 0 ns;
- Wait until
 - the boolean expression is evaluated whenever one of the signals in the expression changes, and the process continues execution when the expression evaluates to TRUE

11/06/2003

UAH-CPE/EE 422/522 ©AM


41

Using Wait Statements (1)

```
library BITLIB;
use BITLIB.all; pack all;

entity SM1_2 is
    port(X,CLK: in bit; Z: out bit);
end SM1_2;

architecture Table of SM1_2 is
    signal State: integer := 0;
begin
    process
    begin
        case State is
            when 0 =>
                if X='0' then Z<='0'; NextState<=1; and if;
                if X='1' then Z<='0'; NextState<=2; and if;
            when 1 =>
                if X='0' then Z<='1'; NextState<=3; and if;
                if X='1' then Z<='0'; NextState<=4; and if;
            when 2 =>
                if X='0' then Z<='0'; NextState<=4; and if;
                if X='1' then Z<='0'; NextState<=4; and if;
            when 3 =>
                if X='0' then Z<='0'; NextState<=5; and if;
                if X='1' then Z<='1'; NextState<=5; and if;
            when 4 =>
                if X='0' then Z<='1'; NextState<=5; and if;
                if X='1' then Z<='0'; NextState<=6; and if;
            when 5 =>
                if X='0' then Z<='0'; NextState<=6; and if;
                if X='1' then Z<='1'; NextState<=6; and if;
        end case;
    end process;
```

 

11/06/2003

UAH-CPE/EE 422/522 ©AM

42


Using Wait Statements (2)

```

when b =>
  if X = 0 then Z := 2; NextState := 0; end if;
when others => null; -- should not occur
end case;

wait on CLK, X;
if rising_edge(CLK) then -- rising edge function is in BITLIB *
  State := NextState; -- wait for State to be updated
  wait for 0 ns;
end if;
end process;
end U0A0;

```

 

To Do

- Read
 - Textbook chapters 2.1, 2.2