

CPE/EE 422/522 Advanced Logic Design L06

Electrical and Computer Engineering
University of Alabama in Huntsville

Outline

- What we know
 - Combinational Networks
 - Sequential Networks:
 - Basic Building Blocks, Mealy & Moore Machines, Max Frequency, Setup & Hold Times, Synchronous Design
- What we do not know
 - Equivalent states and reduction of state tables
 - Hardware Description Languages

13/06/2003

UAH-CPE/EE 422/522 ©AM

2

Intro to VHDL

- Technology trends
 - 1 billion transistor chip running at 20 GHz in 2007
- Need for Hardware Description Languages
 - Systems become more complex
 - Design at the gate and flip-flop level becomes very tedious and time consuming
- HDLs allow
 - Design and debugging at a higher level before conversion to the gate and flip-flop level
 - Tools for synthesis do the conversion
- VHDL, Verilog
- VHDL – VHSIC Hardware Description Language

13/06/2003

UAH-CPE/EE 422/522 ©AM

3

Intro to VHDL


- Developed originally by DARPA
 - for specifying digital systems
- International IEEE standard (IEEE 1076-1993)
- Hardware Description, Simulation, Synthesis
- Provides a mechanism for digital design and reusable design documentation
- Support different description levels
 - Structural (specifying interconnections of the gates),
 - Dataflow (specifying logic equations), and
 - Behavioral (specifying behavior)
- Top-down, Technology Dependent

13/06/2003

UAH-CPE/EE 422/522 ©AM

4

 VHDL Description of Combinational Networks



Concurrent Statements
`C <= A and B after 5 ns;`
`E <= C or D after 5 ns;`
 If delay is not specified, "delta" delay is assumed
`C <= A and B;`
`E <= C or D;`
 Order of concurrent statements is not important
`E <= C or D;`
`C <= A and B;`
 This statement executes repeatedly
`CLK <= not CLK after 10 ns;`
 This statement causes a simulation error
`CLK <= not CLK;`

13/06/2003

UAH-CPE/EE 422/522 ©AM

5

Entity-Architecture Pair

Full Adder Example



```
entity FullAdder is
  port (X, Y, Cin: in bit; -- Inputs
        Cout, Sum: out bit); -- Outputs
end FullAdder;


architecture Equations of FullAdder is
begin
  Sum <= X xor Y xor Cin after 10 ns;
  Cout <= (X and Y) or (X and Cin) or (Y and Cin) after 10 ns;
end Equations;
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

6

VHDL Program Structure

 

```

entity entity-name is
  [port:(interface-signal-declaration);]
end [entity] [entity-name];


architecture architecture-name of entity-name is
  [declarations]
begin
  architecture body
end [architecture] [architecture-name];
  
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

7

4-bit Adder

 

```

entity Adder4 is
  port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
        S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;
  
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

8

4-bit Adder (cont'd)

```

entity Adder4 is
  port (A, B: in bit_vector(3 downto 0); Ci: in bit; -- Inputs
        S: out bit_vector(3 downto 0); Co: out bit); -- Outputs
end Adder4;
  
```

```

architecture Structure of Adder4 is
  component FullAdder
    port (X, Y, Cin: in bit; -- Inputs
          Cout, Sum: out bit); -- Outputs
  end component;
  signal C: bit_vector(3 downto 1);
  begin --instantiate four copies of the FullAdder
    FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
    FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
    FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
    FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
  end Structure;
  
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

9

4-bit Adder - Simulation

```

list A B Co C Ci S -- put these signals on the output list
force A 1111 -- set the A inputs to 1111
force B 0001 -- set the B inputs to 0001
force Ci 1 -- set the Ci to 1
run 50 -- run the simulation for 50 ns
force Ci 0
force A 0101
force B 1110
run 50

ns delta a b co c ci s
0 +0 0000 0000 0 000 0 0000
0 +1 1111 0001 0 000 1 0000
10 +0 1111 0001 0 001 1 1111
20 +0 1111 0001 0 011 1 1101
30 +0 1111 0001 0 111 1 1001
40 +0 1111 0001 1 111 1 0001
50 +0 0101 1110 1 111 0 0001
60 +0 0101 1110 1 110 0 0101
70 +0 0101 1110 1 100 0 0111
80 +0 0101 1110 1 100 0 0011
  
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

10

Modeling Flip-Flops Using VHDL Processes

```

process(sensitivity-list)
begin
  sequential-statements
end process;
  
```

- Whenever one of the signals in the sensitivity list changes, the sequential statements are executed in sequence one time

13/06/2003

UAH-CPE/EE 422/522 ©AM

11

Concurrent Statements vs. Process

A, B, C, D are integers
A=1, B=2, C=3, D=0
D changes to 4 at time 0

```

A <= B; -- statement 1
C <= C; -- statement 2
C <= D; -- statement 3

process (B, C, D)
begin
  A <= B; -- statement 1
  B <= C; -- statement 2
  C <= D; -- statement 3
end process;
  
```

Simulation Results

```

time delta A B C D
0 +0 0 1 2 0
10 +1 1 2 3 4 (stat. 3 exe.)
10 +1 1 2 4 4 (stat. 2 exe.)
10 +2 1 4 4 4 (stat. 1 exe.)
10 +3 4 4 4 4 (no exec.)

time delta A B C D
0 +0 1 2 3 0
10 +0 1 2 3 4 (statements 1,2,3 execute; then update A,B,C)
10 +1 2 3 4 4 (statements 1,2,3 execute; then update A,B,C)
10 +2 3 4 4 4 (statements 1,2,3 execute; then update A,B,C)
10 +3 4 4 4 4 (no further statements execute)
  
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

12

D Flip-flop Model



Bit values are enclosed in single quotes

```
entity DFF is
  port (D, CLK: in bit;
        Q: out bit; QN: out bit := '1');
  -- initialize QN to '1' since bit signals are initialized to '0' by default.
end DFF;


architecture SIMPLE of DFF is
  process (CLK)
  begin
    if CLK = '1' then
      Q <= D after 10 ns;
      QN <= not D after 10 ns;
    end if;
  end process;
end SIMPLE;
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

13

JK Flip-Flop Model

 

```
entity JKFF is
  port (SN, RN, J, K, CLK: in bit;
        Q: inout bit; QN: out bit := '1');
end JKFF;

architecture JKFF of JKFF is
  process (SN, RN, CLK)
  begin
    if RN = '0' then Q <= '0' after 10 ns;
    elsif SN = '0' then Q <= '1' after 10 ns;
    elsif CLK = '0' and CLK event then
      Q <= (J and not Q) or (not K and Q) after 10 ns;
    end if;
  end process;
  QN <= not Q;
end JKFF;
```


13/06/2003

UAH-CPE/EE 422/522 ©AM

14

JK Flip-Flop Model

Note 1: Q is declared as inout (rather than out) because it appears on both the left and right sides of an assignment within the architecture.
Note 2: The flip-flop can change state in response to changes in SN, RN, and CLK, so these 3 signals are in the sensitivity list.
Note 3: The condition (CLK = '0' and CLK event) is TRUE only if CLK has just changed from '1' to '0'.
Note 4: Characteristic equation which describes behavior of J-K flip-flop.
Note 5: Every time Q changes, QN will be updated. If the statement were placed within the process, the old value of Q would be used instead of the new value.

 

```
entity JKFF is
  port (SN, RN, J, K, CLK: in bit;
        Q: inout bit; QN: out bit := '1');
end JKFF;


architecture JKFF of JKFF is
  process (SN, RN, CLK)
  begin
    if SN = '0' then Q <= '0' after 10 ns;
    elsif RN = '0' then Q <= '1' after 10 ns;
    elsif CLK = '0' and CLK event then
      Q <= (J and not Q) or (not K and Q) after 10 ns;
    end if;
  end process;
  QN <= not Q;
end JKFF;
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

15

Using Nested IFs and ELSEIFs

 


```
if (C1) then S1; S2;
else if (C2) then S3; S4;
else if (C3) then S5; S6;
else S7; S8;
end if;
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

16

VHDL Models for a MUX

 

$F \leftarrow \{ \text{not } A \text{ and not } B \text{ and } 0 \} \text{ or } \{ \text{not } A \text{ and } B \text{ and } 1 \} \text{ or } \{ A \text{ and not } B \text{ and } 2 \} \text{ or } \{ A \text{ and } B \text{ and } 3 \};$

MUX model using a conditional signal assignment statement:

```
F <= 00 when Sel = 0
     01 when Sel = 1
     10 when Sel = 2
     11 when Sel = 3;
```

Sel represents the integer equivalent of a 2-bit binary number with bits A and B

If a MUX model is used inside a process, the MUX can be modeled using a CASE statement (cannot use a concurrent statement):

```
case Sel is
  when 0 => F <= 00;
  when 1 => F <= 01;
  when 2 => F <= 10;
  when 3 => F <= 11;
end case;
```

The case statement has the general form:

```
case expression is
  when choice1 => sequential_statements1;
  when choice2 => sequential_statements2;
  [when choice3 => sequential_statements3;]
  [when choice4 => sequential_statements4;]
end case;
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

17

MUX Models (1)

```
library IEEE;
use IEEE_std_logic_1164.all;
use IEEE_std_logic_unsigned.all;
entity SELECTOR is
  port (
    A : in std_logic_vector(15 downto 0);
    SEL : in std_logic_vector(3 downto 0);
    Y : out std_logic;
  );
end SELECTOR;
```

```
architecture RTL1 of SELECTOR is
  begin
    p0: process (A, SEL)
    begin
      if (SEL = "0000") then Y <= A(0);
      elsif (SEL = "0001") then Y <= A(1);
      elsif (SEL = "0010") then Y <= A(2);
      elsif (SEL = "0011") then Y <= A(3);
      elsif (SEL = "0100") then Y <= A(4);
      elsif (SEL = "0101") then Y <= A(5);
      elsif (SEL = "0110") then Y <= A(6);
      elsif (SEL = "0111") then Y <= A(7);
      elsif (SEL = "1000") then Y <= A(8);
      elsif (SEL = "1001") then Y <= A(9);
      elsif (SEL = "1010") then Y <= A(10);
      elsif (SEL = "1011") then Y <= A(11);
      elsif (SEL = "1100") then Y <= A(12);
      elsif (SEL = "1101") then Y <= A(13);
      elsif (SEL = "1110") then Y <= A(14);
      else Y <= A(15);
      end if;
    end process;
  end RTL1;
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

18

MUX Models (2)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
port (
  A : in std_logic_vector(15 downto 0);
  SEL : in std_logic_vector( 3 downto 0);
  Y : out std_logic);
end SELECTOR;
```

```
architecture RTL3 of SELECTOR is
begin
with SEL select
  Y <= A(0) when "0000",
  A(1) when "0001",
  A(2) when "0010",
  A(3) when "0011",
  A(4) when "0100",
  A(5) when "0101",
  A(6) when "0110",
  A(7) when "0111",
  A(8) when "1000",
  A(9) when "1001",
  A(10) when "1010",
  A(11) when "1011",
  A(12) when "1100",
  A(13) when "1101",
  A(14) when "1110",
  A(15) when others;
end RTL3;
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

19

MUX Models (3)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
port (
  A : in std_logic_vector(15 downto 0);
  SEL : in std_logic_vector( 3 downto 0);
  Y : out std_logic);
end SELECTOR;
```

```
architecture RTL2 of SELECTOR is
begin
p1 : process (A, SEL)
begin
  case SEL is
    when "0000" => Y <= A(0);
    when "0001" => Y <= A(1);
    when "0010" => Y <= A(2);
    when "0011" => Y <= A(3);
    when "0100" => Y <= A(4);
    when "0101" => Y <= A(5);
    when "0110" => Y <= A(6);
    when "0111" => Y <= A(7);
    when "1000" => Y <= A(8);
    when "1001" => Y <= A(9);
    when "1010" => Y <= A(10);
    when "1011" => Y <= A(11);
    when "1100" => Y <= A(12);
    when "1101" => Y <= A(13);
    when "1110" => Y <= A(14);
    when others => Y <= A(15);
  end case;
end process;
end RTL2;
```

13/06/2003

UAH-CPE/EE 422/522 ©AM

20

MUX Models (4)

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity SELECTOR is
port (
  A : in std_logic_vector(15 downto 0);
  SEL : in std_logic_vector( 3 downto 0);
  Y : out std_logic);
end SELECTOR;
```

```
architecture RTL4 of SELECTOR is
begin
  Y <= A(conv_integer(SEL));
end RTL4;
```


13/06/2003

UAH-CPE/EE 422/522 ©AM

21

Compilation and Simulation of VHDL Code

 - Compiler (Analyzer) – checks the VHDL source code
 - does it conform with VHDL syntax and semantic rules
 - are references to libraries correct
- Intermediate form used by a simulator or by a synthesizer
- Elaboration
 - create ports, allocate memory storage, create interconnections, ...
 - establish mechanism for executing of VHDL processes




13/06/2003

UAH-CPE/EE 422/522 ©AM

22

Timing Model

 - VHDL uses the following simulation cycle to model the stimulus and response nature of digital hardware




13/06/2003

UAH-CPE/EE 422/522 ©AM

23

Delay Types

 - All VHDL signal assignment statements prescribe an amount of time that must transpire before the signal assumes its new value
- This prescribed delay can be in one of three forms:
 - Transport – prescribes propagation delay only
 - Inertial – prescribes propagation delay and minimum input pulse width
 - Delta – the default if no delay time is explicitly specified




13/06/2003

UAH-CPE/EE 422/522 ©AM

24

Transport Delay

 - Transport delay must be explicitly specified
 - I.e. keyword "TRANSPORT" must be used
- Signal will assume its new value after specified delay




Inertial Delay

- Provides for specification propagation delay and input pulse width, i.e. 'inertia' of output:

```
target <= [REJECT time_expression] INERTIAL waveform;
```

- Inertial delay is default and REJECT is optional:

 
```
output <= NOT Input AFTER 10 ns;
-- Propagation delay and minimum pulse width are 10ns
```



Inertial Delay (cont.)

 - Example of gate with 'inertia' smaller than propagation delay
 - e.g. Inverter with propagation delay of 10ns which suppresses pulses shorter than 5ns

```
Output <= REJECT 5ns INERTIAL NOT Input AFTER 10ns;
```



- Note: the REJECT feature is new to VHDL 1076-1993

Delta Delay

- Default signal assignment propagation delay if no delay is explicitly prescribed
 - VHDL signal assignments do not take place immediately
 - Delta is an infinitesimal VHDL time unit so that all signal assignments can result in signals assuming their values at a future time

```
output <= NOT Input;
-- Output assumes new value in one delta cycle
```


- Supports a model of concurrent VHDL process execution
 - Order in which processes are executed by simulator does not affect simulation output

Simulation Example

```
entity simulation_example is
end simulation_example;

architecture test1 of simulation_example is
    signal A, B, C;
begin
    P1: process(B)
    begin
        A <= '1';
        A <= transport '0' after 5 ns;
    end process P1;

     P2: process(A)
    begin
        if A = '1' then B <= not B after 10 ns; end if;
    end process P2;
end test1;
```



Problem #1

- Using the labels, list the order in which the following signal assignments are evaluated if in2 changes from a '0' to a '1'. Assume in1 has been a '1' and in2 has been a '0' for a long time, and then at time *t* in2 changes from a '0' to a '1'.

```
entity not_another_prob is
    port (in1, in2: in bit;
          a: out bit);
end not_another_prob;

architecture oh_behave of not_another_prob is
    signal b, c, d, e, f: bit;
begin
    L1: d <= not(in1);
    L2: c <= not(in2);
    L3: f <= (d and in2);
    L4: e <= (c and in1);
    L5: a <= not b;
    L6: b <= e or f;
end oh_behave;
```

Problem #2

- Under what conditions do the two assignments below result in the same behavior? Different behavior? Draw waveforms to support your answers.

```
out <= reject 5 ns inertial (not a) after 20 ns;
out <= transport (not a) after 20 ns;
```


13/06/2003

UAH-CPE/EE 422/522 ©AM

31

Modeling a Sequential Machine

 Mealy Machine for
8421 BCD to 8421 BCD + 3 bit serial converter



PS	NS		Z	
	X=0	X=1	X=0	X=1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S6	S6	0	1
S6	S6	-	1	-

How to model this in VHDL?

13/06/2003

UAH-CPE/EE 422/522 ©AM

32

Behavioral VHDL Model

```
entity SM1_2 is
  port (CLK: in bit;
        Z: out bit);
end SM1_2;

architecture Behavioral of SM1_2 is
  signal State: boolean; --state = 0
begin
  process(CLOCK) --Combinational Network
  begin
    case State is
      when 0 =>
        if CLK'event and CLK = '1' then State <= '1'; end if;
      when 1 =>
        if CLK'event and CLK = '0' then State <= '0'; end if;
      when 2 =>
        if CLK'event and CLK = '0' then State <= '1'; end if;
        if CLK'event and CLK = '1' then State <= '0'; end if;
      when 3 =>
        if CLK'event and CLK = '0' then State <= '0'; end if;
        if CLK'event and CLK = '1' then State <= '1'; end if;
      when 4 =>
        if CLK'event and CLK = '0' then State <= '1'; end if;
        if CLK'event and CLK = '1' then State <= '0'; end if;
      when 5 =>
        if CLK'event and CLK = '0' then State <= '0'; end if;
        if CLK'event and CLK = '1' then State <= '1'; end if;
      when 6 =>
        if CLK'event and CLK = '0' then State <= '1'; end if;
        if CLK'event and CLK = '1' then State <= '0'; end if;
      when 7 =>
        if CLK'event and CLK = '0' then State <= '0'; end if;
        if CLK'event and CLK = '1' then State <= '1'; end if;
    end case;
  end process;

  process(CLK) --State Register
  begin
    if CLK'event and CLK = '1' then
      State <= State;
    end if;
  end process;
end Behavioral;
```

PS	X=0	X=1	Z
0	1	0	0
1	1	0	0
2	0	1	1
3	0	1	1
4	0	0	0
5	0	1	0
6	1	0	1
7	1	0	1

Two processes:

- the first represents the combinational network;
- the second represents the state register

13/06/2003

UAH-CPE/EE 422/522 ©AM


33

Simulation of the VHDL Model

Simulation command file:

```
wave CLK X State NextState Z
force CLK 0 0, 1 100 -repeat 200
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
run 1600
```

Waveforms:

 

13/06/2003

UAH-CPE/EE 422/522 ©AM

34

Dataflow VHDL Model

-- The following is a description of the sequential machine of
-- Figure 1-17 in terms of its next state equations.
-- The following state assignment was used:
-- S0->0; S1->1; S2->2; S3->3; S4->4; S5->5; S6->6

```
entity SM1_2 is
  port(X,CLK: in bit;
        Z: out bit);
end SM1_2;

architecture Equations_1_4 of SM1_2 is
  signal Q1,Q2,Q3: bit;
begin
  process(CLK)
  begin
    if CLK='1' then -- rising edge of clock
      Q1 <= not Q2 after 10 ns;
      Q2 <= Q1 after 10 ns;
      Q3 <= (Q1 and Q2 and Q3) or (not X and Q1 and not Q3) or
            (X and not Q1 and not Q2) after 10 ns;
    end if;
    Z <= (not X and not Q3) or (X and Q1) after 20 ns;
  end Equations_1_4;
end;
```

$$Q_1(r') = Q_2$$

$$Q_2(r') = Q_1$$

$$Q_3(r') = Q_1 Q_2 Q_3 + X' Q_1 Q_3 + X' Q_1 Q_2$$

$$Z = X' Q_1 + X Q_3$$

13/06/2003

UAH-CPE/EE 422/522 ©AM


35

Structural Model

```
library BITLIB;
use BITLIB in; pack all;

entity SM1_2 is
  port(X,CLK: in bit;
        Z: out bit);
end SM1_2;

architecture Structure of SM1_2 is
  signal A1,A2,A3,A5,A6,D3: bit := '0';
  signal Q1,Q2,Q3: bit := '0';
  signal Q1A,Q2A,Q3A, XN: bit := '1';
begin
  J1: Inverter port map (X,XN);
  G1: NAND3 port map (Q1,Q2,Q3,A1);
  G2: NAND3 port map (Q1,Q2A,XN,A2);
  G3: NAND3 port map (X,Q2A,Q3A,A3);
  G4: NAND3 port map (A1,A2,A3,D3);
  FF1: DFF port map (Q2A,CLK,Q1,Q1N);
  FF2: DFF port map (Q1,CLK,Q2,Q2N);
  FF3: DFF port map (D3,CLK,Q3,Q3N);
  G5: NAND2 port map (X,Q3,A5);
  G6: NAND2 port map (XN,Q2A,A6);
  G7: NAND2 port map (A5,A6,Z);
end Structure;
```

 

Package bit_pack is a part of library BITLIB – includes gates, flip-flops, counters (See Appendix B for details)

13/06/2003

UAH-CPE/EE 422/522 ©AM

36


Simulation of the Structural Model

Simulation command file:

```

wave CLK X Q1 Q2 Q3 Z
force CLK 0 0, 1 100 -repeat 200
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
run 1600
    
```

Waveforms:

 

13/06/2003

UAH-CPE/EE 422/522 ©AM

37

Wait Statements

- ... an alternative to a sensitivity list
 - Note: a process cannot have both wait statement(s) and a sensitivity list
- Generic form of a process with wait statement(s)

```

process
begin
    sequential-statements
    wait statement
    sequential-statements
    wait-statement
    ...
end process;
    
```

How wait statements work?

- Execute seq. statement until a wait statement is encountered.
- Wait until the specified condition is satisfied.
- Then execute the next set of sequential statements until the next wait statement is encountered.
- ...
- When the end of the process is reached start over again at the beginning.

13/06/2003

UAH-CPE/EE 422/522 ©AM

38

Forms of Wait Statements

```

wait on sensitivity-list;
wait for time-expression;
wait until boolean-expression;
    
```

- Wait on
 - until one of the signals in the sensitivity list changes
- Wait until
 - the boolean expression is evaluated whenever one of the signals in the expression changes, and the process continues execution when the expression evaluates to TRUE
- Wait for
 - waits until the time specified by the time expression has elapsed
 - What is this:
 - wait for 0 ns;

13/06/2003


UAH-CPE/EE 422/522 ©AM

39

Using Wait Statements (1)

```

(library BITLIB;
use BITLIB.all; pack all;
entity SM1_2 is port(X, CLK: in std_logic; out(O0): out std_logic);
architecture Fsm of SM1_2 is signal State, NextState: integer := 0;
begin
process
begin
case State is
when 0 =>
if X = '0' then Z <= '1'; NextState <= 1; end if;
if X = '1' then Z <= '0'; NextState <= 2; end if;
when 1 =>
if X = '0' then Z <= '1'; NextState <= 3; end if;
if X = '1' then Z <= '0'; NextState <= 4; end if;
when 2 =>
if X = '0' then Z <= '0'; NextState <= 4; end if;
if X = '1' then Z <= '1'; NextState <= 4; end if;
when 3 =>
if X = '0' then Z <= '0'; NextState <= 5; end if;
if X = '1' then Z <= '1'; NextState <= 5; end if;
when 4 =>
if X = '0' then Z <= '1'; NextState <= 5; end if;
if X = '1' then Z <= '0'; NextState <= 6; end if;
when 5 =>
if X = '0' then Z <= '0'; NextState <= 6; end if;
if X = '1' then Z <= '1'; NextState <= 6; end if;
end case;
end process;
end Fsm;
    
```

 

13/06/2003

UAH-CPE/EE 422/522 ©AM


40

Using Wait Statements (2)

```

when 0 =>
if X = '0' then Z <= '1'; NextState <= 0; end if;
when others => null; -- SHOULD NOT OCCUR
end case;

 wait on CLK, X;
if rising_edge(CLK) then
State <= NextState;
wait for 0 ns; -- wait for State to be updated
end if;
end process;
end Fsm2;
    
```



13/06/2003

UAH-CPE/EE 422/522 ©AM

41

To Do

- Read
 - Textbook chapters 2.1, 2.2
 - Simulation (Part II): Learn how to use ModelSim

13/06/2003

UAH-CPE/EE 422/522 ©AM

42