

The University of Alabama in Huntsville
ECE Department
EE 202 – 02
Fall 2010
Final Exam Solution

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

D	Q(t+1)
0	0
1	1

T	Q(t+1)
0	Q(t)
1	Q'(t)

- (1 point) A major trend in digital design methodology is the use of a hardware description language to describe and simulate the functionality of a digital circuit.
- (1 point) Propagation delay is the average transition delay time for a signal to propagate from input to output.
- (1 point) A parity bit is an extra bit included with a binary message to make the number of 1's either odd or even.
- (1 point) A multiplexer can be constructed with three-state gates: high, low and high impedance.
- (1 point) A register capable of transferring the binary information held in each cell to its neighboring cell, in a selected direction, is called a shift register.

- (5 points) Convert (1022101_3) to decimal:

$$\begin{aligned}
 1022101_3 &= 1 \times 3^6 + 0 \times 3^5 + 2 \times 3^4 + 2 \times 3^3 + 1 \times 3^2 + 0 \times 3^1 + 1 \times 3^0 \\
 &= 1 \times 729 + 0 \times 243 + 2 \times 81 + 2 \times 27 + 1 \times 9 + 0 \times 3 + 1 \times 1 \\
 &= 729 + 0 + 162 + 54 + 9 + 0 + 1 = 955_{10}
 \end{aligned}$$

- (10 points) Convert decimal +18 and +25 to binary, using the signed-2's-complement representation and enough digits to accommodate the numbers. Then perform the binary equivalent of $(+18) + (-25)$. Convert the answer back to decimal and verify that it is correct.


2 18	2 25	2 7
2 9 0	2 12 1	2 3 1
2 4 1	2 6 0	2 1 1
2 2 0	2 3 0	2 0 1
2 1 0	2 1 1	
2 0 1	0 1	

$+18 = 001\ 0010$ $+25 = 001\ 1001$ $-25 = -32 + 7$ $-25 = 10\ 0111$

$+18 = \quad 001\ 0010$ $18 - 25 = -7$
 $+(-25) = \underline{110\ 0111}$


$$\begin{aligned}
 111\ 1001 &= 1 \times -2^6 + 1 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\
 &= -64 + 32 + 16 + 8 + 0 + 0 + 1 \\
 &= -7 \checkmark
 \end{aligned}$$

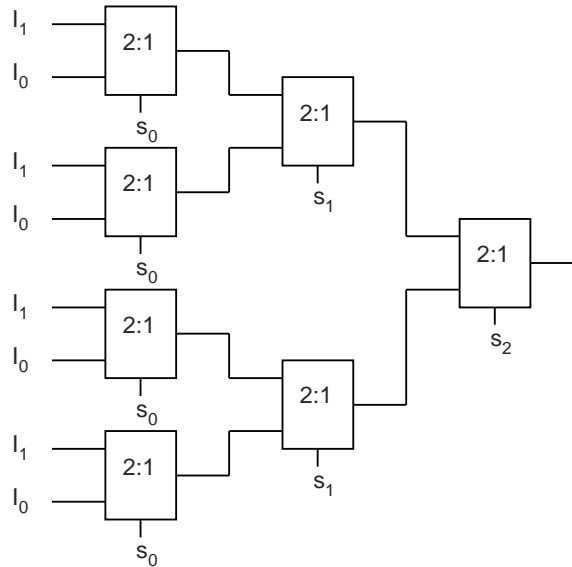8. (10 points) Construct an 8×1 multiplexer with as many 2×1 multiplexers and any additional logic that you might need. Use block diagrams for the components.




9. (15 points) Design a circuit that implements the following truth table. You do not have to draw a circuit diagram.


x	y	z	A	B	C
0	0	0	1	0	0
1	0	1	1	1	0
0	1	0	0	1	0
1	1	1	0	1	1
1	0	0	0	0	1
0	0	1	1	0	1
1	1	0	1	0	0
0	1	1	1	1	0

 

$$A = x'y' + x'z + y'z + xyz'$$

 

$$B = xz + x'y$$

 

$$C = xy'z' + x'y'z + xyz$$

10. (15 points) An XY flip-flop has four operations, clear to 0, complement, no change, and set to 1, when inputs are X and Y are 00, 01, 10, and 11, respectively.

- (a) Tabulate the characteristic table.
- (b) Derive the characteristic equation.
- (c) Tabulate the excitation table.

(a)

X	Y	Q(t)	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(b)

		Q(t+1)		y	
				0	1
x	0	0	0	1	
	0	1	1	1	
		Q(t)			

$Q(t+1) = XQ(t) + YQ'(t)$

(c)

Q(t)	Q(t+1)	X	Y
0	0	d	0
0	1	d	1
1	0	0	d
1	0	1	d

11. (20 points) Design a 4-bit counter which counts in the sequence 0000, 0100, 0110, 0010, 0011, 0111, 1111, 1110, 1010, 1011, 1001, 0001, 0000 using clocked D flip-flops. You do not have to draw the circuit diagram. Is the counter self-correcting if it comes up in an unused state?

Current State	Next State	D _A	D _B	D _C	D _D
0000	0100	0	1	0	0
0100	0110	0	1	1	0
0110	0010	0	0	1	0
0010	0011	0	0	1	1
0011	0111	0	1	1	1
0111	1111	1	1	1	1
1111	1110	1	1	1	0
1110	1010	1	0	1	0
1010	1011	1	0	1	1
1011	1001	1	0	0	1
1001	0001	0	0	0	1
0001	0000	0	0	0	0

D_A

		C	
		0	1
A	0	d	1
	0	d	1
		D	

D_B

		C	
		0	1
A	0	1	1
	0	1	1
		D	

D_C

		C	
		0	1
A	0	1	1
	0	1	1
		D	

D_D

		C	
		0	1
A	0	1	1
	0	1	1
		D	


$D_A = AC + CD$
 $D_B = C'D' + BD + A'CD$
 $D_C = B + A'C + CD'$
 $D_D = AB' + B'C + A'CD$

Unused States	D _A	D _B	D _C	D _D	Next States
0101	1	1	1	0	1110, correcting
1000	0	1	0	1	0101, 1110, correcting
1100	0	1	1	0	0110, correcting
1101	1	1	1	0	1110, correcting

 12. (20 points) Design a Mealy sequential circuit that has one input and one output. This circuit has an output of 1 whenever its input string has the string 0110 in sequence and otherwise has an output of 0. Two sequences can overlap. Use JK flip-flops. You do not have to draw the circuit diagram.

Input: 0110 1101 1101 0111 1110 0011 0101 0111 11
 Output: 0001 0010 0000 0000 0000 0000 1000 0000 00

S0: no valid part of the sequence yet
 S1: received 0
 S2: received 01
 S3: received 011



Current State	Input	Next State	Output
S0	0	S1	0
S0	1	S0	0
S1	0	S1	0
S1	1	S2	0
S2	0	S1	0
S2	1	S3	0
S3	0	S1	1
S3	1	S0	0

Current State	Input	Next State	Output	J _A	K _A	J _B	K _B
00	0	01	0	0	d	1	d
00	1	00	0	0	d	0	d
01	0	01	0	0	d	d	0
01	1	10	0	1	d	d	1
10	0	01	0	d	1	1	d
10	1	11	0	d	0	1	d
11	0	01	1	d	1	d	0
11	1	00	0	d	1	d	1

J _A	B	
A	0	1
0	0	1
1	d	d

$J_A = Bx$

K _B	B	
A	0	1
0	d	1
1	d	1

$K_B = x$

K _A	B	
A	0	1
0	d	d
1	1	1

$K_A = B + x'$

Z	B	
A	0	1
0	0	0
1	0	1

$Z = ABx'$

J _B	B	
A	0	1
0	1	d
1	1	d

$J_B = x' + A$