

CPE 626 CPU Resources: Multipliers

Aleksandar Milenkovic

E-mail: milenka@ece.uah.edu

Web: <http://www.ece.uah.edu/~milenka>

Outline

- Unsigned Multiplication
- Shift and And Multiplier/Divider
- Speeding Up Multiplication
- Array Multiplier
- Signed Multiplication
- Booth Encoding
- Wallace-tree

2

Unsigned Multiplication

```


      0 1 1 1 0 1  multiplicand (29)
x     1 0 1 0 1 1  multiplier (43)
-----
      0 1 1 1 0 1 ← partial product
     0 1 1 1 0 1 ←
    0 0 0 0 0 0 ←
   0 1 1 1 0 1 ←
  0 0 0 0 0 0 ←
 0 1 1 1 0 1 ←
-----
1 0 0 1 1 0 1 1 1 1 ← product
  
```

- product = 0
- for $i = 0$ to $n-1$
 - compute partial product (AND operation)
 - left-shift partial product by i
 - product += partial product

3

Shift and Add Multiplier

 - for $i = 0$ to $n-1$
 - $pp = B \cdot a[i]$
 - $P[2n-1:n] += pp$
 - $P = P \gg 1$



4

Shift and Add Multiplier/Divider


(a) Multiplier (b) Divider

Operands: n-bit unsigned integers

Multiply steps (n steps)

- if $A(0) == 1$ $P \leftarrow P + B$
else $P \leftarrow P + 0$

 - P and A are shifted right with carry out of the sum being moved into the MSB of P, the LSB of P moved into MSB of A, and LSB of A being shifted out



5

Division

Operands (a/b): n-bit unsigned integers

- put a in register A
- put b in register B
- put 0 in register P

Divide steps (n steps)

- Shift (P, A) register pair one bit left
- $P \leftarrow P - B$
- if result is negative, set the low order bit of A to 0, otherwise to 1
- if the result of step 2 is negative, restore the old value of P by adding the contents of B back to P

P	A	Divide 14 = 1110 ₂ by 3 = 11 ₂ . B always contains 0011 ₂ .
00000	1110	step 1(i): shift.
00001	110	step 1(ii): subtract.
-00011	1100	step 1(iii): result is negative, set quotient bit to 0.
-00010	1100	step 1(iv): restore.
00001	100	step 2(i): shift.
00011	100	step 2(ii): subtract.
-00011	1001	step 2(iii): result is nonnegative, set quotient bit to 1.
00001	001	step 3(i): shift.
-00011	001	step 3(ii): subtract.
-00010	0010	step 3(iii): result is negative, set quotient bit to 0.
-00001	0010	step 3(iv): restore.
00010	010	step 4(i): shift.
-00011	010	step 4(ii): subtract.
-00001	0100	step 4(iii): result is negative, set quotient bit to 0.
00010	0100	step 4(iv): restore. The quotient is 0100 ₂ and the remainder is 00010 ₂ .


6

Speeding Up Multiplication (cont'd)

- Reduce the amount of computation in each step by using carry-save adders (CSA)
- CSA is simply collection of n independent full adders
- Each addition operation results in a pair of bits, stored in the sum and carry parts of P
- At each step, only the LSB bit of the sum needs to be shifted
- Steps
 - load the sum and carry bits of P with zero
 - perform first addition
 - shift the LSB sum bit of P into A, as well as A itself
Note: (n-1) bit of P do not need to be shifted because on the next cycle the sum bits are fed into the next lower order adder
- Disadvantages
 - Additional hardware (keep both carry and sum)
 - After the last step, the high order word of the result must be fed into an ordinary adder to combine the sum and carry parts

7

Speeding Up Multiplication

 

8

An Example

- $9 \times 5 \Rightarrow 1001 \times 0101 = 0010\ 1101$
 - $C = 0000$
 $S = 0000$ $A = 0101$
 $P = 1000$
 - $C = 0000$
 $S = 1001$ $A = 1010$
 $P = 0000$
 - $C = 0000$
 $S = 0100$ $A = 0101$
 $P = 1001$
 - $C = 0000$
 $S = 1011$ $A = 1010$
 $P = 0000$
 - Carry Propagate
 $C = 0000$
 $S = 0101$ $A = 1101$
 $S = 0010$ $A = 1101$

9


Speeding Up Multiplication (cont'd)

- Another approach is to examine k low order bits of A at each step, rather than just one bit
 \Rightarrow *higher-radix multiplication*
- Radix-4 Booth recoding
- Radix-8 Booth recoding
- ...

10


Array Multiplier

 - If the space for many adders is available, then multiplication speed can be improved
- E. g. 5-bit multiplier (3 CSA + CPA)
- Advantage
 - could be pipelined
- If space budget is limited, use multiple-pass arrangements



11


6-bit Array Multiplier

 

- Adders a_0 - f_0 may be eliminated \Rightarrow this eliminates adders a_1 - a_6
- Complexity: CSA - 5x6 adders (including 5 half adders) CPA - 6 adders (2 HAs)
- Delay: proportional to $n +$ delay of CPA ($f_6 - b_6$)
- How to improve performance?
 - decrease the number of partial products
 - improve the speed of the addition of the partial


the partial

Floorplan of the 4-bit Array Multiplier

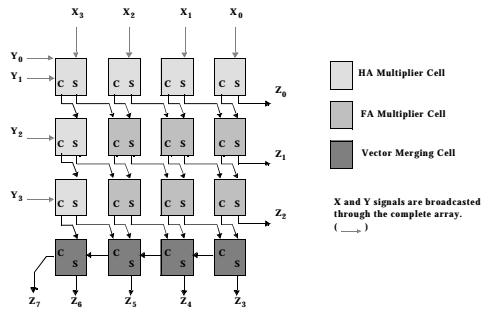

13


Multipass Array Multiplier

 

14

Even/odd Array

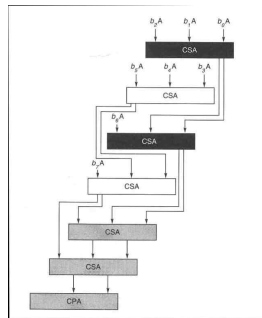- First two adders work in parallel
- Their results are fed into third and fourth adders, which also work in parallel



15

Using CSD Vector

- 15 (multiplicand) $\times 19$ (multiplier) = ?
 $15 \times 19 = 15 \times (20 - 1) = 15 \times 2\bar{1}$
- $A \times B$, $B = 00010111$
 - $B = 16 + 4 + 2 + 1 = 23$
 - Computation: 4 add operations
- It is easier to multiply A with the canonical signed-digit vector (CSD vector) D
 $D = 0010\bar{1}001 = 32 - 8 - 1 = 23$
 - Computation: 3 add/sub operations (a subtraction is as easy as an addition)
- Weight – number of partial products by 1: B has 4, D has 3

16

CSD Vector

- Recode (or encode) any binary number, B, as a CSD vector D

$$D_i = B_i + C_i - 2C_{i+1}$$

$$C_{i+1} = \text{Carry}(B_{i+1} + B_i + C_i), C_0 = 0$$

$$B = 011$$

$$B_2 = 0, B_1 = 1, B_0 = 1$$

$$C_1 = \text{Carry}\{1 + 1 + 0\} = 1, D_0 = 1 + 0 - 2 = \bar{1}$$

$$C_2 = \text{Carry}\{0 + 1 + 1\} = 1, D_1 = 1 + 1 - 2 = 0$$

$$C_3 = \text{Carry}\{0 + 0 + 1\} = 0, D_2 = 0 + 1 - 0 = 1$$

17

CSD Vector

- N – (n + 1)-digit 2's complement number
- Recode it using a Radix other than 2

$$B = B_0 \cdot 2^0 + B_1 \cdot 2^1 + B_2 \cdot 2^2 + \dots + B_{n-1} \cdot 2^{n-1} - B_n \cdot 2^n$$

$$B = 2 \cdot B - B$$

$$= -B_0 \cdot 2^0 + (B_0 - B_1) \cdot 2^1 + \dots + (B_{i-1} - B_i) \cdot 2^i + \dots + (B_{n-1} - B_n) \cdot 2^n$$

$$= (-2 \cdot B_1 + B_0) \cdot 2^0 + (-2 \cdot B_3 + B_2 + B_1) \cdot 2^2 + (-2 \cdot B_5 + B_4 + B_3) \cdot 2^4$$

$$+ \dots + (-2 \cdot B_i + B_{i-1} + B_{i-2}) \cdot 2^{i-1} + (-2 \cdot B_{i+2} + B_{i+1} + B_i) \cdot 2^{i+1} + \dots$$

$$+ (-2 \cdot B_n + B_{n-1} + B_{n-2}) \cdot 2^{n-1}$$

18

CSD Vector: An Example – Radix = 2

- B = 101001, n = 5

$$B = 1 + 8 - 32 = -23$$

$$B = (0 - B_0) \cdot 2^0 + (B_0 - B_1) \cdot 2^1 + (B_1 - B_2) \cdot 2^2 + (B_2 - B_3) \cdot 2^3$$

$$+ (B_3 - B_4) \cdot 2^4 + (B_4 - B_5) \cdot 2^5$$

$$= (-1) + 2 + 0 + (-8) + 16 + (-32) = -23$$

$$E = \bar{1}\bar{1}01\bar{1} = (-1) \cdot 2^5 + 1 \cdot 2^4 + (-1) \cdot 2^3 + 1 \cdot 2^1 + (-1) \cdot 2^0$$


$$= -32 + 16 - 8 + 2 - 1 = -23$$

- To multiply by B
 - encode it as a radix-2 signed digit E
 - Multiply by 2 (a shift) + 6 (n+1) add/subtract operations

19


Encoded Partial Products
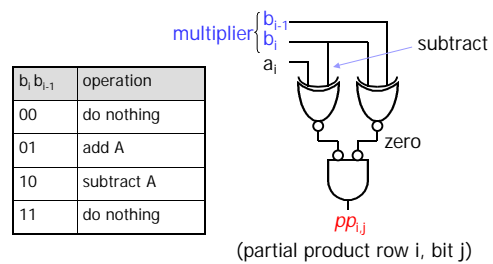
$$B = (0 - B_0) \cdot 2^0 + (B_0 - B_1) \cdot 2^1 + \dots + (B_{i-1} - B_i) \cdot 2^i + \dots + (B_{n-1} - B_n) \cdot 2^n$$




20

Signed Multiplication (1)

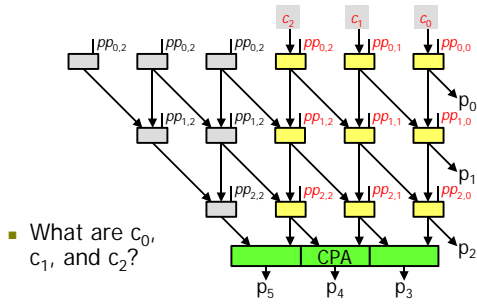

21

Signed Multiplication (2)

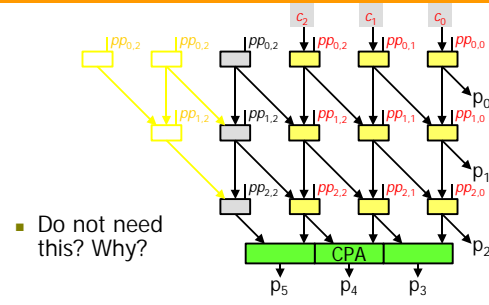

22

CSD Vector: An Example - Radix=4

➤ $B = 101001$, $n = 5$

$$B = 1 + 8 - 32 = -23$$

$$B = (-2 \cdot B_1 + B_0) \cdot 2^0 + (-2 \cdot B_3 + B_2 + B_1) \cdot 2^2 + (-2 \cdot B_5 + B_4 + B_3) \cdot 2^4$$

$$= (2 \cdot 0 + 1) \cdot 2^0 + (-2 \cdot 1 + 0 + 0) \cdot 2^2 + (-2 \cdot 1 + 0 + 1) \cdot 2^4$$

$$= 1 - 8 - 16 = -23$$

$$E = \overline{121} = 1 \cdot 4^0 + (-2) \cdot 4^1 + (-1) \cdot 4^2$$

$$= 1 - 8 - 16 = -23$$

➤ To multiply by B

- encode it as a radix-4 signed digit E
- Multiply by 4 (a shift by 2) + 3 add/subtract operation

23

Booth Encoding (1)

➤ Encode a number by taking groups of 3 bits where each 3-bit group overlaps by 1 bit

$$E_j = -2 \cdot B_j + B_{j-1} + B_{j-2}$$

$$E_{j+1} = -2 \cdot B_{j+2} + B_{j+1} + B_j$$

➤ Consider multiplier B with $(n + 1)$ bit

- Pad B with 0 to match the first term
- if B has an odd number of bits, then extend the sign $B_n, B_n, B_{n-1}, \dots, B_0, 0$

$$B = 01011_2 \Rightarrow B = 8 + 2 + 1 = 11_{10}$$

$$B = 010110 \Rightarrow B = 0010110 \Rightarrow 001, 101, 110$$

$$E = \overline{111} = 1 \cdot 4^2 + (-1) \cdot 4^1 + (-1) \cdot 4^0 = 16 - 4 - 1 = 11$$

24

Booth Encoding (2)

B_i	B_{i-1}	B_{i-2}	Operation
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	2
1	0	0	-2
1	0	1	-1
1	1	0	-1
1	1	1	0


25

Booth Multiply: An Example

- $A = 1100$, $B = 0111$, 2's compl., $n = 3$
- $M = A * B = ?$
- $B = 0111_0 \Rightarrow 011, 110$
- Step 1: $110 \Rightarrow M = -A = 0000\ 0100$
- Step 2: $011 \Rightarrow$
 $M = M + 4*(2A) = 0000\ 0100 + 11100000$
 $= 1110\ 0100 = -28$ (dec)

26


Wallace-Tree

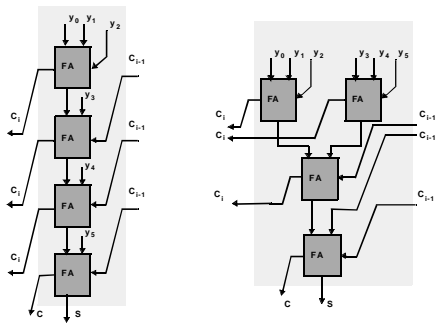

27

Improving Speed

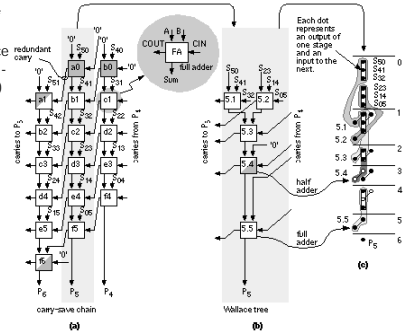
- Collapse the chain of FAs a0-f5 (5 adders delays) to the Wallace tree consisting of 5.1-5.4 (4 adders delays)
- To form P_5 use
 - Summands: $S_{50}, S_{41}, S_{32}, S_{23}, S_{14}, S_{05}$
 - 4 carries from P_4



28

What is Game?


- Dots and holes – the outputs of one stage = inputs of the next
- At each stage we have three choices
 - (1) sum 3 outputs using Full Adder – box with 3 dots
 - (2) sum 2 outputs using Half Adder – box with 2 dots
 - (3) pass outputs directly to the next stage
- Choose (1), (2), or (3) at each stage to maximize the performance of the multiplier
- Tree-based multipliers
 - Work Forward (Wallace-tree Multiplier)
 - Work Backward (Dadda Multiplier)

 

29

6-bit Wallace Multiplier

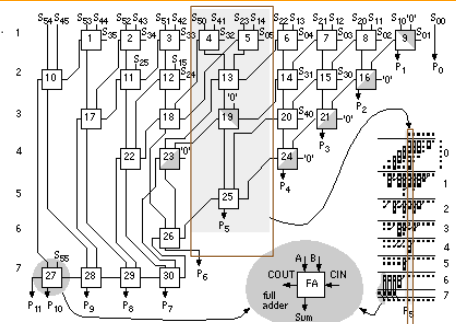
- Complexity
 - CSA – 26 (incl. 6 HAs)
 - CPA – 4
- Delay:
 - CSA – 6 adders delay
 - + CPA – 4



30

6-bit Dadda Multiplier

 - Complexity
 - CSA – 20 (incl. 4 HAs)
 - CPA – 10
- Delay:
 - CSA – 3 adders delay
 - + CPA delay



Work Backward:
each successive stage is 3/2 times larger

31

ARM Multiplier design

- All ARM cores apart from the first prototype have included support for integer multiplication
 - older ARM cores include low-cost multiplication hardware that supports only the 32-bit result multiply and multiply-accumulate
 - recent ARM cores have high-performance multiplication hardware and support 64-bit result multiply and multiply-accumulate
- Low cost implementation
 - Use the datapath iteratively, employing the barrel shifter and ALU to generate 2-bit product in each clock cycle
 - use early termination to stop the iterations when there are no more ones in the multiply register

32

The 2-bit multiplication algorithm, Nth cycle

- Control settings for the Nth cycle of the multiplication
- Use existing shifter and ALU + additional hardware
 - dedicated two-bits-per-cycle shift register for the multiplier and a few gates for the Booth's algorithm control logic (overhead is a few per cent on the area of ARM core)

Carry-in	Multiplier	Shift	ALU	Carry-out
0	x 0	LSL #2N	A + 0	0
	x 1	LSL #2N	A + B	0
	x 2	LSL #(2N + 1)	A - B	1
1	x 3	LSL #2N	A - B	1
	x 0	LSL #2N	A + B	0
	x 1	LSL #(2N + 1)	A + B	0
	x 2	LSL #2N	A - B	1
	x 3	LSL #2N	A + 0	1

33


High speed multiplication

- Where multiplication performance is very important, more hardware resources must be dedicated
 - in some embedded systems the ARM core is used to perform real-time digital signal processing (DSP) – DSP programs are typically multiplication intensive
- Use intermediate results which include partial sums and partial carries
 - Carry-save adders are used for this
- These two binary results are added together at the end of multiplication
 - The main ALU is used for this

34

Carry-propagate (a) and carry-save (b) adder structures

 - Carry propagate adder takes two conventional (irredundant) binary numbers as inputs and produces a binary sum
- Carry save adder takes one binary and one redundant (partial sum and partial carry) input and produces a sum in redundant binary representation (sum and carry)



35

ARM high-speed multiplier organization

- CSA has 4 layers of adders each handling 2 multiplier bits => multiply 8-bits per clock cycle
- Partial sum and carry are cleared at the beginning or initialized to accumulate a value
- Multiplier is shifted right 8-bits per cycle in the 'Rs' register
- Carry sum and carry are rotated right 8 bits per cycle
- Performance: up to 4 clock cycles (early termination is possible)
- Complexity: 160 bits in shift registers, 128 bits of carry-save adder logic (up to 10% of simpler cores)

36

ARM high-speed multiplier organization

