

The University of Alabama in Huntsville
ECE Department
CPE 426 01
Final Exam
April 23, 2020

Name: _____

1. (6 points) Draw the transistor-level diagram of a three input CMOS NAND gate.
2. (5 points) If the NRE costs for FPGA and CBIC circuits are \$50,000 and \$800,000, respectively, and the cost of individual parts for FPGA and CBIC circuits are \$52 and \$11, respectively, what is the break-even manufacturing volume for these two types of circuits?
3. (1 point) A _____ provides stimuli and captures responses.
4. (1 point) A _____ is a set of relational expressions that must be true for the chosen value of the variables.
5. (1 point) _____ are pieces of declarative code that check the relationships between design signals, either once or over a period of time.

6. (6 points) For the process given below, A, B, C, and D are all integers that have a value of 0 at time = 10 ns. If E changes from '0' to '1' at time 20 ns, specify all resulting changes. Indicate the time at which each change will occur, the signal/variable affected, and the value to which it will change.

```

process
  variable F : integer := 1; variable A : integer := 0;
begin
  wait on E;
  A := 1;
  F := A + 5;
  B <= E + 3 after 4 ns;
  A := A + 5;
  C <= F + 2;
  D <= A + 5 after 12 ns;
end process;


```

Scheduling Rules	Transport	Inertial
New before existing	Overwrite existing	Overwrite existing
New after existing	Append new	If $v_{\text{new}} = v_{\text{existing}}$, append new Elself $t_{\text{new}} - t_{\text{existing}} >$ reject append new Else overwrite existing

Time	A	B	C	D	E	F
10 ns	0	0	0	0	0	1
20 ns	1	0	0	0	1	1

7. (1 point) _____ (True/False) Gate delay is the dominant factor in determining the delay of a path.
8. (1 point) _____ (True/False) Design verification is a trivial task.
9. (1 point) _____ are primitives that are all the same height and varying widths.
10. (1 point) A _____ is used in VHDL to bind an architecture to an instantiation of an entity.

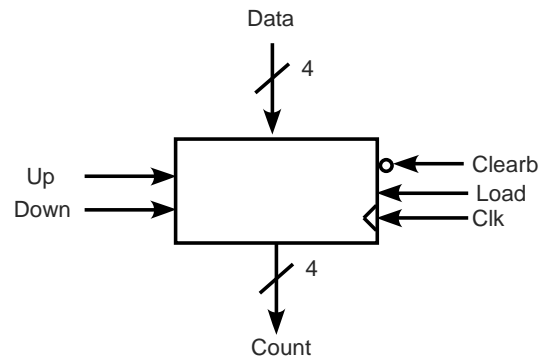11. (8 points) Create a System Verilog interface for a 4 bit counter that has an asynchronous clear input that is active low. It also has active high LOAD, UP and DOWN inputs. When data is loaded into the counter, counting proceeds from that loaded value. Include as part of the interface a clocking block that uses a rising edge clocking scheme. Also include modports from a testbench and from a DUT perspective.



12. (4 points) List the four types of paths that must be considered when determining the maximum frequency of a circuit.

13. (15 points) a. (3 points) VHDL entity, b. (12 points) VHDL architecture Design a finite state machine for control of lights used to start a race, which works as follows.
- Inputs: Reset, Start, Clock Outputs: Red, Yellow, Green
- Only one light can be on at any time.
 - The Reset signal forces the circuit into a state in which the red light is turned on.
 - When the Start signal is activated, the red light stays on for at least one second, then the yellow light is turned on.
 - The yellow light stays turned on one second and then the green light is turned on.
 - The green light stays on for at least three seconds and then the red light is turned on and the circuit returns to its reset state.
 - The input clock has a period of 1 sec.

14. (15 points) Create a VHDL architecture for a 3-to-8 decoder with an active-low enable input which uses a case statement to represent the functionality of the decoder. Create a VHDL entity and its accompanying architecture that represents a 4-to-16 decoder by using two instances of the `en_dec_328` entity. a. (6 points) 3-to-8 decoder architecture, b. (3 points) 4-to-8 decoder entity, c. (6 points) 4-to-8 decoder architecture

```
entity en_dec_328 is  
  port (a : in std_logic_vector (2 downto 0);  
        en : std_logic;  
        d : out std_logic_vector (7 downto 0));  
end entity en_dec_328;
```


15. (1 point) _____ (True/False) Multiple assignments to a signal within a process can cause that signal to have multiple drivers.
16. (1 point). _____ (True/False) If you give a SystemVerilog simulator the same seed and the same testbench, it always produces the same results.
17. (1 point) _____ (True/False) Assertions in System Verilog use negative logic.
18. (10 points) An ARM Advanced High-performance Bus (AHB) has the following signals.

Signal	Width	Direction	Description
HCLK	1	Output	Clock
HADDR	21	Output	Address
HWRITE	1	Output	Write flag: 1=write, 0=read
HTRANS	2	Output	Transaction type: 2'b00=IDLE, 2'b10=NONSEQ
HWDATA	8	Output	Write data
HRDATA	8	Input	Read data

Create a class to encapsulate the AHB transactions. In this class constrain:

- The address (HADDR) to be in the lower 5 addresses and upper 5 addresses each with probability 40% and the other addresses with probability 20%.
- HTRANS to NONSEQ (HTRANS = 2'b10) and IDLE (HTRANS = 2'b00)..
- All other AHB signals are randomized but unconstrained.

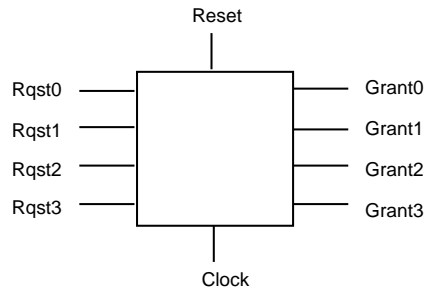19. (15 points) An arbiter is a circuit that allows at most one subsystem at a time to use a shared resource. A four-way arbiter is shown below. Each subsystem sets its request signal to 1 when it wants to use the resource. When the arbiter sets the grant signal to 1, the subsystem uses the resource. The subsystem sets its request back to 0 when it has finished, and waits for grant to be 0 before starting a subsequent request. While a subsystem is granted use of the resource, other requests must wait, rather than pre-empting the active subsystem. Subsystems are granted requests in order, starting with 0, then 1, 2, 3 and back to 0. A subsystem is skipped if it has no pending request.



As part of creating a SystemVerilog testbench for this device, an interface and a packet for randomization has been created. The requests are being driven by the request device modeled in VHDL below. Each req_dev has an associated test program. The test program is responsible for issuing a signal to the req_dev to reset it and providing a time parameter. After reset, the requesting device raises its request line high and keeps it high for the amount of time provided by the test program. Since req_dev works on the positive edge of the clock, the test program will provide inputs to it on the negative edge of the clock. Complete the test0 program so that it repeats the following process 100 times.

- 1) waits a random number of clock cycles to set the reset for reqdev to 1.
- 2) then provides a random number of cycles that reqdev will hold a request high.
- 3) sets the reset to 0 after one clock cycle
- 4) waits one more cycle
- 5) waits for req_dev to lower request to 0
- 6) waits one more clock cycle

```
interface arbiter_if(input bit clk);
    logic [3:0] REQUEST, GRANT, GEN_REQ;
    logic RESET;
    int REQ_TIME3, REQ_TIME2, REQ_TIME1, REQ_TIME0;
endinterface
```

```
module top;
    bit clk;
    always #5ns clk = ~clk;
    arbiter_if arbiterif(clk);
    arbiter u1 (.CLK (clk), .REQ (arbiterif.REQUEST),
               .GRANT (arbiterif.GRANT), RESET (arbiterif.RESET));
    req_dev u2 (.GEN_REQ (arbiterif.GEN_REQ[3]), .REQ_TIME (arbiterif.REQ_TIME3),
               .REQUEST (arbiterif.REQUEST[3]), .GRANT (arbiterif.GRANT[3]),
               .RESET (arbiterif.RESET), .CLK (clk));
    req_dev u3 (.GEN_REQ (arbiterif.GEN_REQ[2]), .REQ_TIME (arbiterif.REQ_TIME2),
               .REQUEST (arbiterif.REQUEST[2]), .GRANT (arbiterif.GRANT[2]),
               .RESET (arbiterif.RESET), .CLK (clk));
    req_dev u4 (.GEN_REQ (arbiterif.GEN_REQ[1]), .REQ_TIME (arbiterif.REQ_TIME1),
               .REQUEST (arbiterif.REQUEST[1]), .GRANT (arbiterif.GRANT[1]),
               .RESET (arbiterif.RESET), .CLK (clk));
    req_dev u5 (.GEN_REQ (arbiterif.GEN_REQ[0]), .REQ_TIME (arbiterif.REQ_TIME0),
```

```
        .REQUEST (arbiterif.REQUEST[0]), .GRANT (arbiterif.GRANT[0]),
        .RESET (arbiterif.RESET), .CLK (clk));
test3 t1(arbiterif);
test2 t2(arbiterif);
test1 t3(arbiterif);
test0 t4(arbiterif);
testr t5(arbiterif);
endmodule : top

package mine;
class Packet_g;
    // The random variables
    rand int generate_t, request_t;
    // Limit the values
    constraint c1 {generate_t < 300; generate_t > 100;
                  request_t < 101; request_t > 0;}
endclass : Packet_g
endpackage : mine

entity REQ_DEV is
    port(GEN_REQ : in std_logic;
         REQ_TIME : in integer range 0 to 100;
         REQUEST : out std_logic;
         GRANT : in std_logic;
         RESET, CLK : in std_logic);
end REQ_DEV;

import mine::*;
module test0(arbiter_if arbif);
```

```
endmodule : test0
```


20. (6 points) Given the following constraints, what are the solution probabilities?

```
Class MemTrans;  
  Rand bit x;  
  Rand bit [1:0] y;  
  Constraint c_xy  
  {  
    y inside {[x:3]};  
    solve x before y;  
  }  
Endclass
```

Solution	x	y	Probability
A	0	0	
B	0	1	
C	0	2	
D	0	3	
E	1	0	
F	1	1	
G	1	2	
H	1	3	